 


Unit-2

CHARACTERISTICS OF OPAMP

Ideal Op-Amp characteristics - DC characteristics, AC characteristics, differential amplifier, frequency response of Op-AMP, Basic applications of Op-AMP - Inverting and Non-Inverting Amplifiers, Summer, differentiator and Integrator, V/I and I/V converters.




* Operational Amplifier called as Op-Amp a linear device.

Three stage circuit: Input stage, gain stage and output stage.

* Used extensively in signal conditioning, filtering or to perform mathematical operations such as addition, subtraction, integration, differentiation etc.

 
* Op-amp amplifies only the difference between two input signal and generates single output.



* Five Basic terminals - two input, one output and two power supply terminals.

Inverting amplifier: 180° phase difference b/w Input-output sgl

 Non-Inverting amplifier: 0° phase difference b/w Input-output sgl



If $V_1 = 0$, output V_0 is 180° out of phase with input signal V_2 .
 If $V_2 = 0$, output V_0 will be in phase with input signal V_1 .

$$V_0 = A(V_1 - V_2)$$

Output in phase V_1
 Output out of phase V_2

differential gain


non-inverting input terminal

inverting input terminal

$$V_0 = AV_d \quad [\because V_d = V_1 - V_2]$$

The characteristics of ideal op-amp:

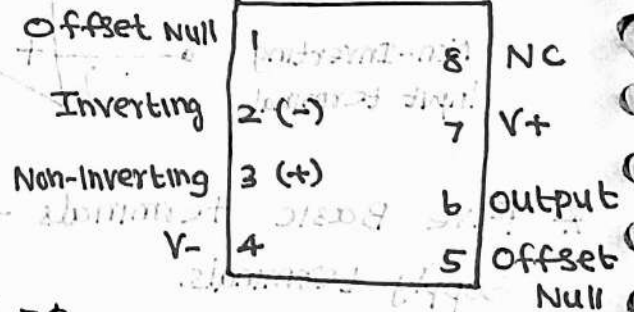- * Infinite input resistance $[R_i = \infty]$
- * Zero output resistance $[R_o = 0]$
- * Infinite Voltage gain $A_v = \infty$
- * Infinite Band width $BW = \infty$
- * Zero offset (i.e.) when $V_1 = V_2$, $V_0 = 0$
- * Slew Rate = infinite
- * Common Mode Rejection Ratio $CMRR = \infty$




It can be observed that,

- * draws no current at both input terminal [$i_1=0, i_2=0$]. Bcoz of infinite input Impedance, any sgl with source impedance can drive the op-amp w/o getting any loading effect.
- * Gain is infinite. Hence, the voltage b/w the inverting & non-inverting terminal is essentially zero for an finite o/p voltage
- * Output voltage V_o is independent of the current drawn from the output $R_o=0$.

Open loop operation of OP-Amp

V_1 : Inverting

V_2 : Non-inverting

 


- * Infinite gain, so V_o is either at its +ve or -ve saturation region/voltage ($+V_{sat}/-V_{sat}$) as $V_1 > V_2$ or $V_2 > V_1$.

* Application: Voltage Comparator, Zero crossing detector.

* Amplifier acts as switch.

Inverting Amplifier

 

* output voltage (V_o) is fed back to the inverting input terminal through (R_f) feedback resistor.

* Input signal V_i applied to the inverting input terminal through R_i and non-inverting input terminal - grounded.

Analysis: For simplicity, assume ideal op-amp

As $V_d = 0$,

$$i_1 = \frac{V_i}{R_i}$$

Also since op-amp draws no current, current thru R_i must flow through R_f .

$$V_o = -i_1 R_f = -V_i \frac{R_f}{R_i}$$

Gain of inverting amplifier (closed loop gain)

$$A_{cl} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

Alternatively, nodal equation @ node 'a',

$$\frac{V_a - V_i}{R_i} + \frac{V_a - V_o}{R_f} = 0$$

($V_a = 0$ bcoz node 'a' @ virtual ground)

$$\therefore A_{cl} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

* -ve sign indicates 180° phase shift b/w V_o and V_i .
 Also inverting input is @ virtual ground, effective resistance is R_i (input resistance)

So, R_i kept large to avoid loading effect.

$$[R_f > R_i \text{ gain} > 1] [R_f < R_i \text{ gain} < 1] [R_f = R_i \text{ gain} = 1]$$

* Load resistor R_L put at the output, otherwise the input impedance of measuring device act as load.

* R_i and R_f are replaced by impedance then $A_{CL} = -\frac{Z_f}{Z_i}$


Non-Inverting Amplifier

* Amplifies the input without producing any phase shift between input and output.

* Input signal - non inverting input terminal

* negative feedback signal output is fed back to the inverting input terminal.

Analysis

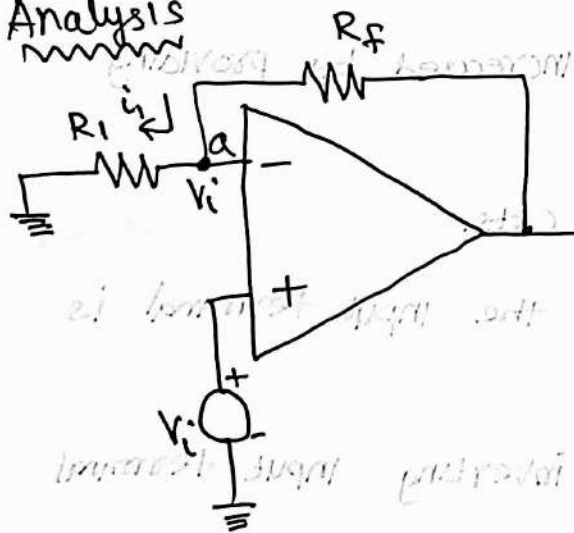

* V_d @ input terminal = 0

* nodal eqn @ node a

$$\frac{V_i - 0}{R_i} + \frac{V_i - V_o}{R_f} = 0$$

$$\frac{V_i}{R_i} = -\left(\frac{V_i - V_o}{R_f}\right)$$

$$\frac{V_i}{R_i} = -\frac{V_i}{R_f} + \frac{V_o}{R_f}$$

$$\frac{V_i}{R_1} + \frac{V_i}{R_f} = \frac{V_o}{R_f} \quad V_i \left[\frac{1}{R_1} + \frac{1}{R_f} \right] = \frac{V_o}{R_f}$$

$$\frac{V_o}{V_i} = R_f \left[\frac{1}{R_1} + \frac{1}{R_f} \right]$$

$$= \frac{R_1 + R_f}{R_1}$$

$$A_{CL} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$$

* Gain must be adjusted to unity by proper selection of resistor R_f and R_1 .

* Compared to inverting amplifier, R_i of non-inverting amplifier is extremely large ($=\infty$), op-amp draws negligible current from signal source.

Feedback in Ideal op-amp

* Utility of an op-amp can be greatly increased by providing negative feedback.

* Two important negative feedback ckts.

(a) current drawn by either of the input terminal is negligible.

(b) V_d between non-inverting and inverting input terminal is essentially zero.

1. Design an amplifier with a gain of -10 and input resistance equal to $10\text{ k}\Omega$

$$R_1 = 10\text{ k}\Omega$$

$$A_{CL} = -\frac{R_f}{R_1}$$

$$R_f = -A_{CL} \cdot R_1$$

$$= -(-10) \times 10\text{ k}\Omega$$

$$= 100\text{ k}\Omega$$

2. A load of $25\text{ k}\Omega$ is connected to the output terminals. calculate (i) i_1 (ii) V_o (iii) i_L (iv) total current i_o in to the output pin. Consider $R_1 = 10\text{ k}\Omega$ $R_f = 100\text{ k}\Omega$ $V_i = 1\text{ V}$

$$i_1 = \frac{V_i}{R_1} = \frac{1\text{ V}}{10\text{ k}\Omega} = 0.1\text{ mA}$$


$$\frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

$$V_o = -\frac{R_f}{R_1} V_i$$

$$= -\frac{100\text{ k}\Omega}{10\text{ k}\Omega} \cdot 1\text{ V} = -10\text{ V}$$

$$i_L = \frac{V_o}{R_L} = \frac{10\text{ V}}{25\text{ k}\Omega} = 0.4\text{ mA}$$
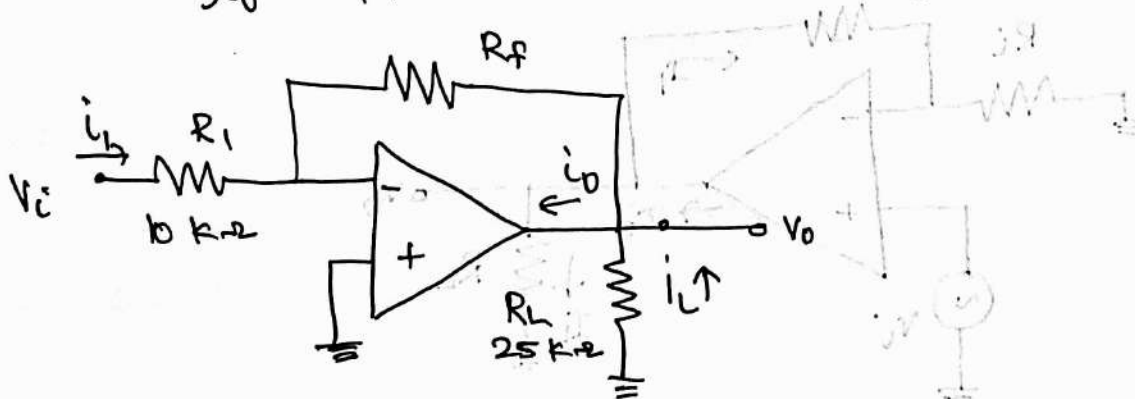
$$i_o = i_1 + i_L = 0.1\text{ mA} + 0.4\text{ mA} = 0.5\text{ mA}$$



Determine the voltage gain of an inverting amplifier

with $R_1 = 10 \text{ k}\Omega$ $R_f = 47 \text{ k}\Omega$

$$A_{CL} = -\frac{R_f}{R_1} = -\frac{47 \times 10^3}{10 \times 10^3} = -4.7 \quad A_{CL} = 4.7$$

negative sign indicates phase shift

A sine wave of 0.5V peak voltage is applied to an inverting amplifier using $R_1 = 10 \text{ k}\Omega$ $R_f = 50 \text{ k}\Omega$. It uses the supply voltage of $\pm 12\text{V}$. Determine the output voltage.

$R_1 = 10 \text{ k}\Omega$
 $R_f = 50 \text{ k}\Omega$
 $V_i = 0.5 \text{ V}$

$$A_{CL} = -\frac{R_f}{R_1} = -\frac{50 \text{ k}}{10 \text{ k}} = -5$$

$$A_{CL} = \frac{+V_o}{V_i} \quad V_o = V_i \cdot A_{CL}$$

$$A_{CL} = -5 \quad = \frac{0.5 \times 5}{1} = 2.5 \text{ Volt}$$


An input of 3V is fed to the non-inverting terminal of an op-amp. The amplifier has $R_1 = 10 \text{ k}\Omega$ $R_f = 10 \text{ k}\Omega$. Find V_o .

$V_i = 3\text{V}$ $R_1 = R_f = 10 \text{ k}\Omega$

$$A_{CL} = 1 + \frac{R_f}{R_1} = 1 + \frac{10}{10} = 2$$

$$V_o = V_i \cdot A_{CL} = 3 \times 2 = 6 \text{ Volt}$$

 For non-inverting amplifier, $R_1 = 5 \text{ k}\Omega$ $R_f = 20 \text{ k}\Omega$ $V_i = 1 \text{ Volt}$. $R_L = 5 \text{ k}\Omega$ connected at output. Determine V_o , A_{CL} , I_L and I_o



$$V_o = \left[1 + \frac{R_f}{R_i} \right] V_i = \left[1 + \frac{20 \text{ k}\Omega}{5 \text{ k}\Omega} \right] [1 \text{ V}] = 5 \text{ V}$$

$$A_{CL} = \frac{V_o}{V_i} = \frac{5 \text{ V}}{1 \text{ V}} = 5$$

$$i_L = \frac{V_o}{R_L} = \frac{5 \text{ V}}{5 \text{ k}\Omega} = 1 \text{ mA}$$

$$i_i = \frac{V_i}{R_i} = \frac{V_o - V_i}{R_f} = 0.2 \text{ mA}$$

$$i_o = i_i + i_L = 0.2 + 1 \text{ mA} = 1.2 \text{ mA}$$

Design an amplifier with a gain of 5 using one op-amp

$$A_{CL} = 1 + \frac{R_f}{R_i}$$

$$5 = 1 + \frac{R_f}{10 \text{ k}\Omega}$$

$$R_f = 4 \times 10 = 40 \text{ k}\Omega$$

DC Performance Characteristics

- * Ideal op-amp draws no current from source; response is also independent of temperature variations.
 - * Real/practical op-amp shifts its operation with temperature.
 - * Due to mis-match of transistors, two inputs respond differently to input voltage and current.
- These non-ideal dc characteristics that add error components to the dc output voltage are

- * Input Bias current
- * Input offset current
- * Input offset voltage
- * Thermal drift.

* Op amp input
 ↓ BJT/FET
 differential amplifier


- * Ideal op-amp: No current
- * Practical op-amp: current
 DC current

Input Bias current

* Input Bias current is the average of the current that flows into the inverting and non-inverting input terminals of an op-amp.

- * this current affects all the application of op-amp.
- * practically, input terminals do conduct a small value of dc current to bias the input transistor.

FET: pA BJT: μ A IC741 = 80nA

 


* when lower input bias currents are achieved the possible imbalances in the circuit will be minimized.

I_{B1} and I_{B2} : Base current

* though transistors are identical

$I_{B1} \neq I_{B2}$ due to imbalances

 during fabrication. Hence manufacturers specify the I_B .



$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

I_{B1} : Bias current entering non-inverting input


I_{B2} : Bias current entering inverting input

Consider the basic inverting amplifier, if $V_i = 0$ then $V_o = 0$
 However V_o is found to be offset by a value of Application sig level & measured in millivolt, is not acceptable.

$$V_o = (I_{B2}) R_f$$

This offset effect can be compensated by the use of a Compensation Resistor R_{comp} .

 The current I_{B1} flowing through R_{comp} develops a voltage V_{comp} across it.



Apply KVL,

$$-V_{comp} + 0 + V_2 - V_o = 0$$

$$V_o = V_2 - V_{comp}$$

So to achieve $V_o = 0$ proper R_{comp} should be selected to get $V_2 = V_{comp}$ and thus offset effect gets cancelled.

To find R_{comp} :

$$V_{comp} = R_{comp} I_{B1}$$

$$R_{comp} = \frac{V_{comp}}{I_{B1}}$$

KCL at node a, $I_{B2} = I_1 + I_2$

$$I_1 = \frac{V_{comp}}{R_i}$$

$$I_2 = \frac{V_2}{R_f}$$

Entering current @ node = leaving current @ node

For offset compensation $V_2 = V_{comp}$

$$I_2 = \frac{V_{comp}}{R_f}$$

$$I_{B2} = \frac{V_{comp}}{R_1} + \frac{V_{comp}}{R_f}$$

$$I_{B2} = \left(\frac{1}{R_1} + \frac{1}{R_f} \right) V_{comp}$$

Assume $I_{B1} = I_{B2}$, $I_{B1} = \frac{V_{comp}}{R_{comp}}$

$$\frac{V_{comp}}{R_{comp}} = V_{comp} \left(\frac{1}{R_1} + \frac{1}{R_f} \right)$$


$$\therefore R_{comp} = \frac{R_1 R_f}{R_1 + R_f} = R_1 \parallel R_f$$

R_{comp} must be equal to the parallel combination of input and feedback resistors connecting @ the inverting input terminal

For non-inverting amplifier,

$$R_{comp} = R_1 \parallel R_f$$

 effect of I_B compensated by R_{comp} in series with input signal V_i .



Input offset current

- * I_B compensation is achieved when I_B are equal $I_{B1} = I_{B2}$
- * But input transistors cannot be made identical and there exists diff. b/w I_{B1} and I_{B2} . The difference in magnitude b/w I_{B1} and $I_{B2} \rightarrow$ input offset current I_{os}

$$I_{os} = |I_{B1}| - |I_{B2}|$$

To find the effect of I_{os} consider the bias current compensation circuit assuming $V_i = 0$

$$V_o = V_2 - V_{comp} \quad * \text{BJT } 200 \text{ nA}$$

$$V_o = I_2 R_f - V_{comp} \quad \text{FET } 10 \text{ pA}$$

$$I_{B2} = I_1 + I_2$$

$$I_2 = I_{B2} - I_1$$

$$I_2 = I_{B2} - \frac{V_{comp}}{R_1} \quad \left[I_1 = \frac{V_{comp}}{R_1} \right] \quad \left[V_{comp} = I_{B1} \cdot R_{comp} \right]$$

$$I_2 = I_{B2} - I_{B1} \frac{R_{comp}}{R_1}$$

$$\left(V_{comp} = I_{B1} \cdot R_{comp} \right)$$

$$\therefore V_o = \left(I_{B2} - I_{B1} \frac{R_{comp}}{R_1} \right) R_f - I_{B1} \cdot R_{comp}$$

$$= I_{B2} R_f - \frac{I_{B1} R_f R_{comp}}{R_1} - I_{B1} R_{comp}$$

$$= \left[I_{B2} - \frac{I_{B1} R_{comp}}{R_1} \right] R_f - I_{B1} R_{comp}$$

Use $R_{comp} = \frac{R_1 R_f}{R_1 + R_f}$ in above eqn we get

$$V_o = R_f (I_{B2} - I_{B1})$$

$$V_o = R_f I_{Os}$$

$$V_o = \left[I_{B2} - \frac{I_{B1} (R_1 R_f)}{R_1 (R_1 + R_f)} \right] R_f - \frac{I_{B1} R_1 R_f}{R_1 + R_f}$$

$$= \left[\frac{I_{B2} R_1 (R_1 + R_f) - I_{B1} R_1 R_f}{R_1 (R_1 + R_f)} \right] R_f - \frac{I_{B1} R_1 R_f}{R_1 + R_f}$$

$$= \frac{I_{B2} R_1 R_f (R_1 + R_f) - I_{B1} R_1 R_f^2}{R_1 (R_1 + R_f)} - \frac{I_{B1} R_1 R_f}{R_1 + R_f}$$

$$= \frac{I_{B2} R_1 R_f (R_1 + R_f) - I_{B1} R_1 R_f^2 - I_{B1} R_1 R_f}{R_1 + R_f}$$

$$= \frac{I_{B2} R_f R_1 + I_{B2} R_f^2 - I_{B1} R_f^2 - I_{B1} R_1 R_f}{R_1 + R_f}$$

$$= \frac{I_{B2} R_f (R_1 + R_f) - I_{B1} R_f (R_f - R_1)}{R_1 + R_f}$$

$$= \frac{I_{B2} R_f (R_1 + R_f) + I_{B1} R_f (R_1 + R_f)}{R_1 + R_f}$$


$$= I_{B2} R_f + I_{B1} R_f = R_f (I_{B2} + I_{B1})$$

$$V_o = R_f I_{Os}$$

Offset current can be minimized by keeping $R_f \rightarrow$ small

R_f value has to be large to compensate the effect produced by I_{os} . Compensation of I_{os}

 If $R_i \rightarrow$ large
 R_t also large
 To obtain gain



"T-network is a good solution"

$R_t \ll \frac{R_f}{2}$ (To design a 'T' network)


$R_s = \frac{R_t^2}{R_f - 2R_t}$

$R_f = \frac{R_t^2 + 2R_t R_s}{R_s}$

Input offset voltage


* defined as voltage that is to be applied b/w two input terminals for making the output voltage zero.

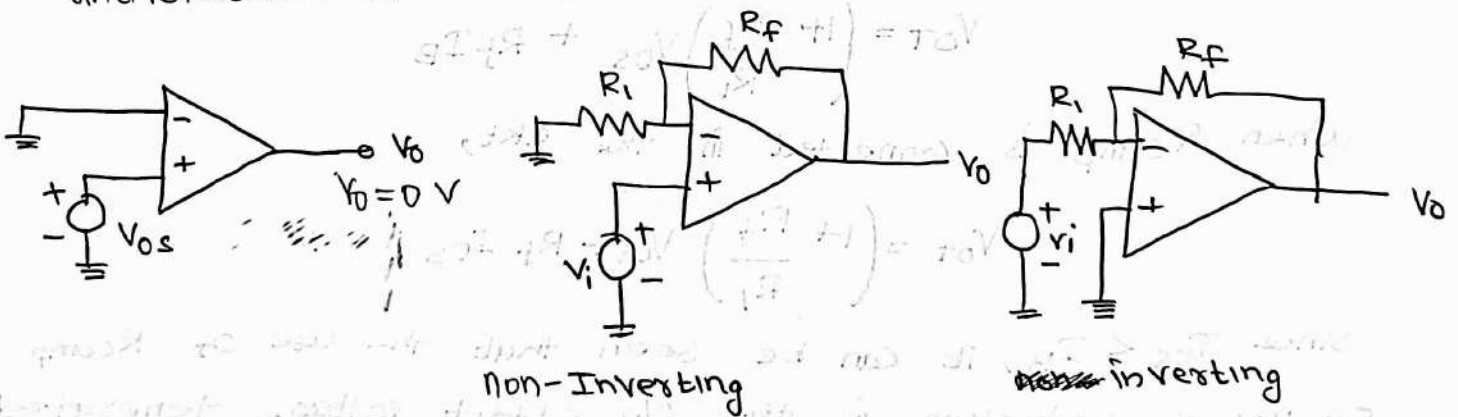* I/p offset voltage - introduced due to mismatches in the o/p transistor and active load resistor. Unavoidable imbalances



Non-Inverting

~~Non~~ Inverting

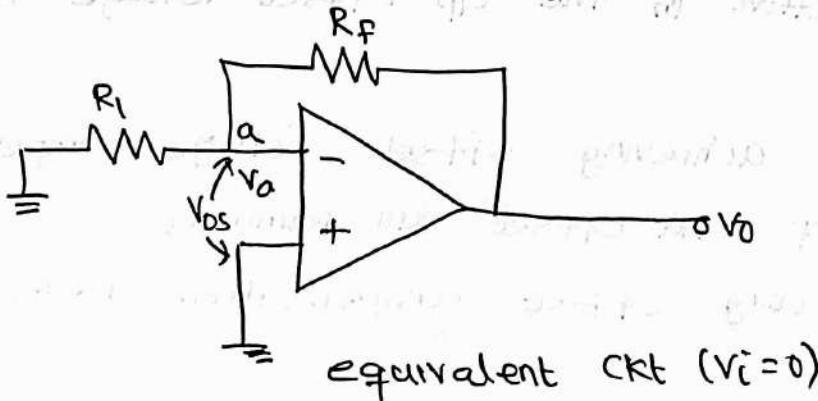

equivalent ckt ($V_i = 0$)

Nodal equation @ node a

$$\frac{V_a - 0}{R_1} + \frac{V_a - V_o}{R_f} = 0 \quad \frac{V_a}{R_1} + \frac{V_a}{R_f} = \frac{V_o}{R_f}$$

$$V_a = V_o \left(\frac{R_1}{R_f + R_1} \right) \quad V_o = \left(1 + \frac{R_f}{R_1} \right) V_a$$

$$V_{os} = |V_i - V_a| \quad \text{with } V_i = 0$$

$$V_{os} = |0 - V_a| = V_a (V_2)$$

$$V_{os} = \left(1 + \frac{R_f}{R_1} \right) V_{os} \quad \text{Output offset voltage in closed loop configuration.}$$

Total output offset voltage

* V_{OT} can be due to either the I_B or the V_{os} and also it can be either +ve or -ve w.r.t ground. Considering both effects the total output offset voltage is

$$V_{OT} = \left(1 + \frac{R_f}{R_1} \right) V_{os} + R_f I_B$$

When R_{comp} is connected in the ckt,

$$V_{OT} = \left(1 + \frac{R_f}{R_1} \right) V_{os} + R_f I_{os}$$

Since $I_{os} < I_B$, it can be seen that the use of R_{comp} ensures a reduction in the o/p offset voltage generated due to I_B .

Two methods of achieving offset voltage compensation.

* op-amp with offset null terminals



* connecting offset compensation network.

* In op-amp with offset null terminal method manufacturers recommend a 10 k Ω potentiometer to be placed across offset null pin 1 and 5 and the wiper to be connected to the negative supply pin 4.

* When no offset null pins are provided, external balancing techniques are used.

$$V_{os} = \pm V \left(\frac{R_3}{R_3 + R_4} \right)$$
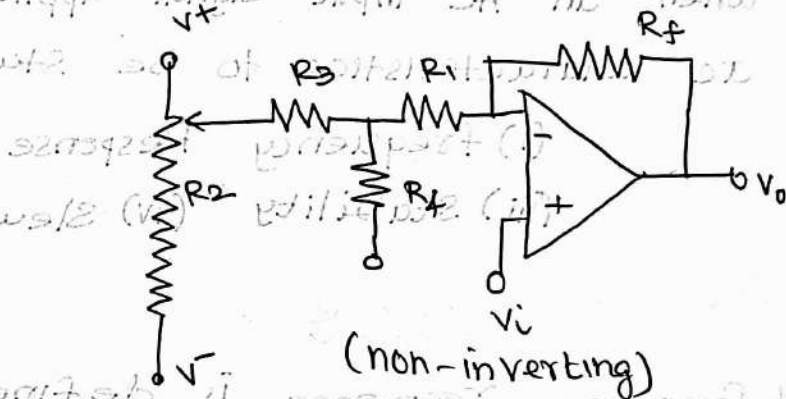 
$$\Delta V = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1 + R_f}$$



Thermal drift

* I_B , I_{os} , V_{os} \rightarrow changes with temperature

* Change in temperature ΔT , change in time Δt , change in supply voltage ΔV_i will create a challenge to those parameter.

* ΔT cause most serious variation in the value of I_B , I_{os} , V_{os} .

* Thermal drift \rightarrow ~~used~~ used to identify such changes and defined as average rate of change of input offset voltage per unit change in temperature.

$$\frac{\Delta V_{os}}{\Delta T} \quad \text{unit: } \mu\text{V}/^\circ\text{C}$$

Thermal drift \rightarrow input offset current $\frac{\Delta I_{os}}{\Delta T}$ ($\mu\text{A}/^\circ\text{C}$)

\rightarrow input bias current $\frac{\Delta I_B}{\Delta T}$ ($\mu\text{A}/^\circ\text{C}$)

Thermal drift \rightarrow not a constant value

\rightarrow not uniform over a specified temperature range

AC performance characteristics

When an AC input signal is applied to op-amp, the following AC characteristics are to be studied.

(i) frequency Response (ii) Bandwidth

(iii) Stability (iv) Slew Rate


Frequency Response

* Frequency response is defined as the manner in which the gain of op-amp responds to different frequencies.

* Ideal op-amp has infinite bandwidth. i.e. if its open loop gain is 90 dB with DC signal, its gain remains the same 90 dB through audio and onto high frequencies.

* Gain of practical op-amp decreases @ high frequencies. bcoz of capacitive component in the equivalent circuit of op-amp.

 * Capacitive component \rightarrow present due to the stray capacitances or physical characteristics of device.



high frequency model of an op-amp with single corner frequency.

Open loop Voltage gain of an op-amp with only the corner frequency is obtained from

$$V_o = \frac{-j\omega C}{R_o - j\omega C} A_{OL} V_d$$

$$A = \frac{V_o}{V_d} = \frac{A_{OL}}{1 + j2\pi f R_o C} = \frac{A_{OL}}{1 + j(f/f_1)}$$

$$f_1 = \frac{1}{2\pi R_o C} \quad A_{OL} = \text{Open loop gain @ low frequency}$$



$$f_1 = \text{break frequency / dominant pole frequency}$$

The magnitude

$$|A| = \frac{A_{OL}}{\sqrt{1 + (f/f_1)^2}}$$


The phase angle

$$\phi(f) = -\tan^{-1}(f/f_1)$$

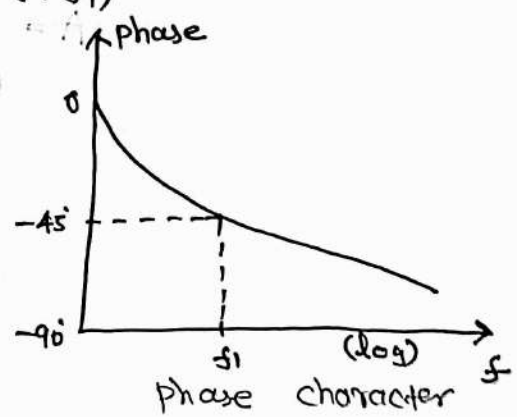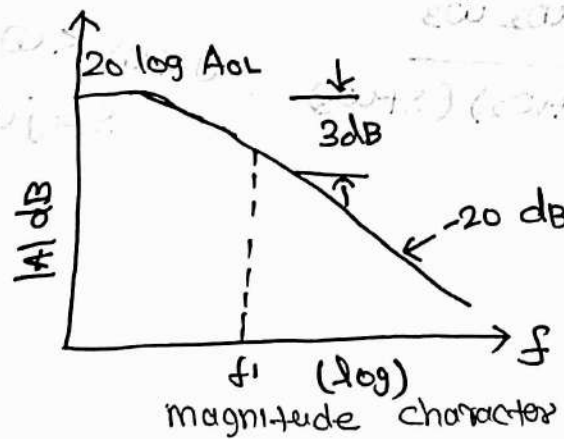

From magnitude curve,

 - * Frequency $f \ll f_1$, the magnitude of the gain is $20 \log A_0$ in dB
- * At $f = f_1$, the gain is 3 dB down from the dc voltage/ value of A_0 is dB. f_1 : corner frequency
- * $f \gg f_1$, the gain rolls off at the rate of -20 dB/decade



From phase plot,

- * At $f = 0$, phase angle is zero
- * At f_1 , phase angle is -45° lagging
- * At infinite phase angle is -90° . this shows the maximum of phase shift 90° can occur with a single capacitor.

The Voltage transfer function in s-domain



$$A = \frac{A_{OL}}{1 + j(f/f_1)} = \frac{A_{OL}}{1 + j(\omega/\omega_1)} = \frac{A_{OL} \omega_1}{j\omega + \omega_1} = \frac{A_{OL} \omega_1}{s + \omega_1}$$

A practical op-amp has number of stages and each stage produce a different capacitive component. The transfer function with three break frequency


$$A = \frac{A_{OL}}{(1 + jf/f_1)(1 + jf/f_2)(1 + jf/f_3)} \quad 0 < f_1 < f_2 < f_3$$

$$A = \frac{A_{OL} \cdot \omega_1 \omega_2 \omega_3}{(s + \omega_1)(s + \omega_2)(s + \omega_3)} \quad 0 < \omega_1 < \omega_2 < \omega_3$$

$s = j\omega$

  

 As frequency increases, cascading effect of RC pair (poles) come into effect. Roll off rate increased by -20dB/decade @ each corner frequency.



Each pole also introduces lagging phase of maximum up to -90°

Bandwidth with feedback


- * Bandwidth of an amplifier - range of frequencies within which the gain remain constant
- * Gain and Bandwidth \rightarrow inversely proportional to one another
- * Gain \times Bandwidth \rightarrow always constant

* Bandwidth \rightarrow increased \rightarrow providing feedback sig to input

$A_{CL} BW_{CL} = A_{OL} B_{OL}$

Stability of an op-amp

 - * op-amp rarely used in open loop configuration bcoz of high gain
- * Let us consider Resistive feed back inverting amplifier ($V_2=0$)



Closed loop to. fn

$$A_{CL} = \frac{A}{1+AB}$$

(A = open loop voltage gain)

β = feedback ratio

If $1+AB = 0$, the ckt becomes unstable, it leads to characteristic eqn

Sustained oscillation. Rewrite the characteristic eqn

$$1 - (-AB) = 0 \text{ leads to}$$

loop gain $-AB = 1$, which is complex quantity

So, magnitude $|AB| = 1$

Phase condition

$$\angle -AB = 0 \text{ (or multiple of } 2\pi)$$

$$\angle AB = \pi \text{ (or odd multiple of } \pi)$$

Here β is a constant if only resistive components are used and hence they do not provide any phase shift.

When $(1+AB) < 1$, $AB < 0$ (a) $AB = \text{negative value}$, which results in instability or unbounded output. Then


$A_{CL} > A$, (b) closed loop gain increases and leads to stability.


In a given resistive feedback n/w, there is no phase shift. Since op-amp is connected in inverting mode, it

provide a phase shift of 180° @ low frequencies. and

Contribution of A is low so $AB > 0$ $A_{CL} < A$ and the

s/m is stable.

 

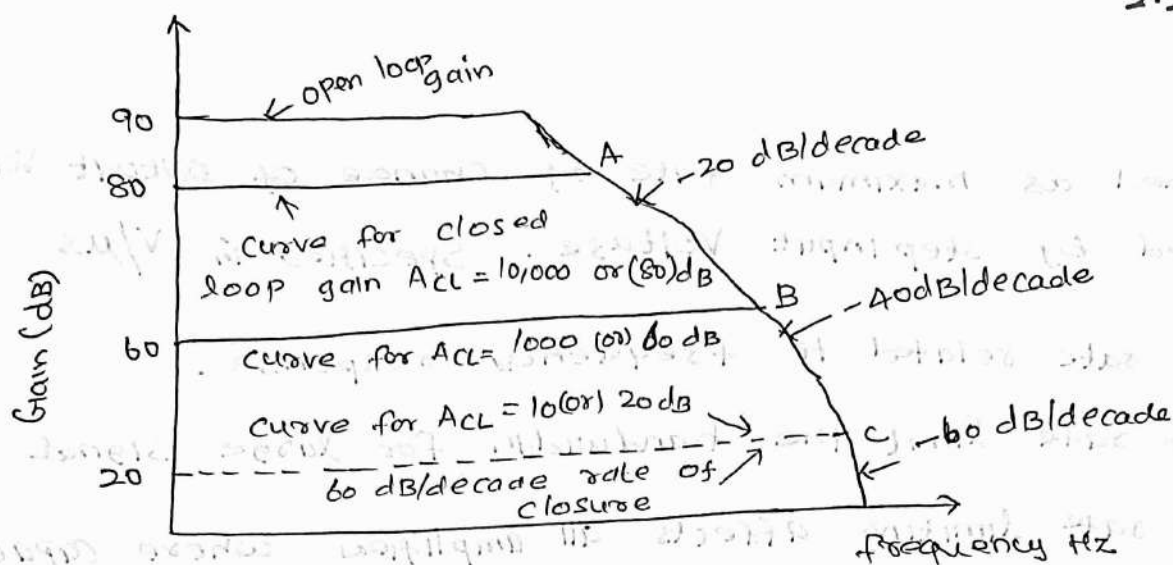

* At high frequency, at each corner frequency an additional phase shift of -90° takes place. For two corner frequency additional phase shift will be -180° .

* @ high frequency, for some value of β , the magnitude of $A\beta$ become unity and an additional phase shift of 180° makes phase shift to zero. leads to amplifier to oscillate and unstable.

* From graph, three break pts \rightarrow leads to -270° phase shift resulting in unstable operation.

* For stable operation, the rate of closure b/w A_{CL} and A_{OL} curve should not exceed -20 dB/decade .

transfer function with three poles,

$$A = \frac{A_{OL} \omega_1 \omega_2 \omega_3}{(s + \omega_1)(s + \omega_2)(s + \omega_3)} \quad 0 < \omega_1 < \omega_2 < \omega_3$$

$$1 + A\beta = 0$$

\therefore The poles

$$1 + \frac{\beta A_{OL} \omega_1 \omega_2 \omega_3}{(s + \omega_1)(s + \omega_2)(s + \omega_3)} = 0$$

Slew Rate

- * defined as maximum rate of change of output voltage caused by step input voltage. Specified in $V/\mu s$
- * Slew rate related to frequency response.
- * Slew rate limit the bandwidth for large signal output
- * Slew rate limiting affects all amplifiers where capacitance has to be charged and discharged as voltage level vary.

Causes of Slew Rate

- * Slew rate caused due to limited charging rate of the compensating capacitor, current limiting and saturation of the internal stages of an op-amp.

The rate @ which voltage across capacitor

$$\frac{dV_c}{dt} = \frac{I}{C} \quad (I = \text{maxi. current furnished by op-amp to capacitor } C)$$

OP-amp must have either a higher current or a small compensation capacitor. Slew rate reduces due to rise in temperature.

$$I_C \text{ 741, } I_C = 15 \mu A, C = 30 \text{ pF}$$

$$\begin{aligned} \text{Slew rate} &= \frac{dV_c}{dt} = \frac{I_{\text{max}}}{C} \\ &= \frac{15 \mu A}{30 \text{ pF}} = 0.5 \text{ V}/\mu s \end{aligned}$$

Slew Rate Limiting of sine wave

* S.R limits the response of all the large signal wave-shapes

$$V_i = V_m \sin \omega t$$

$$V_o = V_m \sin \omega t$$

Rate of change of o/p,

$$\frac{dV_o}{dt} = V_m \omega \cos \omega t$$

Maximum rate of change of o/p occur when $\cos \omega t = 1$

$$SR = \left. \frac{dV_o}{dt} \right|_{\text{max}} = V_m \omega \quad (\omega = 2\pi f)$$

$$SR = 2\pi f V_m \text{ V/s} = \frac{2\pi f V_m}{10^6} \text{ V/\mu s}$$

$$f_{\text{max}} = \frac{SR}{2\pi V_m}$$

full power response




$$V_m(\text{max}) = \frac{\text{Slew Rate}}{2\pi f}$$

maximum peak (max frequency of a sinusoidal voltage large amplitude sine wave which op-amp have w/o distortion)

$$FPB = \frac{SR}{2\pi V_{\text{sat}}}$$

Full power Bandwidth $\pm V_{\text{sat}} = \text{Saturation Voltage}$

   maximum frequency at which op-amp can produce an undistorted o/p with maximum possible amplitude.



Methods of Improving Slew Rate

* Increasing f_t (gain bandwidth product)

Internal capacitor value must be reduced. For uncompensated op-amps, compensating n/w be used

* Increasing $I_{O1}(\text{sat})$ (saturation current level of input stage)

→ Increase I_{O1} w/o affecting the value of g_{m1} and f_t an alternative method for charging and discharging of C has to be provided.

→ This is possible by using additional input transistor pair which will go into conduction region.

* Reducing g_{m1}

→ g_{m1} can be reduced by using suitable resistance in series with the emitter of differential input transistors.

→ Use FET instead of BJT differential input pair

* By using proper frequency compensation and other compensating networks higher slew rate op-amps can be selected for high speed applications.

Assuming slew rate for 741 is $0.5 \text{ V}/\mu\text{s}$, what is the maximum undistorted sine wave that can be obtained for 12V and 2V peak?

$$f_{\max} = \frac{S.R}{2\pi V_m} = \frac{0.5 \text{ V}/\mu\text{s}}{2\pi \times V_m}$$

$$\text{if } V_m = 12\text{V} \quad \text{then } f_{\max} = 6.63 \text{ kHz}$$

$$\text{if } V_m = 2\text{V} \quad \text{then } f_{\max} = 39.8 \text{ kHz}$$

IC 741 is used as an inverting amplifier with a gain of 100. The voltage gain vs frequency curve is flat up to 10 kHz. Determine the maximum peak to peak input signal that can be applied without any distortion to the output

$$V_m(\max) = \frac{\text{Slew Rate}}{2\pi f}$$

$$= \frac{0.5 \text{ V}/\mu\text{s}}{2\pi \times 10 \text{ kHz}} = \frac{0.5}{2\pi \times 10^3 \times 10^{-6}} = 7.96 \text{ Volt}$$

The output voltage of a certain op-amp circuit changes by 20 Volt in $4 \mu\text{s}$. What is Slew Rate?

$$\text{Slew Rate} = \frac{dV_o}{dt}$$

$$= \frac{20 \text{ V}}{4 \mu\text{s}} = 5 \text{ V}/\mu\text{s}$$

Frequency Compensation

* Achieve large Bandwidth and lower closed loop gain
Suitable Compensation techniques used

(a) External Compensation

(b) Internal Compensation


Internal Frequency Compensation

* Broad Bandwidth may not be required for some applications. Such cases internally compensated op-amps called compensated op-amp can be employed

* found to be stable - regardless of value of closed loop gain and w/o any external compensation methods

* op-amp 741 internally contains a capacitance of 30 pF that shunts off the s_{cl} current @ higher frequencies, leading to decrease in O/p s_{cl}

 * Internal Compensation capacitor causes the open loop gain to roll off @ -20 dB/decade that assure a stable characteristic for the ckt.



External Frequency Compensation

- * Compensating n/w connected externally to the op-amp for modifying the response suiting the requirement.
- * -20 dB/decades - roll off rate - achieved by compensating n/w
- * Commonly used external compensation:
 - (a) Dominant pole compensation
 - (b) Pole-zero (lag) compensation
 - (c) Miller effect compensation

Dominant pole compensation


Assume $A \rightarrow$ uncompensated transfer function,

$$A = \frac{A_0 \omega_1 \omega_2 \omega_3}{(s + \omega_1)(s + \omega_2)(s + \omega_3)} \quad 0 < \omega_1 < \omega_2 < \omega_3$$

For compensation introduce a dominant pole by adding RC-network in series with op-amp or by connecting a capacitor C from a suitable high resistance point to ground.

$$A' = \frac{V_o}{V_i} = A \cdot \left[\frac{1/j\omega C}{R + 1/j\omega C} \right]$$

$$A = \frac{A_0}{1 + j(f/f_d)}$$

 

Dominant pole compensation

$f_d = \frac{1}{2\pi RC}$, break frequency of compensating n/w.


$$A' = \frac{A_0}{(1 + jf/f_d)(1 + jf/f_1)(1 + jf/f_2)(1 + jf/f_3)}$$

$$f_d < f_1 < f_2 < f_3$$

* Capacitance C is selected such that the modified loop gain drops down to 0 dB with a roll-off rate as given by 20 dB/decade @ a frequency, where the poles of the uncompensated S/m transfer fn A , \rightarrow contributes negligible phase shift.

* Dis-advantage: Bandwidth of op-amp ckt reduces drastically from f_1 to f_d .

 * Advantage: Improved noise immunity of the S/m .



Pole-Zero (lag) Compensation

* Uncompensated transfer function $A \rightarrow$ altered by adding both pole and zero.

* Zero should be @ higher frequency than pole.

Tr. fn of compensating n/w alone,

$$\frac{V_0}{V_2} = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2 + 1/j\omega C_2}{R_1 + R_2 + 1/j\omega C_2}$$


where $Z_1 = R_1$

$$Z_2 = \frac{1}{j\omega C_2} + R_2$$

$$\frac{V_o}{V_i} = \frac{1 + j\omega R_2 C_2}{1 + j\omega (R_1 + R_2) C_2} = \frac{1 + (j f / f_1)}{1 + (j f / f_0)}$$

$$f_1 = \frac{1}{2\pi R_2 C_2}$$

$$f_0 = \frac{1}{2\pi (R_1 + R_2) C_2}$$

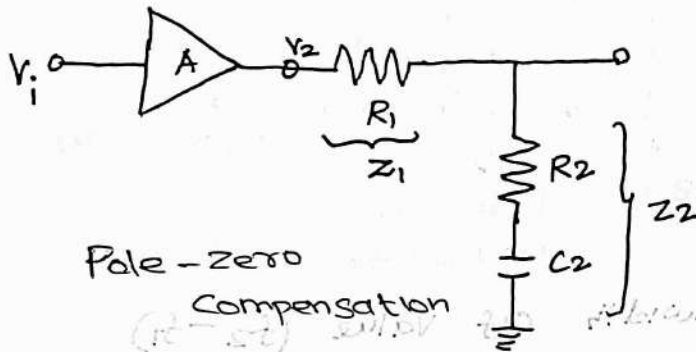

* Zero @ first corner frequency \rightarrow cancel the effect of pole at f_1 .

* pole of compensating n/w $\omega_0 = \frac{\omega_0}{2\pi}$ is selected. So that the transfer function 'A' passes thru 0 dB @ the 2nd corner frequency f_2 of the uncompensated tr. fn A.

Assume, compensating n/w does not load the amplifier

$R_2 \gg R_1$, then overall transfer function,


$$A' = \frac{V_o}{V_i} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_i} = A \frac{(1 + j f / f_1)}{(1 + j f / f_0)}$$

$$= \frac{A_0 (1 + j f / f_1)}{(1 + j f / f_0)(1 + j f / f_1)(1 + j f / f_2)(1 + j f / f_3)}$$

$$= \frac{A_0}{(1 + j f / f_0)(1 + j f / f_2)(1 + j f / f_3)}$$

$$0 < f_0 < f_1 < f_2 < f_3$$

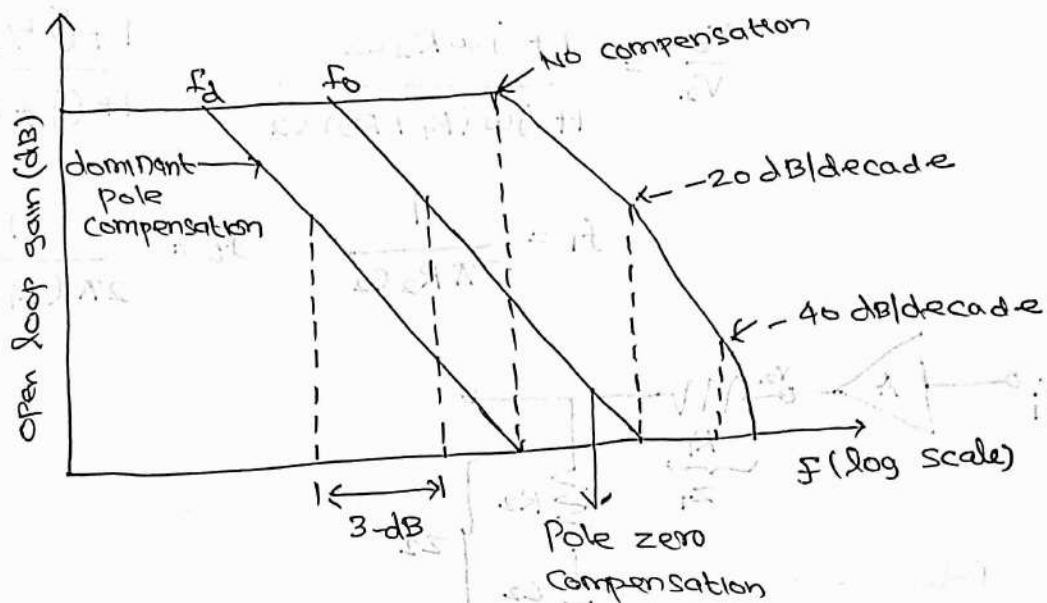$R_2 \gg R_1$ So that $\frac{R_2}{R_1 + R_2} \approx 1$




* Advantage: Improved Bandwidth of value $(f_2 - f_1)$

* Dis-advantage: size of compensation capacitance is large, standard IC op-amps have external pins provided to facilitate the external component connection.

This drawback eliminated in miller effect compensation method.

Miller effect compensation

 * Combination of C_1 and R_1 behaves as phase-lead n/w in the feedback loop of op-amp. Thus C_1 and R_1 introduce a phase lead to cancel some amount of phase-lag in loop.




Voltage follower : Basic application of OP-Amp

* If a Non-Inverting amplifier, ($R_f = 0$, $R_1 = \infty$) we get Voltage follower.

* output voltage = Input voltage
(Both magnitude and phase)

Output voltage follows the input voltage

 

* used as buffer for impedance matching (to connect a high impedance source to a low impedance load)

* unity gain ckt $\rightarrow Z_i = \text{high}$

$Z_o = 0$ draws negligible current from source.


Differential Amplifier

* Amplifies the difference b/w two input voltage sgl.

V_o : Output sgl

V_1, V_2 : Input signal

 V_d : difference input voltage
 $V_1 - V_2$



$V_o \propto (V_1 - V_2)$
 $V_o \propto V_d$ } Ideal differential amplifier. (1)

Each sgl is measured with respect to ground

Differential Gain A_d

From (1) $\rightarrow V_o = A_d (V_1 - V_2)$

\downarrow
Constant of Proportionality

$A_d \rightarrow$ gain with which differential amplifier amplifies the difference b/w two input sgl. Called as differential gain of the differential amplifier.

$A_d =$ differential gain

$V_d = V_1 - V_2$

$\therefore V_o = A_d V_d$

\downarrow
difference voltage

$$A_d = \frac{V_o}{V_d}$$

In terms of decibel

$$A_d = 20 \log_{10} (A_d) \text{ in dB.}$$

Common Mode Gain A_c

* When two i/p voltages which are equal is applied to the differential amplifier. ($V_1 = V_2$) then o/p voltage $V_o = 0$.

* Output voltage of practical differential amplifier depends on average common level of two inputs.

$$V_c = \frac{V_1 + V_2}{2}$$

\downarrow
Average level of two i/p sgl.

Called as Common mode Signal.

* differential amplifier output \propto Common mode sigl V_c

$$V_o = A_c V_c$$

$$\therefore V_o = A_d V_d + A_c V_c$$

For ideal differential amplifier,

$A_d = \infty$, while common mode gain = 0.

This ensure $V_1 = V_2$; $V_o = 0$

* practically $A_c \neq 0$, $A_d = \text{very large}$. At this stage one important parameter called Common mode Rejection Ratio (CMRR)

Common mode Rejection Ratio (CMRR)

* Common mode configuration: When same voltage is applied to both inputs

* many disturbance sigl (noise) \rightarrow appear as input sigl to both the inputs of diff. amplifier. Such sigl should be rejected by diff. amplifier.

* CMRR: ability of a differential amplifier to reject a common mode sigl.

$$CMRR, e = \left| \frac{A_d}{A_c} \right|$$

Ideally, $A_c = 0$, $CMRR = \infty$ (infinite) CMRR in dB

$$\text{CMRR in dB} = 20 \log \left| \frac{A_d}{A_c} \right| \text{ dB}$$

$$V_o = A_d V_d + A_c V_c$$

$$= A_d V_d \left[1 + \frac{A_c V_c}{A_d V_d} \right]$$

$$= A_d V_d \left[1 + \frac{1}{\left(\frac{A_d}{A_c} \right) \frac{V_d}{V_c}} \right]$$

$$V_o = A_d V_d \left[1 + \frac{1}{\text{CMRR}} \cdot \frac{V_c}{V_d} \right]$$

Output of difference sig. Common mode Component is rejected.

CMRR is large, V_c and $V_d \rightarrow$ present.

Features of diff amplifier

1. High voltage gain
2. low common mode gain
3. High CMRR
4. Two input terminals
5. Large Bandwidth
6. High input impedance
7. Low output impedance
8. Low offset voltage; current.



Transistorised differential amplifier

* Two emitter biased circuit

↳ Identical emitter biased circuit.

$Q_1, Q_2 =$ Transistor (exactly matched characteristic)
 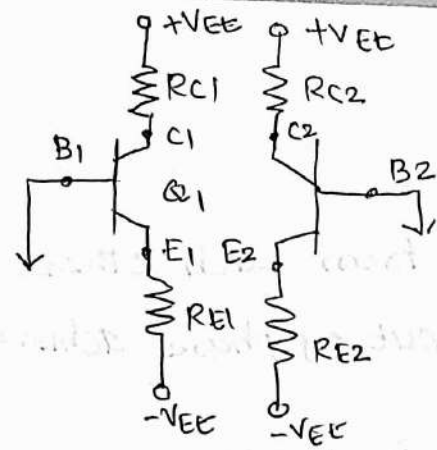
$$R_{C1} = R_{C2} \quad R_{E1} = R_{E2} \quad +V_{CC} = -V_{EE}$$



* Connections:

- (a) E_1 of Q_1 to E_2 of Q_2
 RE_1, RE_2 becomes parallel and replaced by RE
- (b) b_1 of Q_1 to V_{S1}
 b_2 of Q_2 to V_{S2}

* measure supply voltage wrt ground.

Balanced output between C_1 and C_2 . Emitter Coupled differential amplifier.

$$R_{C1} = R_{C2} = R_C$$

* output taken b/w two collector. called as balanced o/p or double ended o/p or floating o/p.

* output ^{collector} to ground, called as unbalanced o/p / single ended o/p.

Two modes of ckt operation

- (a) Differential mode
- (b) Common mode

* Two input sgl's are different from each other.
 Same in magnitude but 180° out of phase achieved by centre tap transformer.


* Assume sine wave on the base Q_1 is positive
 Sine wave on the base Q_2 is negative

* Positive sgl on base of Q_1 , an amplified negative going sgl develops on the collector Q_1 , R_E also increases Hence Positive going wave developed across R_E

* negative sgl on base of Q_2 , an amplified negative going sgl develops on collector of Q_2 , Positive going sgl develops across R_E b coz of emitter follower action Q_2

* Sgl voltage across R_E , due to effect of Q_1, Q_2 are equal in magnitude and 180° out of phase. due to matched pair transistor.

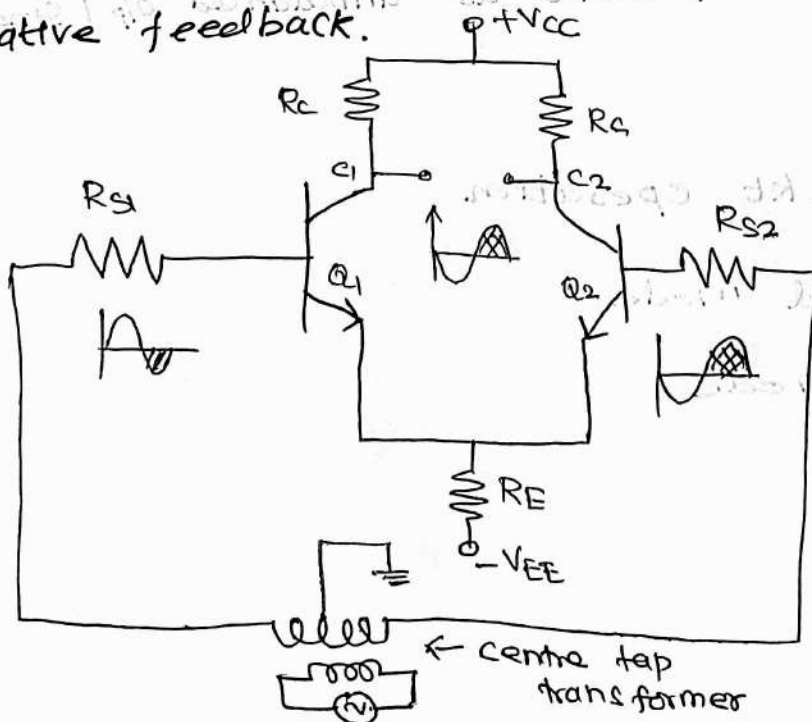
* Two sgl cancel each other and there is no AC sgl current flowing through the emitter resistance. R_E not introduce negative feedback.



Common mode operation

- * Sgl applied to the base Q_1 and Q_2 are derived from the same source. Two sgl's are equal in magnitude & phase.
- * Sgl voltages at the bases Q_1 and Q_2 causes in-phase signal voltages to appear across R_E which add together.
- * R_E carries a sgl current and provide a negative feedback which reduces the common mode gain of diff. amplifier.

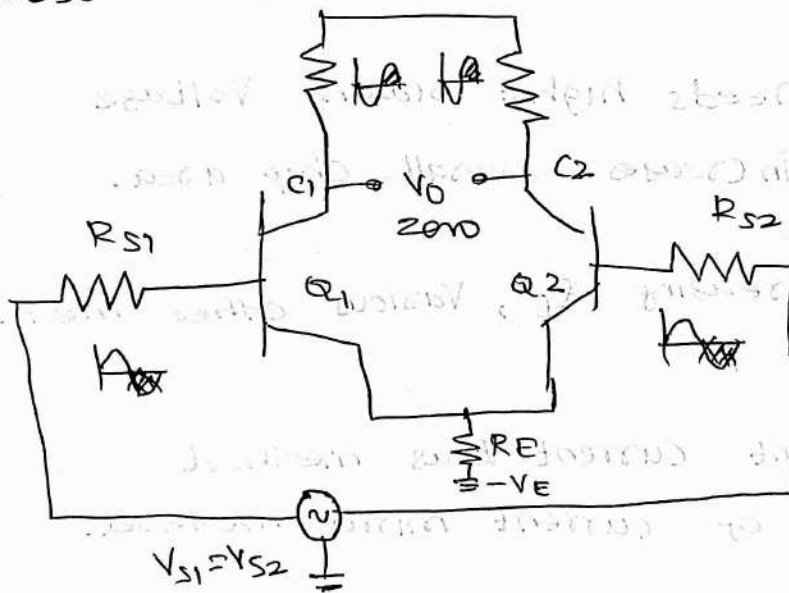V_o : difference b/w the two signal @ collector
 V_o almost zero, negligibly small. Ideally it should be zero.



Differential amplifier circuit configurations

- (i) dual input, Balanced output
- (ii) dual input, Unbalanced output
- (iii) single input, balanced output
- (iv) single input, Unbalanced output

Methods of improving CMRR

- * higher value of CMRR better performance
- * To improve CMRR, Common mode gain $A_c \rightarrow$ reduced
- * $A_c = 0$; $R_E = \infty$ because R_E introduce negative feedback in common mode operation which reduce A_c .
- * Higher value of R_E , lesser value of A_c , higher value of CMRR.

$A_d \rightarrow$ not depend on R_E

- * Practically R_E cannot be selected very high due

(a) Large R_E needs higher biasing voltage

(b) Large R_E increases overall chip area.

Instead of increasing R_E , various other methods are used.

- * Constant current bias method

- * Usage of current mirror method.

Differential amplifier circuit configurations

(i) Dual input, Balanced output

(ii) Dual input, Unbalanced output

(iii) Single input, Balanced output

(iv) Single input, Unbalanced output

Adder or Summing Amplifier

Op-amp may be used to design a circuit whose output \rightarrow sum of several input signal. Depending upon the sign of input


(a) Inverting Summer (b) Non-Inverting Summer

Inverting Summer

3 I/p voltage: V_1, V_2, V_3

3 Resistor R_i : R_1, R_2, R_3

1 feedback Resistor.

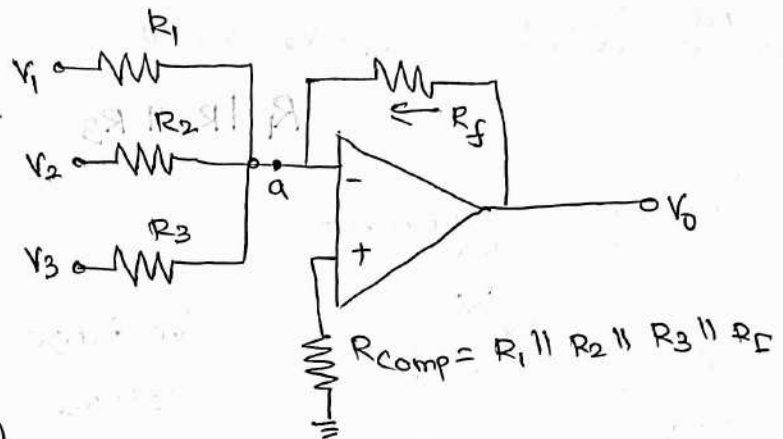

* Open loop gain $A_{OL} = \infty$

$$R_i = \infty$$

\therefore Input bias current $= 0$; no voltage drop across R_{comp}

non-inverting i/p terminal @ ground potential.

* Voltage at node 'a' = Zero

Apply nodal eqn by KCL at node a,

$$\frac{V_a - V_1}{R_1} + \frac{V_a - V_2}{R_2} + \frac{V_a - V_3}{R_3} + \frac{V_a - V_0}{R_f} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_f} = 0$$

$$V_0 = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Special case: $R_1 = R_2 = R_3 = R_f$

$$\therefore V_0 = -(V_1 + V_2 + V_3)$$

$V_0 =$ inverted sum of i/p sgl


$$\therefore V_0 = -\left(\frac{V_1 + V_2 + V_3}{3}\right) \text{ if } R_1 = R_2 = R_3 = 3R_f$$

Thus the output is the average of i/p sgl.

To find R_{comp} : $V_1 = V_2 = V_3 = 0$

$$R_i = R_1 \parallel R_2 \parallel R_3 \quad \therefore R_{comp} = R_i \parallel R_f$$

Non-Inverting Summer

 

Voltage @ (-) input terminal be V_a

Voltage @ (+) input terminal V_a

Node eqn @ a,

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} = 0$$

$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$V_a = \frac{(V_1/R_1) + (V_2/R_2) + (V_3/R_3)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

The o/p amp and two resistors R_f and R constitute non-inverting amplifier,


$$V_0 = \left(1 + \frac{R_f}{R}\right) V_a$$

$$\therefore V_0 = \left(\frac{V_1/R_1 + V_2/R_2 + V_3/R_3}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right) \left(1 + \frac{R_f}{R}\right)$$

$R_1 = R_2 = R_3 = R = R_f/2$ then $V_0 = V_1 + V_2 + V_3$

Subtractor or difference amplifier

 * Basic differential amplifier used as subtractor



* Assume all resistors are equal
 $R_1 = R_2 = R_3 = R_f$

* O/p voltage determined by superposition theorem.
 $V_2 = 0 \therefore V_2$ is grounded then V_{01} due to V_1 alone

$$V_{01} = \frac{V_1}{2} \left(1 + \frac{R}{R} \right) = V_1$$

Similarly $V_1 = 0 \therefore V_{02}$ due to V_2 alone

$$V_{02} = -V_2$$

$$V_0 = V_{01} + V_{02} = V_1 - V_2$$

This act as difference amplifier with unity gain.

Differentiator

* circuit in which o/p voltage is differentiation of input voltage. This operation is useful to find rate at which a sgl varies with time.


Ideal Differentiator: constructed from a basic inverting amplifier if R_1 is replaced by C_1 .

Apply KCL at node a,

$$i_c = i_B + i_f$$

$$i_B = 0,$$

$$i_c = i_f$$

 

$$i_c = C_1 \frac{d}{dt} (V_i - V_a)$$

$$i_c = C_1 \frac{dV_i}{dt}$$

$$C_1 \frac{d}{dt} (V_i - V_a) = \frac{V_a - V_o}{R_f} \quad V_a = V_b = 0$$

$$C_1 \frac{dV_i}{dt} = -\frac{V_o}{R_f} \quad \therefore V_o = -R_f C_1 \frac{dV_i}{dt}$$

Thus the output voltage V_o is equal to $R_f C_1$ times the derivative of input voltage. The negative sign indicates 180° phase shift of the output w.r.t input signal.

* V_o in frequency domain

$$V_o(s) = -R_f C_1 s V_i(s)$$

Put $s = j\omega$

$$V_o(j\omega) = -R_f C_1 j\omega V_i(j\omega)$$



magnitude of ts. fn

$$|A| = \left| \frac{V_o}{V_i} \right|$$

$$= |-j\omega R_f C_1| = \omega R_f C_1$$

$$|A| = \frac{f}{f_a}$$

$$f_a = \frac{1}{2\pi R_f C_1}$$

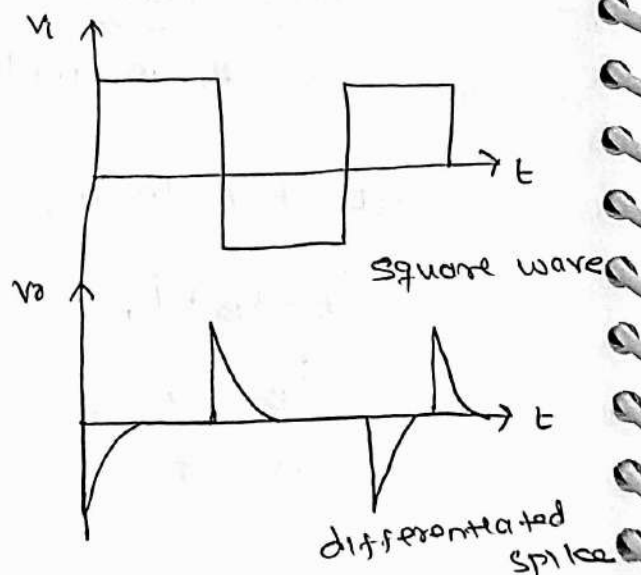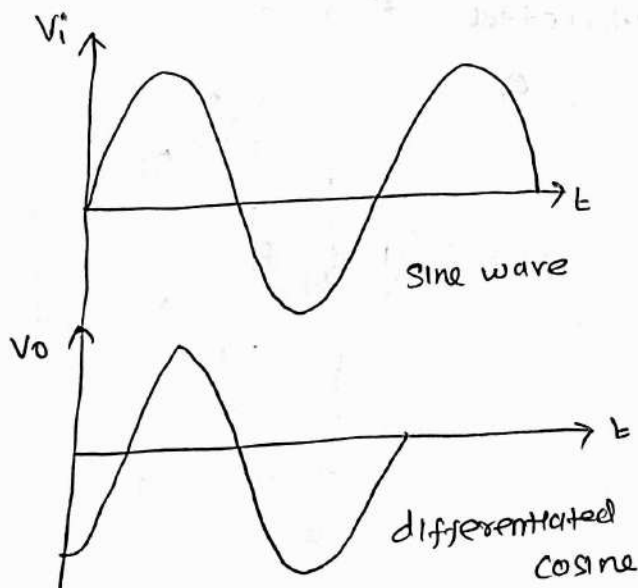

* Input noise fluctuation of small amplitude will have larger derivative, when differentiation, these signals will generate noise, resulting in poor-signal to noise ratio.

* This drawback overcome/minimized by a series resistor with input capacitor, (constant high frequency gain).

* Stability and input impedance is overcome by a small capacitor placed parallel to R_f .

Practical Differentiator

Apply KCL at node 'a',

$$\hat{i}_c = \hat{i}_{f1} + \hat{i}_{f2}$$

$$\frac{V_i - V_a}{R + X_c} = \frac{V_a - V_o}{R_f} + C_f \frac{d}{dt} (V_a - V_o)$$

WKT $V_a = V_b = 0$


$$\frac{V_i}{R + X_c} = \frac{-V_o}{R_f} - C_f \frac{dV_o}{dt}$$

Taking Laplace transform

$$\frac{V_i(s)}{R + \frac{1}{sC_1}} = \frac{-V_o(s)}{R_f} - s C_f V_o(s)$$

$$V_i(s) \frac{sC_1}{1 + sC_1R_1} = -V_o(s) \left(\frac{1}{R_f} + sC_f \right)$$
 
$$\frac{V_o(s)}{V_i(s)} = - \frac{sC_1 R_f}{(1 + sR_f C_f)(1 + sC_1 R_1)}$$



Let $R_f C_f = R_1 C_1$

$$\frac{V_o(s)}{V_i(s)} = \frac{-s R_f C_1}{(1 + s R_1 C_1)^2} = \frac{-s R_f C_1}{(1 + j f / f_c)^2} \quad f_b = \frac{1}{2\pi R_1 C_1}$$

∴ Gain increases at +20 dB/decade for $f < f_b$
decreases at -20 dB/decade for $f > f_b$

This 40 dB/decade change in gain is caused by $R_1 C_1$ & $R_f C_f$


For basic differentiator, freq. response would have increased continuously @ a rate of 20 dB/decade even beyond f_b .

$f_a < f_b < f_c$ → Gain @ high freq reduced by avoid high freq. noise and stability problem
 $f_c \rightarrow$ unity gain bandwidth

Good Differentiator $T_1 \geq R_f C_1$

Steps to design practical differentiator

 - (i) choose f_a as the highest freq of up sgl
- (ii) choose $C_1 < 1\mu F$ and calculate R_f
- (iii) choose $f_b = 10f_a$, ensure $f_a < f_b$
- (iv) calculate R_1, C_f from $R_1 C_1 = R_f C_f$
- (v) $R_{comp} = R_1 \parallel R_f$



frequency response

Application

- (i) wave shaping ckt
- (ii) convert triangular to square wave
- (iii) edge detector in FM demodulator

Integrator

↳ Output waveform is the time integral of input voltage
 "Integrating amplifiers"

Ideal Integrator

Basic inverting amplifier can be used R_f replaced by C_f .

Apply KCL @ node 'a',

$$\hat{i}_1 = \hat{i}_B + \hat{i}_f$$

\hat{i}_B is negligibly small, $\therefore \hat{i}_1 = \hat{i}_f$

$$\frac{V_i(t) - V_a(t)}{R_1} = C_f \frac{d}{dt} (V_a(t) - V_o(t))$$

$$\left[i = C \frac{dv}{dt} \right]$$

Gain (A_v) is large, $V_a(t) = V_b(t) = 0$

$$\frac{V_i(t)}{R_1} = C_f \frac{d}{dt} (-V_o(t)) \quad \left[\frac{dV_o}{dt} = -\frac{1}{R_1 C_f} V_i \right]$$


Integrate on both sides,

$$\int_0^t \frac{V_i(t)}{R_1} dt = \int_0^t C_f \frac{d}{dt} (-V_o(t)) dt$$

$$\int_0^t \frac{V_i(t)}{R_1} dt = -C_f V_o(t) + V_o(0)$$

$$V_o(t) = -\frac{1}{R_1 C_f} \int_0^t V_i(t) dt + V_o(0)$$

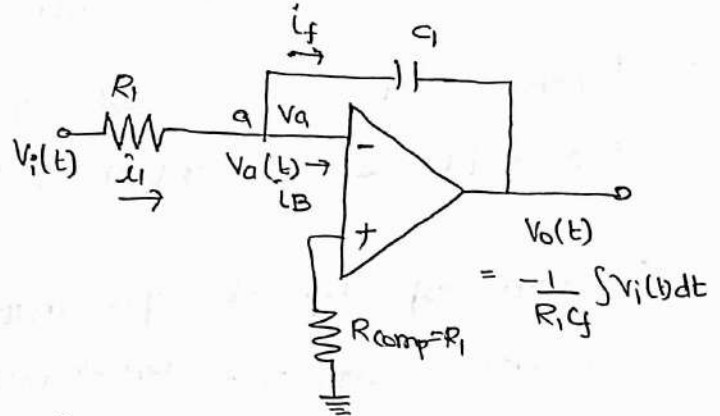$V_o(0)$ = integration constant and proportional to the value of $V_o(t)$ at $t=0$.



$\therefore V_o \propto$ Negative integral of V_i

$$V_o \propto \frac{1}{\text{time constant of } R_1 C_f}$$

* Presence of (-)ve sign so, inverting integrator.

* $R_{comp} = R_1$ connected to (+) input terminal to minimize the effect of input bias current

* Gain of ideal op-amp $= \infty$, so, time constant \rightarrow large makes perfect integration.

In frequency domain

$$V_o(s) = \frac{-1}{s R_1 C_f} V_i(s)$$

Let, $s = j\omega$ in steady state

$$V_o(j\omega) = \frac{-1}{j\omega R_1 C_f} V_i(j\omega)$$



$$|A| = \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = \left| \frac{j}{\omega R_1 C_f} \right|$$

$$= \frac{1}{\omega R_1 C_f}$$

* At $\omega = 0$, gain $= \infty$

* Capacitor acts as an open ckt, no negative feedback thus gain $= \infty$

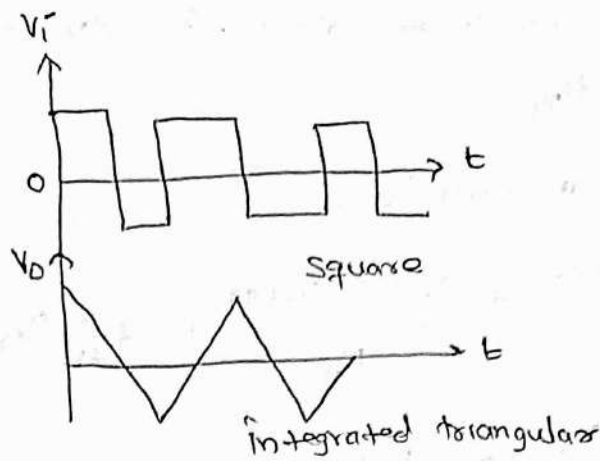 * Frequency \uparrow , gain of integrator \downarrow



- * Absences of I_p sgl, the Offset Voltage and I_B produces an error voltage @ output. o/p waveform distorted.
- * Bandwidth \rightarrow very small ; used for very small range of I_p frequency
- * Small dc offset @ input cause continuous charging of feedback capacitor that results o/p drift into +ve / -ve saturation.

Practical Integrator

* A resistor is placed in parallel with the integrator capacitor to minimize the effect of error voltage.


* Parallel combination of R_f and C_f dissipates power, called as a lossy integrator.

* Gain of integrator @ low frequency is limited to avoid any saturation problem.

$R_{comp} = R_i \parallel R_f$

$R_f \gg R_i$

$R_{comp} = R_i$

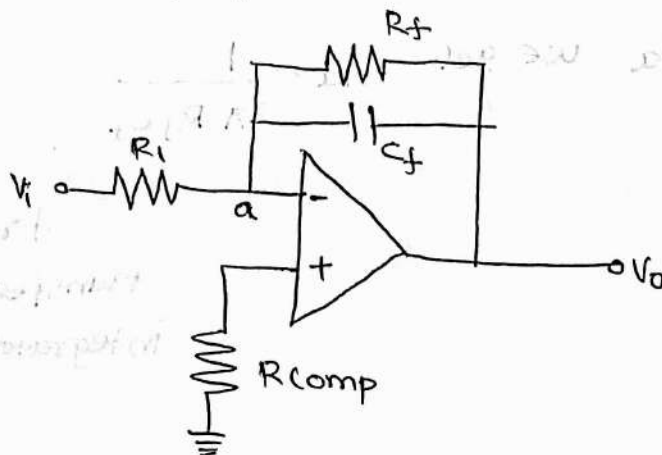

* R_f provides dc stabilization, by limiting low frequency gain to $-R_f/R_1$

Nodal eqn at node 'a',

$$\frac{V_a(s) - V_i(s)}{R_1} + \frac{V_a(s) - V_o(s)}{R_f} + sC_f \frac{d}{dt} (V_a(s) - V_o(s)) = 0$$

$$V_a(s) = 0$$

$$\frac{V_i(s)}{R_1} + \frac{V_o(s)}{R_f} + sC_f V_o(s) = 0$$

$$V_o(s) \left[\frac{1}{R_f} + sC_f \right] = -\frac{V_i(s)}{R_1}$$

$$V_o(s) = -\frac{R_f}{(1 + sC_f R_f)} \frac{V_i(s)}{R_1} = -\frac{V_i(s)}{sR_1 C_f + R_1/R_f}$$

Sub $j\omega = s$, the transfer function,

$$|A| = \left| \frac{V_o}{V_i} \right| = \frac{1}{1 - (j\omega R_1 C_f + \frac{R_1}{R_f})} = \frac{1}{\sqrt{\omega^2 R_1^2 C_f^2 + \frac{R_1^2}{R_f^2}}}$$

$$|A| = \frac{R_f/R_1}{\sqrt{1 + (\omega R_f C_f)^2}}$$

$R_f =$ Very large, lossy integrator, become ideal integrator

$$f = f_a \text{ we get } f_a = \frac{1}{2\pi R_f C_f} \quad f_b = \frac{1}{2\pi R_1 C_f}$$

↓
frequency at which the transfer function or gain of the integrator is 1 or 0 dB.


If frequency $< f_a$, then

ckt will not act as integrator, ($R_f/R_s = 3\text{dB}$)

act as simple inverting amplifier.

$f = f_a$ 50% accuracy

$f = 10 f_a$ 99% accuracy

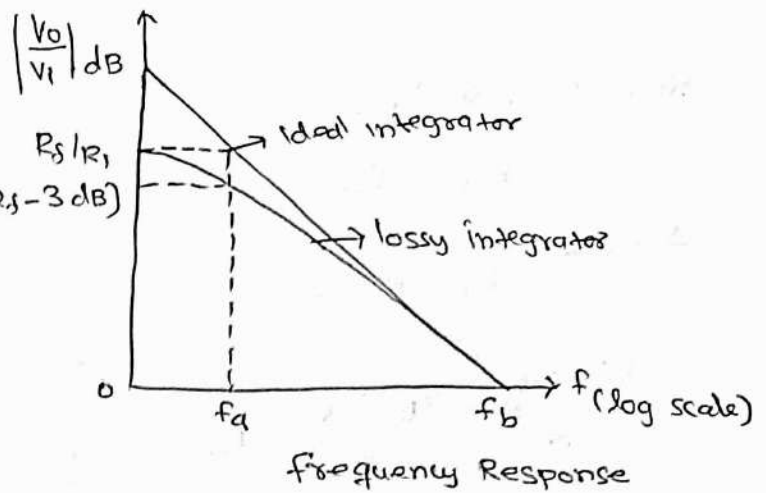


Applications

- * wave shaping ckts, ramp generator
- * convert square wave to triangular wave
- * analog to digital converter.

Voltage to Current Converter (Transconductance Amplifier)

 Converting a voltage signal to a proportional o/p current



* Input voltage: V_i

* Output current: I_L

* R_L is floating, neither side of R_L is grounded

V to I converter floating load

$$I_B \approx 0, \quad I_L = \frac{V_i}{R_i}$$

$$I_L \propto V_i$$

Proportionality constant is $1/R_i$. Hence the ckt is

called as Transconductance amplifier, also called as

Voltage Controlled Current Source (VCCS)

KCL @ node 'a',

$$I_1 + I_2 = I_L$$

Assume


$$R_f = R_1 = R$$

$$\frac{V_i - V_a}{R} + \frac{V_o - V_a}{R} = I_L$$

$$V_i - V_a + V_o - V_a = R I_L$$

$$V_i + V_o - 2V_a = R I_L$$

$$V_a = \frac{V_i + V_o - R I_L}{2}$$

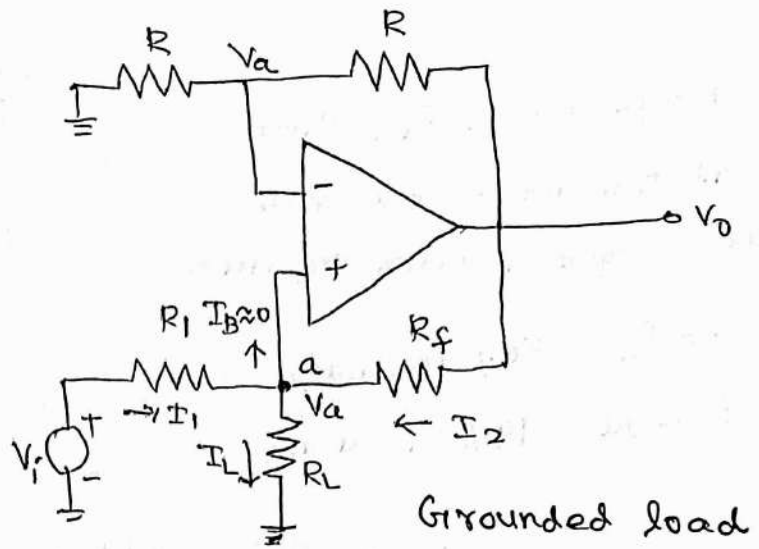

Gain of non-inverting OP-amp $1 + R/R = 2$

$$V_o = 2V_a$$

$$V_o = V_i + V_o - R I_L$$

$$I_L = \frac{V_i}{R}$$

Trans conductance (g_m) = $\frac{I_L}{V_i} = \frac{1}{R}$ called as VCCS

Application

* Input Impedance very high, draws negligible current from source. Used in low voltage voltmeters, LED and Zener testers.

Current to Voltage Converter Transresistance amplifier

Current to Voltage Converter (or) Ideal Current Controlled Voltage Source

Transresistance amplifier


* $V_o = \text{Constant } k \text{ times the magnitude of an independent Input current}$

$$V_o = k I_i$$

* V_o is independent of load connected to it

* Output current from photo devices (photo cell or photo diode) can be converted to voltage by using I-V converter

 * In this circuit due to virtual ground $V_b = V_a = 0$,
current through $R_i = 0$
 I_i flows through R_f



$$I_i = \frac{V_a - V_o}{R} = -\frac{V_o}{R}$$

$$V_o = -I_i R$$


* To reduce the high frequency and oscillations, a capacitor C_f is connected across R_f

* I_i has return path to ground

$$V_i = I_i R_i$$

$$V_o = \left[1 + \frac{R_f}{R_i} \right] V_i$$
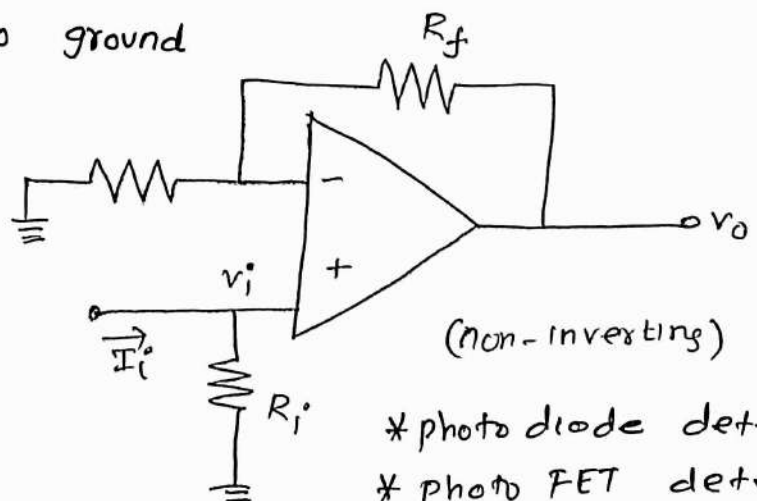
$$V_o = \left[1 + \frac{R_f}{R_i} \right] I_i R_i$$



* photo diode detector
* photo FET detector

* Determine the output voltage of a differential amplifier for the input voltage $300 \mu\text{V}$ and $240 \mu\text{V}$. The differential gain is 5000 and the value of CMRR is 100 and 10^5

$$V_1 = 300 \mu\text{V} \quad V_2 = 240 \mu\text{V} \quad A_d = 5000$$

$$V_o = A_d V_d + A_c V_c$$

$$V_d = (300 - 240) \mu\text{V} = 60 \mu\text{V}$$

$$V_c = \frac{V_1 + V_2}{2} = \frac{300 + 240}{2} = 270 \mu\text{V}$$

$$\text{CMRR} = \frac{A_d}{A_c}$$

$$(i) \quad 100 = \frac{5000}{A_c}$$

$$\therefore A_c = 50$$


$$V_o = (5000 \times 60) + (50 \times 270) \\ = 313500 \mu\text{V} = 313.5 \text{ mV}$$

$$(ii) \quad 10^5 = \frac{5000}{A_c}$$

$$A_c = 0.05$$

$$V_o = (5000 \times 60) + (0.05 \times 270) \\ = 300.0135 \text{ mV}$$

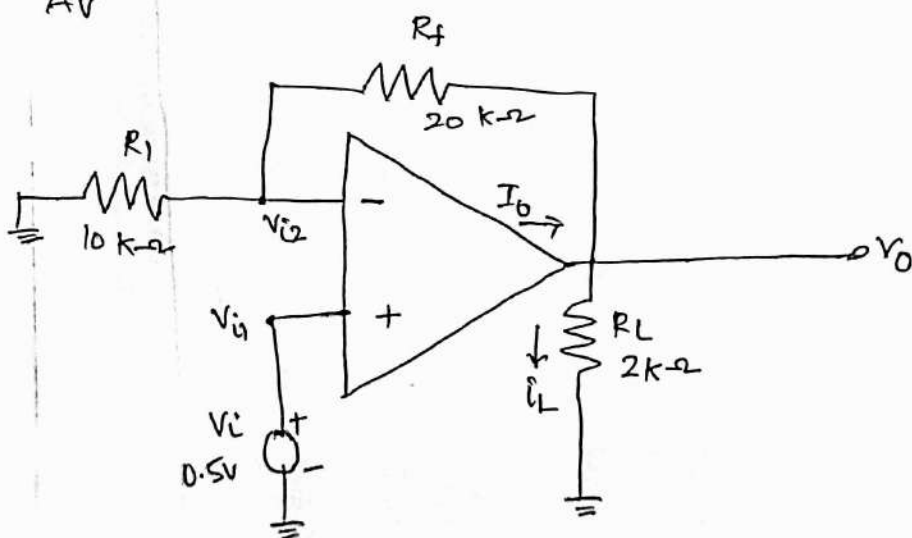* For the given non-inverting amplifier, determine V_o , I_L , I_o and A_v



$$V_o = \left[1 + \frac{R_f}{R_i} \right] V_i$$

$$= \left[1 + \frac{20 \times 10^3}{10 \times 10^3} \right] 0.5$$

$$\boxed{V_o = 1.5 \text{ volt}}$$

$$A_v = \frac{V_o}{V_i}$$

$$= \frac{1.5}{0.5}$$

$$\boxed{A_v = 3}$$

$$i_L = \frac{V_o}{R_L} = \frac{1.5}{2 \times 10^3} = 7.5 \times 10^{-4}$$

$$= \frac{15 \times 10^{-1}}{2 \times 10^3} = \boxed{0.75 \text{ mA} = i_L}$$

$$i_o = i_1 + i_L$$

$$i_1 = \frac{V_o - V_i}{R_f} = \frac{1.5 - 0.5}{2 \times 10^3} = \boxed{0.5 \text{ mA} = i_1}$$

$$i_o = 0.75 \text{ mA} + 0.5 \text{ mA}$$
$$= i_1 + i_L$$

$$\boxed{i_o = 1.25 \text{ mA}}$$