


## Unit - 4

555Timer!Introduction:

- The 555 Timer is a highly stable device for generating accurate time delay or oscillation.
- It contains two 555 timers & is a 14 Pin DIP.
- Supply voltage is +5V to +18V & can drive load upto 200mA.

Applications:-


- oscillator
- pulse generator
- ramp & square wave generator
- mono-shot multivibrator
- traffic light control
- voltage monitor

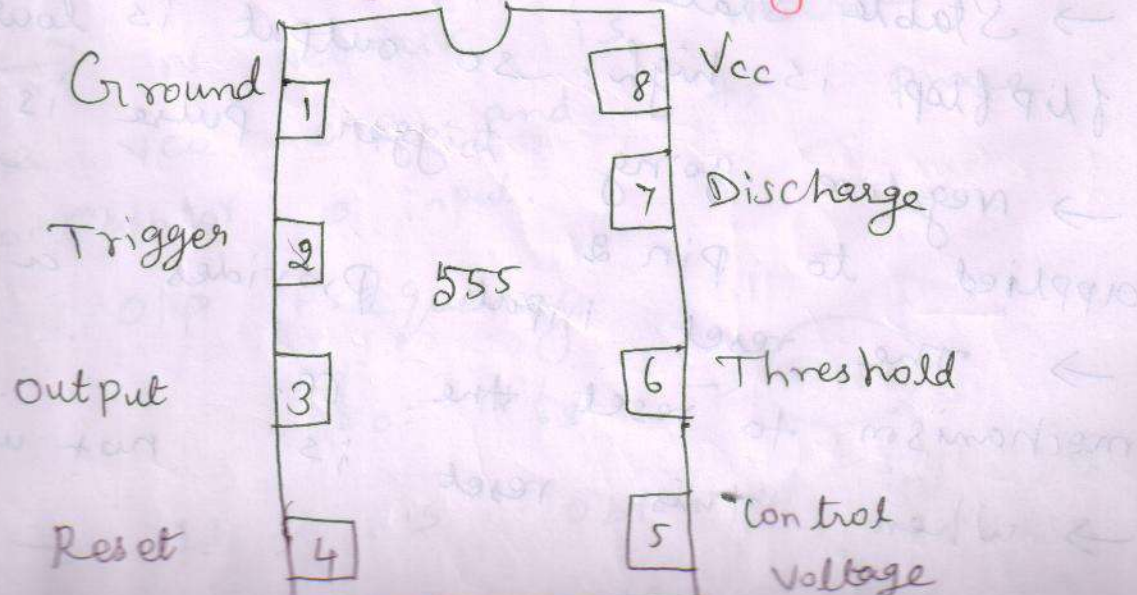8 Pin Package



## functional Diagram

STUDENTSFOCUS.COM

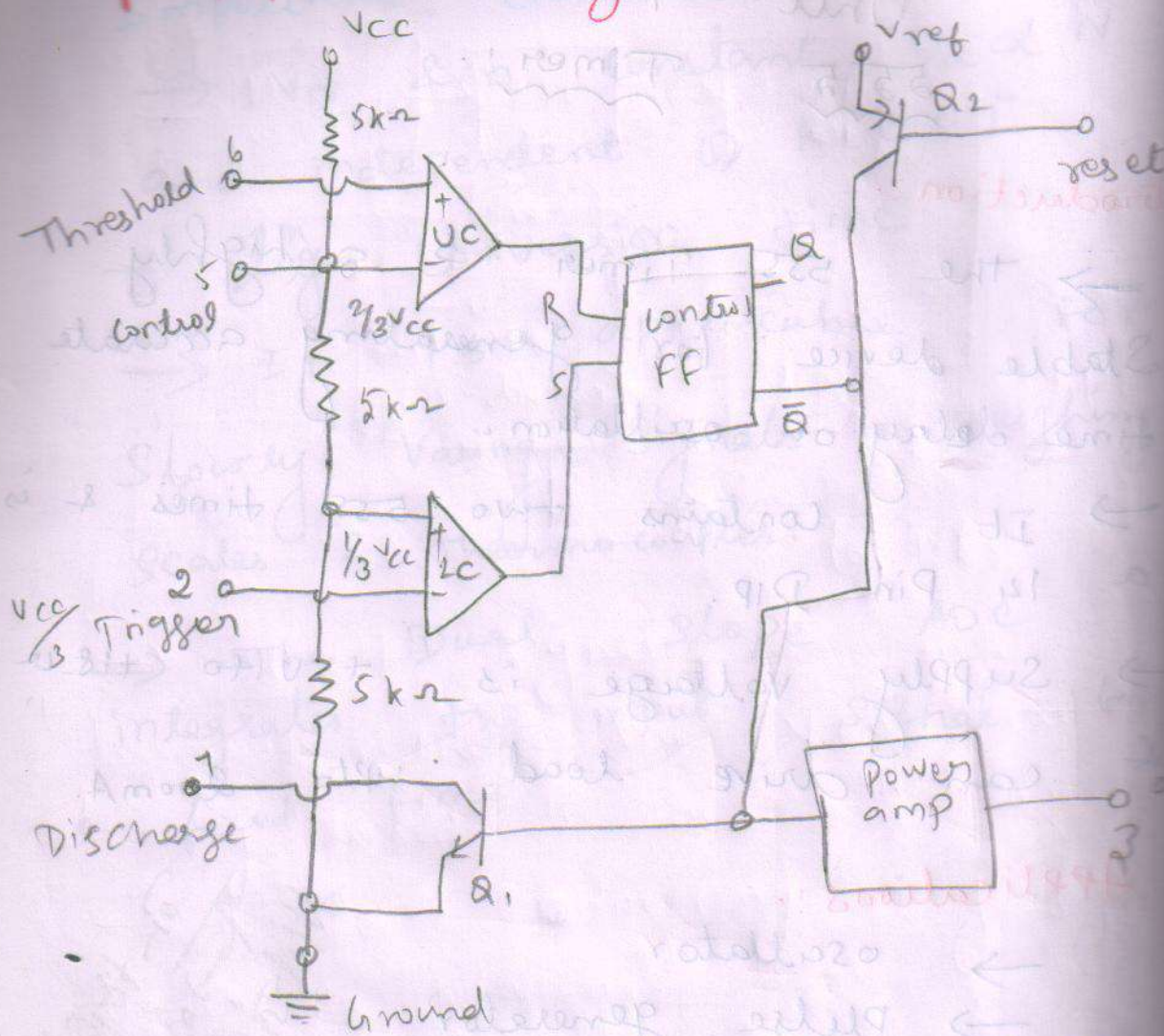

→ Three  $5k\Omega$  internal resistors act as voltage divider,

→ Upper comparator  $\frac{2}{3}V_{cc}$

→ Lower comparator  $\frac{1}{3}V_{cc}$

→ Stable state, O/P  $\bar{Q}$  is the control flip flop is high, so output is low

→ negative going trigger pulse is applied to pin 2

→ The reset input provides a mechanism to reset the FF.

→ When this reset is not used



returned to  $V_{CC}$ .

→ The transistor  $Q_2$  is driven by an internal ref voltage  $V_{ref}$  obtained from supply voltage  $V_{CC}$ .

**PLL**

**Applications**

→ Output from a PLL can be obtained either as the voltage signal  $V_c(t)$  to the error voltage in the f/b loop.

Some typical applications of PLL are.

- 1) Frequency Multiplication / Division
- 2) Frequency translation
- 3) FM Demodulation
- 4) Frequency shift keying Demodulation.

1) Frequency Multiplication / Division

→  $N$  Netublx is inserted b/w the VCO o/p and the phase comparator input.


o/p frequency

$$f_o = N f_s \rightarrow (9.42)$$

→ It is obtained in its



# Frequency multiplier using IC PLL

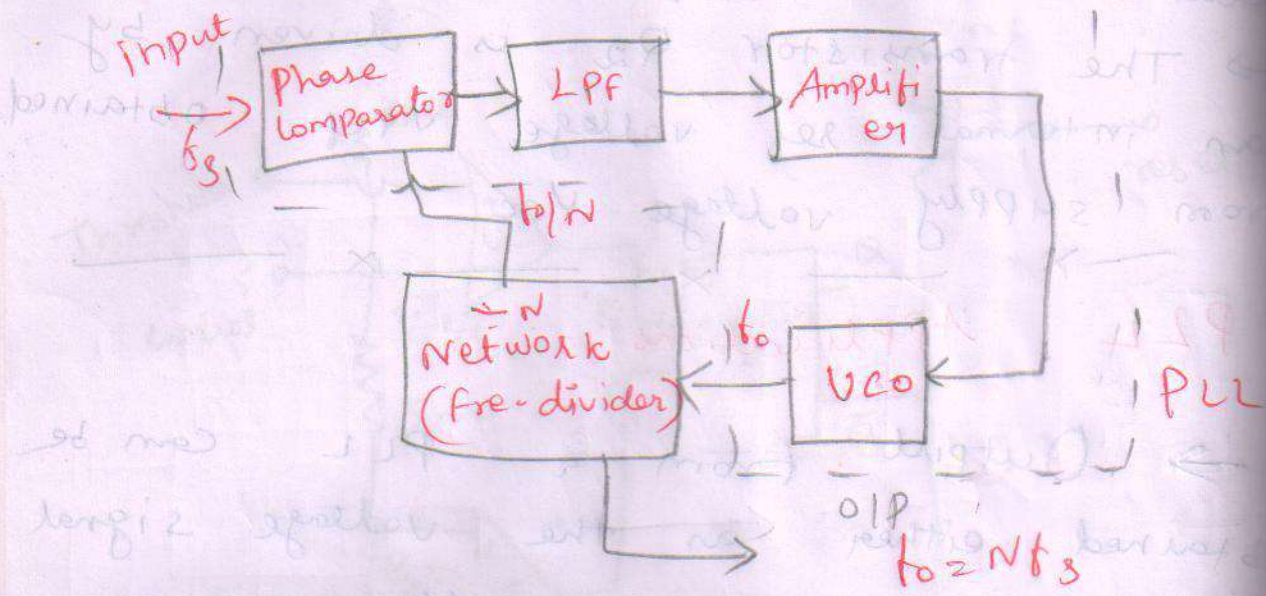

→ If the PLL signal is rich in harmonics, then the VCO can be directly locked to the  $n$ th harmonic.

→ without connecting any frequency divider in between.

→ This PLL circuit is used for frequency division.

The output  $f_o$  of VCO is given by  $f_o = \frac{f_n}{m}$ .

## Frequency Translation:

→ The low pass filter & multiplier are connected externally to the PLL.




→  $f_s$  has to be shifted to the VCO and applied as inputs to the mixer.

→ when PLL is a locked state,

$$f_o - f_s = f_1$$

$$f_o = f_s + f_1$$

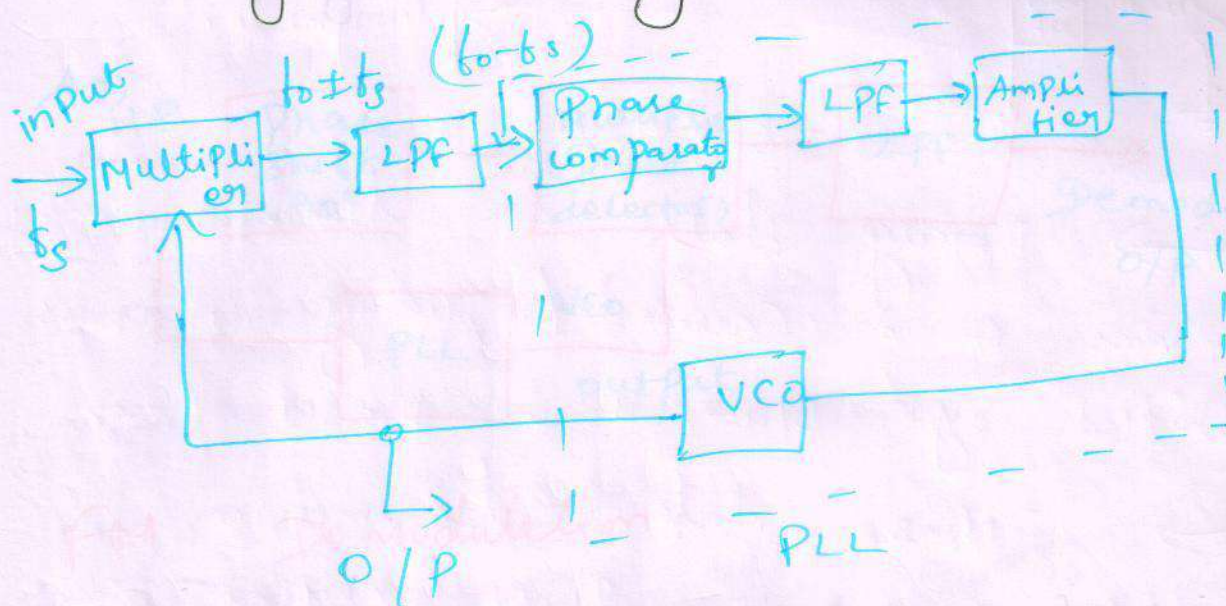it is possible to shift the incoming frequency  $f_s$  by  $f_1$



PLL used as a frequency translator.

### AM Modulation:

→ PLL is locked to the carrier frequency of the incoming AM signal


→ VCO o/p is same frequency as the carrier, but unmodulated



→ VCO o/p is always  $90^\circ$  phase before fed to multiplier.

→ The o/p of multiplier contains both the sum & difference signals.

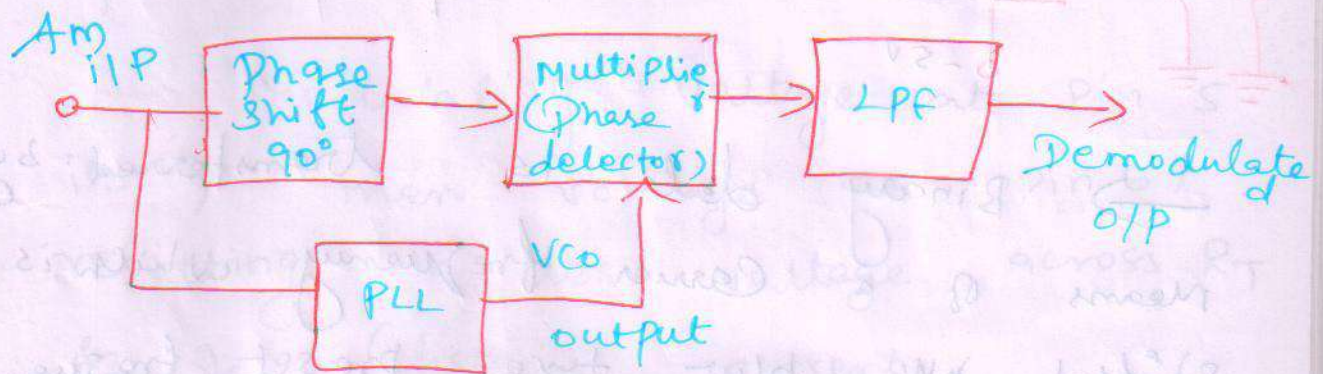→ The PLL AM detector exhibits a high degree of selectivity & noise immunity.



## FM Demodulation:

→ If PLL is locked to a FM signal, the VCO tracks the instantaneous frequency of the input.


→ Filtered error voltage which controls the VCO & maintains lock with the input signal.

→ VCO used in PLL is highly linear, it is possible to realize highly linear FM demodulators.



# Frequency Shift Keying FSK

## Demodulator :-

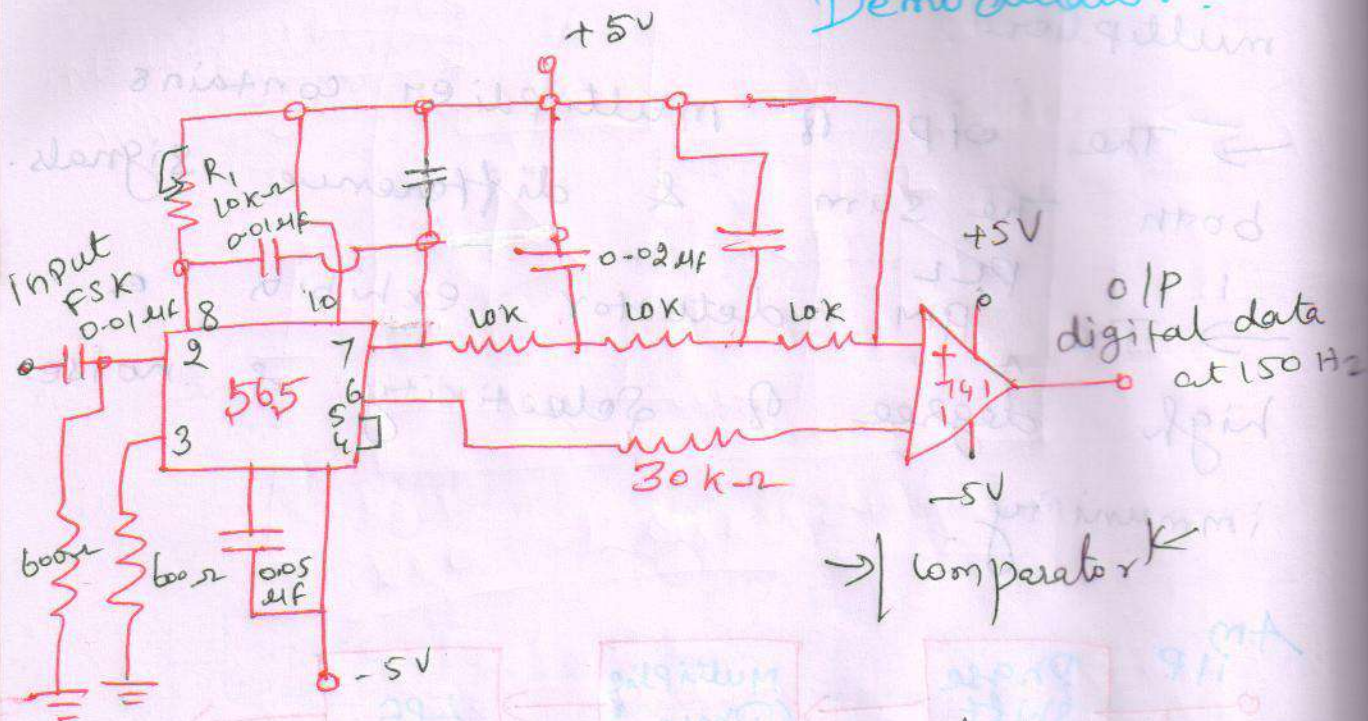

Binary data is transferred by means of a carrier frequency which is shifted by two preset frequencies.

This data transmission is called frequency shift keying technique.

### Use :-

The 567 PLL is very useful as FSK demodulator.

A three stage filter removes the carrier component and the o/p signal is made logic compatible by a voltage comparator.



# Voltage

Controlled


Oscillator (VCO)

→ Common type of VCO available in IC form is Signetics NE/SE66.


→  $C_T$  is charged or discharged by a constant current source/sink.

→ Amount of current is controlled by changing  $V_c$  at the Modulating input.

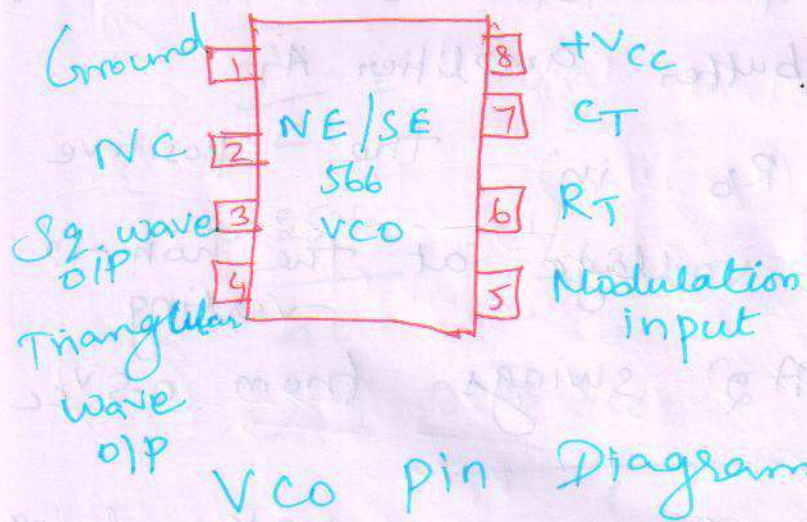→ Modulating voltage at Pin 5 is  $\uparrow$  then voltage at Pin 6  $\uparrow$  resulting in less voltage across  $R_T$  &  $\downarrow$  Charging current.





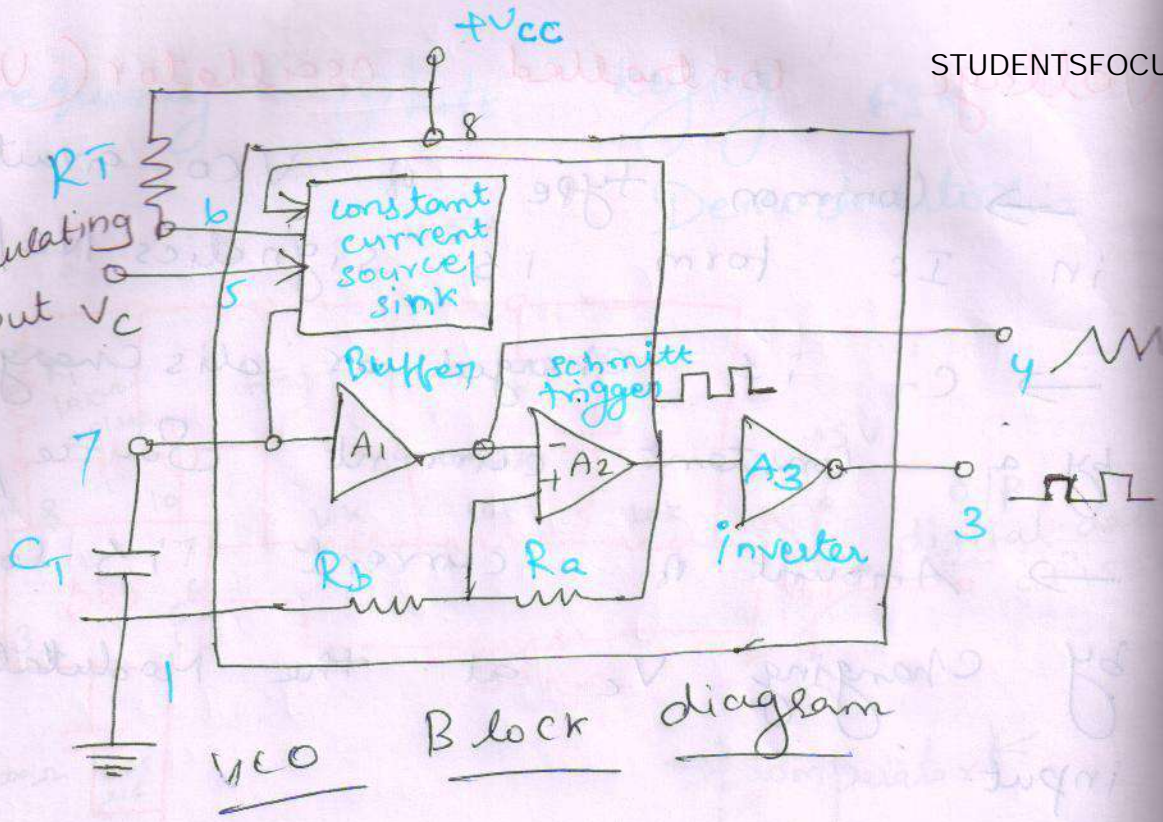

VCO Block diagram

→ It is used in converting low frequency signals such as EEGs, EKG into an audio frequency range


→ Voltage across  $C_T$  is applied to the inverting input terminal Schmitt trigger  $A_2$  via buffer amplifier  $A_1$

→ If  $R_a = R_b$  in the positive feedback loop, the voltage at the non-inverting terminal of  $A_2$  swings from  $0.5V_{cc}$  to  $0.25V_{cc}$ .

→ Voltage across  $C_T$  exceeds  $0.5V_{cc}$  during charging, the output of the Schmitt trigger goes Low.



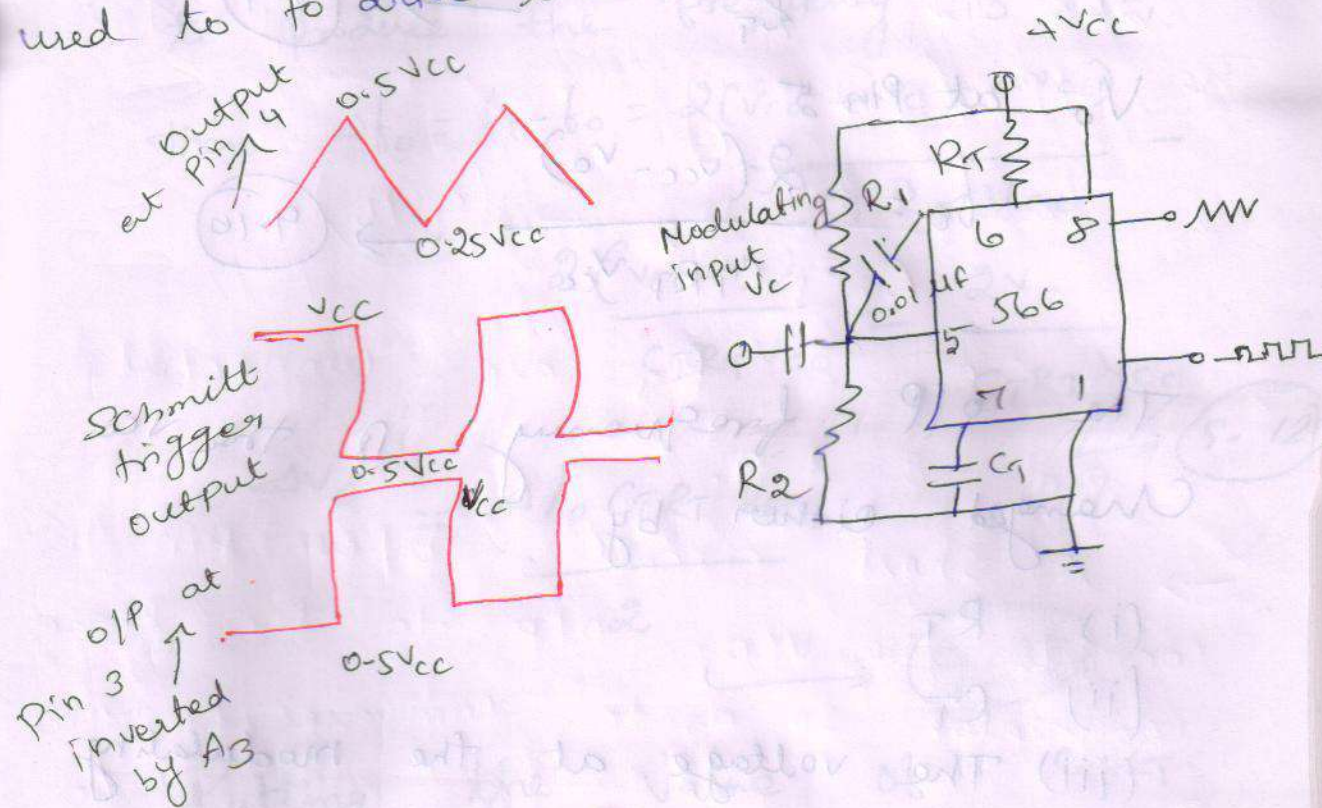→ Inverter  $A_3$  is a current Amplifier used to drive the load.



→ Total voltage across the capacitor changes from  $0.25V_{cc}$  to  $0.5V_{cc}$ . Thus  $\Delta V = 0.25V_{cc}$ .

$$\frac{\Delta V}{\Delta t} = \frac{i}{C_T}$$

$$\frac{0.25V_{cc}}{\Delta t} = \frac{i}{C_T}$$

$$\Delta t = \frac{0.25V_{cc} C_T}{i} \rightarrow 9.8$$

The frequency of oscillator  $f_0$  is

$$f_0 = \frac{1}{T} = \frac{1}{2\Delta t} = \frac{i}{0.5V_{cc} C_T}$$



$$i = \frac{V_{CC} - V_c}{R_T} \rightarrow (9.9)$$

$V_o$  at Pin 5

$$f_o = \frac{2(V_{CC} - V_o)}{C_T R_T V_{CC}} \rightarrow (9.10)$$

The o/p frequency of the VCO changed either by

(i)  $R_T$

(ii)  $C_T$

(iii) The voltage at the modulating input terminal Pin 5.

→ Now Modulating input voltage is usually varied from  $0.75 V_{CC}$  to  $V_{CC}$

→ It can produce a frequency variation of about 10 to 1.

$$f_o = \frac{2(V_{CC} - (7/8)V_{CC})}{C_T R_T V_{CC}} = \frac{1}{4R_T C_T}$$

$$= \frac{0.25}{R_T C_T} \rightarrow (9.11)$$

Voltage to Frequency Conversion factor:-

→  $k_v$  is defined as

$$k_v = \frac{\Delta f_o}{\Delta V_o}$$



## MonoStable operation:-

→ stand by state, FF holds transistor  $Q_1$  on, thus clamping the external timing capacitor  $C$  to ground.

→  $Q_1 = 0$  then  $Q_1$  off

→ The upper comparator resets the FF,

$$R = 1, S = 0.$$


The voltage across the capacitor,

$$V_c = V_{cc} (1 - e^{-t/RC})$$

$$V_c = \frac{2}{3} V_{cc}$$

$$T = RC \ln \frac{4}{3}$$

$$T = 1.1 RC \text{ (Sec) .}$$

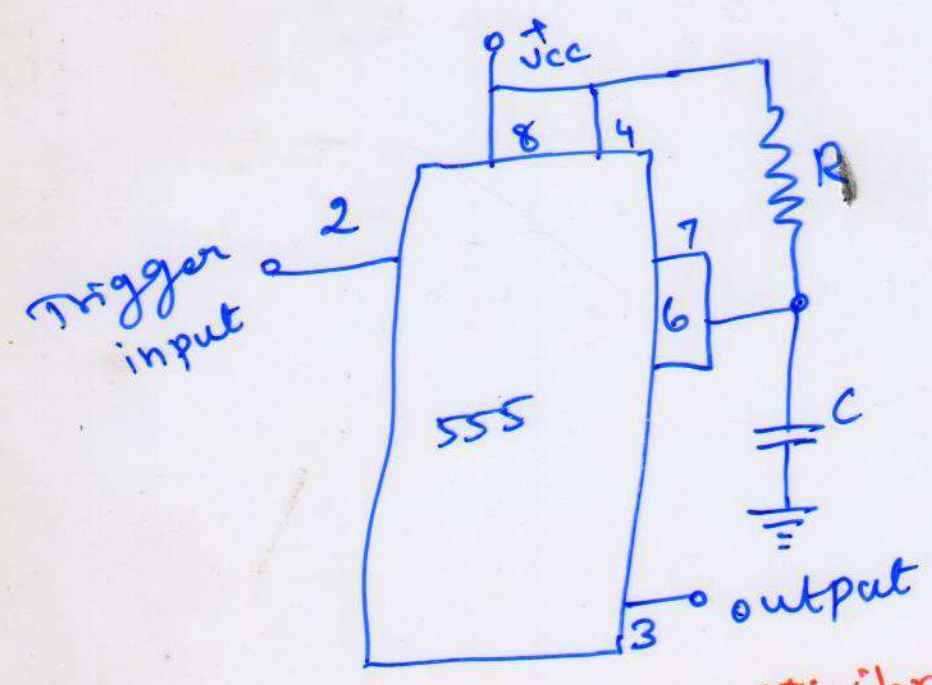

Mono stable multivibrator



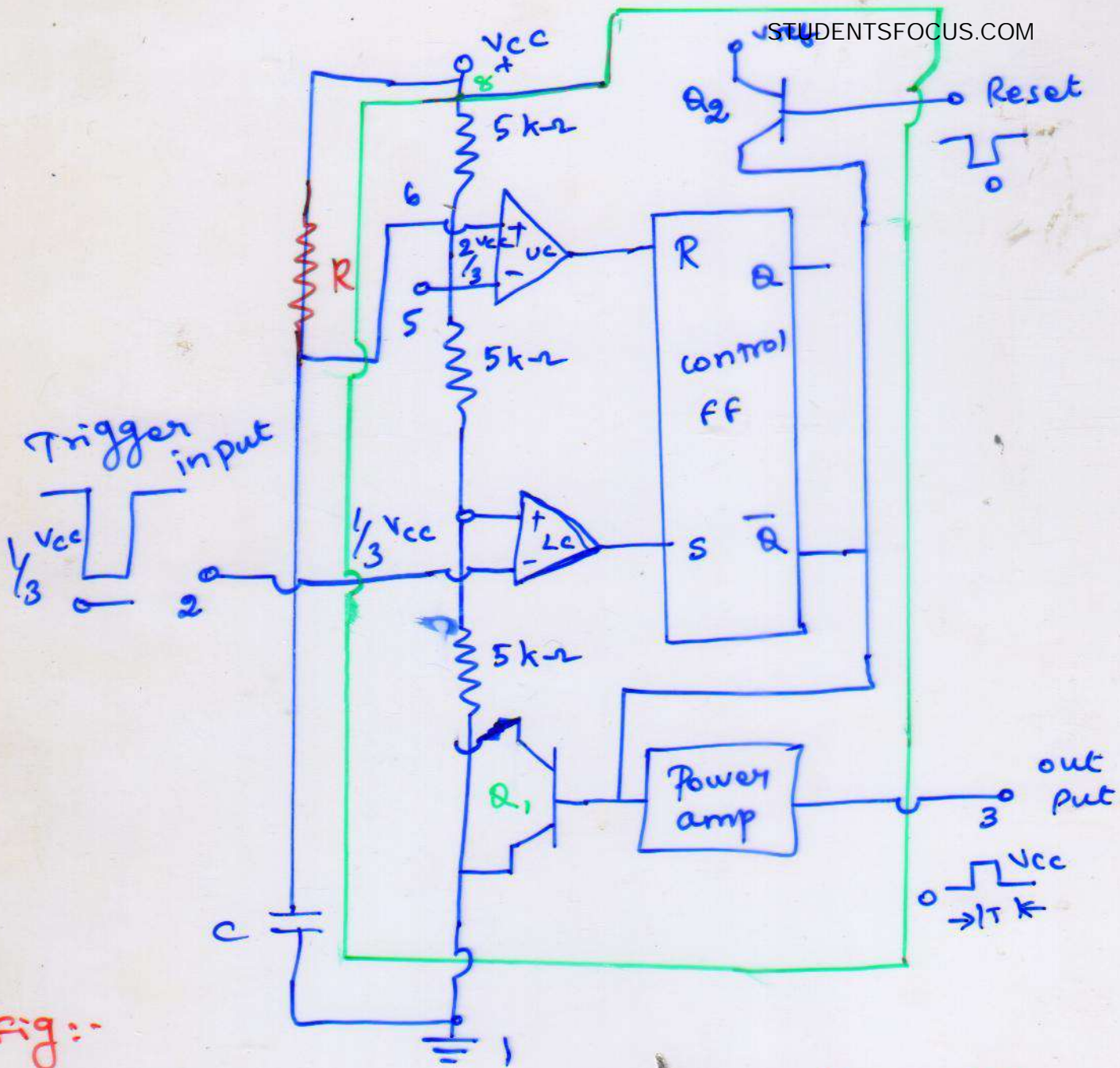


Fig:-

Time in monostable operation with  
functional diagram



→ Timing interval is independent of supply voltage.

→ It is once trigger, the o/p remains in the high state until time T elapse. which depends on R & C.



→ The negative reset pulse is applied to the reset terminal,  $Q_2$  goes off,  $Q_1$  on, capacitor  $C$  is immediately discharged.

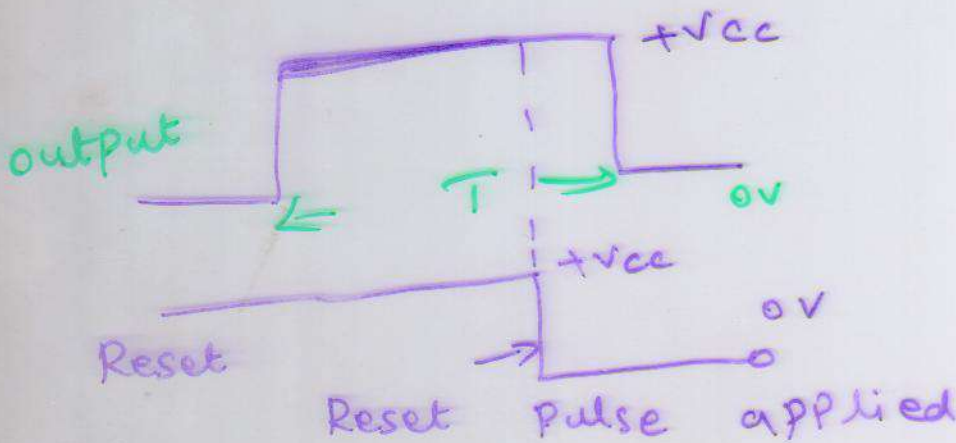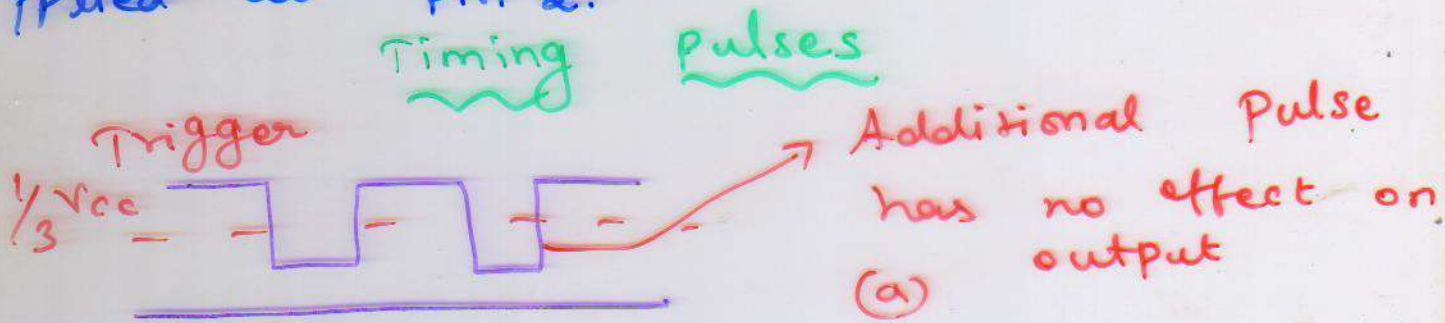→ If reset is released, the o/p will still remain low until a negative going trigger pulse is again applied at Pin 2.






## Applications of 555 Timer :-


STUDENTSFOCUS.COM
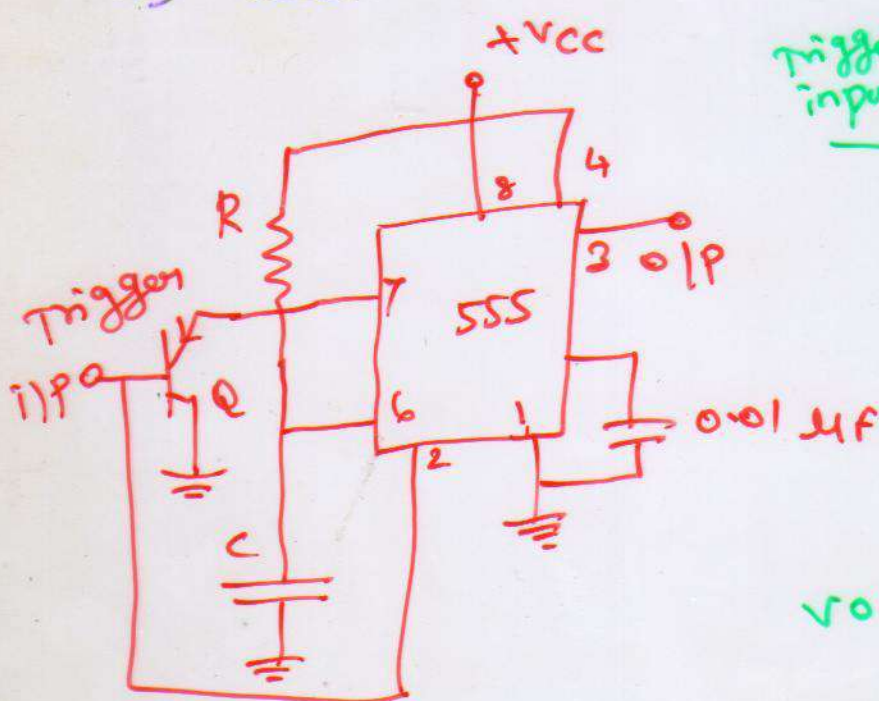
## Missing pulse detector :-

- The input trigger is low, the emitter diode of the transistor Q is forward biased.
- C gets clamped to few tenths of a volt  $\sim 0.7V$
- Output of timer goes high.
- If a pulse misses, the trigger I/P is high & Q is cut off
- Timer enters into normal state of monostable operation.
- used to detect missing heart beat.



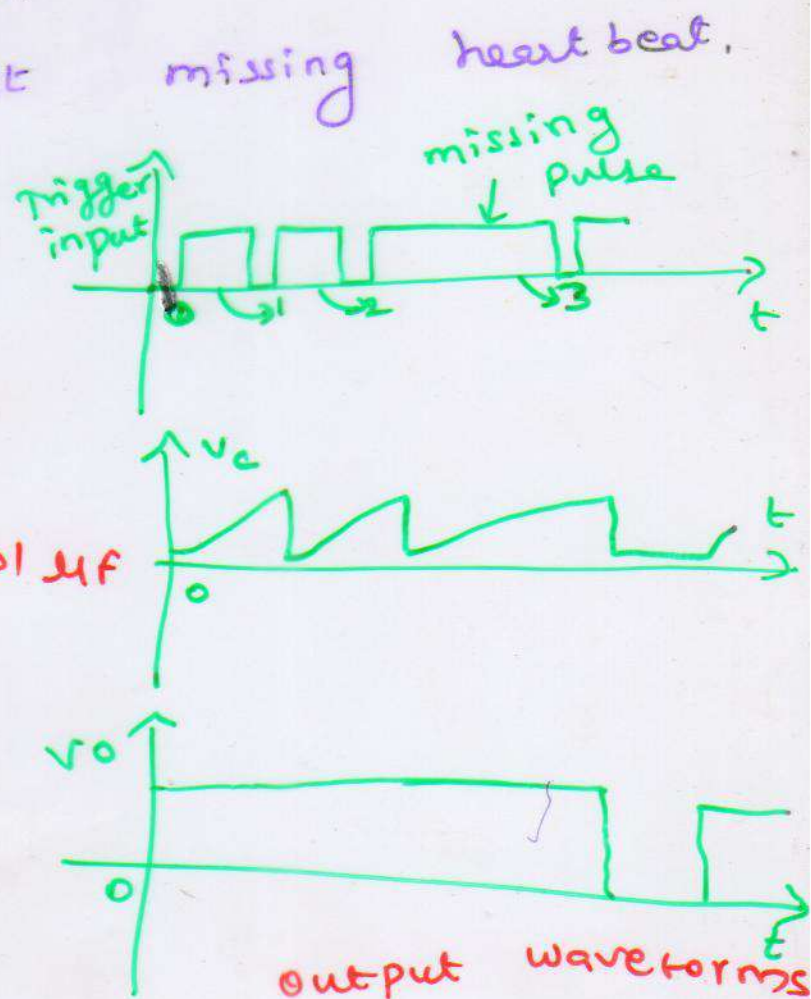Missing pulse detector  
monostable  
circuit



output waveforms



## Linear Ramp Generator:-

→ In linear ramp generator, the resistor  $R$  of the Monostable circuit is replaced by constant current source.

The capacitor voltage

$$V_c = \frac{1}{C} \int_0^t i dt \quad \rightarrow (8.3)$$

KVL law

$$\frac{R_1}{R_1 + R_2} V_{cc} - V_{BE} = (\beta + 1) I_B R_E \approx \beta I_B R_E \\ = I_C R_E = i R_E \quad \rightarrow (8.4)$$

$I_B, I_C \rightarrow$  base, collector currents  
 $\beta \rightarrow$  current amplification factor.

So

$$i = \frac{R_1 V_{cc} - V_{BE} (R_1 + R_2)}{R_E (R_1 + R_2)} \quad \rightarrow (8.5)$$

Putting the value of current 'i'

$$V_c = \frac{R_1 V_{cc} - V_{BE} (R_1 + R_2)}{C R_E (R_1 + R_2)} \times t \quad (8.6)$$


$$t = T \quad V_c = \frac{2}{3} V_{cc}$$



$$\frac{2}{3} V_{CC} = \frac{R_1 V_{CC} - V_{BE} (R_1 + R_2)}{R_E (R_1 + R_2) C} \times T \rightarrow (8.7)$$

$$T = \frac{\frac{2}{3} V_{CC} R_E (R_1 + R_2) C}{R_1 V_{CC} - V_{BE} (R_1 + R_2)} \rightarrow (8.8)$$

o/p waveforms

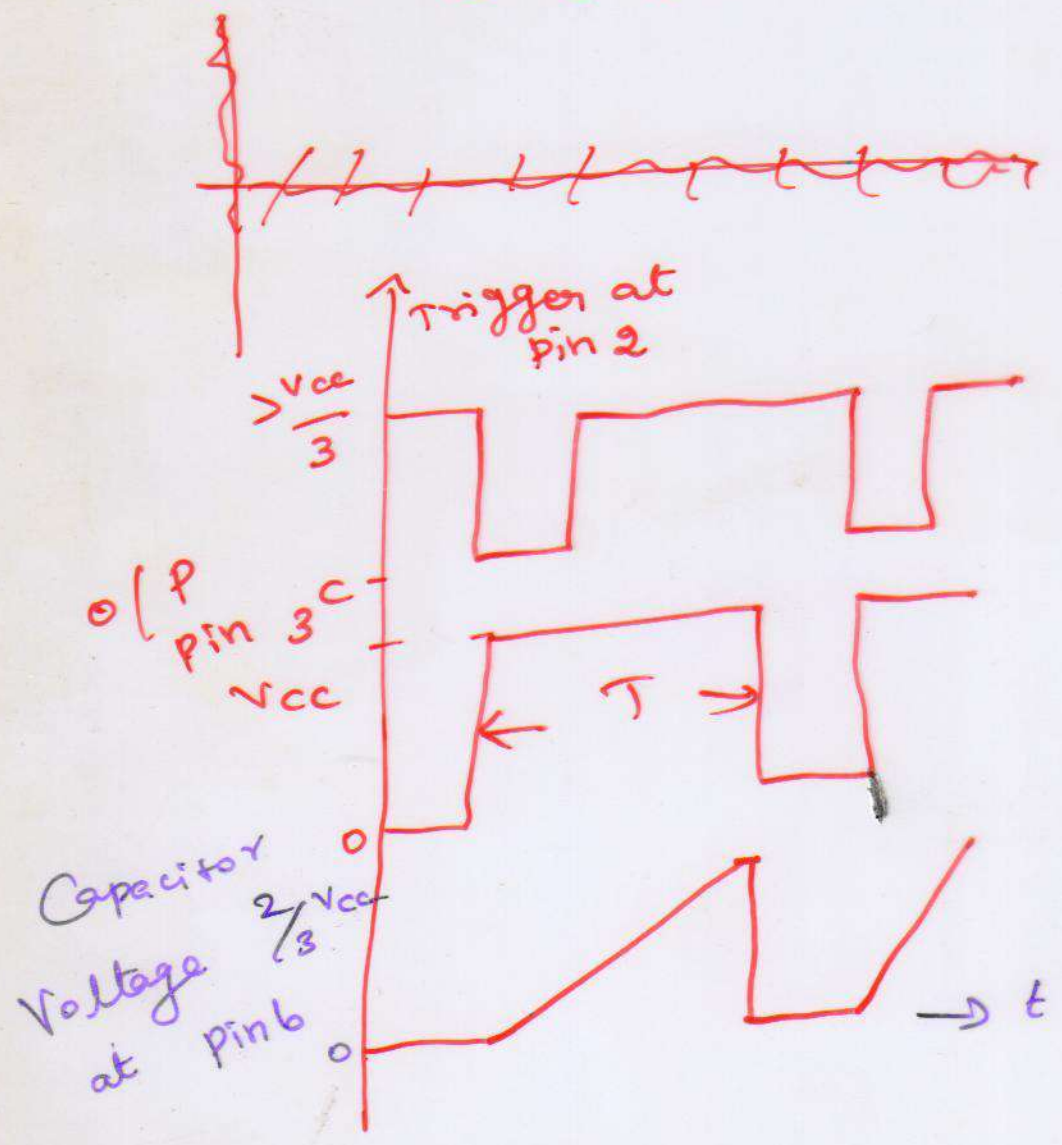


Frequency divider :-

→ Continuously triggered monostable circuit & triggered by a square wave generator.



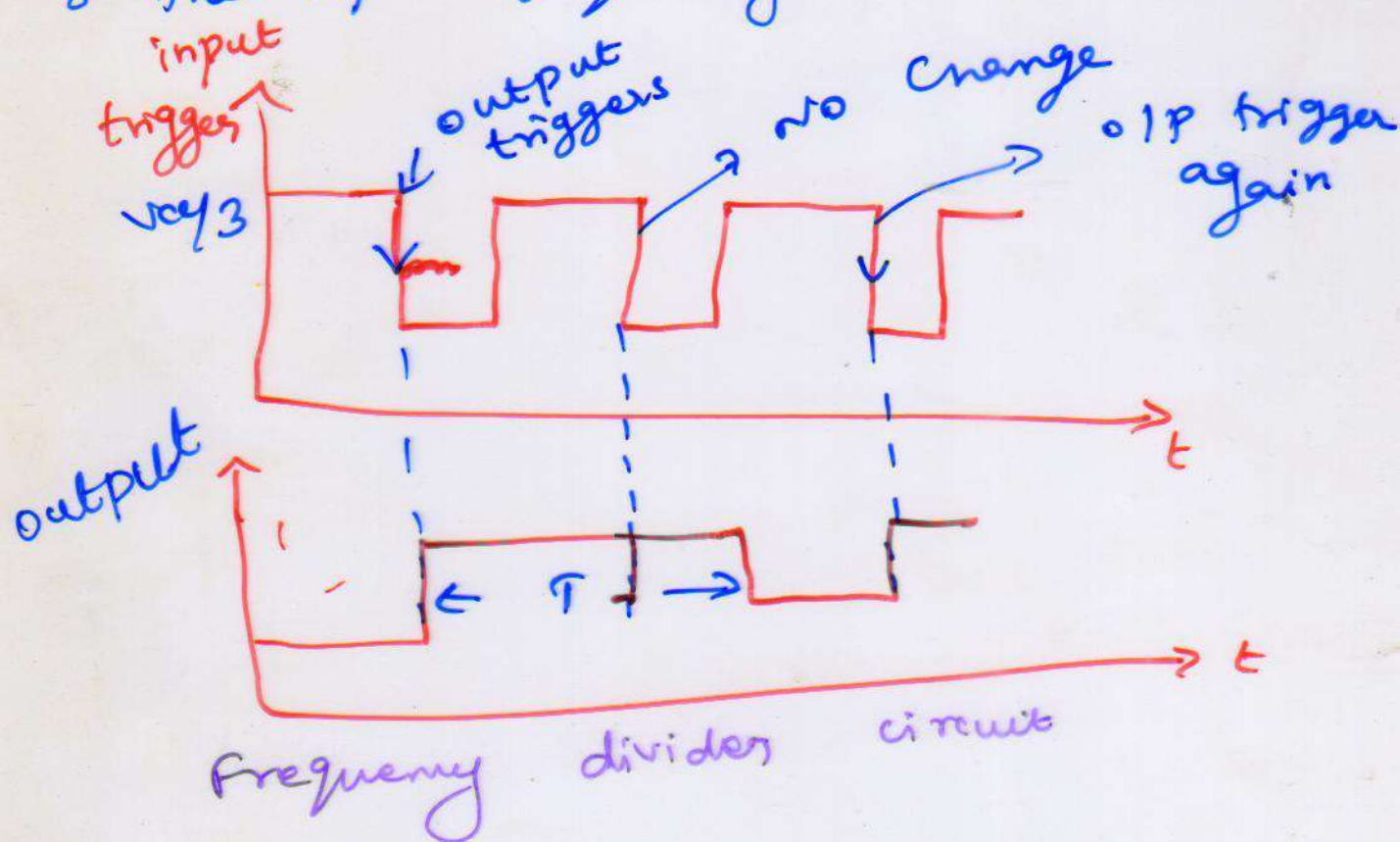
- i/p first '-' going edge then o/p will remain high
- o/p can be made integral fractions of the input frequency


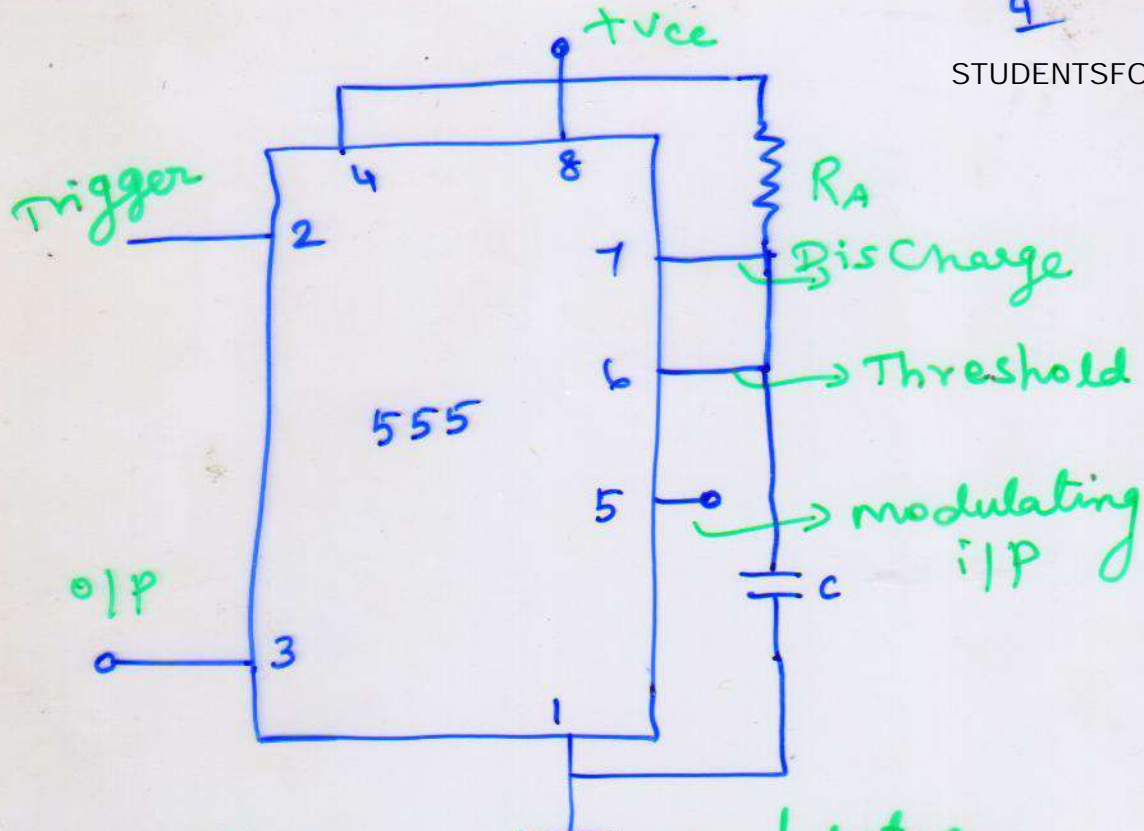
### Pulse width Modulation:-

- Modulating i/p signal applied at pin 5.
- This signal superimposed upon the already existing voltage  $\frac{2}{3}V_{cc}$
- In output waveform that the pulse duration, the duty cycle only varied keeping the frequency same.






Pulse width Modulator

Modulating input

Output

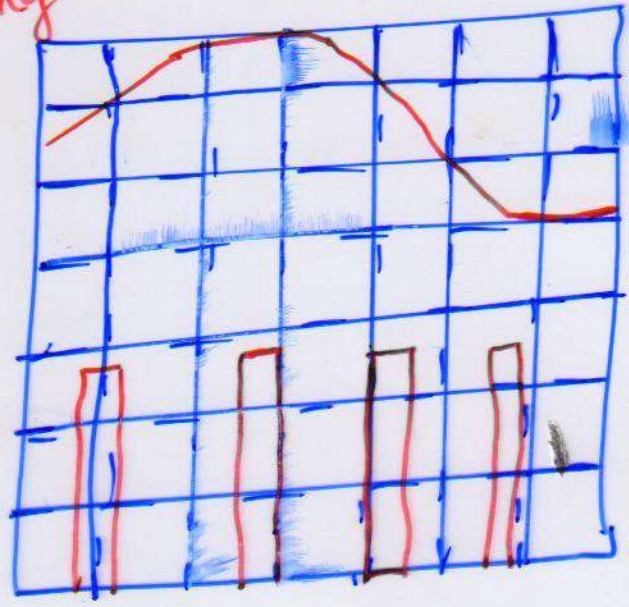



$\Delta V_c \Rightarrow$  Modulation voltage  
to produce the frequency is  $f_1$ ,

$$\text{then } \Delta f_0 = f_1 - f_0 = \frac{2(V_{CC} - V_c + \Delta V_c)}{C_T R_T V_{CC}}$$

$$\frac{2(V_{CC} - V_c)}{C_T R_T V_{CC}} = \frac{2V_c}{C_T R_T V_{CC}}$$

$$\Delta V_c = \frac{\Delta f_0 C_T R_T V_{CC}}{2}$$

$$\rightarrow (9.12)$$

Putting the value of  $C_T R_T$

$$\Delta V_c = \Delta f_0 V_{CC} / 8 f_0 \rightarrow (9.14)$$

$$k_v = \frac{\Delta f_0}{\Delta V_c} = \frac{8 f_0}{V_{CC}} \rightarrow 9.15$$

Monolithic Phase locked loop :-

$\rightarrow$  Different building blocks of PLL are available,

$\rightarrow$  Some important monolithic PLLs, are SE / NE 560 Series introduced by Signetics & LM560 series by National Semi Conductor.



## IC PLL 565 :-


565 is a 14 Pin DIP Package.

The o/p frequency

$$f_o = \frac{0.25}{C_T R_T} \text{ Hz} \rightarrow \textcircled{9.16}$$

→ Where  $C_T$  &  $R_T$  are connected to pin 8 & 9.

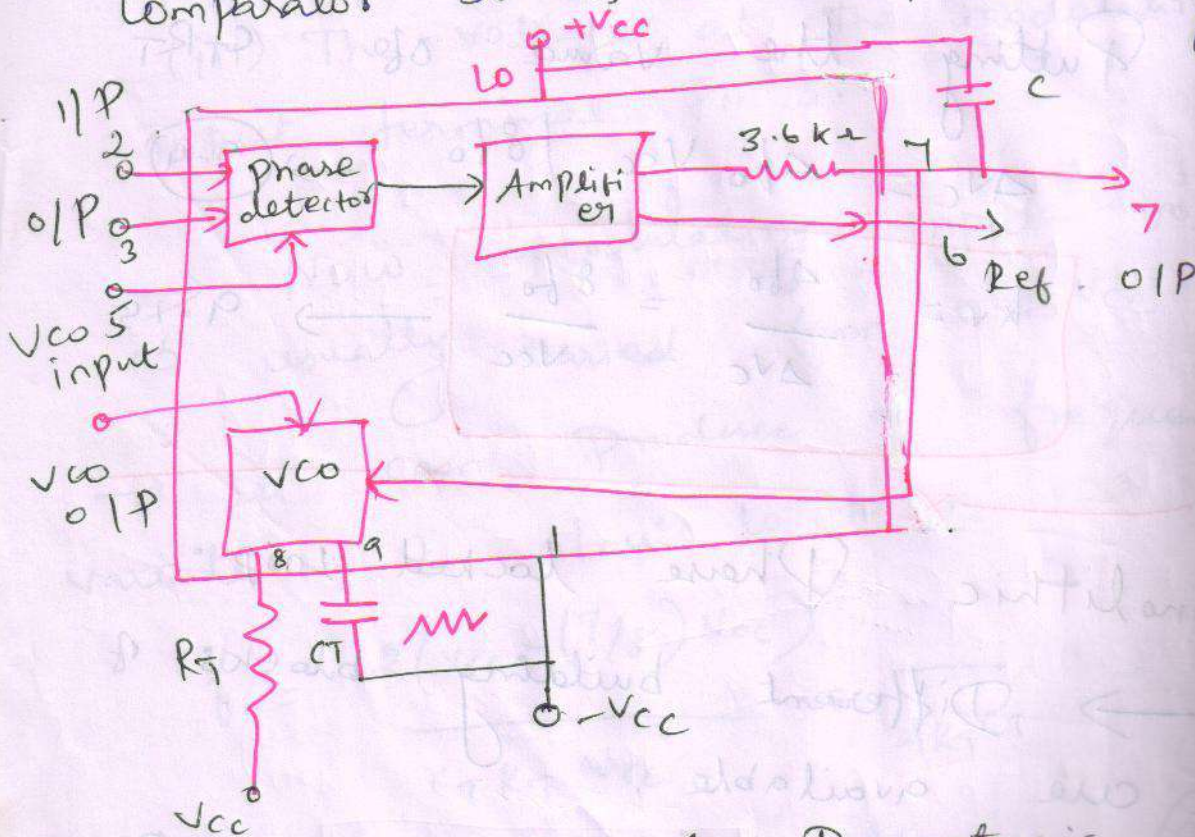→ A short circuit blue pin 4 connects the VCO o/p to the Phase Comparator so as to compare to with  $f_s$ .



Important electrical Parameters :-

Operating frequency range: 0.001 Hz to 500 kHz

Operating voltage range:  $\pm 6V$  to  $\pm 12V$

Output level: 10mV rms min to 3V rms



O/P sink voltage

current : 1 mA

Input impedance : 10 k $\Omega$ Drift in VCO  
Center frequency } : 300 ppm/ $^{\circ}$ CDrift in VCO centre  
frequency with supply  
voltage } : 1.5 Per cent/V MAXTriangle wave  
amplitude : 2.4 V<sub>pp</sub> at  $\pm 6$  VTriangle wave amplitude : 5.4 V<sub>pp</sub> at  $\pm 6$  VBandwidth adjustment  
range :  $\pm 1$  to  $\pm 60$ %

Derivation of lock in range :-

If  $\phi$  radians is the Phase difference b/w the signal & VCO, then the O/P voltage of the analog Phase detector

$$V_e = k_{\phi} (\phi - \pi/2) \rightarrow (9.18)$$

$k_{\phi} \rightarrow$  angle to voltage transient efficient

$$V_c = A k_{\phi} (\phi - \pi/2) \rightarrow (9.19)$$

$$f = f_0 + k_v V_c \rightarrow (9.20)$$

$k_v \rightarrow$  is the voltage to frequency transfer coefficient.

$$f = f_s = f_0 + k_v V_c \rightarrow (9.21)$$



Maximum o/p voltage magnitude available from the phase detector occurs for  $\phi = \pi$  &  $0$  radians,

$$V_{e(\max)} = \pm k_{\phi} A^{1/2}$$

$$V_{CO} = \pm (\pi/2) k_{\phi} A \rightarrow (9.24)$$

The maximum  $V_{CO}$  frequency swing that can be obtained is given by,

$$(f - f_0)_{\max} = k_V V_{CO(\max)} = k_V k_{\phi} A^{1/2}$$

$$f_s = f_0 \pm (f - f_0)_{\max} = f_0 \pm k_V k_{\phi} A^{1/2} \rightarrow (9.25)$$

$$= f_0 \pm \Delta f_L \rightarrow (9.26)$$

$$2\Delta f_L = k_V k_{\phi} A^{1/2} \rightarrow (9.27)$$

$$\Delta f_L = \pm k_V k_{\phi} A^{1/2} \rightarrow (9.28)$$

$$k_V = \frac{8f_0}{V}$$

$$V = +V_{CC} - (-V_{CC})$$

$$k_{\phi} = \frac{1.4}{\pi}$$

lock in range

$$\Delta f_L = \pm 7.8 f_0 / V$$

Derivation of Capture range:-

The Low Pass filter (LPF)

$$T(f) = \frac{1}{1 + j(f/f_H)}$$



$$T(\Delta t) = f_i / \Delta t = t_i / (t_s - t_0)$$

$$V_c = V_e \times T(t) \times A \rightarrow 9.35$$

$$V_c(\max) = V_c(\max) \times T(t) \times A$$

$$\pm k\phi (\pi/2) A (t_i / \Delta t) \rightarrow 9.36$$

Total capture range

$$2\Delta f_c = 2\sqrt{f_c \Delta f_L}$$

→ LPF band-width is first set

for a large value

→ This will minimize the interference

& undesirable signals and noise.

### Analog Multiplier:-

→ There are a number of applications of analog Multipliers such

- (i) frequency doubling
- (ii) measurement of real power
- (iii) detecting phase angle difference
- (iv) dividing one signal by another.
- (v) multiplying two signals.


The O/P voltage

$$V_o = \frac{V_x V_y}{V_{ref}} \rightarrow 4.55$$

$$V_{ref} \Rightarrow 10V$$


$$V_o = \frac{V_x V_y}{10}$$



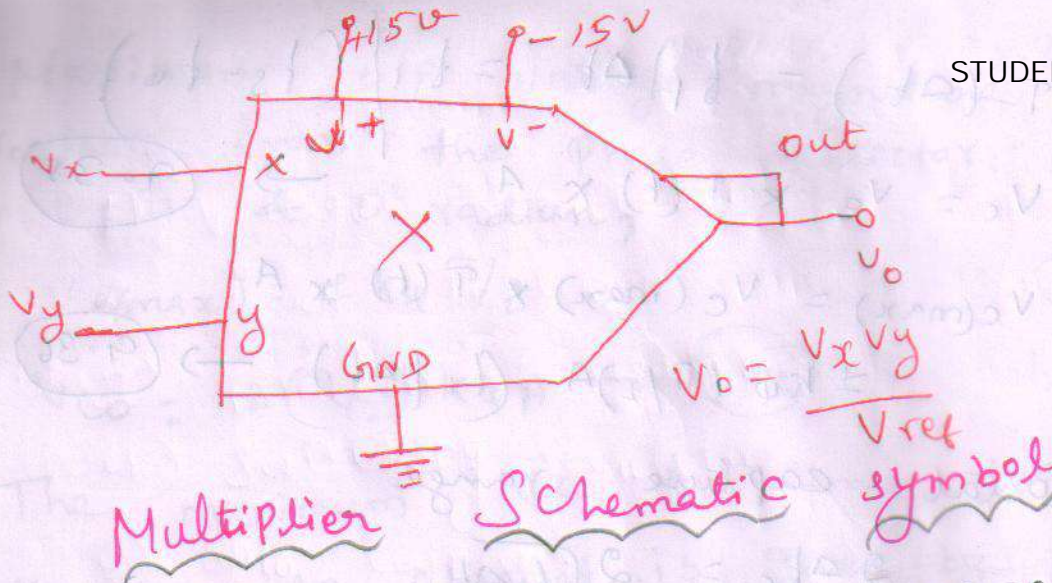

→ supply voltage can range from  $\pm 8V$  to  $\pm 18V$

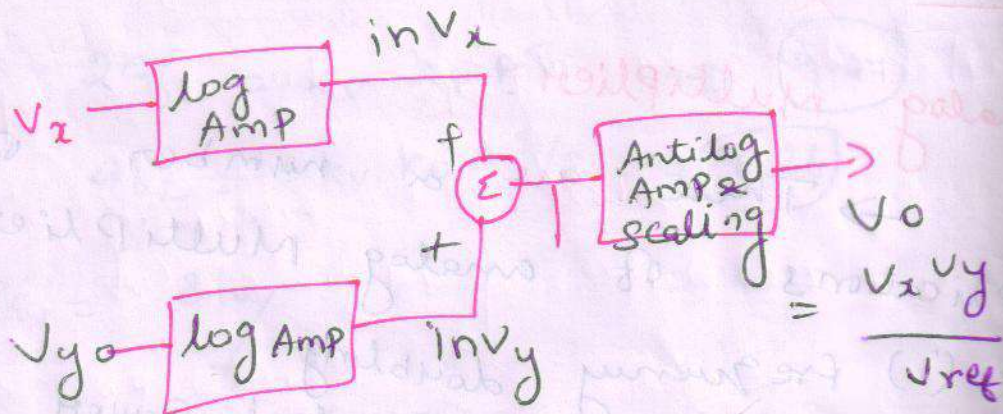Block diagram of a log antilog Multiplier:-



→ This log-antilog multipliers are restricts log-antilog Multipliers.

Some of the multiplier IC chips are AD533, AD534, AD633.

Squarer Circuit:-

→ used to square any positive or negative number provided




→  $V_i$  representing the  
connected to both the inputs

$$V_o = \frac{V_i^2}{V_{ref}}$$

$$V_i = 5 \sin 2\pi \times 10^4 t \quad \& \quad V_{ref} = 10$$
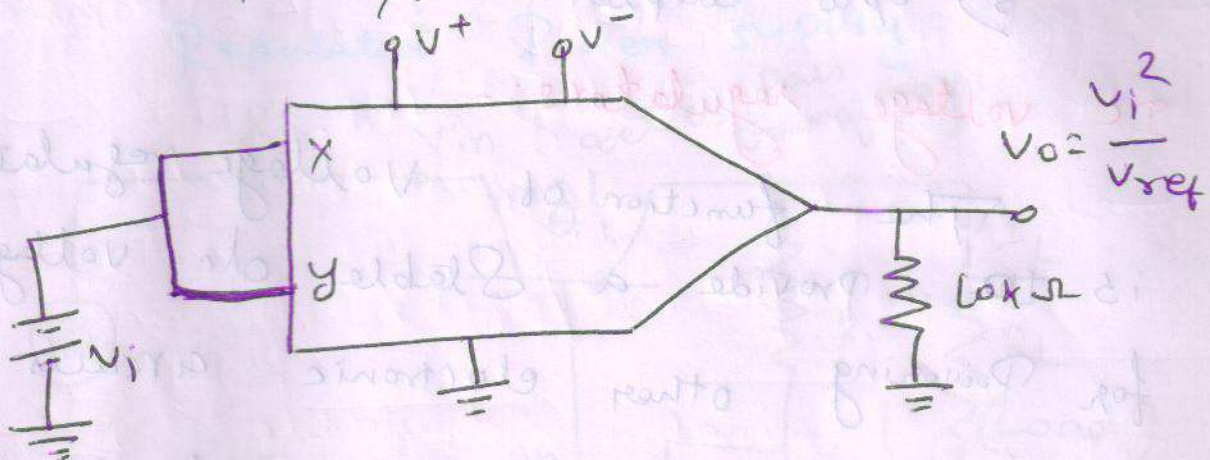
$$V_i = \frac{5^2}{10} (\sin 2\pi \times 10^4 t)^2$$



**Phase angle detection :-**

If the IIP signals applied to a Multiplier are

$$V_x = V_{mx} \sin \omega t$$

$$V_y = V_{my} \sin(\omega t + \theta)$$

$$= \frac{V_{mx} V_{my}}{V_{ref}} \sin \omega t \sin(\omega t + \theta)$$

$$= \frac{V_{mx} V_{my}}{V_{ref}} \times \frac{1}{2} [\cos \theta - \cos(2\omega t + \theta)]$$

$$V_o, dc = \frac{V_{mx} V_{my}}{V_{ref}} \times \cos \theta$$



## Unit 5

### Application IC's

STUDENTSFOCUS.COM

- 1) Voltage regulator
- 2) Power Amplifier
- 3) Function Generator
- 4) Switching regulator
- 5) Opto coupler.

### IC voltage regulators:-

The function of Voltage regulator is to provide a stable dc voltage for powering other electronic circuits.

Voltage regulators can be classified

- as,
- a) Series Regulator
  - b) Switching regulators

### Series regulator:-

Series regulator use a Power transistor connected in series b/w the unregulated dc input and load, O/P voltage is controlled by continuous voltage drop place across series PNP transistor.


→ The transistor conducts in the active or linear region.



## Switching regulators:-

Can Operate Power transistor as a high frequency on/off switch, so Power transistor does not conduct current continuously.


## Regulated Power supply

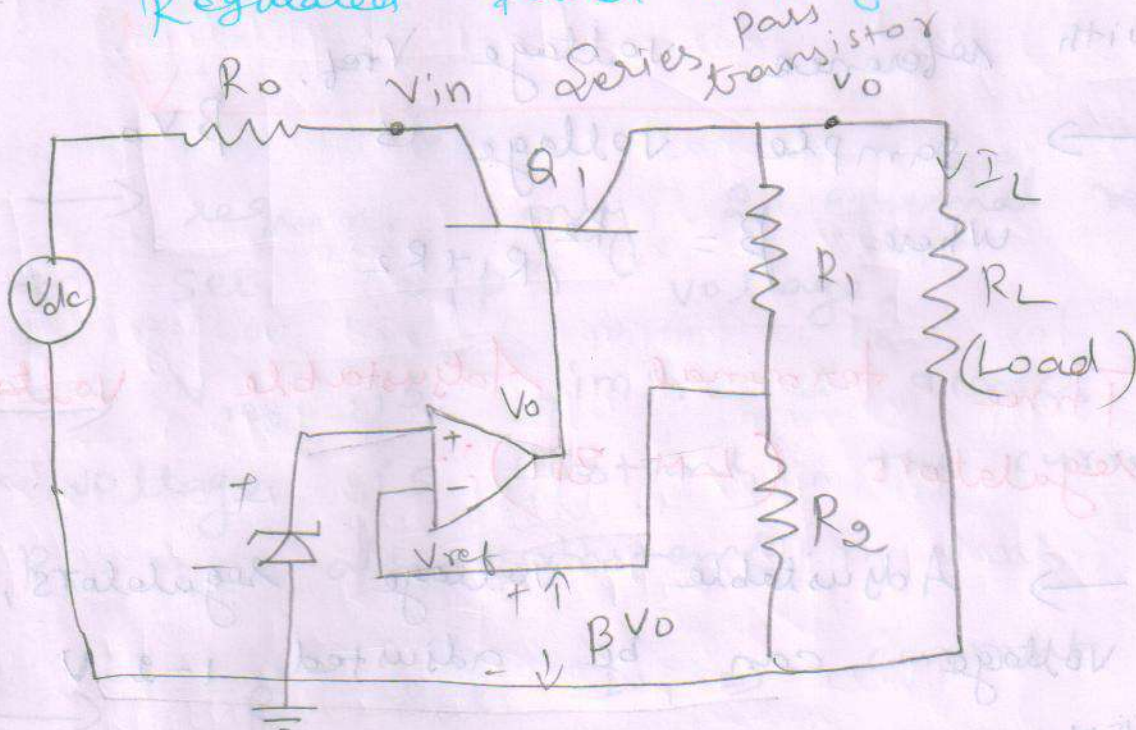

A regulated Power supply using discrete components and circuit consists of following four parts,

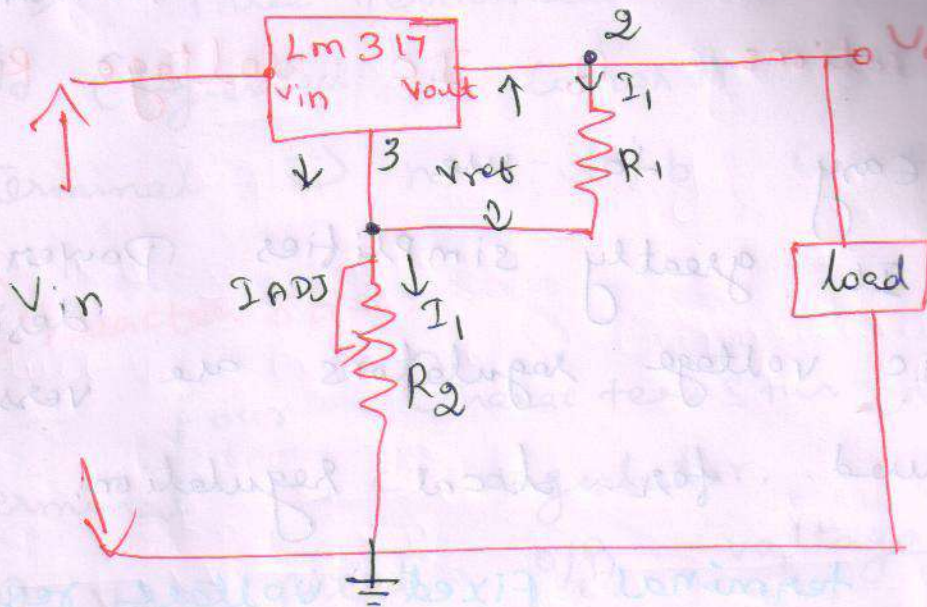- Reference voltage
- Error Amplifier
- Series Pan transistor
- Feed back n/w



Lm 317 regulator

→ requires only 2 external resistors, to set o/p voltage.

→  $V_{ref}$  is impressed across  $R_1$  & voltage is constant, the current  $R_1$  is also constant.

→  $R_1$  set  $I_1 \Rightarrow$  current set or Program resistor.

→ o/p voltage =  $R_1 I_1 + R_2 (I_1 + I_{ADJ}) \rightarrow \textcircled{1}$

Where  $I_1 = \frac{V_{ref}}{R_1}$

Sub  $\textcircled{1}$  in equ  $\textcircled{1}$

$$V_o = R_1 \left( \frac{V_{ref}}{R_1} \right) + R_2 (I_1 + I_{ADJ})$$

$$V_o = V_{ref} + \frac{V_{ref}}{R_1} R_2 + R_2 I_{ADJ}$$



→ Power transistor  $Q_1$  is with unregulated dc voltage  $V_{in}$  and regulated o/p voltage  $V_o$ .

→  $Q_1$  is also connected as an emitter follower.

→ Sampled voltage is compared with reference voltage  $V_{ref}$ .

→ sample voltage is  $\beta V_o$

where  $\beta = \frac{R_2}{R_1 + R_2}$

### Three terminal Adjustable Voltage regulators (LM 317):-

→ Adjustable voltage regulators, o/p voltage can be adjusted 1-2 V upto 57V.

→ LM 317 series is most commonly used general purpose adjustable voltage regulators.

### Advantages:-

- Improved S/m performance
- Improved overload protection
- Improve system reliability.



Where  $V_{ref} = 1.25V = V_{ref}$  Voltage

b/w and adjustment terminals

### Applications of IC Voltage Regulators :-

- 1) Easy to use
- 2) It greatly simplifies power supply design,
- 3) IC voltage regulators are versatile
- 4) used for local regulation.

### Three terminal fixed voltage regulators

78XX Series are three


terminal, Positive fixed voltage regulators with screen O/P voltage,

In 78XX last 2 nos XX indicate O/P voltage.

These regulators are 2 types.

Metal Package (3 types).

Plastic Package (20 types)

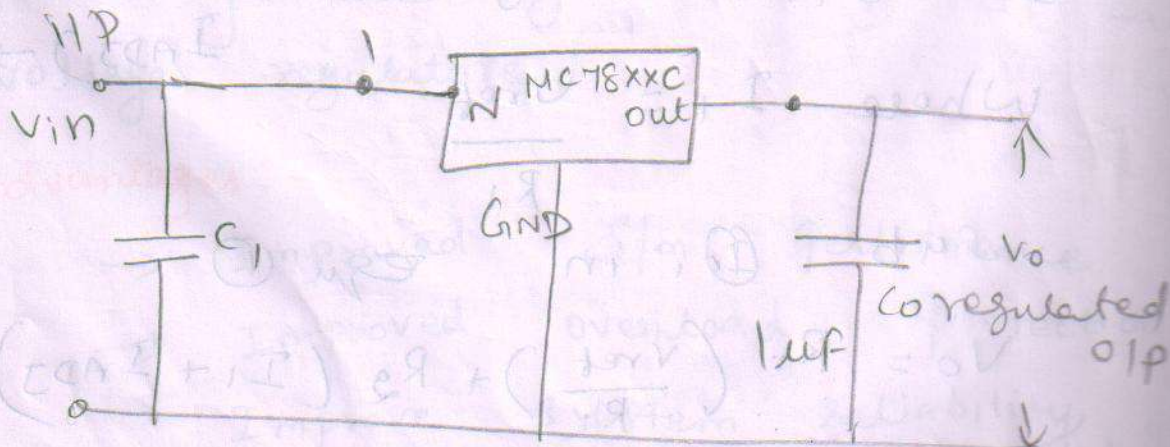



- Three terminal voltage regulator  
 → Three terminals O/P,  $V_{in}$  &  $V_o$  (regulated & common ground terminal) ⇒ no t/b connection.

### Characteristics:-

Four Characteristics terminal IC regulator.

- 1)  $V_o$ : fixed O/P voltage as specified by manufacturer.
- 2)  $V_{in} > V_o + 2$  volts  
 i.e. If  $V_o = 7V$ ,  $V_{in} = 5V$
- 3)  $I_{o1}$  max, load current may vary from 0 to rated max O/P I
- 4) Thermal shutdown: IC has temperature sensor, which turns off IC when it becomes too hot.

### IC 723 General Purpose Regulator:-

Limitation & 3 terminal voltage  
regulation.

- 1) No short circuit protection
- 2) O/P voltage is fixed

The limitation can be overcome by 723 General Purpose regulators




which can be adjusted over a wide range of both positive or negative regulated voltage

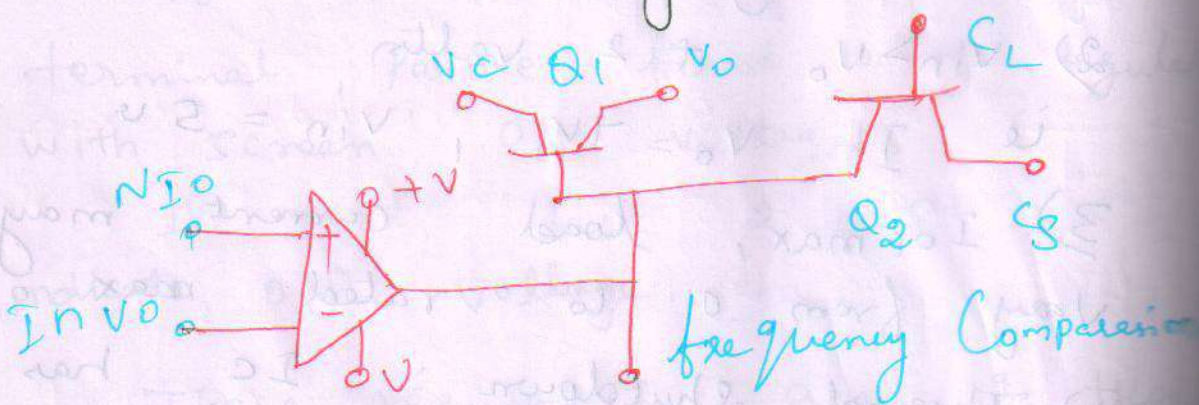**Important features of IC 723 :-**

→ It has good line and load regulation

→ Relative ease with which Power Supply can be designed & Provides a choice of supply voltage.



→ Two Separate sections,

- (i) Zener Diode
- (ii) Error amp