

UNIT- 5Application: ICS

1. Voltage Regulator
2. Power Amplifier
3. Function Generator
4. Switching Regulator
5. Opto Coupler.

IC Voltage Regulators

The function of a voltage Regulator is to provide a stable dc voltage for powering other electronic circuits. A voltage regulator should be capable of providing substantial output current.

Voltage Regulators can be classified as

- a) Series Regulator
- b) Switching Regulator

Series Regulators

Series Regulators use a power transistor connected in series with the unregulated dc input and load, o/p voltage is controlled by continuous voltage drop taking place across series pass transistor.

→ The transistor conducts in the active or linear region, these regulators are also called linear regulators


→ Linear voltage regulators are 78xx, 79xx series, 7232c.

### Switching Regulator

Can operate power transistor as a high frequency on/off switch, so power transistor does not conduct current continuously.

### Series op-amp Regulator

Stable dc voltage vs ac line voltage variations

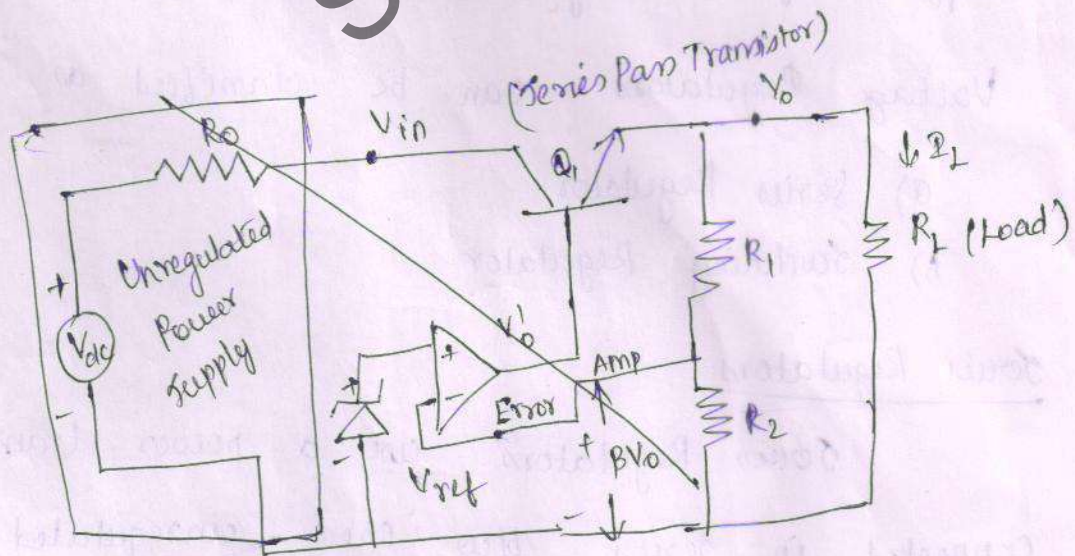

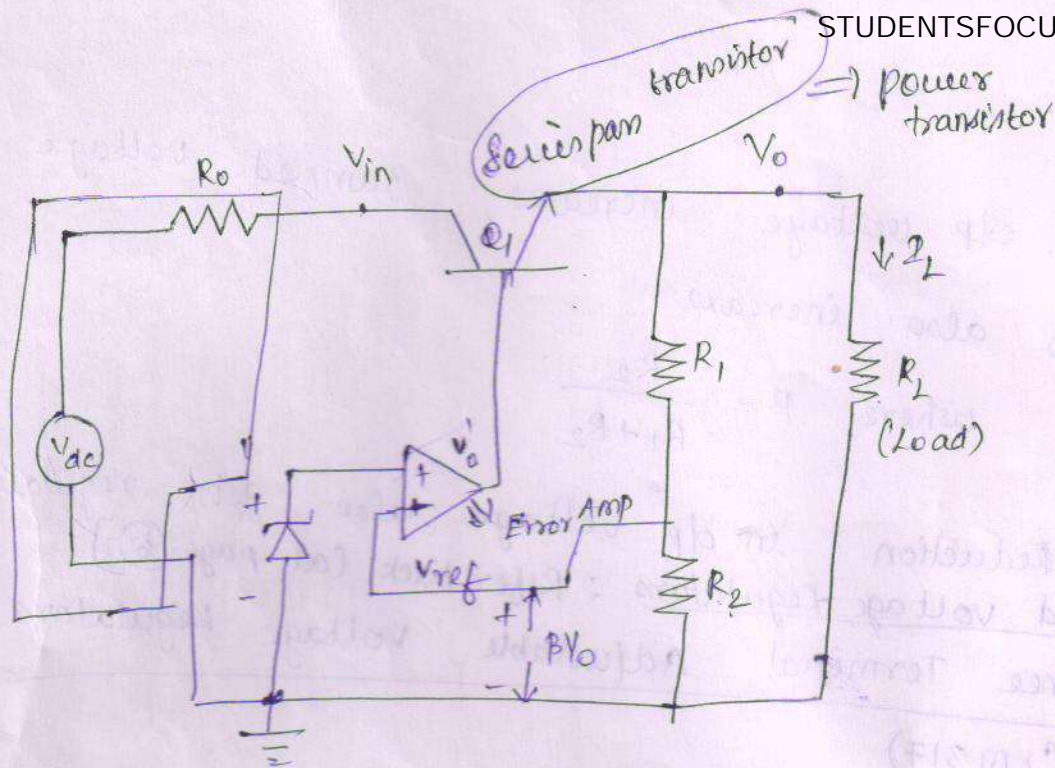


Fig1: A regulated Power supply

A regulated power supply using discrete components and circuit consists of following four parts

- Reference voltage circuit
- Error Amplifier
- Series pass transistor
- Feedback network

→ Power transistor  $Q_1$  is in series with unregulated dc voltage  $V_{in}$  and regulated op voltage  $V_o$ .

→  $Q_1$  is also connected as an emitter follower and provides sufficient current gain to drive the load.

→ Sampled voltage is compared with reference voltage  $V_{ref}$ .

∴ o/p voltage increases, sampled voltage  
 BVo also increases  
 where  $\beta = \frac{R_2}{R_1 + R_2}$

→ Reduction in o/p voltage also gets regulated  
Fixed voltage Regulators : Refer back (at page 6)

Three Terminal Adjustable Voltage Regulators


(LM317)

- Adjustable voltage regulators, output voltage can be adjusted by 1.2V upto 57V. The adjustable voltage regulators have become more popular because of versatility & reliability.
- LM317 series is most commonly used general purpose adjustable voltage Regulator.

Advantages :-

- Improved system Performance
- Improved overload protection
- Improved system reliability
- LM317 series regulators available in standard transistor packages and it has 3 terminals.

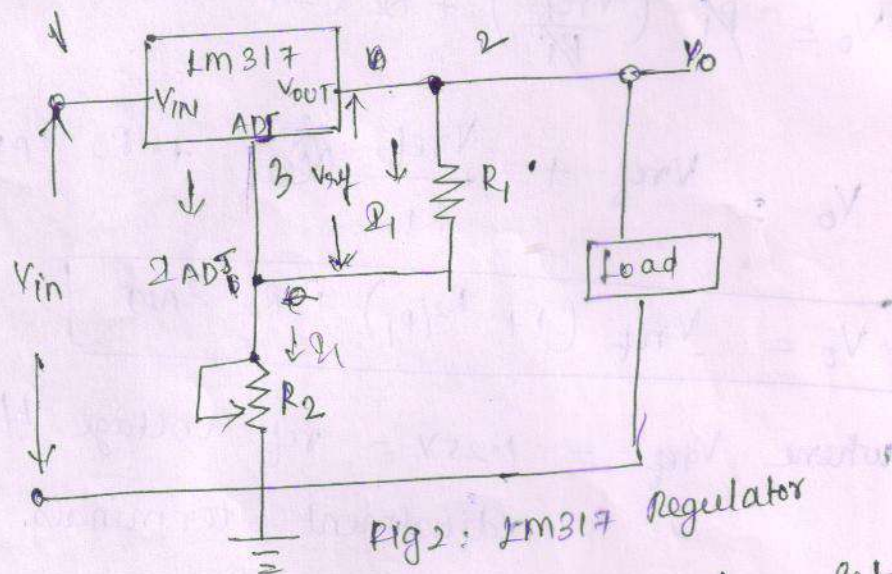→ The three terminals are  $V_{in}$ ,  $V_{out}$  & Adjustment (ADJ)



\* Requires only 2 external resistors to set o/p voltage.

\*  $V_{ref}$  is impressed across Resistor  $R_1$  & voltage is constant, the current  $I_1$  is also constant for a given value of  $R_1$ .

\*  $R_1$  set  $I_1 \Rightarrow$  current set or program resistor and constant with line & load changes.

$$\text{o/p voltage } V_o = R_1 I_1 + R_2 (I_1 + I_{ADJ}) \rightarrow \textcircled{1}$$

$$\text{Where } I_1 = \frac{V_{ref}}{R_1}$$

$R_1$  -  $I_1$  set resistor  
 $R_2$  - o/p set resistor  
 $I_{ADJ}$  - Adjustment pin current)

⑥

$$\text{Sub } I_c = \frac{V_{ref}}{R_1} \text{ in } \textcircled{1}$$

$$V_o = R_1 \left( \frac{V_{ref}}{R_1} \right) + R_2 (I_1 + I_{ADJ})$$

$$V_o = V_{ref} + \frac{V_{ref}}{R_1} R_2 + R_2 I_{ADJ}$$

$$V_o = V_{ref} \left( 1 + \frac{R_2}{R_1} \right) + R_2 I_{ADJ}$$

where  $V_{ref} = 1.25V =$  ref voltage b/w o/p and adjustment terminals.

Applications of DC voltage regulators  $\Rightarrow$  (After 723 General purpose Regulators)

1. Easy to use
2. It greatly simplifies power supply design
3. DC voltage regulators are versatile
4. Used for local regulation  $\Rightarrow$  low current, powers

Three Terminal Fixed voltage regulators


$\rightarrow$  78XX series are three terminal, positive fixed voltage regulators with seven o/p voltage options available such as 5, 6, 8, 12, 15, 18 & 24V

In 78XX, the last 2 nos XX indicate o/p voltage. eg 7815 represents 15V regulator

These regulators are 2 types of package

Metal package (TO-3 type)

Plastic package (TO-220 type)

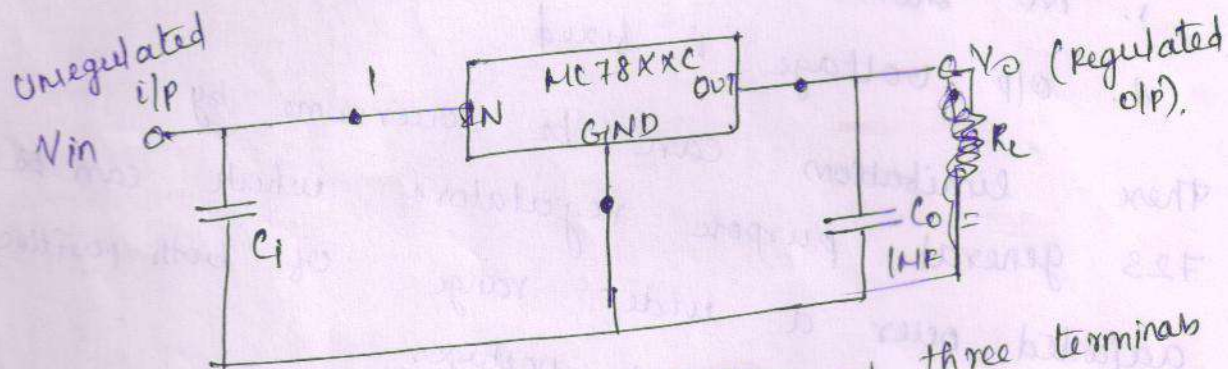

- Three terminal voltage regulators → three terminals  
o/p,  $V_{in}$  (unregulated) &  $V_o$  (regulated) & common or  
ground terminal,  $\Rightarrow$  no feedback connection.
- Capacitor to cancel inductive effects due to  
long distribution leads

### Characteristics

Four characteristics of 3 terminal IC regulator

- 1)  $V_o$ : fixed o/p voltage as specified by manufacturer (78xx has 5, 6, 8 etc)
- 2)  $V_{in} > V_o + 2\text{Vols}$  [2mV more than  $V_o$ ]  
i.e. if  $V_o = 7\text{V}$ ,  $V_{in} = 9\text{V}$
- 3)  $I_{o(max)}$ : load current may vary from 0 to rated max o/p I
- 4) Thermal shutdown: IC has temperature sensor (built-in) which turns off IC when it becomes too hot. & o/p current will drop & remains until IC has cooled significantly

## IC 723 General Purpose Regulator

### Three terminal voltage regulators


1. NO short circuit protection
2. o/p voltage is fixed

These limitations can be overcome by 723 general purpose regulators which can be adjusted over a wide range of both positive or negative regulated voltage.


### Important features of IC 723

- 1) Works as a voltage regulator at o/p ranges from 2 to 37 volts at currents upto 150mA.
- 2) has good line and load regulation
- 3) Relative easy with which power supply can be designed and provides a choice of supply voltage.
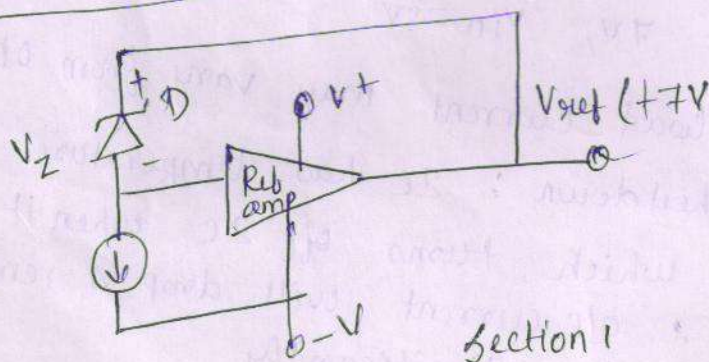
### Functional block diagram of IC 723 voltage regulator





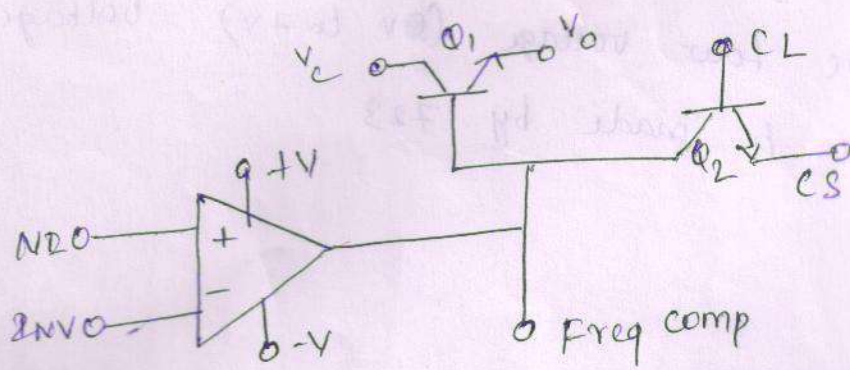


Section (2)

- Two separate sections: 1) Zener diode, constant current source & reference amp.
- 2) Error amp, Series pass transistor or power transistor (acts as switch or gate of electronic S/Ws)

→ Reference amplifier produces a fixed voltage of 7V at  $V_{ref}$ . Constant current source produces Zener to operate at fixed point so Zener o/p is a fixed voltage. (regulated)

→ Series pass transistor  $Q_1$ , current limit transistor  $Q_2$ .

Pin diagram of IC723

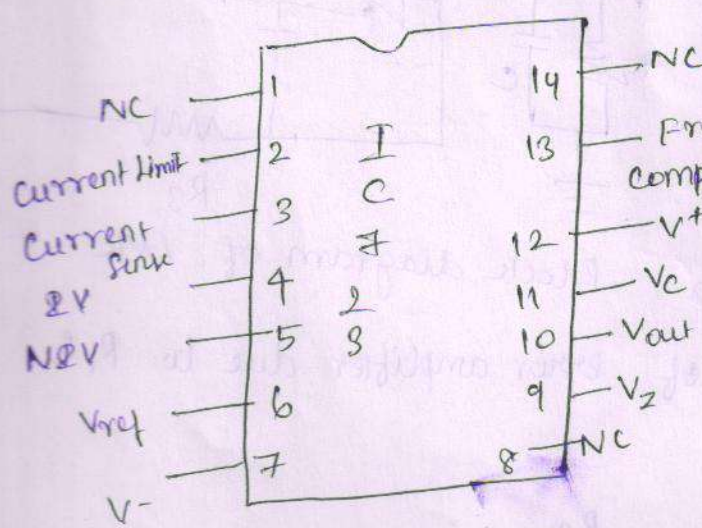

→ Error amplifier compares a sample of o/p voltage applied at 2NVO o/p terminal with the ref voltage  $V_{ref}$  applied at N2 i/p terminal. Error signal controls conduction of  $Q_1$ .

1. Simple positive low voltage (0V to 7V) voltage Regulator can be made by 723

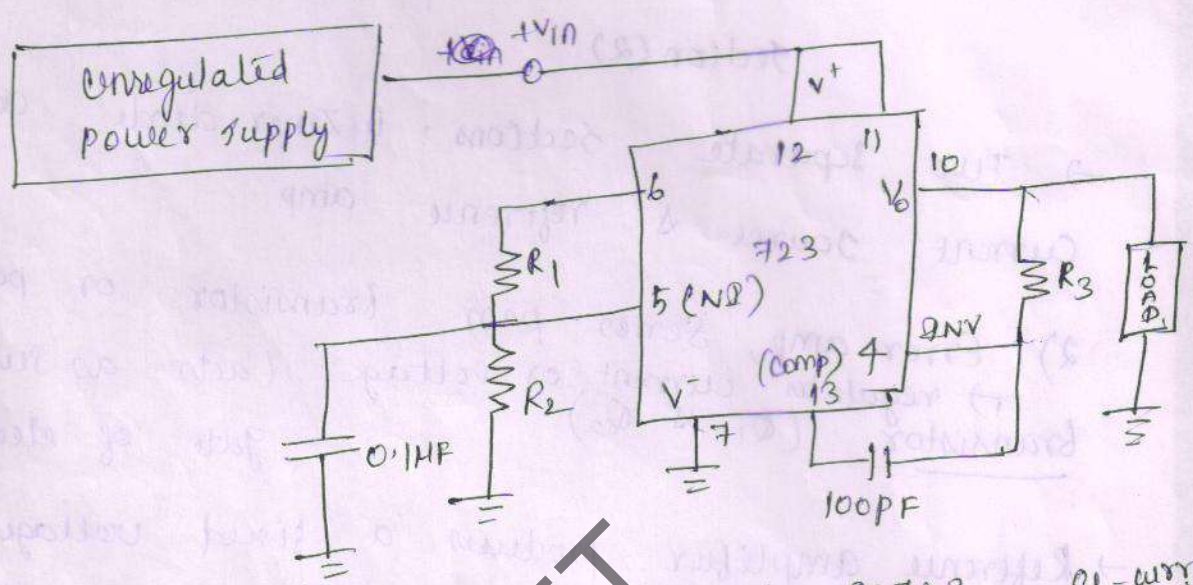


Fig1: Low voltage regulator using 723  
 CL-current limit  
 CS-current sense

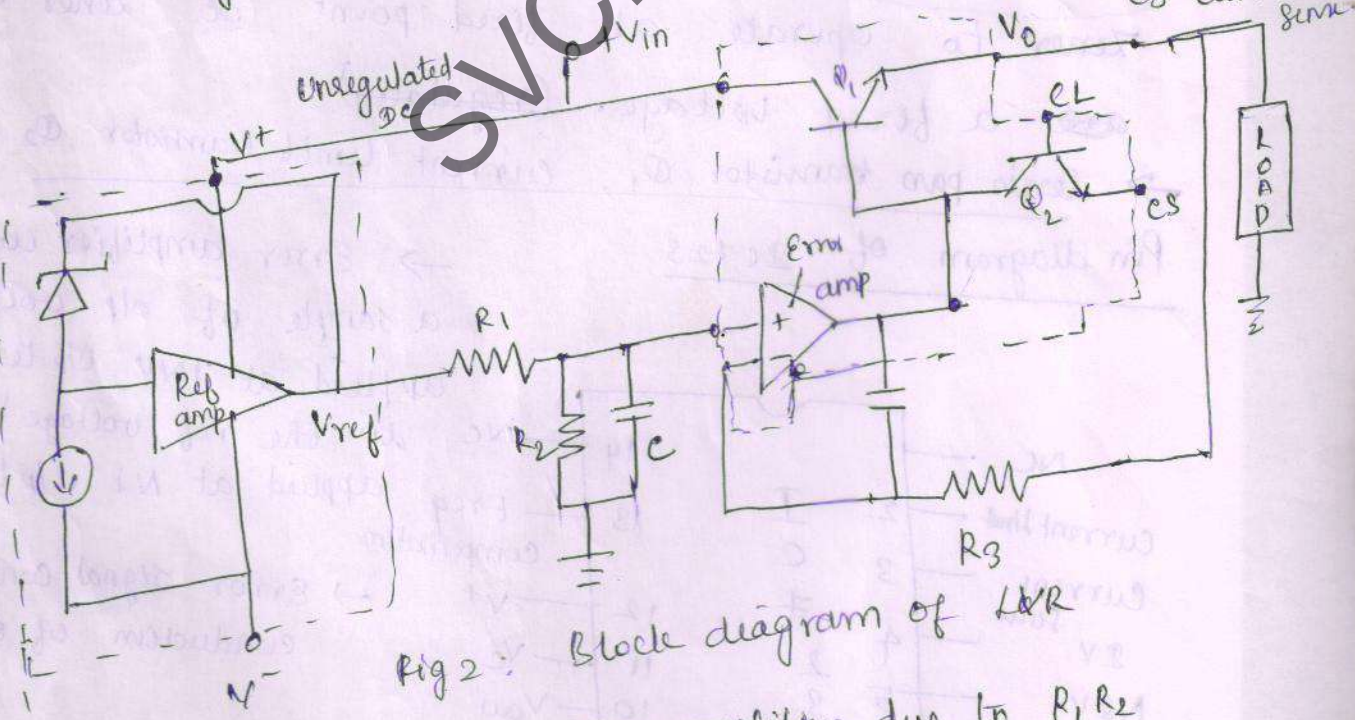


Fig 2: Block diagram of LVR  
 Voltage at NR of error amplifier due to R1, R2

divider is

$$V_{NR} = V_{ref} \frac{R_2}{R_1 + R_2}$$

→ The difference b/w  $V_{N2}$  and o/p voltage  $V_o$  which is directly feedback to  $\Delta V_V$  terminal is amplified by error amplifier

→ o/p of error amplifier drives the pnp transistor  $Q_1$  so as to minimize the difference b/w  $N2$  and  $\Delta V_V$  inputs of error amplifier

$Q_1$  is an operating emitter follower

$$V_o = V_{ref} \frac{R_2}{R_1 + R_2}$$

→ o/p becomes low, voltage at  $\Delta V_V$  terminal of error amplifier also goes down.  $\Rightarrow$  o/p of error amplifier become more positive, thereby driving  $Q_1$  into conduction.

→ This reduces voltage across  $Q_1$  & drives more current into load causing voltage across load to increase.

→ initial drop in load voltage has been compensated ~~offly~~ any increase in load voltage, or changes in ~~o/p~~ o/p voltage, get regulated.

ref voltage = 7.15  $\Rightarrow V_o = 7.15 \frac{R_2}{R_1 + R_2} < 7V.$

$\therefore$  it is low voltage 723 regulator.

A simple high voltage ( $>7V$ ) voltage regulator can be made using 723

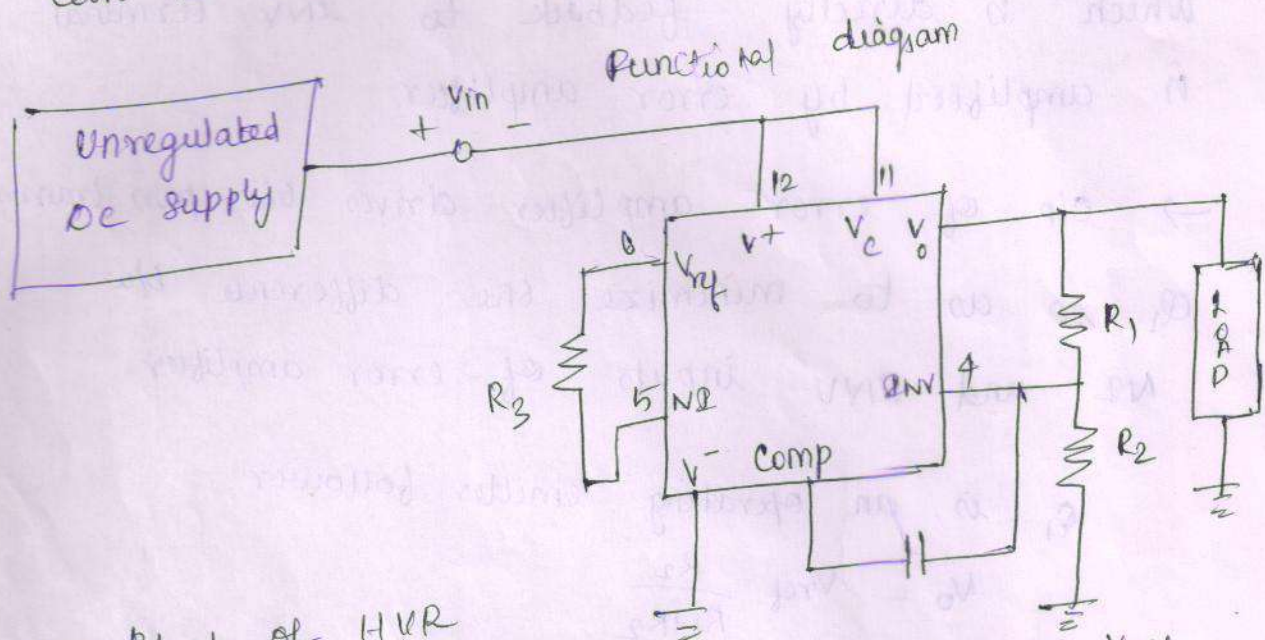


Fig. 3 Block of HVR

The NR terminal is connected directly to  $V_{ref}$  through  $R_3$ . So the voltage at NR is  $V_{ref}$

$$V_{NR} = V_{ref}$$

∴ error amplifier operates at Non inverting amplifier with gain  $A_v = \left(1 + \frac{R_1}{R_2}\right)$


∴ o/p voltage  $V_o = 7.15 \left(1 + \frac{R_1}{R_2}\right)$

Protection circuits in Regulators

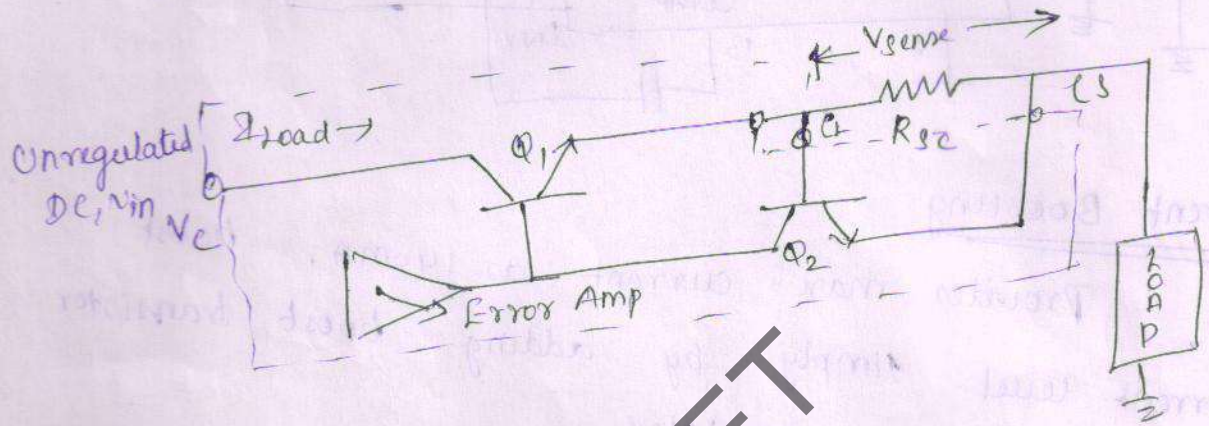- 1. current limit protection (current sensing technique)
- 2. current foldback
- 3. current Boosting

Current limit protection

→ Load demands more current [Eg under short circuit condition,  $V_e$  provides constant voltage getting hotter all time.  
 →  $V_e$  is provided with current limit facility




Current limiting facility ⇒ prevent load current from increasing above present value

$$I_{limit} = \frac{V_{sense}}{R_{sc}}$$

current limiting ⇒ current sensing technique.


Current foldback

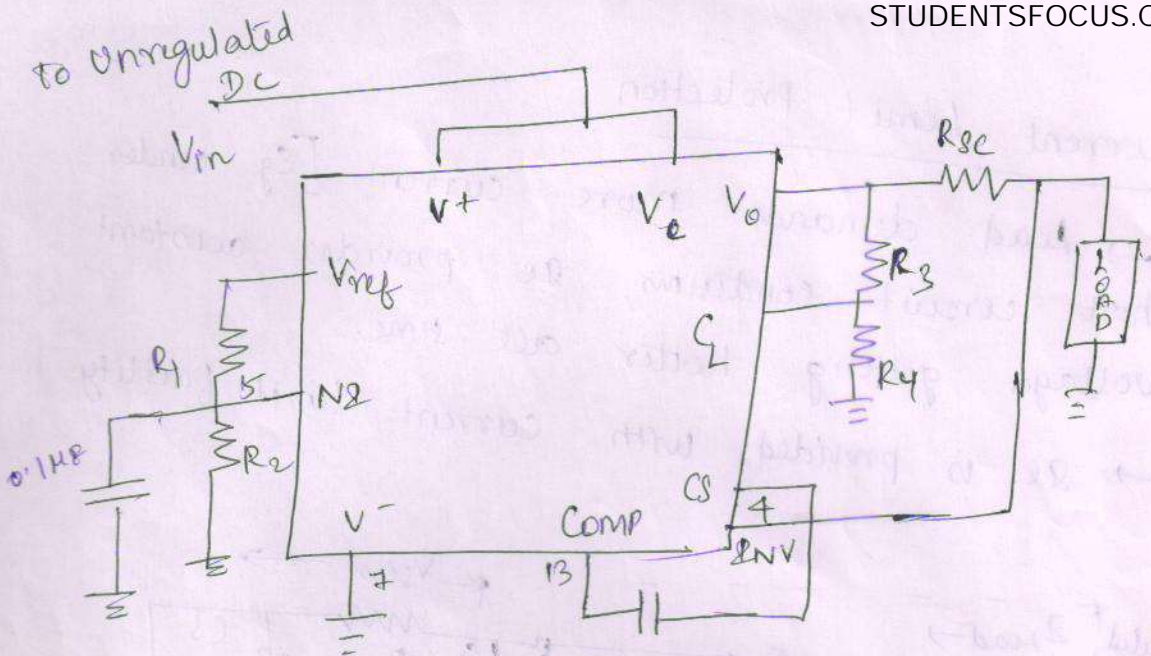→ In current limiting technique, load current is maintained at present value & when overload condition occurs,  $V_o$  drops to zero  
 → load is short circuited, max current flow through regulator. To protect regulator one method is used to limit short circuit current and to allow higher to load such method is current foldback



Current Boosting

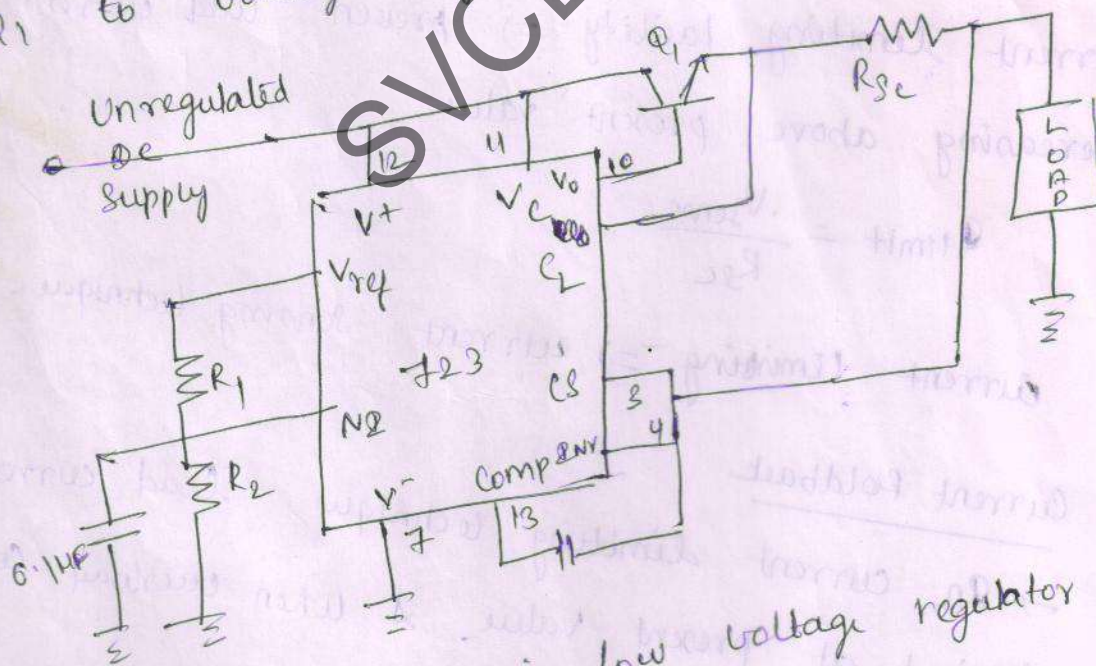Provides max current as 140mA. boost current level simply by adding boost transistor  $Q_1$  to voltage regulator



current Boosting low voltage regulator

~~$$P_{load} = P_{pam} + I_{B} \times V_{O} \text{ (723)}$$~~  $\rightarrow$  Base current

Limitations of 7805 :-

- 1) no in built thermal protection
- 2) no short circuit current limits

## Isolation Amplifier

### Limitations of Linear Voltage Regulators


1. Efficiency is very low
2. Input must be greater than the output voltage
3. As large is the difference between input and output voltage, more is the power dissipated in the series pass transistor.
4. Need of dual supply is not economical and feasible to achieve with the help of linear regulators

Switching Regulator  $\Rightarrow$  overcome all these limitations

The operating principle of switching regulators is completely different than that of linear regulators. The switching regulators are also called as switch mode regulators. Such a switching regulator requires external transistor and a choke. The series pass transistor in such a regulator is used as a controlled switch and is operated in cut off or saturation region. Hence power transmitted across such a transistor is in the form of discrete pulses rather than a steady flow of current.


When the transistor is operated in the cut off region, there is no current and dissipates no power. While when it is operated in the saturation region, a negligible voltage drop appears across it and hence dissipates very small power, providing maximum current to load. In any case, the power dissipated in the transistor is very small. Almost the entire power gets transmitted to the load. Hence efficiency of switching regulators is almost very high. Used for larger powers large current

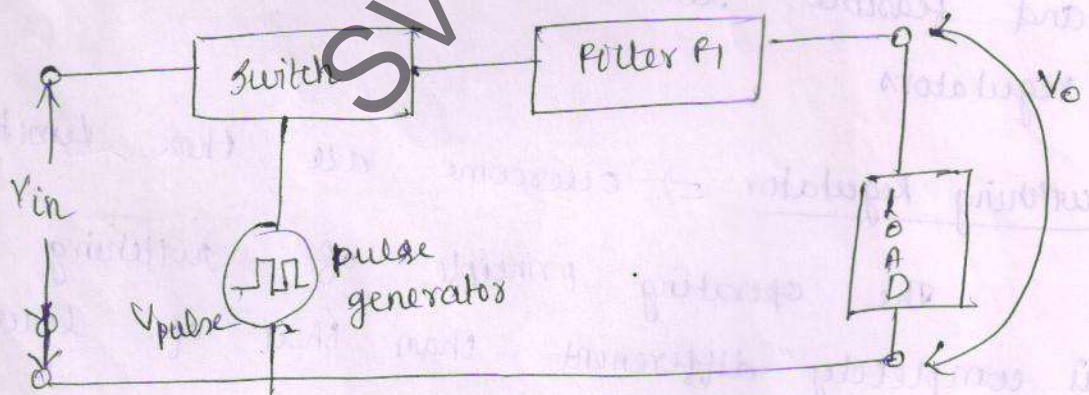Basic Switching Regulator → batteries, phone chargers, personal computers




Basic switching Regulator consists of ↓  
four major components  
Functional block diagram shown in page next page

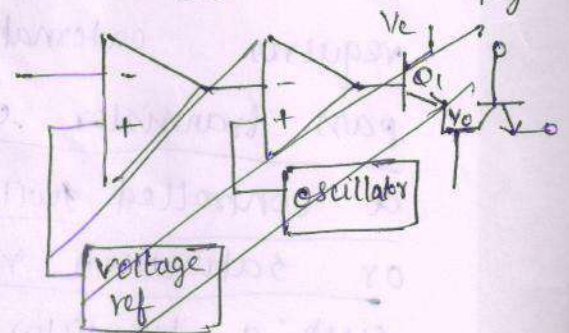- a) Voltage source  $V_{in}$
- b) Switching transistor
- c) pulse generator,  $V_{pulse}$
- d) Filter  $P_1$





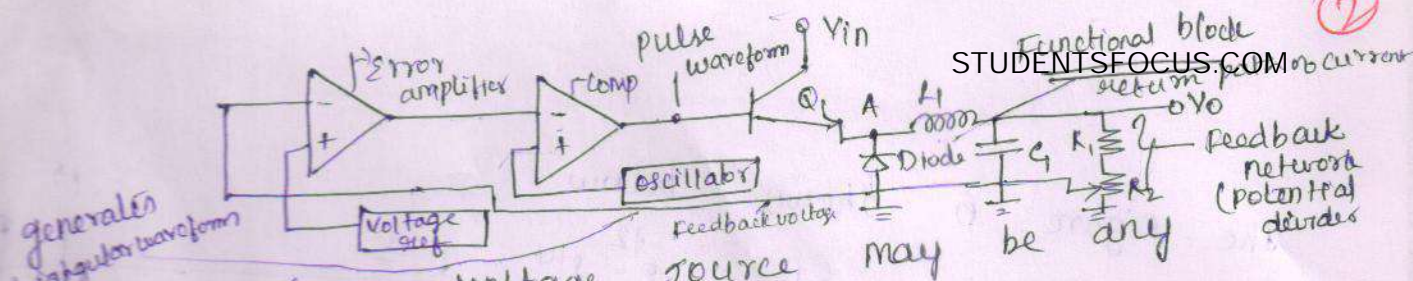

$V_{in}$  is a voltage source a battery or an unregulated or a regulated voltage. The pulse generator output makes it ON and OFF. The pulse generator produces a required pulse waveform. The filter converts the pulse waveform obtained from switch into a dc output voltage.  $\left[ \frac{R_2}{R_1 + R_2} \right]$  of output is feedback to inv inp of error amp. It is compared with ref voltage - comparator determines regulated voltage.


Switching Regulator IC (LM7840)

Due to non availability of high speed switching transistors and low pass inductors, the design of switching regulator was much more complicated in earlier days. But due to IC technology, now a days it has become easy.

→ Integrated Regulators

The LM7840 switching regulator consists of a temperature compensated voltage reference, controllable oscillator, high gain comparator, high voltage output switch, a power switching diode and an op-amp.

The figure is shown below

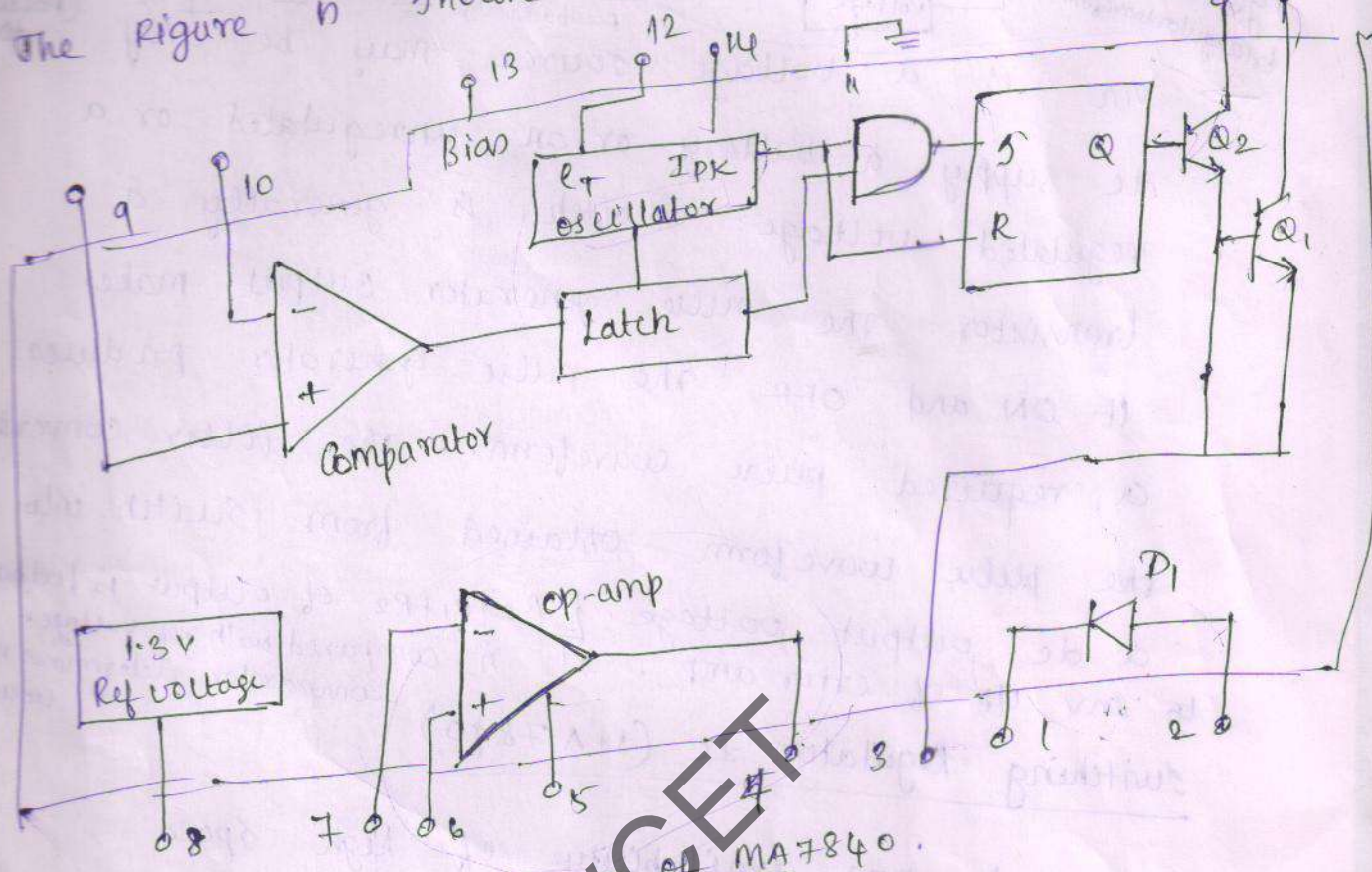


Block diagram of MA7840.

- It is a 16 pin dual package and is available as ceramic or plastic package
- Initial switching frequency is set by  $C_T$ . The comparator controls the off time of switch transistor  $Q_1$  &  $Q_2$ . When o/p is at desired value, comparator o/p is high and has no effect on circuit operation. But if o/p too high then voltage at inverting terminal is higher than the noninverting and comparator o/p goes low. In the low state comparator inhibits the turn on of the switching transistors. So the comparator o/p is low, the system is in off state.

3

- As the output current rises or voltage decreases, the off time of system decreases,
- The comparator can prevent several on cycles, one on cycle or any portion of on cycle.
- The current limit modifies the on time
- The increased load results in more current which increases on time and provide less off time.
- $V_{sat}$  is voltage across  $Q_1$  and  $Q_2$  when the switch is closed or on. This is output saturation voltage.
- power diode will bind the regulator efficiency

~~The better~~ Pin diagram of MA7840

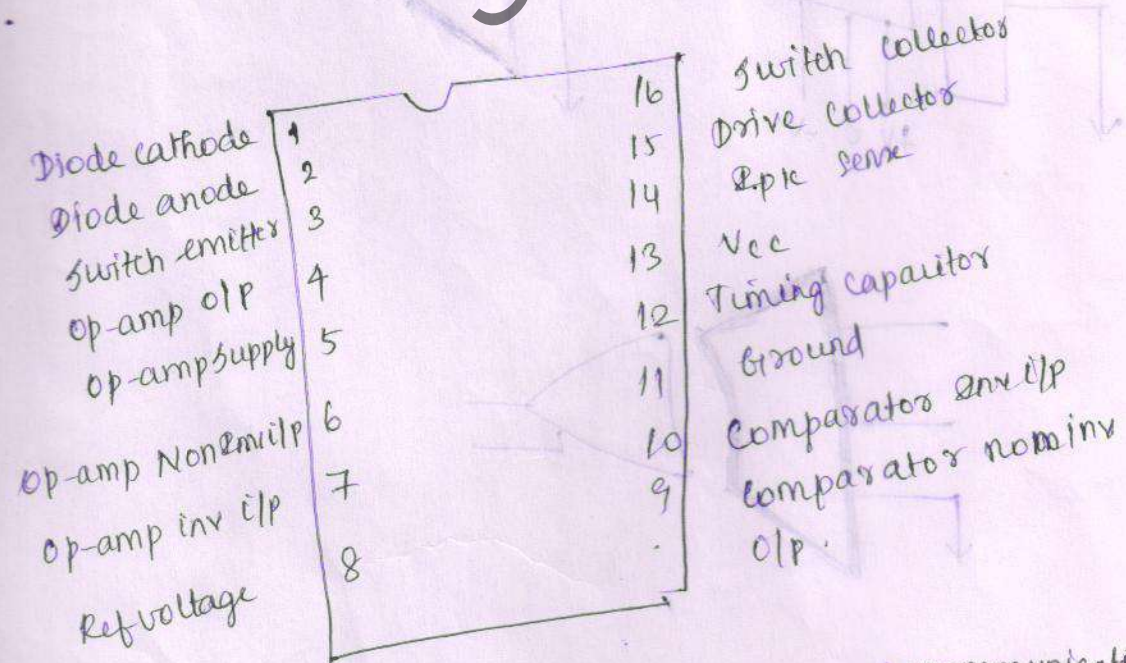


Application :- Battery Powered systems, Telecommunication circuit, Personal computers, printers, video games and automotive application.

Isolation Amplifiers

An Isolation amplifier is an amplifier that offers an ohmic or electrical isolation between its input and output terminals. Isolation amplifiers are often used when there is a very large common mode voltage difference between input and output side of device.

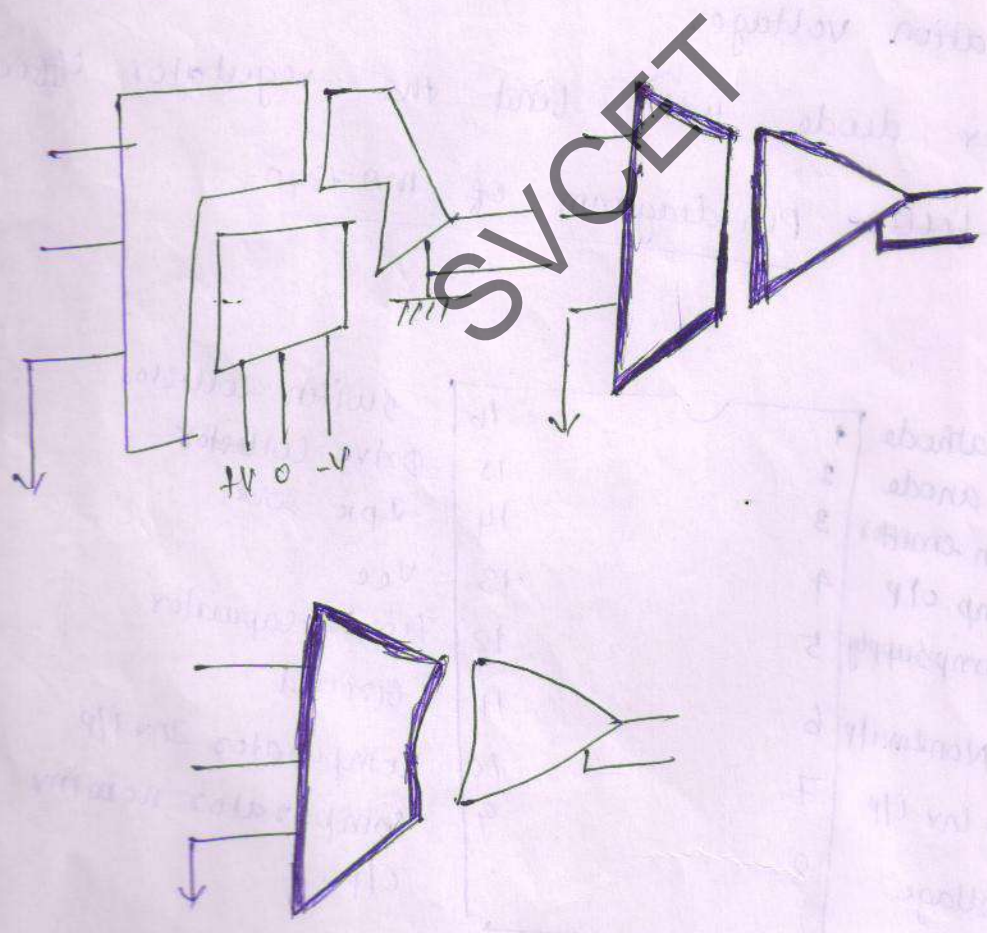Different symbols used for Isolation Amplifiers




9

→ An important characteristics of an isolation amplifier is the linearity of the input to output transfer characteristic. There are various methods of achieving high degree of linearity in optically coupled isolation amplifiers.

→ Such two examples of isolation amplifiers are discussed in following.

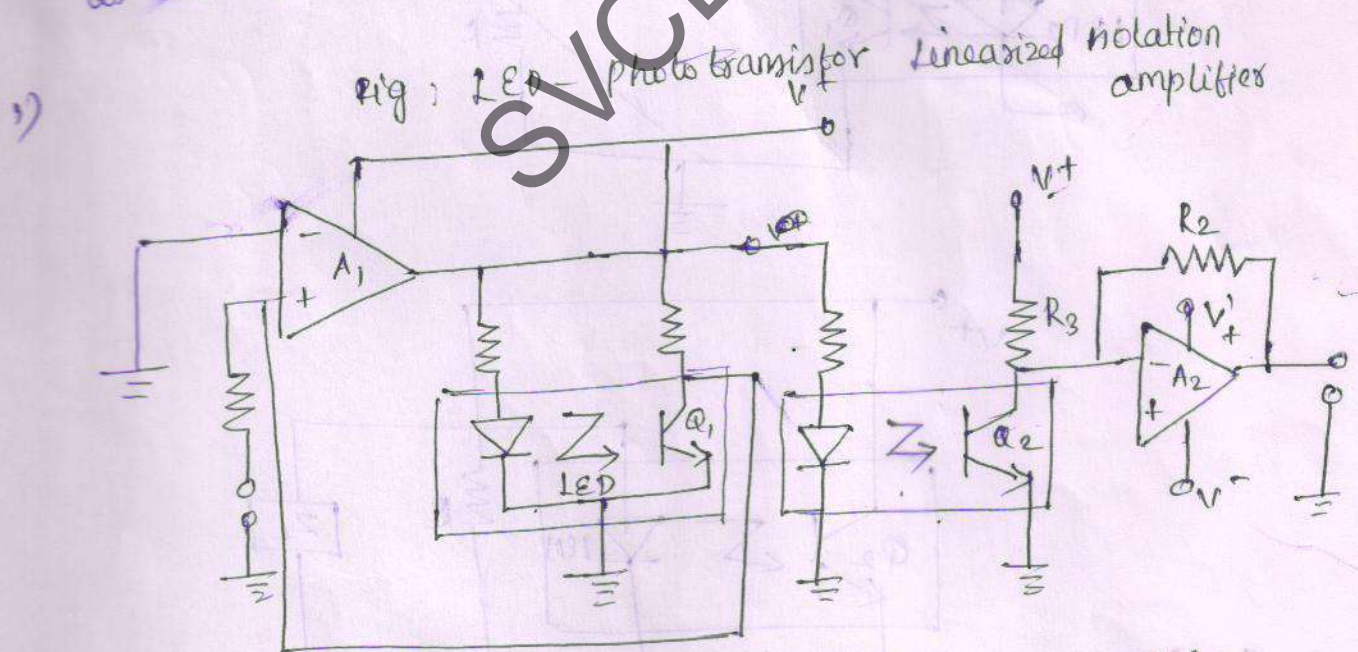→ Fig 1 shows an isolation amplifier in which a LED-photo transistor couplers are used as an opto isolators.




→ The first LED-photo transistor coupler is used in the feedback loop of amplifier A1 and second LED-photo transistor coupler is used at the input of amplifier A2.

→ Both LED-photo transistor couplers are used with matched characteristics are driven by the same amplifier  $A_1$ . Due to the matched characteristics of 2 LED-photo transistor pairs, the non linear characteristics and temperature dependence get

Compensated  
2) Linearized current amplifiers.

Fig 2: Isolated current amplifier with feedback

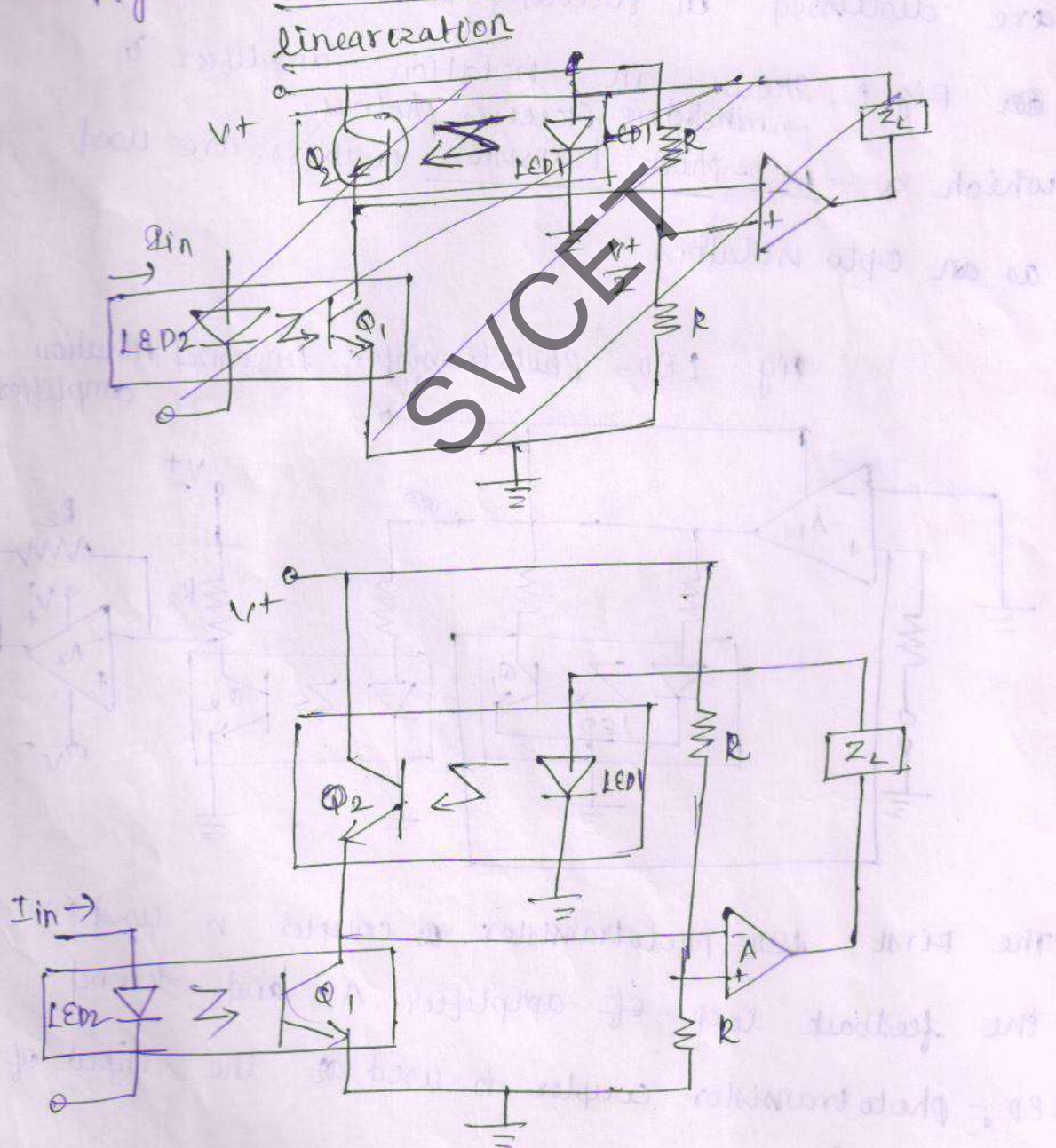

Isolation is provided by LED - phototransistor opto

Coupler. The current through  $Q_1$  &  $Q_2$  is same because they are connected in series. Temperature get compensated by matched characteristics of LED and phototransistor pairs. To maintain the equal current through  $Q_1$  and  $Q_2$ , current through  $Z_L$  and LED1 is equal to current  $I_{in}$  through LED2.


Type of Isolation Amplifier IC: 250100

250100 is an optically coupled isolation amplifier. High accuracy, linearity and time-temperature stability are achieved by coupling light from an LED back to the input as well as forward to output.

Features:-

- (i) Easy to use. Similar to an op-amp
- (ii) 100% tested for break down
- (iii) Wide Bandwidth

## Pin Configuration and Block Diagram

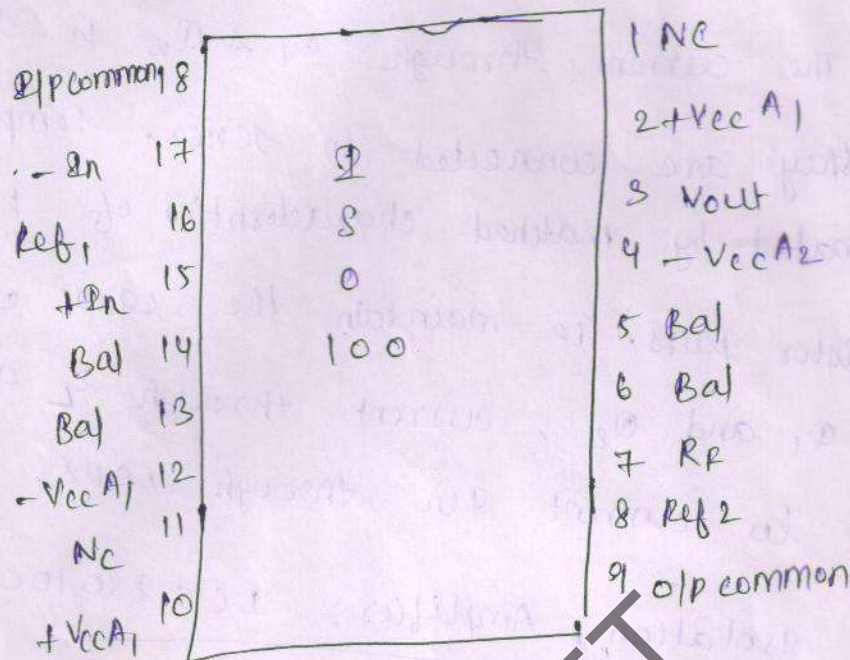

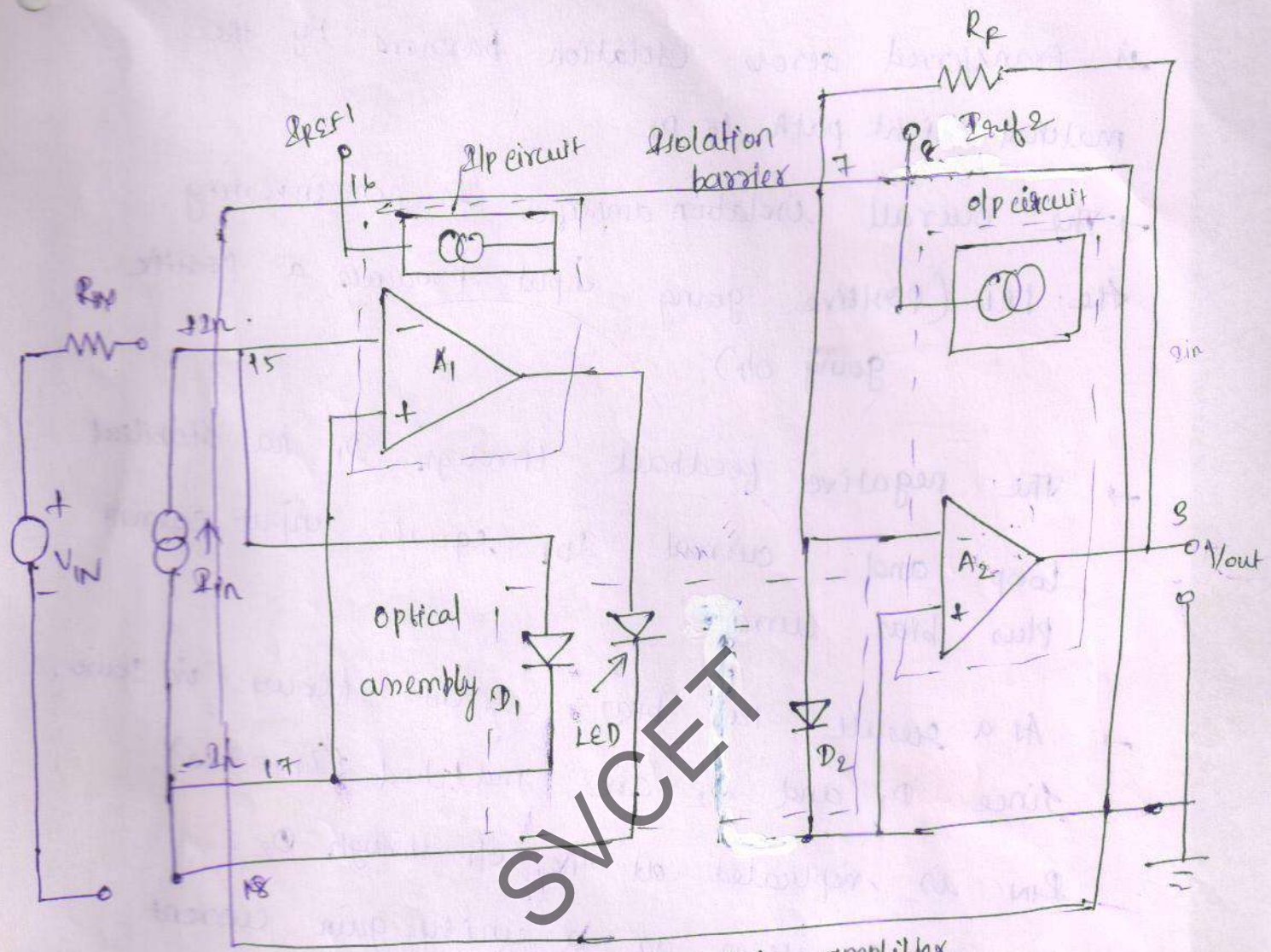
## Operation of ISO100

ISO 100 is fundamentally a unity gain current amplifier intended to transfer small signals or different electrical circuits separately by high voltages by passing o/p current through  $R_f$ .

The ISO 100 uses single light emitting diode (LED) and a pair of photodiode detectors coupled together to isolate the output signal from input.





Type of Isolation amplifier

- $I_{REF1}$  and  $I_{REF2}$  are required only for bipolar operation to generate a midscale reference
- The LED and photodiodes ( $D_1$  and  $D_2$ ) are arranged, the same amount of light falls on each photodiode. Thus the currents generated by the diodes match very closely
- Negative feedback around  $A_1$  occurs through optical path formed by LED and  $D_1$ . The signal

is transferred across isolation barriers by the matched light path to  $D_2$

→ The overall isolation amplifier is non inverting  
the led (positive going input produces a positive going o/p).

→ The negative feedback through  $D_1$  has stabilized loop and current  $I_{D1}$  equals input current plus bias current.

→ As a result, no bias current flows in source.  
since  $D_1$  and  $D_2$  are matched ( $I_{D1} = I_{D2}$ ).

$I_{IN}$  is replicated at the o/p through  $D_2$ .

thus  $A_1$  functions as a unity gain current amplifier and  $A_2$  is current to voltage converter

→ current produced by  $D_2$  must either flow into  $A_2$  or  $R_f$ . since  $A_2$  is designed for bias current, almost all of current flows through  $R_f$  to output.

$$\text{O/P Voltage } V_o = I_{IN} R_f$$

### Characteristics

1. CMRR (Common mode Rejection Ratio) change in applied common mode voltage and change in  $I_{os}$ .

EMRR (Isolation Mode Rejection Ratio)


Relationship b/w a change in applied isolation mode voltage and change in  $\beta_{os}$  required to maintain amplifier's o/p to zero.

Opto Coupler and Opto Electronic  $\beta_{os}$

→ The combined package of LED and photodiode is called an optocoupler. It is also called an optoisolator or an ~~opto cou~~ optically coupled isolator.

→ The basic circuit consists of an LED on the input side and a photodiode on the output side

1) LED & Photodiode

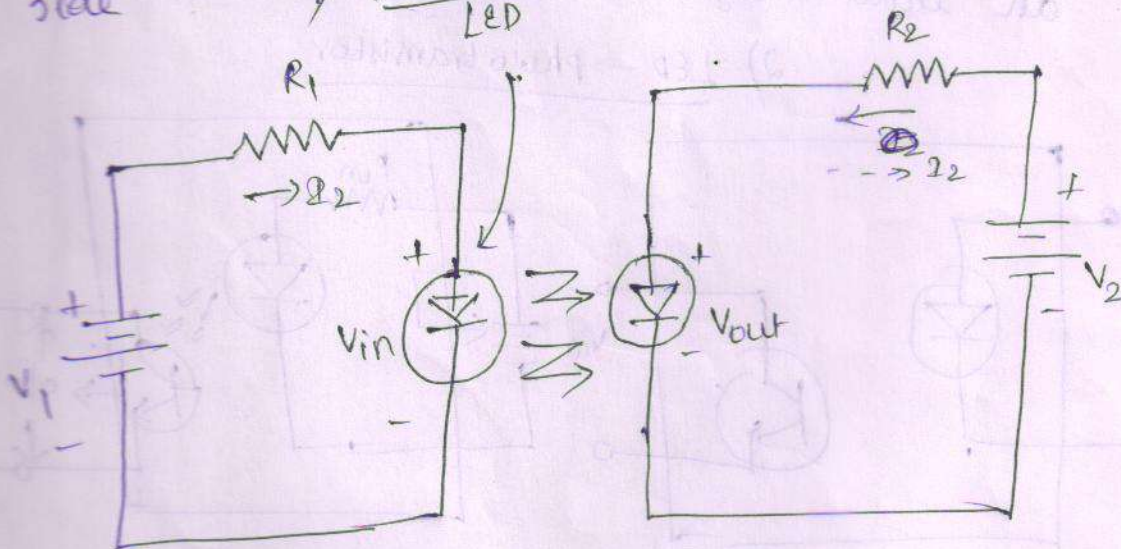


→ The source  $V_1$  and series resistance  $R_1$  decide the forward current  $I_1$  through LED. Thus LED emits the light. This light is incident on a photodiode.

→ A reverse bias current is set up in the output circuit. The output voltage is the difference b/w supply voltage  $V_2$  and drop across resistor  $R_2$ .

$$V_{out} = V_2 - I_2 R_2$$

→ If the input voltage is changed, the amount of light emitted by LED changes. This varies the reverse current in the output circuit and hence output voltage. This coupling between LED and photodiode is called optocoupler. As the name suggests this device can couple an input signal to output circuit.

2) LED - phototransistor

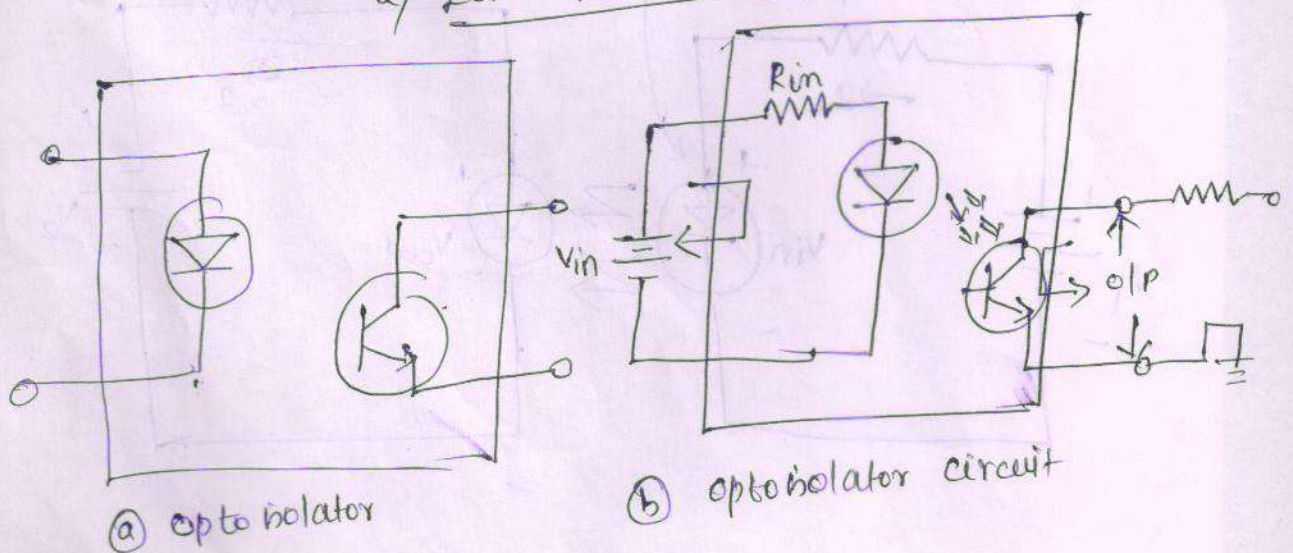

8



→ optocoupler consists of LED and phototransistor.  
 When input voltage forward biases LED, the light emitted to the phototransistor turns it ON, the resulting current through external load

Types of optocouplers

Other than the combination of LED and photodiode, two more types of optocouplers are:

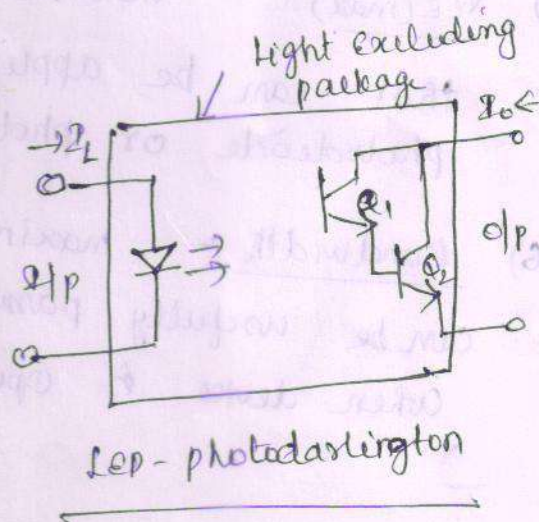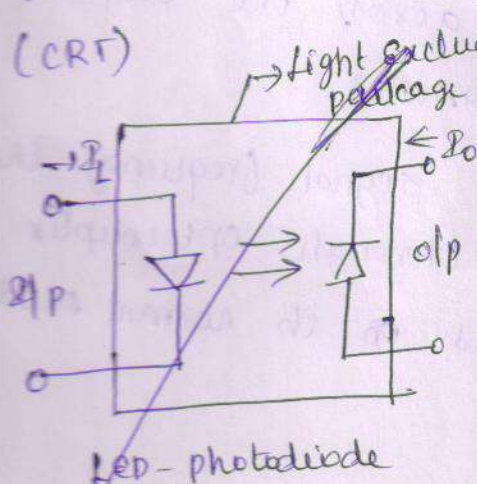- a) LED-photodiode
- b) LED-photodarlington

→ The input current which is the forward current of LED, results in emission of light by LED. This light is detected by photodiode and photodarlington to produce output current. The ratio of output current  $I_o$  to the input LED current  $I_i$  is called current transfer ratio (CTR)



## Characteristics of optocoupler

### 1) Current Transfer Ratio (CTR)

It refers to ratio of output collector current ( $I_c$ ) to input forward current  $I_f$

$$CTR = \frac{I_c}{I_f} \times 100 \%$$

### 2) Isolation voltage between I/P & O/P

It is a factor in choosing a photocoupler.

### 3) Response time

The response time of a photocoupler depends mainly on the output phototransistor

### 4) Common Mode Rejection Ratio


Photocouplers output is electrically isolated from its input for relatively low frequency signal, an impulsive input voltage may cause displacement current  $I_{cd} = C_f \frac{dv}{dt}$

5)  $V_{ce(max)}$  :- maximum allowable dc voltage that can be applied across the output photodiode or phototransistor

6) Bandwidth :- maximum signal frequency that can be usefully passed through optocoupler when device is operated in its normal mode
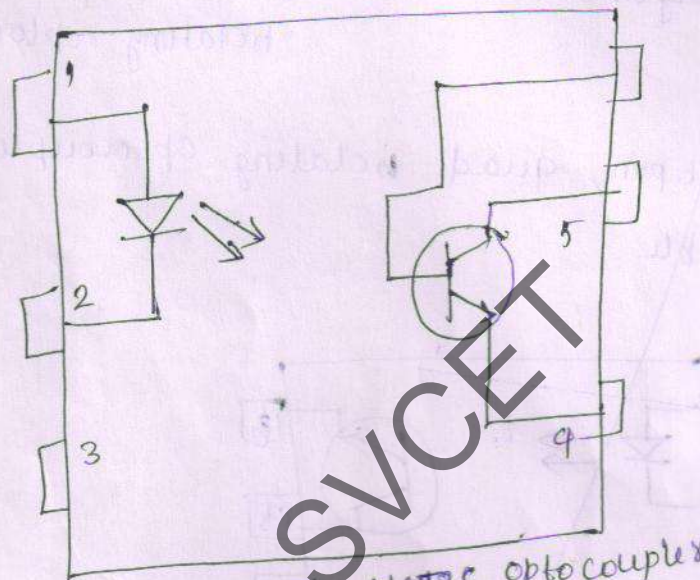
## Opto Electronic IC

MCT2E is optically coupled isolator consisting of a Gallium Arsenide infrared emitting diode and an NPN Silicon phototransistor, mounted




Circuit of MCT2E optocoupler

### Features of IC optocoupler

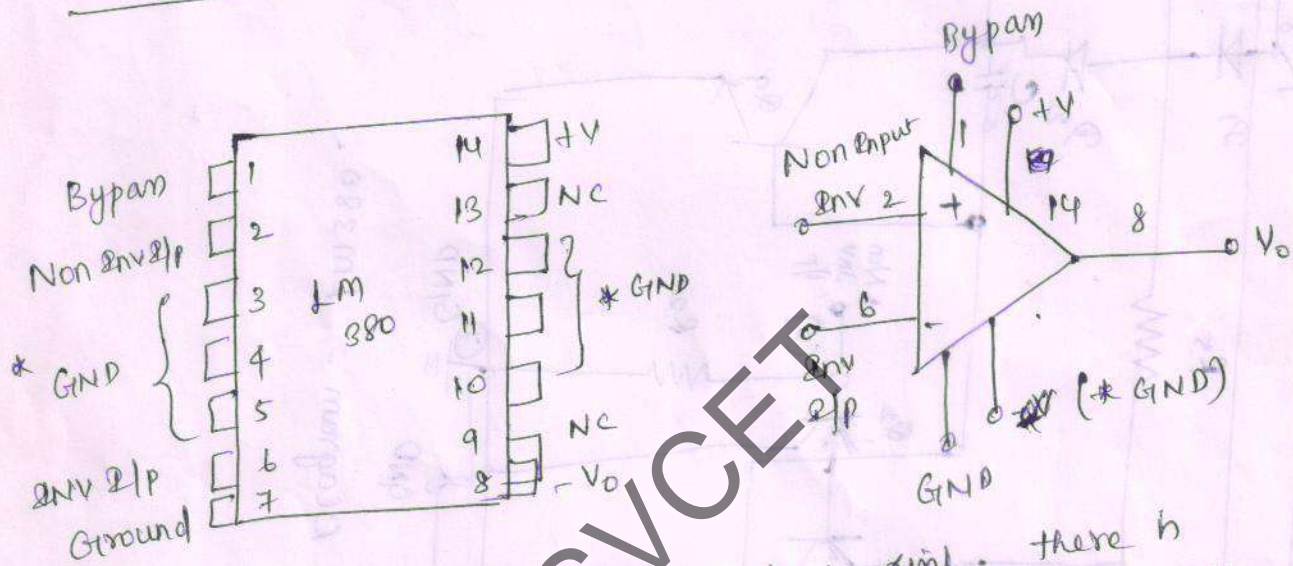- 1) Isolation voltage of  $\pm 2500V$
  - 2) High dc current transfer ratio
  3. Low cost dual in line package.
- Other Various packages of IC optocoupler
- In the six pin dual in line package, optocoupler with photodarlington is also available

Audio Amp Power Amp Lifter - basically used to amplify audio signals  
 Deliver various amount of power are nearly compact.  
 Features of LM380 popular power audio amplifier => Delivers 2.5watts min 8Ω load

→ High Impedance  
 → standard dual in-line package. 14 pins  
 Power amplifier also called as large signal amplifier  
LM380 pin diagram \* circuit description




DIP package of LM380 comprises heat sink. there is no need to use separate heat sink for audio amplifier (\* GND for heat sink).

Schematic Diagram of LM380

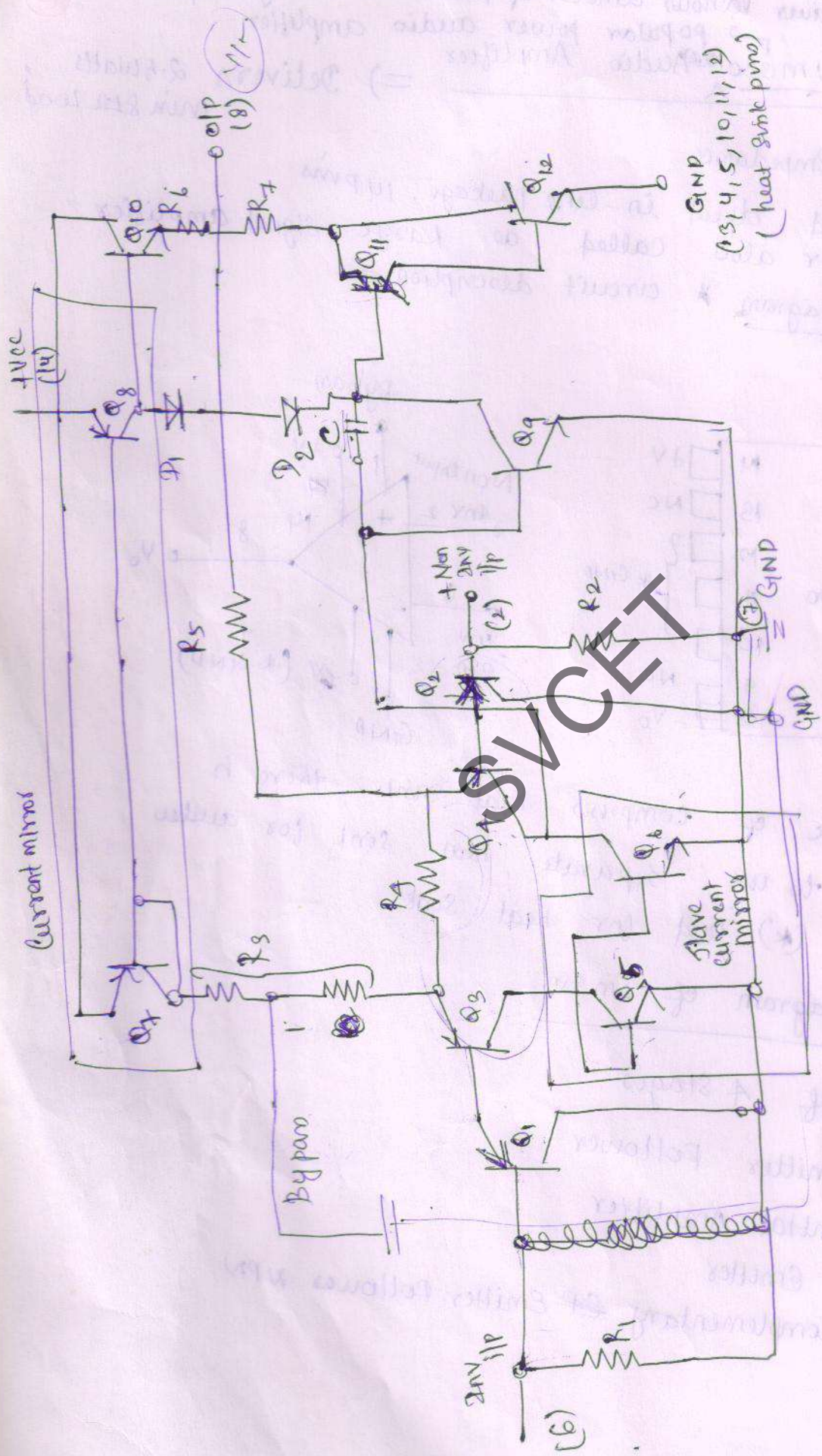- Composed of 4 stages
- a) PNP Emitter Follower
  - b) Differential Amplifier
  - c) Common Emitter
  - d) Quasi complementary ~~PP~~ Emitter Follower NPN





LM380 Pin Diagram  
 → standard power amplifier circuit design  
 → high gain  
 → standard power amplifier circuit design  
 → standard power amplifier circuit design

Schematic Diagram - LM380

SECRET



- 21P is emitter followers composed of PNP transistors  $(Q_1, Q_2)$
- This is  $Q_3 - Q_4$ , the differential amplifier. PNP transistor input is coupled through  $2N \times 2N$  terminal
- $Q_1$  &  $Q_2$  allows input to be referenced to ground
- i/p can be given to inverting or non inverting terminals. It is biased by  $R_3$  &  $R_5$
- current in PNP differential pair  $Q_3 - Q_4$  is established by  $Q_7$ ,  $R_3$  and  $+V_{cc}$  current mirror formed by transistors  $Q_7, Q_8$  and associated resistors then establishes collector current  $Q_9$
- $Q_5$  &  $Q_6$  constitute collector load. o/p of differential amplifier is taken at  $Q_4$  &  $Q_6$  transistor and applied to o/p of common emitter voltage gain ( $Q_9$ )
- common emitter stage is formed by  $Q_9$  with  $Q_1, Q_2$  &  $Q_8$  as current source load.
- C between collector & base of  $Q_9$  provides internal compensation. [feedback capacitor used to stabilize amplifier against any type of oscillation]
- $R_6$  &  $R_7$  used as current limiting resistor.  $Q_7$  &  $Q_8$  forms current mirror, the current through  $Q_1$  &  $Q_2$  is same as  $R_3$
- for transistors  $Q_{10}$  &  $Q_{11}$ . to avoid cross over distortion compensating diodes →
- ~~$Q_{10}$  current through  $Q_{10}, Q_{11} - Q_{12}$  is approximately equal to current through diodes.~~
- o/p is false complementary pair emitter follower formed by NPN transistors  $Q_{10} - Q_{12}$ . The o/p

- Combination of PNP  $Q_{11}$  & NPN  $Q_{12}$  but characteristics of power capability of NPN
- ~~otp~~ stage, o/p voltage is centered at one  $(+V)$ , which allows max peak to peak voltage swing  $\times$  therefore max ac o/p voltage
- negative feedback applied through  $R_5$  balances differential amplifier, so dc o/p voltage is stabilized at  $+V/2$
- To decouple otp stage from supply voltage  $+V$ , a bypass capacitor on the order of microfarads should be connected b/w bypass terminal (pin 1) & ground (pin 7)
- voltage gain can be increased by positive feedback.


### Applications of LM380 Audio Amplifier.

The number of external components in LM380 is very less. It is used for consumer applications.

1. LM380 as Audio power amplifier
2. Bridge power audio amplifier
3. Intercom System
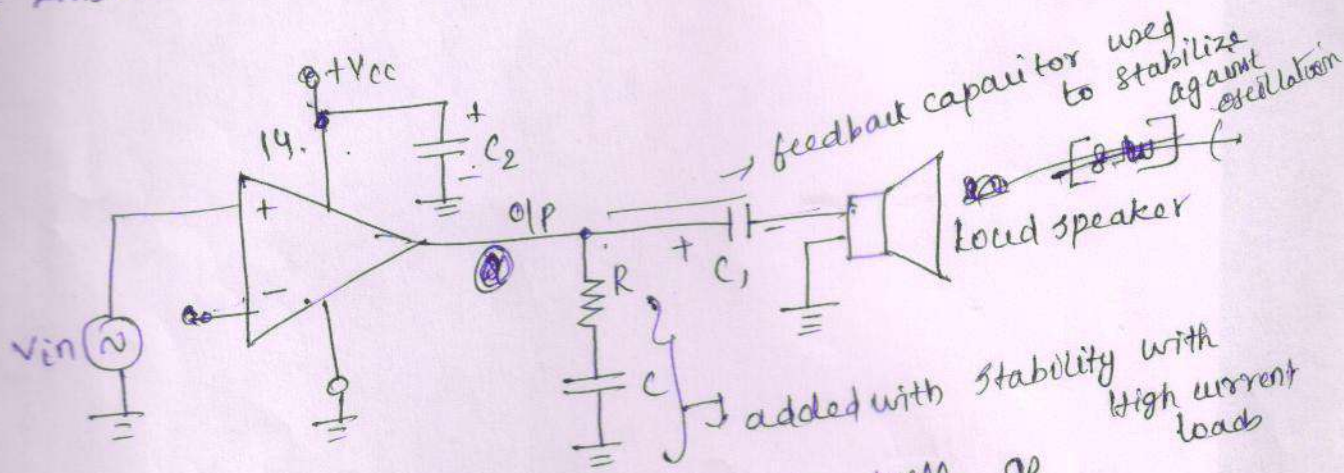
# 1. LM380 as Audio Power Amplifier

The simplest and most basic application of LM380 is an audio power amplifier



→ The RC can be used in inverting as well as non inverting configuration. In inverting mode, inverting can be grounded through resistor or capacitor. In non inverting mode, inverting can be grounded through resistor or capacitor.


→ In both the configurations, supply voltage must be decoupled by connecting a capacitor between terminal <sup>+V</sup> and ground.

→ precautionary measure RC combination should be used as output to eliminate 5 to 10 MHz oscillation


→ The capacitor C<sub>2</sub> is used to eliminate effects of inductance in power supply leads

Switch mode Power supply - (100 - 240 V) AC [personal computers Mobile phone chargers] [get power from most main electricity]

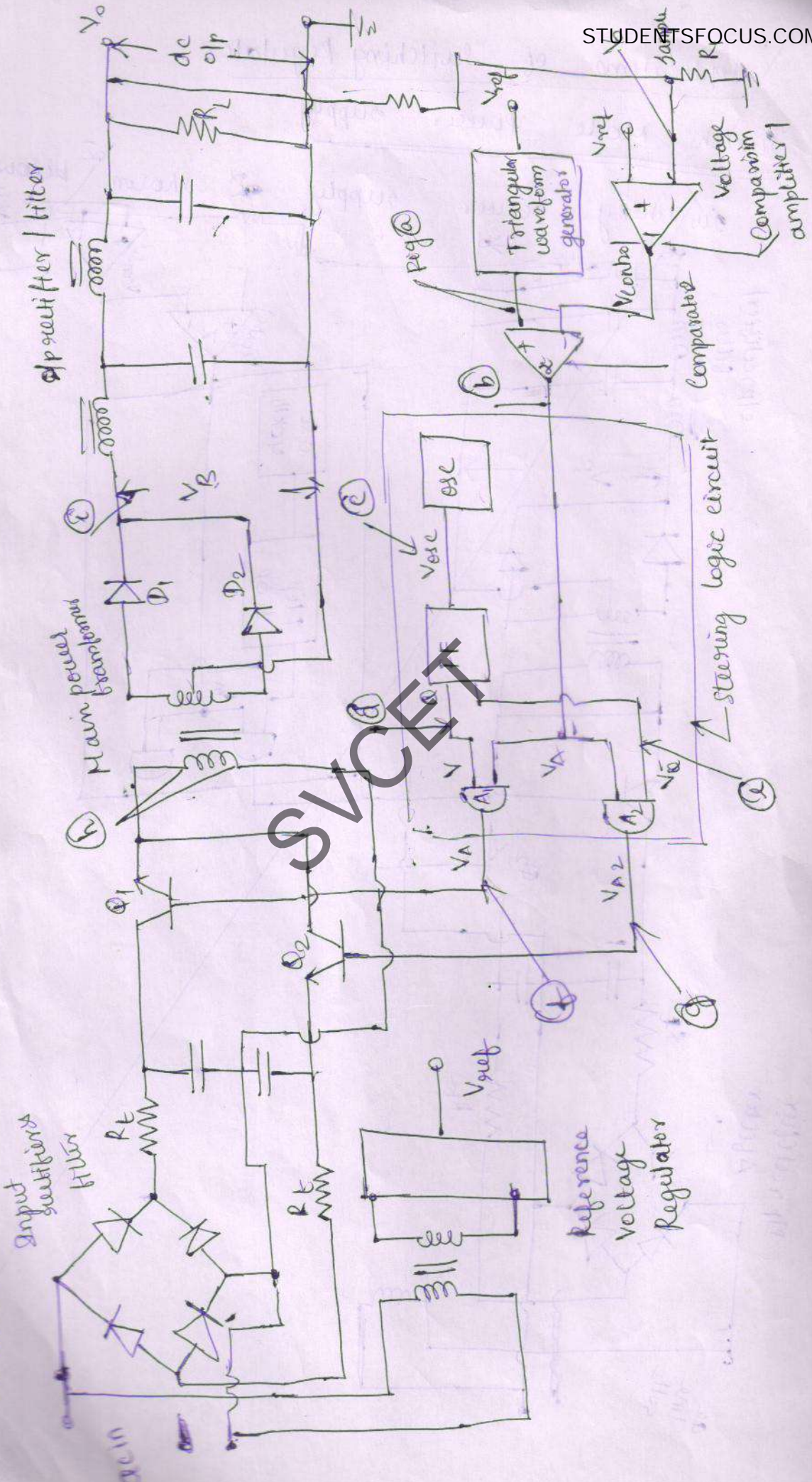
The transformer is driven at much H.F than main the switch mode power supply is shown below



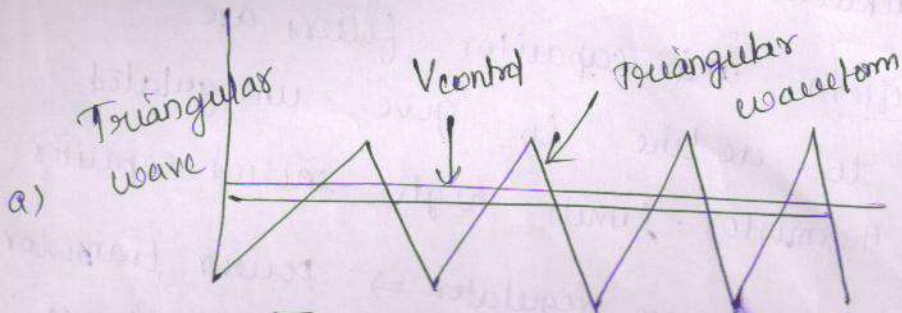
- 1) The bridge rectifiers and capacitor filters are connected directly to ac line to give unregulated dc output.  $R_t$  - thermistor. limits high inrush capacitor charge current.  $\rightarrow$  reference regulator  $\Rightarrow$  power transistor reference voltage,  $V_{ref}$  which serves as a power supply voltage. current small and power loss wont affect efficiency of switched mode power supply.
- 2)  $Q_1$  &  $Q_2$  are alternatively switched off and on. Dissipate very little power.
- 3) These transistors drive the primary of main transformer. The secondary is centre tapped and full wave rectification is achieved by diodes  $D_1$  &  $D_2$ .
- 4) Unidirectional square wave is next filtered through a stage LC filter to produce  $V_o$ .
- 5) Regulation of  $V_o$  is achieved by feedback circuit consisting of pulse width modulator and steering logic circuit.
- 6)  $V_o$  is sampled by  $R_1, R_2$  divider (voltage divider) is compared with  $V_{ref}$  in comparator. o/p of voltage comparison is called  $V_{control}$ .




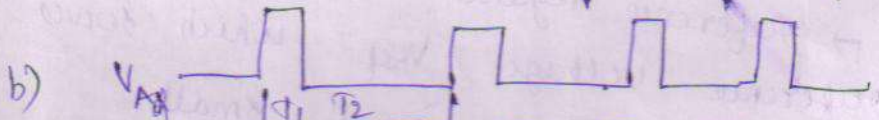
→ Vcontrol is applied to - of comparator 2 & triangular wave is applied to +ve



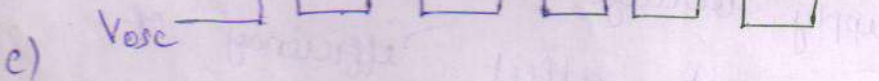
→ Comp 2 functions as pulse width modulator & its o/p square wave  $V_A$



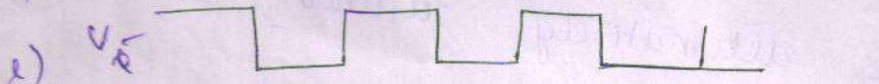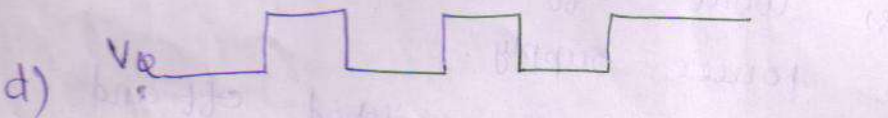→  $V_A$  produces  $V_{\phi}$ ,  $V_{\phi}^*$  ( $V_A$  drives steering logic)




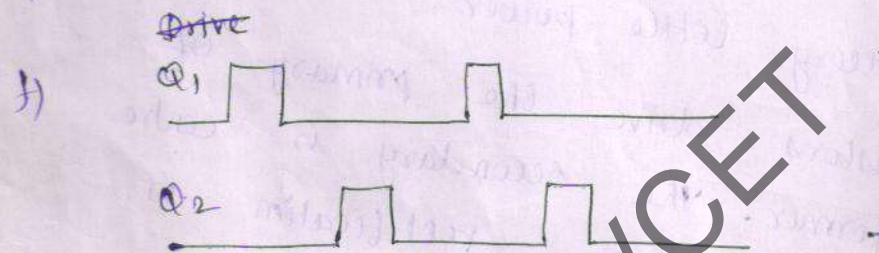
→ o/p  $V_{A1}$  &  $V_{A2}$  of AND  $\times 1 \times 2$   $Q_1$  or  $Q_2$  on, waveform will be square or  $V_B$



→ If  $Q_1$ , Vcontrol ↑ will reduce pulse width

→ Reduction in pulse width lowers average value of dc o/p  $V_o$ .

→ initial ↑ in dc voltage gets nullified

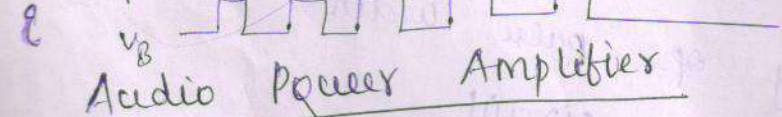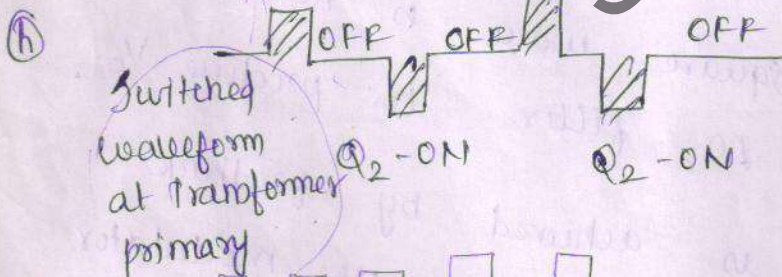

Audio Power Amplifiers

→ After this Refer

→ The power amplifier differs from general purpose op-amps in delivering various amount of power are nearly compact.  
 → LM380 is a popular power audio amplifier produced by National Semiconductor