

## Unit 1 - Introduction

The function of Power System is to convert energy from other forms to electricity and distribute it to the consumers. The primary objective of an electric Power system is to deliver the power (or) Energy demanded by all the consumers, in full during all the time by generating the required power. The

Power system components are

- \* Generating station
- \* Transmission system
- \* Distribution system


The power system analysis is required for different purposes. They are

- (a) To monitor the voltage at various buses, real and reactive power flow between all the buses.
- (b) To maintain system frequency within  $\pm 0.5\%$
- (c) To maintain system voltage within  $\pm 5\%$  of rated system voltage

(d) To study the ability of the system for large disturbances and small disturbances

(e) To analyze the system under different fault conditions (3 $\phi$  fault, LG, LL, LLG, faults)

### Structure of Power System

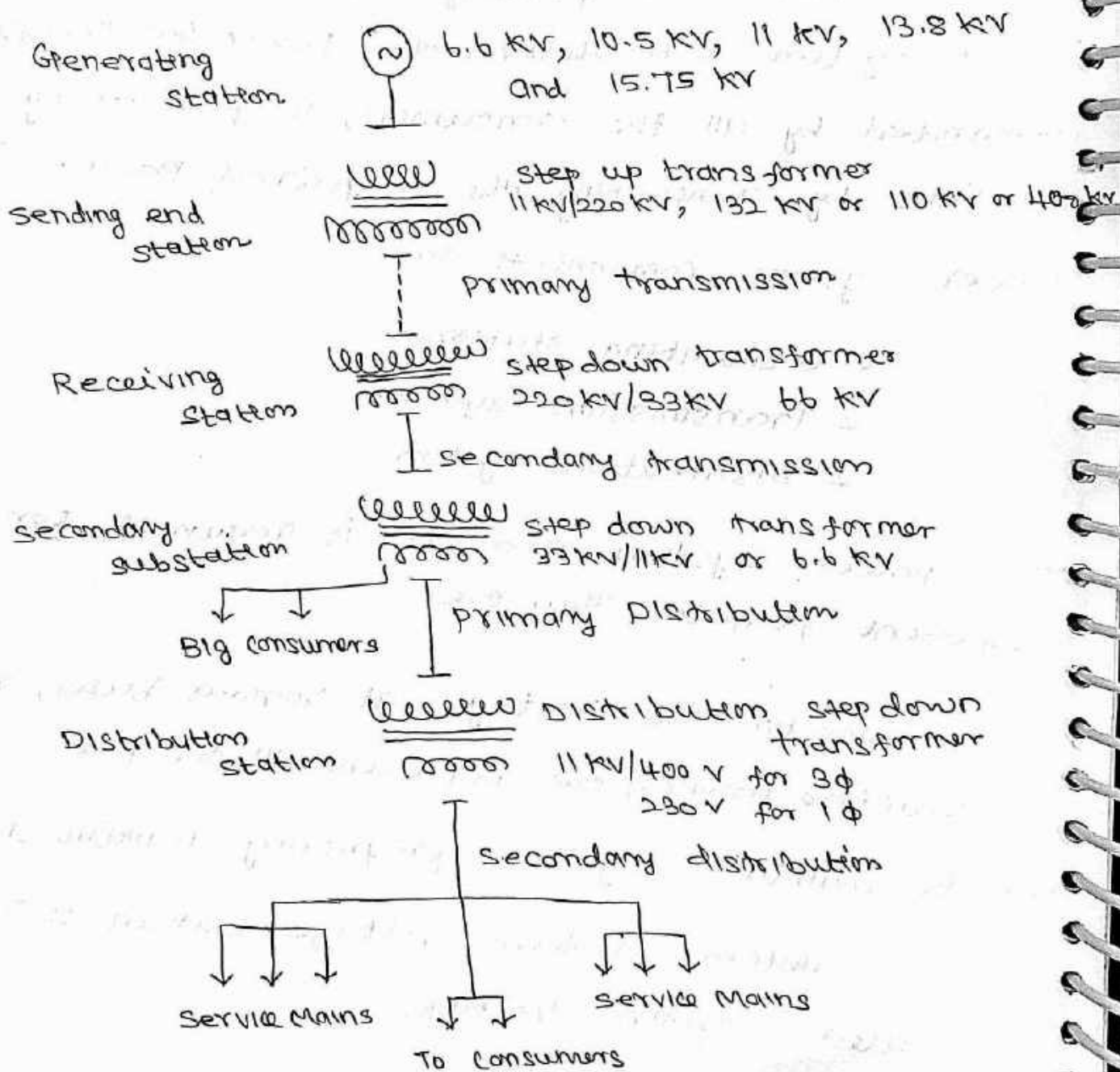

# Components of an electric power system

## Generators

\* Mechanical energy into electrical energy

## Transformers

\* One circuit to other circuit without change of frequency

## Transmission line

\* Transform power from one location to other

## Control equipments

\* protection devices

### primary Transmission

10 kv, 132 kv, 220 kv, 400 kv

765 kv 3 $\phi$  3 wire system

### primary distribution

11 kv or 6.6 kv

3 $\phi$ , 3 wire system

### Secondary Transmission

33 kv or 66 kv feeders

3 $\phi$ , 3 wire

### Secondary distribution

400 v - 3 phase

230 v - single phase

## Vertically Integrated power system

\* Generation

\* Transmission

\* Distribution

## Deregulated Power System

\* Pool market

\* Spot market

\* Bilateral market

## Various studies in power system:

- \* Load flow
- \* Short circuit studies
- \* Stability studies
- \* Economic dispatch
- \* Electromagnetic Transient Analysis
- \* Load frequency control


## Need for system planning and operational studies:

### Power Balance equation

$$P_D = \sum_{i=1}^N P_{Gi}, \quad i=1, 2, \dots, N$$

- \* When this relation is satisfied, it gives good economy and security.
- \* Planning and Operational analysis covers the maintenance of G-T-D facility. Planning for future expansion of a power system is essential.
- \* The following analysis are more important for planning and operation of the system.

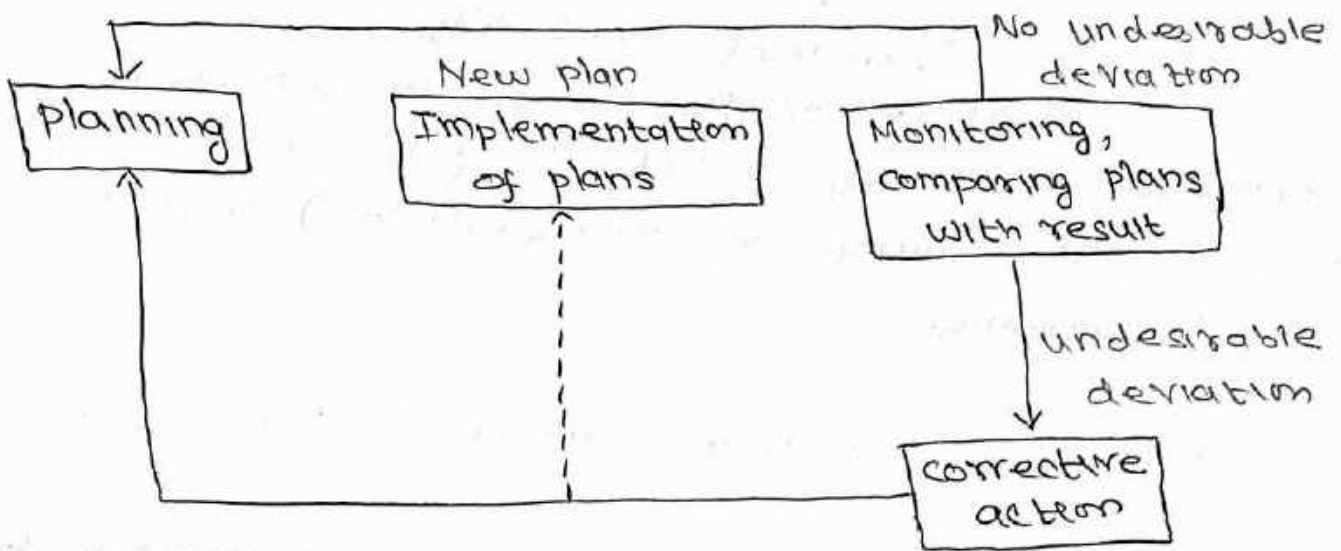Load flow analysis  
Short circuit analysis  
Transient analysis



\* These studies simulate the behavior of the system under normal and abnormal operating conditions.

\* To overcome the deficiencies remedial planning actions and corrective operational control actions are taken.

Load flow Analysis - Power flow studies - determine the voltage, current, active and reactive power flow

Short circuit studies - precisely determine the current and voltages at different locations of the system corresponding to different type of fault.

Transient stability Analysis - ability of PS to continue to operate after a change occurs on the system.


Stability - steady state

Transient stability


ability of power s/m to remain in synchronism following relatively (slow load change or continued change in generation.) under large disturbances

Components and equivalent circuit of power system


Generator

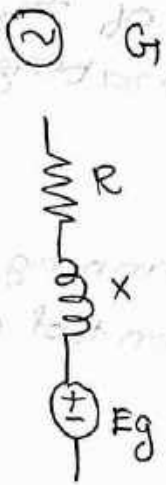


Motor

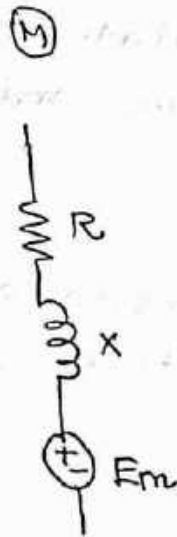

Transmission line

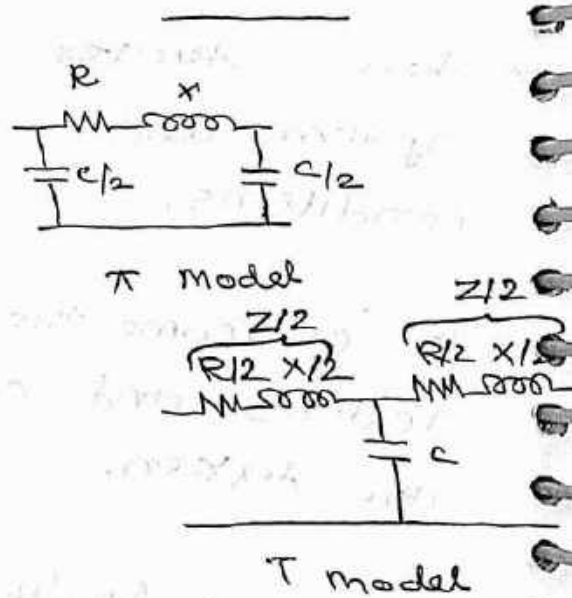

Transformer

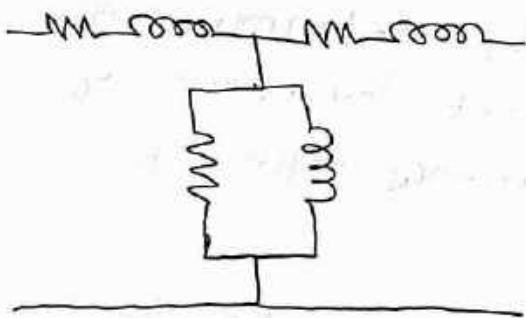

Current transformer



Potential transformer



3-winding transformer



2-winding transformer








Single line Diagram - diagrammatic representation of Power system in which the components are represented by their symbols and interconnections them are shown by a straight line.

Purpose of SLD: To represent power system network in simplest form without loosing significance about the system.

Per phase Analysis:

Balanced 3 $\phi$  s/m - per phase basis - considering one of 3 $\phi$  line and neutral



Per phase representation of Generator

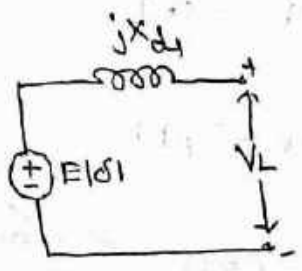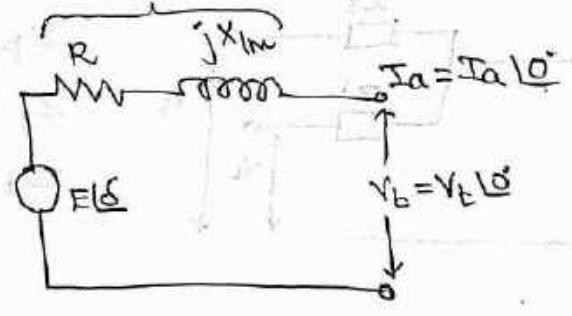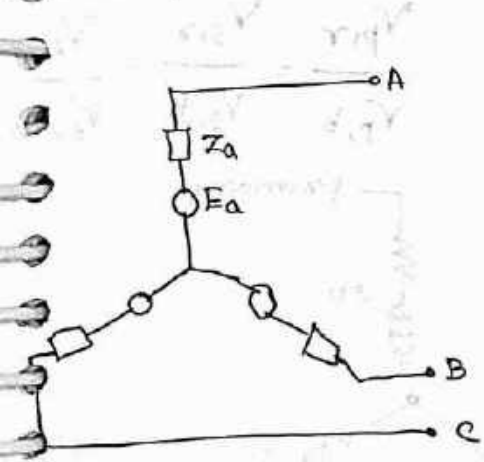


$$V_a = E - I_a (R + jX_{Lm})$$

$$X_{Lm} = X_d + X_m$$

Transmission line

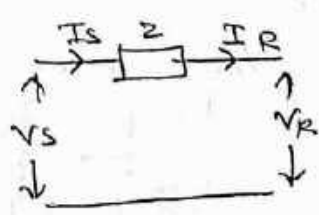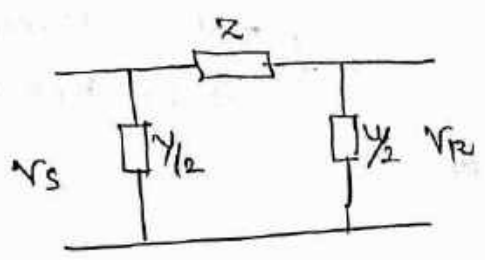

# Two Winding Transformer


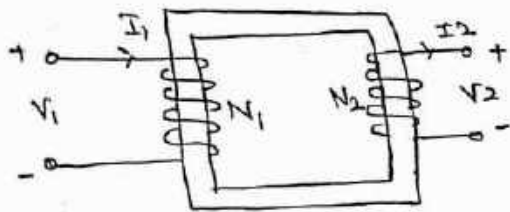


$$K = \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$


$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$

$$I_2' = \frac{I_2}{K}$$

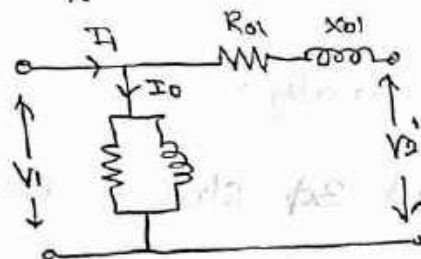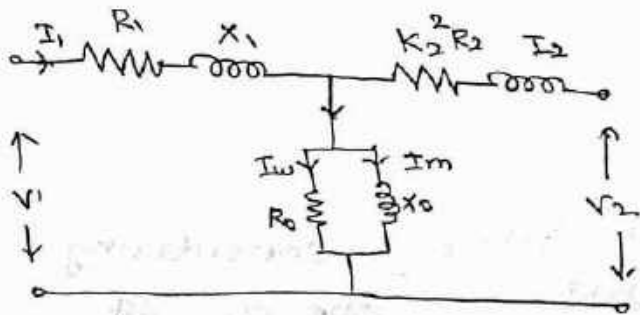

# Three winding Transformer

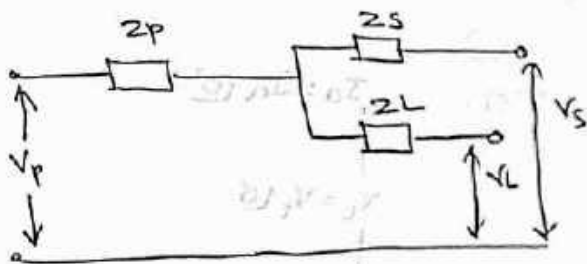

$$Z_{ps} = Z_p + Z_s$$

$$Z_{pt} = Z_p + Z_L$$


$$Z_{st} = Z_s + Z_L$$

$$\frac{V_{p,r}}{V_{p,b}} = \frac{V_{s,r}}{V_{s,b}} = \frac{V_{t,b}}{V_{t,r}}$$

$$Z_p = \frac{1}{2} (Z_{ps} + Z_{pt} - Z_{st})$$


$$Z_s = \frac{1}{2} (Z_{ps} + Z_{st} - Z_{pt})$$
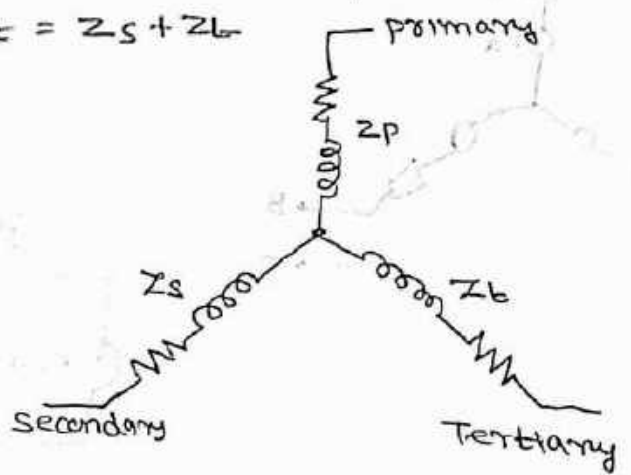
$$Z_L = \frac{1}{2} (Z_{pt} + Z_{st} - Z_{ps})$$



Two

# winding Transformer with tap

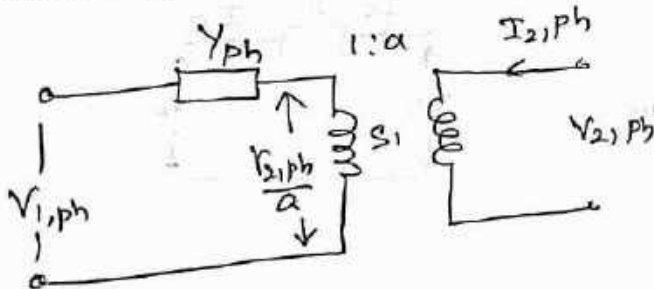

If  $a = 1$  nominal tr.

$a \neq 1$  tr with tap



$$S_1 = -S_2$$

$$\frac{V_2}{a} I_1^* = -V_2 I_2^* \quad ; \quad I_2^* = +\frac{I_1^*}{a}$$


$$I_1 = \left[ V_1 - \frac{V_2}{a} \right] Y = V_1 Y - \frac{V_2}{a} Y$$

$$I_2 = -\frac{Y}{a^2} V_1 + \frac{V_2}{|a|^2} Y$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y & -Y/a \\ -Y/a & Y/a^2 \end{bmatrix}$$

Singular matrix  
Non-symmetrical matrix

Auto-transformer

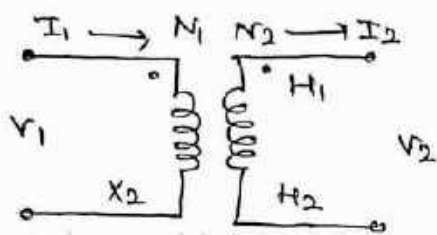

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a \quad \frac{I_2}{I_1} = \frac{N_1}{N_2} = a$$

$$V_H = V_1 + V_2$$

$$V_H = V_2 + \frac{N_1}{N_2} V_2$$

$$V_2 = V_L$$

$$= (1+a) V_L$$

$$\frac{V_H}{V_L} = 1+a$$

For Ideal Transformer

$$N_2 I_2 = N_1 I_1$$

$$I_L = \frac{N_1 + N_2}{N_2} I_1$$

$$\frac{I_L}{I_1} = 1+a$$

# Load Representation

(i) constant current

Voltage vary  
frequency vary

$$I_1 = I_2$$

$$I = \frac{P - jQ}{V^*}$$

$$V = |V| \angle \theta$$

$$\theta = \tan^{-1}\left(\frac{Q}{P}\right)$$

(ii) constant power

MVAR } constant  
MW }

$$P_1 = P_2 \quad Q_1 = Q_2$$

## Per Unit Analysis - Representation

\* Ratio of the actual value of any quantity to the base value of same quantity

$$\text{Per unit value} = \frac{\text{Actual value}}{\text{Base value}}$$

## Advantages of P.U. System

\* Manufacturer's - specify ratings in per unit.

\* Reduce complexity

\* Computerized analysis and simulation of complex power s/m problems

\* circuit law are valid, bcoz  $\sqrt{3}$  and 3 are eliminated


\* 3  $\phi$  transformer, p.u analysis is same for star and delta connected networks

Base value the voltage, current and impedance rating of components of PS are expressed with reference to common value.
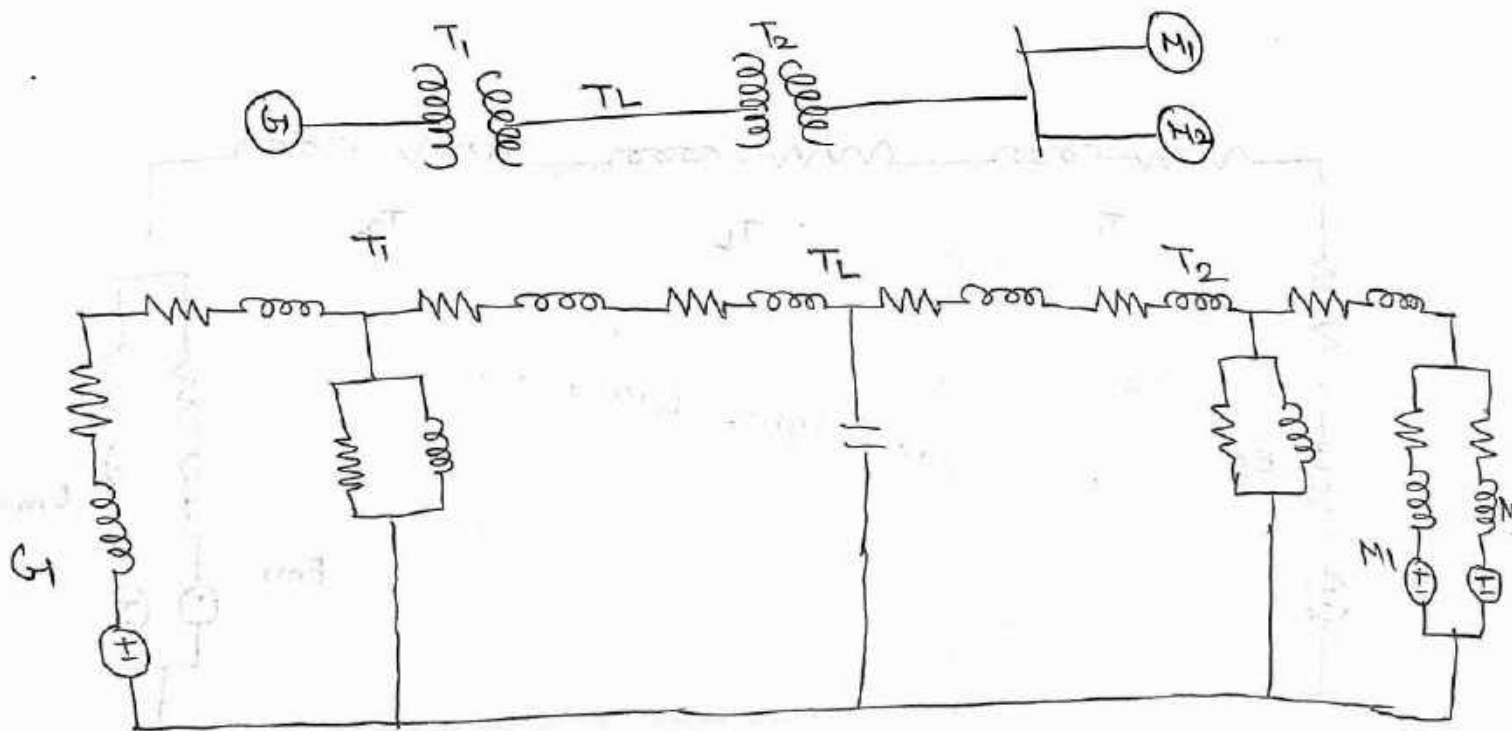
### Selection of Base Values

\* Base MVA chosen - Same MVA will be used in all parts of S/m.

\* Rated voltage of largest section - Base kV depends on turns ratio.





Impedance diagram - equivalent circuit of power S/m various components - represented - simplified equivalent circuit.

Reactance Diagram - represented by reactances - used for fault calculations

Reactance Diagram - obtained from Impedance diagram  
 ↳ We omit all static loads, all resistance, shunt branches of br's and capacitance of Tr. line

Assumptions to make Reactance diagram

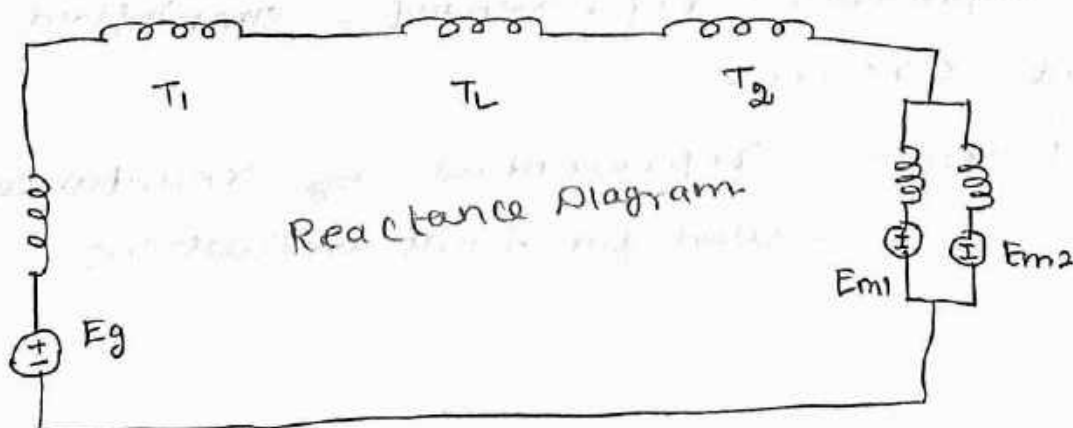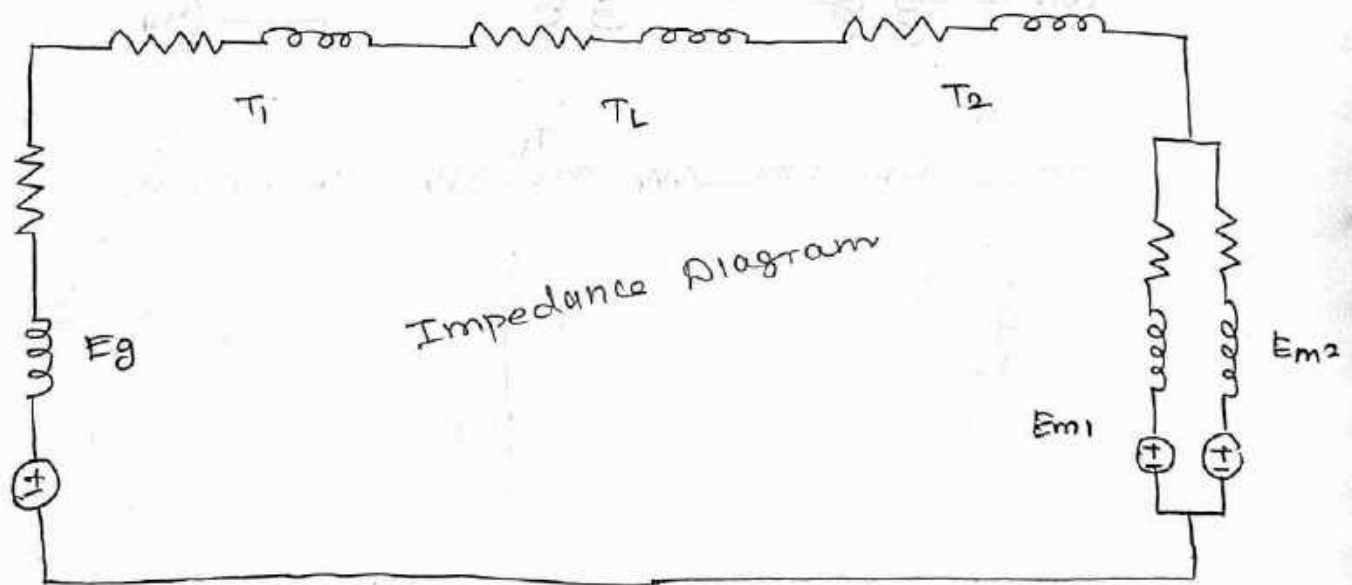- \* Neutral reactances are neglected
- \* resistance, static loads, capacitance neglected
- \* shunt branches in equivalent ckt of transformer are neglected



Per Unit Impedance - Single phase system

$$P = VI$$

$$I = \frac{P}{V} = \frac{KVAB_b}{KV_b}$$

$$\text{P.u Voltage} = \frac{V}{V_b} \text{ p.u} \quad \text{P.u current} = \frac{I}{I_b} \text{ p.u}$$

$$\text{Base Impedance} = Z_b = \frac{V_b}{I_b} \text{ ohm} = \frac{V_b}{I_b} \times \frac{1000}{1000}$$

$$Z_b = \frac{KV_b}{I_b} \times 1000$$

$$\text{Base current } I_b = \frac{KVAB_b}{KV_b} \times \frac{1000}{1000}$$

$$I_b = \frac{MVA_b}{KV_b} \times 1000 \text{ amps}$$

$$Z_b = \frac{KV_b \times 1000}{\frac{MVA_b \times 1000}{KV_b}}$$

$$Z_b = \frac{(KV_b)^2}{MVA_b}$$

$$Z_{p.u} = \frac{Z_{actual}}{Z_{Base}}$$

$$= \frac{Z_{actual}}{KV_b^2 / MVA_b}$$

$$\therefore Z_{p.u} = \frac{Z_{actual} \times MVA_b}{KV_b^2}$$

Per unit Impedance - 3 $\phi$  system

$$\text{Base current } I_b = \frac{\text{KVAB} \times 1000}{\sqrt{3} \text{KV}_b \times 1000}$$

$$I_b = \frac{\text{MVA}_b \times 1000}{\sqrt{3} \text{KV}_b}$$

$$Z_b = \frac{\text{KV}_b}{\sqrt{3} I_b} \times 1000 = \frac{\text{KV}_b}{\sqrt{3} I_b} \times 1000$$

Substitute  $I_b$   
value here

$$\therefore Z_b = \frac{\text{KV}_b^2}{\text{MVA}_b}$$

Change of Base Values:

$$Z_{p.u}(\text{old}) = \frac{Z_{\text{act}}}{Z_{\text{base}}} = \frac{Z_{\text{actual}}}{\frac{\text{KV}_b^2(\text{old})}{\text{MVA}_b(\text{old})}}$$

$$Z_{p.u}(\text{old}) = Z_{\text{act}} \times \frac{\text{MVA}_b(\text{old})}{\text{KV}_b^2(\text{old})}$$

$$Z_{p.u}(\text{new}) = Z_{\text{act}} \times \frac{\text{MVA}_b(\text{new})}{\text{KV}_b^2(\text{new})}$$

$$\therefore Z_{\text{act}} = \frac{Z_{p.u}(\text{old}) \times \text{KV}_b^2(\text{old})}{\text{MVA}_b(\text{old})}$$

old values  $\rightarrow$  given values



$$Z_{pu}(new) = \frac{Z_{pu}(old) \times KV_b^2(old) \times MVA_b(new)}{MVA_b(old) \times KV_b^2(new)}$$

$$\therefore Z_{pu}(new) = Z_{pu}(old) \times \left[ \frac{KV_b(old)}{KV_b(new)} \right]^2 \times \frac{MVA_b(new)}{MVA_b(old)}$$

Similarly

$$X_{pu,new} = X_{pu,old} \times \left[ \frac{KV_b(old)}{KV_b(new)} \right]^2 \times \frac{MVA_b(new)}{MVA_b(old)}$$

Procedure to form P.u. Impedance (or) Reactance


diagram:

Step 1: Choose a common base KV and base MVA for the entire section.

Step 2: Divide the s/m into various section - different voltage level

Step 3: Base MVA will be remaining the same for all the sections of the system

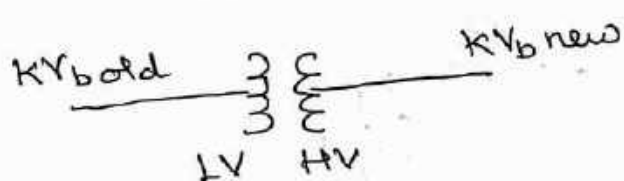
Step 4: Find out the base KV for each and every section by using the relation.



$$\frac{\text{Base KV on HT side}}{\text{Base KV on LT side}} = \frac{\text{Voltage on HT side}}{\text{Voltage on LT side}}$$

$$KV_{b,new} = KV_{b,old} \times \frac{\text{HT side rating}}{\text{LT side rating}}$$

$KV_{b,new}$

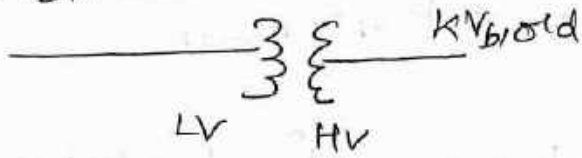

$$\frac{\text{Base KV on LT side}}{\text{Base KV on HT side}} = \frac{\text{Voltage on LT side}}{\text{Voltage on HT side}}$$

$$KV_{b,new} = KV_{b,old} \times \frac{\text{LT side rating}}{\text{HT side rating}}$$

Step 5: Calculate per unit value


$$Z_{pu} = \frac{Z_{act}}{Z_b} \quad Z_b = \frac{KV_b^2}{MVA_b}$$

Step 6: Convert pu value to New base values


$$Z_{pu,new} = Z_{pu,old} \times \left[ \frac{KV_{b,old}}{KV_{b,new}} \right]^2 \times \left[ \frac{MVA_{b,new}}{MVA_{b,old}} \right]$$

Reactance Diagrams for Power Sys Components:


Alternator

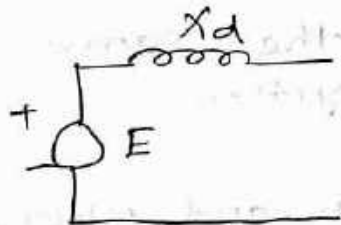


Transmission line

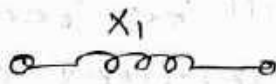


Transformer

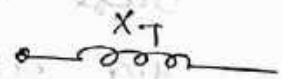

Load

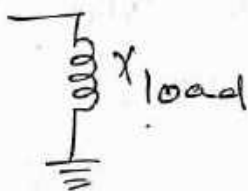

Synchronous motor

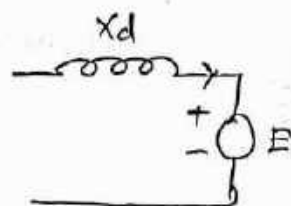

U1.19

generator has a reactance of 10 ohm. Find the value for the base values of 11 kV, 5 MVA.

$$Z_{act} = 10 \Omega \quad kV_b = 11 \text{ kV} \quad MVA_b = 5 \text{ MVA}$$

$$Z_{pu} = \frac{Z_{act}}{Z_b} \quad Z_b = \frac{kV_b^2}{MVA_b} = \frac{11^2}{5} = 24.2 \Omega$$

$$= \frac{10}{24.2} = 0.4132 \text{ pu}$$

A 3 $\phi$  generator with rating 1000 kVA, 33 kV has its armature resistance and synchronous reactance as 20  $\Omega$ /p and 70  $\Omega$ /p. Calculate pu impedance of the generator.

$$kV_b = 33 \text{ kV} \quad kVA_b = 1000 \text{ kVA}$$

$$MVA_b = 1 \text{ MVA}$$

$$Z_{act} = (20 + j70) \text{ Ohm/phase}$$

$$Z_b = \frac{kV_b^2}{MVA_b} = \frac{33 \times 33}{1} = 1089 \Omega$$

$$\therefore Z_{pu} = \frac{20 + j70}{1089} = 0.0184 + j0.064 \text{ pu}$$

If base MVA is 50, base kV is 22 kV.

(a) find base current

For 1 $\phi$  system,

$$I_b = \frac{MVA_b \times 1000}{kV_b} = \frac{50 \times 1000}{22} = 2272.22 \text{ AMPS}$$

For 3 $\phi$  system

$$I_b = \frac{MVA_b \times 1000}{\sqrt{3} KV_b} = \frac{50 \times 1000}{\sqrt{3} \times 22} = 1312.159 \text{ Amps}$$

b) What is the new pu impedance, if the new base MVA is twice the old base MVA?

$$\begin{aligned} MVA_{b, \text{new}} &= 2 \times MVA_{b, \text{old}} \\ &= 2 \times 50 = 100 \text{ MVA.} \end{aligned}$$

$$KV_b = 22$$

$$Z_b = \frac{KV_b^2}{MVA_b} = \frac{22^2}{100} = 4.84 \Omega$$

④ A generator rated 500 MVA, 22 kV. Its Y-connected winding has a reactance of 1.1 pu. Find the actual value of the reactance of winding.

$$MVA_b = 500 \text{ MVA} \quad KV_b = 22 \text{ kV}$$

$$Z_b = \frac{KV_b^2}{MVA_b} = \frac{22 \times 22}{500} = 0.968 \Omega$$

$$X_{pu} = \frac{X_{\text{actual}}}{X_{\text{base}}} = \frac{X_{\text{actual}}}{0.968}$$

$$\begin{aligned} X_{\text{actual}} &= 1.1 \times 0.968 \\ &= 1.0648 \end{aligned}$$

⑥ The new base values are 100 MVA, 20 kV. Then find the p.u value of reactance diagram of generator winding on the specified base.

$$X_{pu, \text{new}} = X_{pu, \text{old}} \times \left[ \frac{KV_{b, \text{old}}}{KV_{b, \text{new}}} \right]^2 \times \left[ \frac{MVA_{b, \text{new}}}{MVA_{b, \text{old}}} \right]$$

$$= 1.1 \times \left( \frac{22}{20} \right)^2 \times \frac{100}{500} = 0.2662 \text{ pu}$$

A generator has a reactance of  $j0.2$  pu under the base voltage of 13 kV and base MVA of 10. Find the new pu value of the generator when referred to base value of 11 kV and 15 MVA.

$$X_{pu,old} = j0.2 \quad KV_{b,old} = 13 \text{ kV}$$

$$MVA_{b,old} = 10 \text{ MVA}$$

$$KV_{b,new} = 11 \text{ kV} \quad MVA_{b,new} = 15 \text{ MVA}$$

$$X_{pu,new} = X_{pu,old} \times \left[ \frac{KV_{b,old}}{KV_{b,new}} \right]^2 \times \frac{MVA_{b,new}}{MVA_{b,old}}$$

$$= j0.2 \times \left[ \frac{13}{11} \right]^2 \times \frac{15}{10}$$

$$= j0.419 \text{ pu}$$

A 120 MVA, 19.5 kV generator has a synchronous reactance of 0.15 pu and it is connected to a transmission line through a transformer rated 150 MVA 230/18 kV (Y/A) with  $X = 0.1$  pu

(a) calculate the p.u reactance by taking generator ratings as base value.

$$X_{pu,old} = 0.1 \text{ pu}$$

$$KV_{b,old} = 18 \quad MVA_{b,old} = 150$$

$$KV_{b,new} = 19.5 \quad MVA_{b,new} = 120$$

New pu reactance of the transformer  
( $X_{pu,new}$ ) = 0.0682 pu

⑥ Calculate the p.u reactance by taking transformer rating as base values.

$$\begin{aligned} \text{MVA}_{b, \text{new}} &= 150 \text{ MVA} & X_{\text{p.u}} &= 0.1 \text{ pu} \\ \text{kV}_{b, \text{new}} &= 18 \text{ kV} & & \text{(old)} \end{aligned}$$

$$X_{\text{pu, new}} = 0.1 \times \left( \frac{18.5}{18} \right)^2 \times \frac{150}{120}$$

$$= 0.22 \text{ pu}$$

⑦ The three phase ratings of a three-winding transformer are:

primary  $\gamma$ -connected 132 kV, 20 MVA  
 secondary  $\gamma$ -connected 33 kV, 15 MVA  
 tertiary  $\Delta$ -connected 11 kV, 10 MVA

Neglecting resistance, the leakage impedances are:

$$Z_{ps} = 8\% \text{ on } 20 \text{ MVA, } 132 \text{ kV base}$$

$$Z_{pt} = 10\% \text{ on } 20 \text{ MVA, } 132 \text{ kV base}$$

$$Z_{st} = 9\% \text{ on } 15 \text{ MVA, } 33 \text{ kV base}$$

Find the p.u impedances of per-phase equivalent circuit for a base of 20 MVA, 132 kV in primary circuit

$$\text{kV}_{\text{base}} = 132 \quad \text{MVA}_{\text{base}} = 20$$

$$Z_{\text{p.u, new}} = Z_{\text{p.u, given}} \times \left[ \frac{\text{kV}_{b, \text{given}}}{\text{kV}_{b, \text{new}}} \right]^2 \times \frac{\text{MVA}_{b, \text{new}}}{\text{MVA}_{b, \text{given}}}$$

$$Z_{ps, \text{pu}} = j0.08 \times \left( \frac{132}{132} \right)^2 \times \frac{20}{20} = j0.08 \text{ pu}$$

$$Z_{pt, \text{pu}} = j0.1 \times \left( \frac{132}{132} \right)^2 \times \frac{20}{20} = j0.1 \text{ pu}$$



$$KV_{b, new} = KV_{b, old} \times \frac{LT \text{ side rating}}{HT \text{ side rating}} = 132 \times \frac{33}{132} = 33 \text{ KV}$$


$$Z_{st} = j0.09 \times \left(\frac{33}{33}\right)^2 \times \left(\frac{20}{15}\right) = j0.12 \text{ pu}$$

$$Z_p = \frac{1}{2} [Z_{ps} + Z_{pt} - Z_{st}] = \frac{1}{2} [j0.08 + j0.1 - j0.12] = j0.03 \text{ pu}$$

$$Z_s = \frac{1}{2} [Z_{ps} + Z_{st} - Z_{pt}] = j0.05 \text{ pu}$$

$$Z_t = \frac{1}{2} [Z_{pt} + Z_{st} - Z_{ps}] = j0.07 \text{ pu}$$

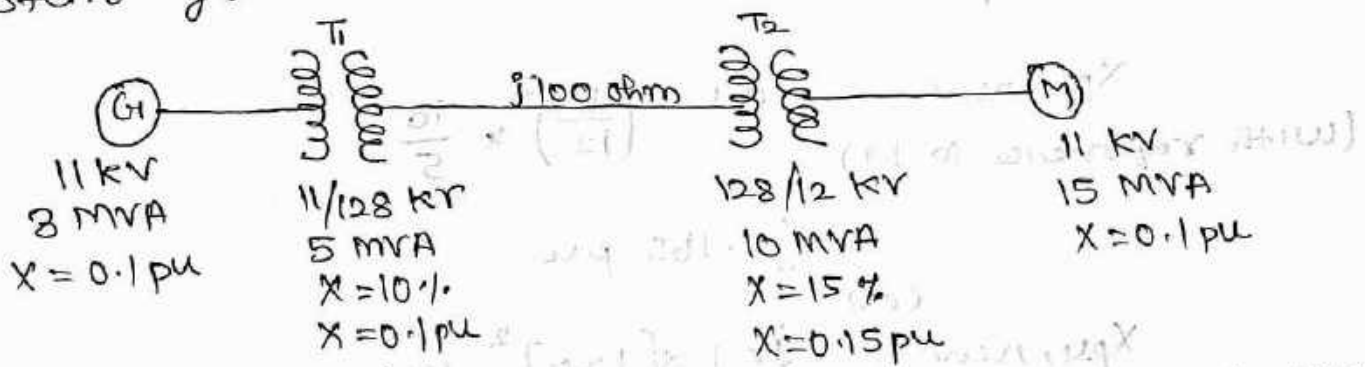Draw the reactance diagram for the sample power system given below



Choose a base KV of 12 KV and base MVA of 10 MVA on the generator side.

$$MVA_{b, new} = 10 \text{ MVA} \quad \text{Remain same for all s/m}$$

Section 1 :  $KV_{b, new} = 12 \text{ KV}$

Section 2 :

$$KV_b \text{ on HT side of } T_1 = KV_b \text{ on LT side} \times \frac{V.R \text{ on HT}}{V.R \text{ on LT}}$$

$$= 12 \times \frac{128}{11}$$

$$= 139.636 \approx 140 \text{ KV}$$

Section 3:

$$\begin{aligned}KV_b \text{ on HT side of } T_2 &= KV_b \text{ on HT side } T_2 \times \frac{LT \text{ Voltage}}{HT \text{ Voltage}} \\(KV_{b, \text{new}}) &= (KV_{b, \text{old}}) \times \frac{12}{128} \\&= 140 \times \frac{12}{128} \\&= 13.125 \text{ KV}\end{aligned}$$

For Generator

$$\begin{aligned}X_{pu, \text{new}} &= X_{pu, \text{old}} \times \left[ \frac{KV_{b, \text{old}}}{KV_{b, \text{new}}} \right]^2 \times \left[ \frac{MVA_{b, \text{new}}}{MVA_{b, \text{old}}} \right] \\&= j0.1 \times \left( \frac{11}{12} \right)^2 \times \frac{10}{3} \\&= j0.28 \text{ pu}\end{aligned}$$

For Transformer 1

$$\begin{aligned}X_{pu, \text{new}} &= j0.1 \times \left( \frac{11}{12} \right)^2 \times \frac{10}{5} \\(\text{with reference to LT}) \\&= j0.168 \text{ pu}\end{aligned}$$

(or)

$$\begin{aligned}X_{pu, \text{new}} &= j0.1 \times \left( \frac{128}{140} \right)^2 \times \left( \frac{10}{5} \right) \\(\text{with reference to HT}) \\&= j0.168 \text{ pu}\end{aligned}$$

For Transmission line:

$$X_{\text{base}} = \frac{KV_b^2}{MVA_b} = \frac{140 \times 140}{10} = 1960 \Omega$$

$$X_{p.u.} = \frac{X_{\text{actual}}}{X_{\text{base}}} = \frac{j100}{1960}$$

$$= j0.051 \text{ pu}$$

or transformer 2,


$$X_{pu, new} = j0.15 \times \left[ \frac{128}{140} \right]^2 \times \frac{10}{10}$$

$$= 0.125j \text{ pu}$$


For motor

$$X_{pu, new} = j0.1 \times \left[ \frac{11}{13.125} \right]^2 \times \frac{10}{15}$$

$$= j0.6146 \text{ pu}$$

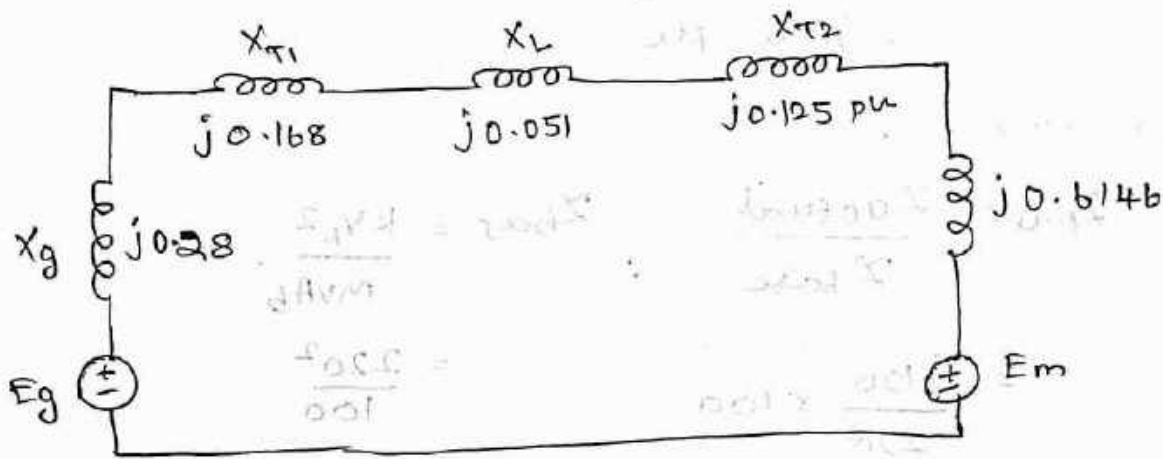

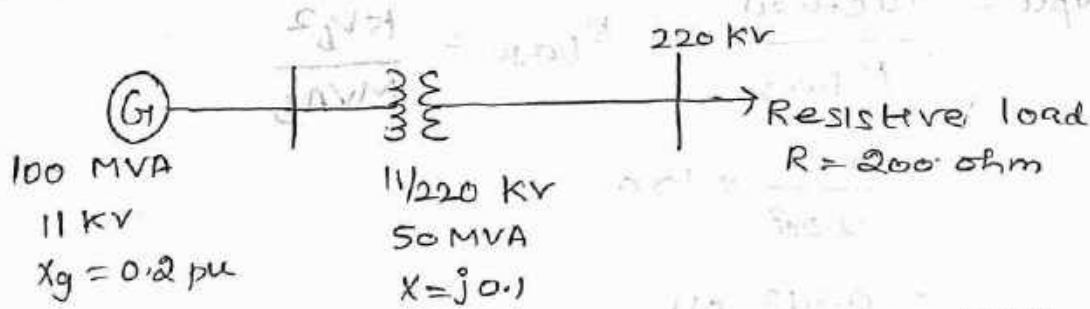For the system shown in below figure, obtain the impedance diagram



$$MVA_B = 100 \text{ MVA} = MVA_{B, new}$$

Section 1:  $kV_B = 11 \text{ kV}$

Section 2:

$$kV_B \text{ new (HT side)} = kV_{B, old} \times \frac{\text{HT voltage rating}}{\text{LT voltage rating}}$$

$$= 11 \times \frac{220}{11} = 220 \text{ kV}$$

For Generator:

$$Z_{pu, new} = Z_{p.u. old} \times \left[ \frac{KV_{b, old}}{KV_{b, new}} \right]^2 \times \frac{MVA_{b, new}}{MVA_{b, old}}$$
$$= j0.2 \times \left[ \frac{11}{11} \right]^2 \times \frac{100}{100}$$
$$= j0.2 \text{ pu}$$

For Transformer:

$$Z_{pu, new} = j0.1 \times \left[ \frac{11}{11} \right]^2 \times \frac{100}{50}$$
$$= j0.2 \text{ pu}$$

Transmission line:

$$Z_{pu} = \frac{Z_{actual}}{Z_{base}}$$

$$= \frac{j120}{220^2} \times 100$$

$$= j0.248 \text{ pu}$$

$$Z_{base} = \frac{KV_b^2}{MVA_b}$$


$$= \frac{220^2}{100}$$

For Resistive load:


$$R_{pu} = \frac{R_{actual}}{R_{base}}$$

$$= \frac{200}{220^2} \times 100$$

$$R_{base} = \frac{KV_b^2}{MVA_b}$$

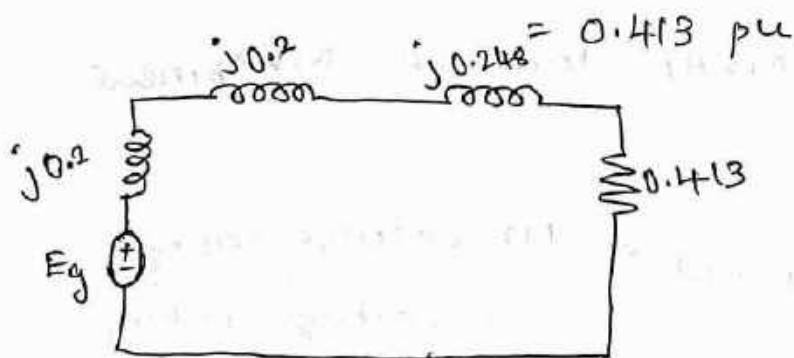

A 300 MVA, 20 kV, 3φ generator has a subtransient reactance of 20%. The generator supplies 2 synchronous motor thru a 64 km transmission line having transformer at both ends as shown in figure. In, this T<sub>1</sub> is 3φ transformer and T<sub>2</sub> is made of 3 single φ transformer of rating 100 MVA, 127/13.2 kV, 10% reactance. The series reactance of transmission line is 0.5 ohm/km. Draw the reactance diagram with all the reactances marked in pu. Select the generator rating as base values.

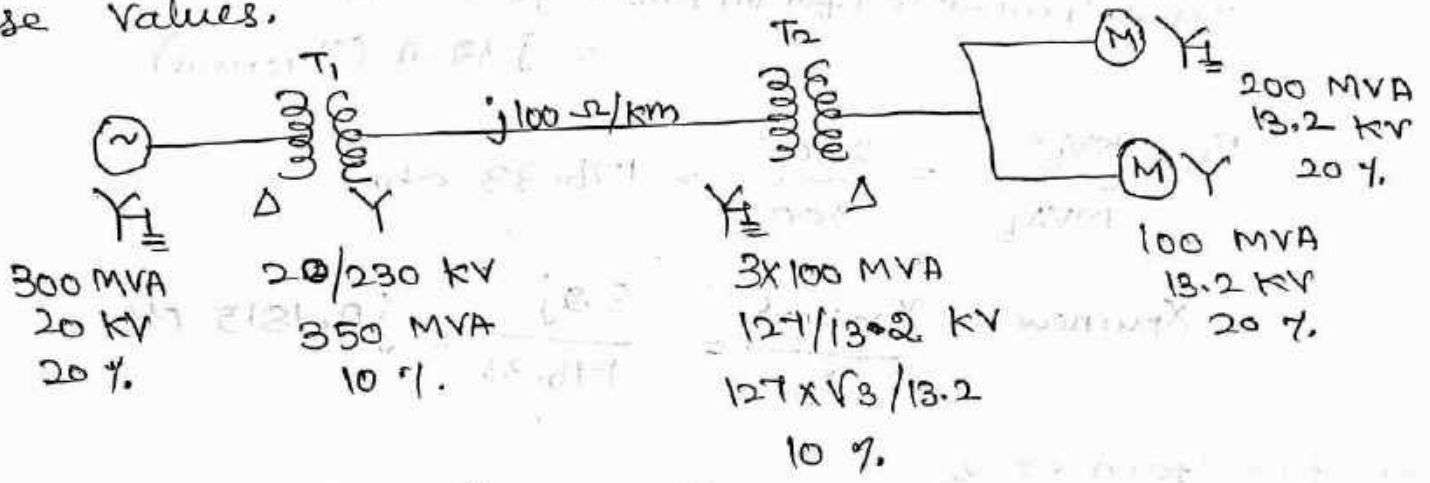

Section 1:  $kV_{b,new} = 20 \text{ kV}$      $MVA_{b,new} = 300 \text{ MVA}$

Section 2:  
 $kV_{b,new} \text{ (HT side)} = T_1 = kV_b \text{ on LT side} \times \frac{\text{HT Voltage}}{\text{LT Voltage}}$   
 $= \frac{230}{20} \times 20 = 230 \text{ kV}$

Section 3:  
 $kV_{b,new} \text{ (HT side)} = T_2 = kV_b \text{ on HT side} \times \frac{\text{LT Voltage}}{\text{HT Voltage}}$   
 $= \frac{13.2}{220} \times 230$   
 $= 13.8 \text{ kV}$

For generator:  
 $X_{pu,new} = X_{pu,old} \times \left[ \frac{kV_{b,old}}{kV_{b,new}} \right]^2 \times \frac{MVA_{b,new}}{MVA_{b,old}}$   
 $= j0.2 \text{ pu}$

For transformer 1:

$$\begin{aligned} X_{pu, new} &= X_{pu, old} \times \left[ \frac{KV_{b, old}}{KV_{b, new}} \right]^2 \times \frac{MVA_{b, new}}{MVA_{b, old}} \\ &= j0.1 \times \left[ \frac{20}{20} \right]^2 \times \frac{300}{350} \\ &= j0.0857 \text{ pu} \end{aligned}$$

For transmission line:

$$\begin{aligned} \text{Reactance of tr. line} &= j0.5 \Omega/\text{km} \\ \text{Total reactance (for 64 km)} &= j0.5 \times 64 \\ &= j32 \Omega \text{ (X actual)} \end{aligned}$$

$$Z_b = \frac{KV_b^2}{MVA_b} = \frac{230^2}{300} = 176.33 \Omega \text{ km}$$

$$X_{pu, new} = \frac{X_{actual}}{Z_b} = \frac{32j}{176.33} = j0.1815 \text{ pu}$$

For transformer 2:


$$\begin{aligned} X_{pu, new} &= X_{pu, old} \times \left[ \frac{KV_{b, old}}{KV_{b, new}} \right]^2 \times \frac{MVA_{b, new}}{MVA_{b, old}} \\ &= j0.1 \times \left[ \frac{220}{230} \right]^2 \times \frac{300}{300} = j0.0915 \text{ pu} \end{aligned}$$

For motor 1

$$X_{pu, new} = j0.2 \times \left[ \frac{13.2}{13.8} \right]^2 \times \frac{300}{200} = j0.2745 \text{ pu}$$


For motor 2
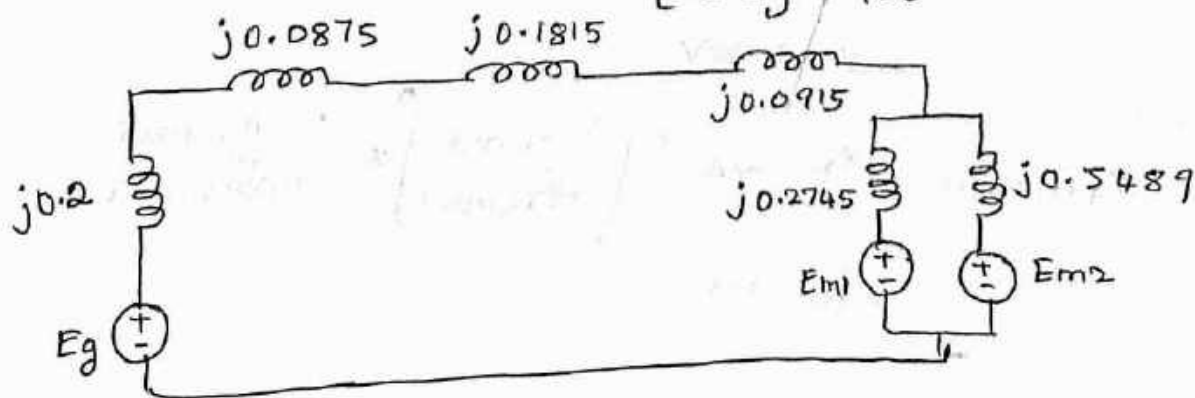
$$X_{pu, new} = j0.2 \times \left[ \frac{13.2}{13.8} \right]^2 \times \frac{300}{100} = j0.5489 \text{ pu}$$





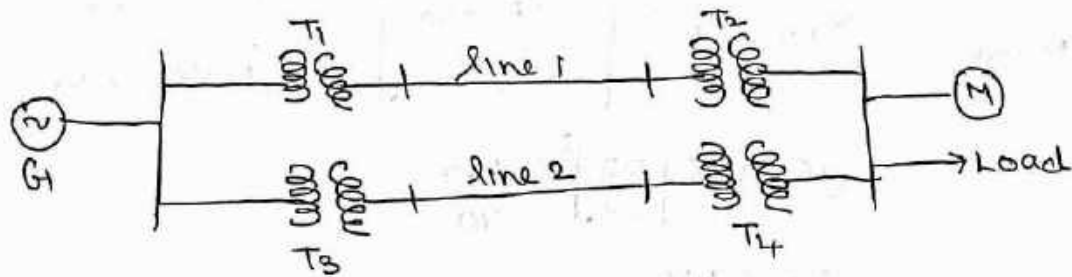The single line diagram of a 3φ sm is shown below:



Select a common base of 100 MVA and 22 kV on the generator side. Draw an impedance diagram with given data

Generator: 90 MVA, 22 kV,  $X = 18\% = j0.18$

Transformer 1: 50 MVA, 22/220 kV,  $X = 10\%$

Transformer 2: 40 MVA, 220/11 kV  $X = 6\%$

Transformer 3: 40 MVA 22/110 kV  $X = 6.4\%$

Transformer 4: 40 MVA 110/11 kV  $X = 8\%$

Motor: 66.5 MVA, 10.45 kV  $X = 18.5\%$

Load: 3φ load, 57 MVA 0.6 pf lagging 10.45 kV

Line 1:  $j 48.4 \text{ ohm}$

Line 2:  $j 65.43 \text{ ohm}$

MVA<sub>base, new</sub> = 100 MVA

Section 1:

$$KV_{b, \text{new}} = 22 \text{ kV}$$

Section 2:

$$KV_b \text{ on HT side of section 2} = \frac{220}{22} \times 22 = 220 \text{ kV}$$

Section 3:

$$KV_b \text{ on LT side of section 3} = \frac{11}{220} \times 220 = 11 \text{ kV}$$

Section 4:

$$KV_b \text{ on HT side of section 4} = \frac{110}{11} \times 11 = 110 \text{ kV}$$

Generator:

$$\begin{aligned}X_{pu, new} &= X_{pu, old} \times \left[ \frac{KV_{b, old}}{KV_{b, new}} \right]^2 \times \frac{MVA_{b, new}}{MVA_{b, old}} \\&= j0.18 \times \left[ \frac{22}{22} \right]^2 \times \frac{100}{90} \\&= j0.2 \text{ pu}\end{aligned}$$

For Transformer-1

$$\begin{aligned}X_{pu, new} &= j0.1 \times \left( \frac{22}{22} \right)^2 \times \frac{100}{50} \\&= j0.2 \text{ pu}\end{aligned}$$

For line 1

$$\begin{aligned}X_{pu} &= \frac{X_{act}}{X_{base}} \\X_{base} &= \frac{220^2}{100} \\&= 484 \text{ ohm} \\X_{pu} &= \frac{j48.4}{484} \\&= j0.1 \text{ pu}\end{aligned}$$

For line 2

$$\begin{aligned}X_{base} &= \frac{110^2}{100} \\&= 110 \text{ ohm} \\X_{pu} &= \frac{j65.43}{110} \\&= j0.54 \text{ pu}\end{aligned}$$

Transformer 2

$$\begin{aligned}X_{pu, new} &= j0.06 \times \left[ \frac{220}{220} \right]^2 \times \frac{100}{40} \\&= j0.15 \text{ pu}\end{aligned}$$

Transformer 3

$$\begin{aligned}X_{pu, new} &= j0.064 \times \left[ \frac{22}{22} \right]^2 \times \frac{100}{40} \\&= j0.16 \text{ pu}\end{aligned}$$

Transformer 4

$$\begin{aligned}X_{pu, new} &= j0.08 \times \left[ \frac{110}{110} \right]^2 \times \frac{100}{40} \\&= j0.2 \text{ pu}\end{aligned}$$

For motor:

$$X_{pu, new} = j0.185 \times \left[ \frac{10.45}{11} \right]^2 \times \frac{100}{66.5}$$

$$= j0.25 \text{ pu}$$

Load:

Power = 57 MVA      pf = 0.6 lag      Voltage = 10.45 kV

$$S = VI^*$$

$$S^* = V^* I$$

$$S^* = V^* \frac{V}{Z} = \frac{V^2}{Z}$$

$$S^* = \frac{|V|^2}{Z}$$

$$Z = \frac{|V|^2}{S} = \frac{(10.45)^2}{57 \angle -\cos^{-1}(0.6)}$$

$$= \frac{(10.45)^2}{57 \angle -53.13}$$

$$= 1.916 \angle 53.13$$

$$= 1.149 + j1.533 \text{ ohm}$$

$$S = P + jQ$$

$$= VI \cos \phi + jVI \sin \phi$$

$$= VI \angle \phi$$


$$Z_{pu} = \frac{Z_{abc}}{Z_b}$$

$$Z_b = \frac{11^2}{100}$$


$$= 1.21 \text{ ohm}$$

$$Z_{pu} = \frac{1.149 + j1.533}{1.21}$$

$$Z_{pu} = 0.9496 + j1.266 \text{ pu}$$

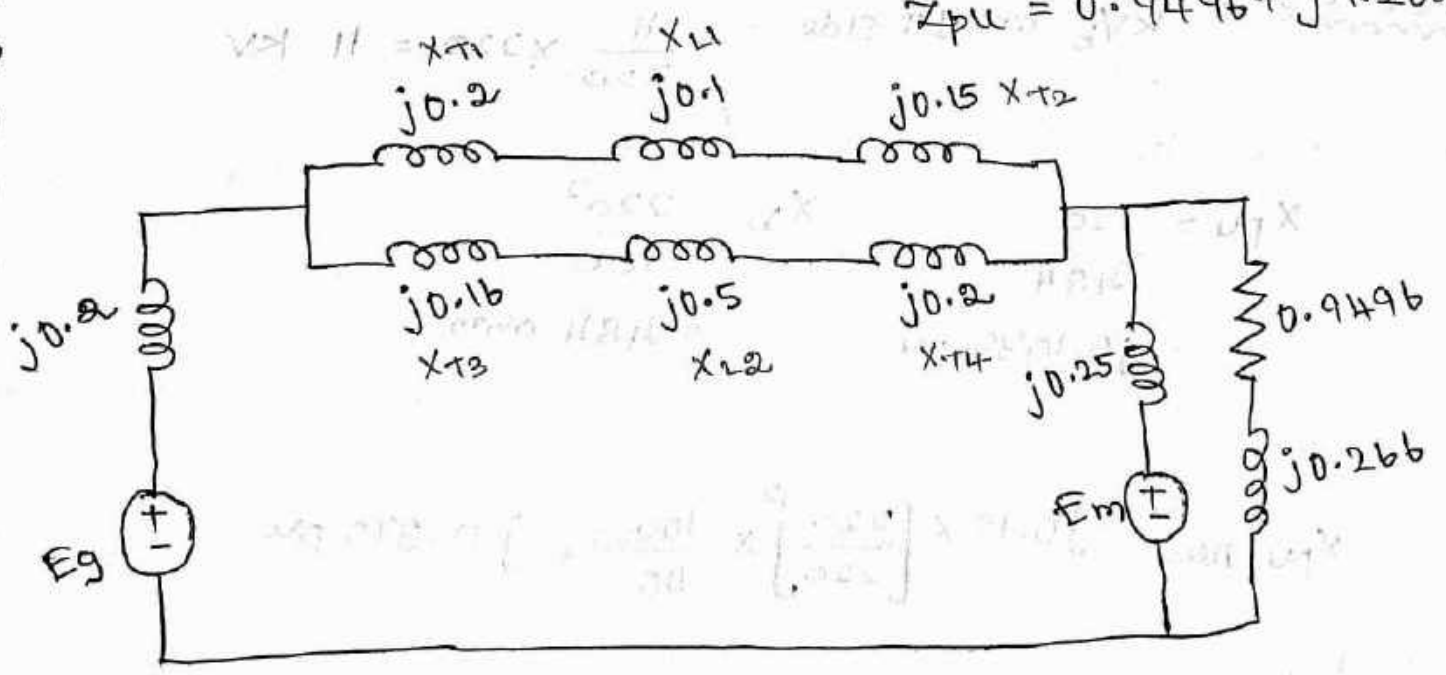

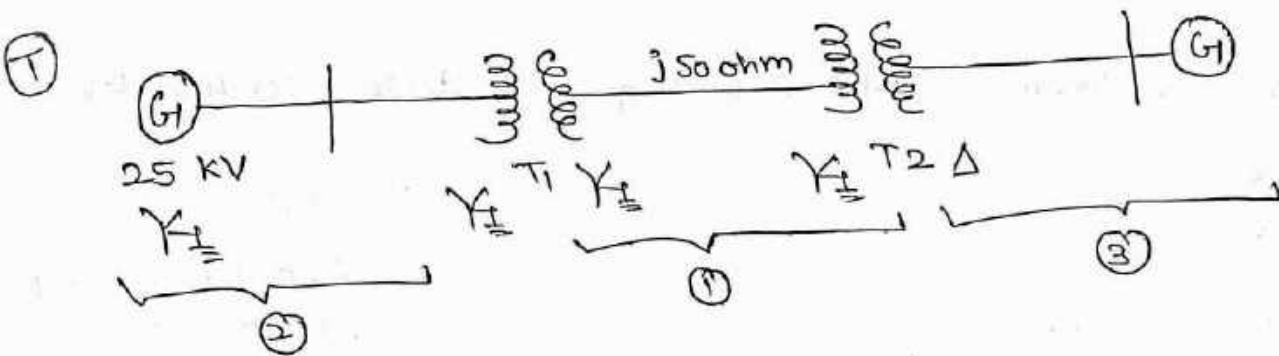Draw the pu reactance diagram for the power s/m shown. Neglect resistance and use a base of 100 MVA, 220 kV in 50 ohm line. The ratings of the generator, motor and transformer are



Generator: 40 MVA, 25 kV  $X = 20\%$

Motor: 50 MVA, 11 kV,  $X = 30\%$

Transformer 1: 40 MVA, 33/220 kV  $X = 15\%$

Transformer 2: 30 MVA, 11/220  $X = 15\%$

Section 1:  $kV_b, \text{new} = 220 \text{ kV}$

Section 2:  $kV_b \text{ on LT side} = 220 \times \frac{33}{220} = 33 \text{ kV}$

Section 3:  $kV_b \text{ on LT side} = \frac{11}{220} \times 220 = 11 \text{ kV}$

Transmission line

$$X_{pu} = \frac{j50}{484}$$

$$= j0.1033 \text{ pu}$$

$$X_b = \frac{220^2}{100}$$

$$= 484 \text{ ohms}$$

Transformer 1

$$X_{pu, \text{new}} = j0.15 \times \left[ \frac{220}{220} \right]^2 \times \frac{100}{40} = j0.375 \text{ pu}$$

Generator:

$$X_{pu, \text{new}} = j0.2 \times \left[ \frac{25}{33} \right]^2 \times \frac{100}{40} = j0.287 \text{ pu}$$

Transformer 2:


$$X_{pu, new} = j0.15 \times \left(\frac{11}{11}\right)^2 \times \frac{100}{30}$$

$$= j0.5 pu$$


Motor:

$$X_{pu, new} = j0.3 \times \left(\frac{11}{11}\right)^2 \times \frac{100}{50}$$

$$= j0.6 pu$$

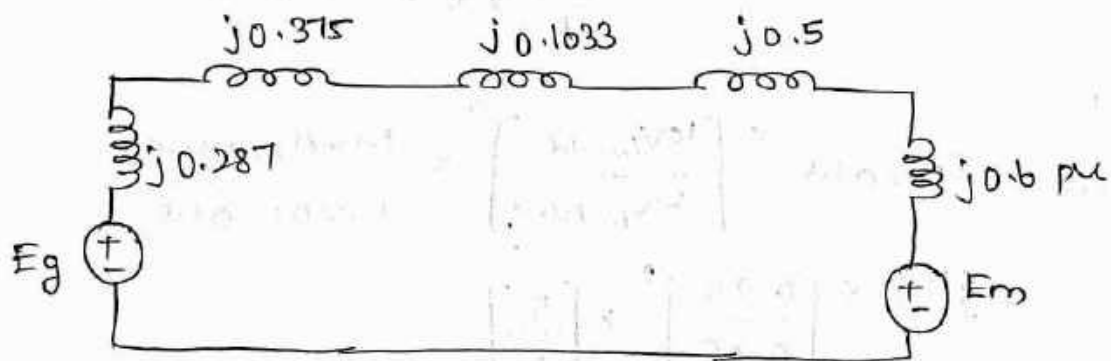

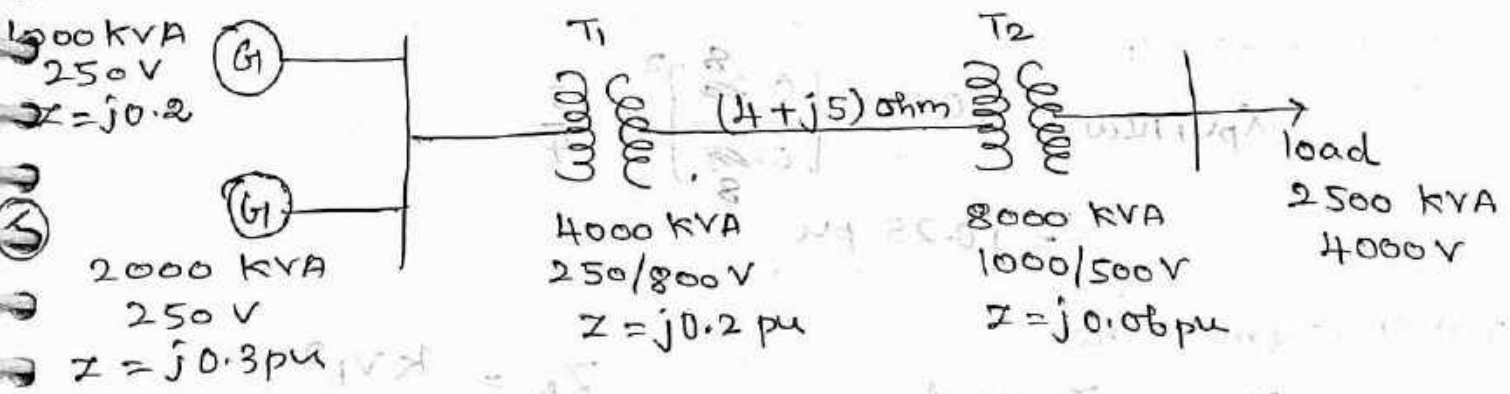Sample power s/m is shown in figure. Redraw this system where the pu impedance of the components are represented on a common 5000 KVA base and common system base voltage of 250 V.



$$MVA_{b, new} = 5 \text{ MVA}$$

Section 1  $kV_{b, new} = 0.25 \text{ kV}$

Section 2  $kV_b \text{ on HT side } T_1 = kV_b \times \frac{LT \text{ rating}}{HT \text{ rating}}$

$$= \frac{0.8}{0.25} \times 0.25 = 0.8 \text{ kV}$$

### Section 3

$$\begin{aligned}KV_B \text{ on LT section (T}_2) &= KV_B \times \frac{\text{LT rating}}{\text{HT rating}} \\ &= \frac{0.5}{1} \times 0.8 = 0.4 \text{ kV}\end{aligned}$$

Generator 1

$$\begin{aligned}X_{pu, \text{new}} &= X_{pu, \text{old}} \times \left[ \frac{KV_{b, \text{old}}}{KV_{b, \text{new}}} \right]^2 \times \frac{MVA_{b, \text{new}}}{MVA_{b, \text{old}}} \\ &= j0.2 \times \left[ \frac{0.25}{0.25} \right]^2 \times \left[ \frac{5}{1} \right] \\ &= j0.1 \text{ pu}\end{aligned}$$

Generator 2:

$$\begin{aligned}X_{pu, \text{new}} &= j0.3 \times \left[ \frac{0.25}{0.25} \right]^2 \times \frac{5}{2} \\ &= j0.75 \text{ pu}\end{aligned}$$

Transformer T<sub>1</sub>

$$\begin{aligned}X_{pu, \text{new}} &= j0.2 \times \left[ \frac{0.25}{0.25} \right]^2 \times \frac{5}{4} \\ &= j0.25 \text{ pu}\end{aligned}$$

Transmission line:

$$\begin{aligned}Z_{pu} &= \frac{Z_{\text{actual}}}{Z_{\text{base}}} \\ &= \frac{4 + 5j}{0.128}\end{aligned}$$

$$\begin{aligned}Z_b &= \frac{KV_b^2}{MVA_b} \\ &= \frac{0.8^2}{5} \\ &= 0.128 \text{ ohms}\end{aligned}$$

$$= 31.25 + j 39.0625$$

For transformer T<sub>2</sub>


$$X_{pu, new} = j0.06 \times \left[ \frac{1}{0.8} \right]^2 \times \frac{5}{8}$$

$$= j0.0585 \text{ pu}$$


load:

$$Z_{pu, new} = \frac{2500}{5000} = j0.5 \text{ pu}$$
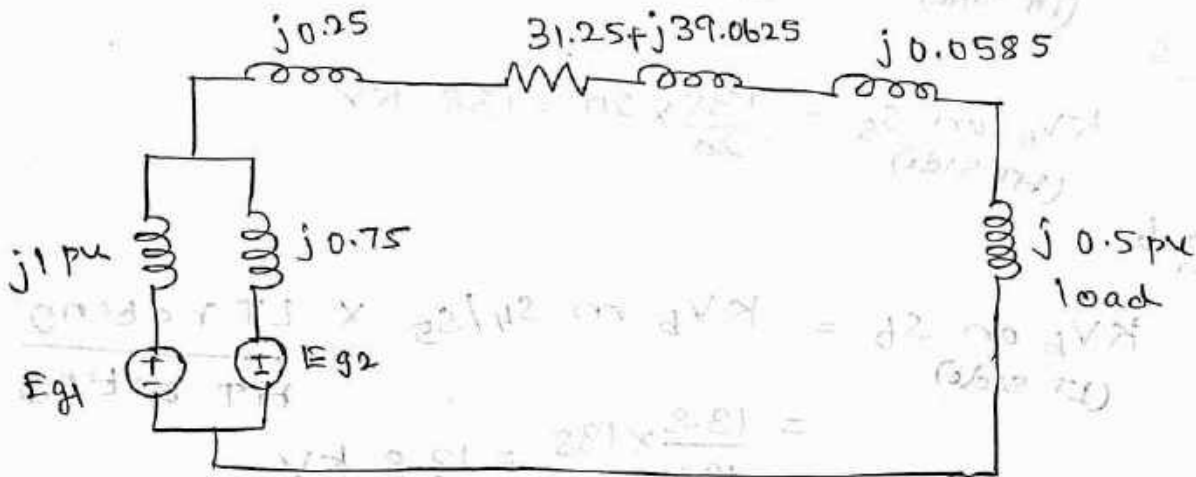
$$\frac{\text{KV}^2}{\text{MVA} \cdot \text{b}} = \frac{4 \times 4}{5}$$



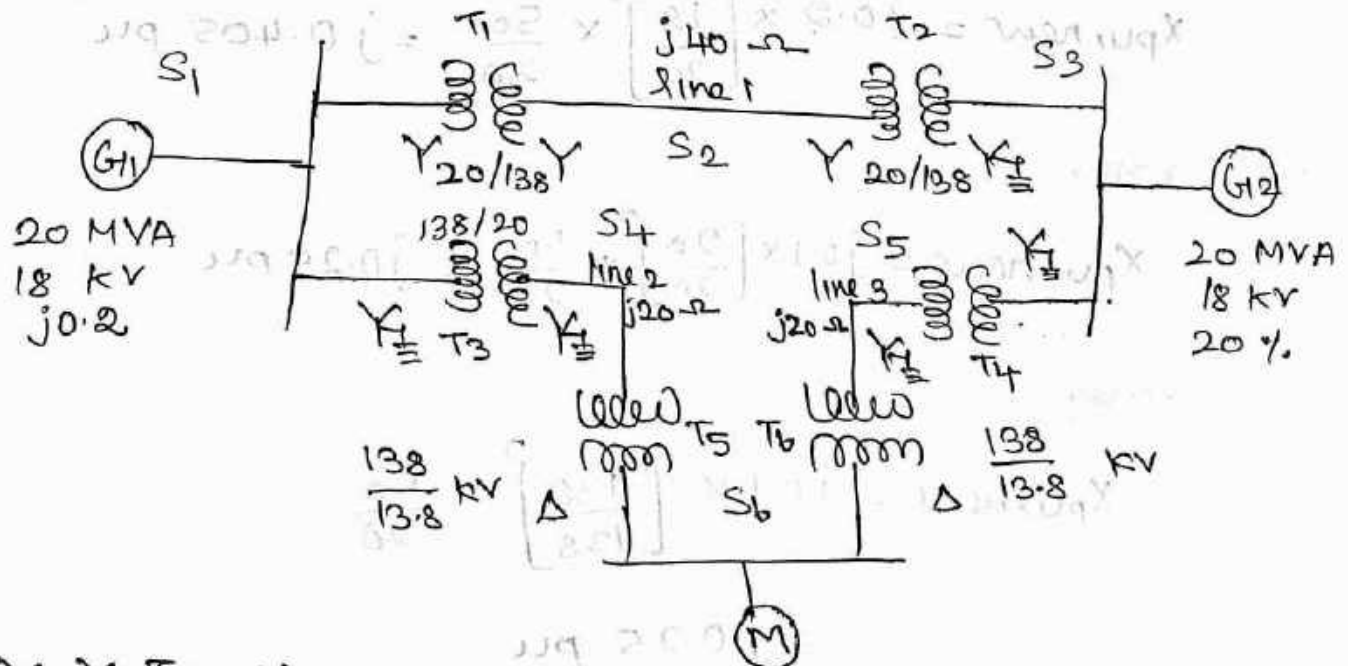Draw the reactance diagram for the given system by using a base of 50 MVA, 138 KV in 40 ohm transmission line



- Y-Y Transformer = 20 MVA, 138/20 KV X=10%
- Y-Δ Transformer = 15 MVA, 138/13.8 KV X=10%
- Motor = 30 MVA, 13.8 KV, X=20%



Section 2:  
KV<sub>B, new</sub> = 138 kV      MVA<sub>B, new</sub> = 50 MVA

Section 1:  
KV<sub>B</sub> on S<sub>1</sub> (LT side)

$$KV_B \text{ on } S_1 \text{ (LT side)} = KV_B(S_2) \times \frac{LT \text{ rating}}{HT \text{ rating}} = \frac{20}{138} \times 138 = 20 \text{ kV}$$

Section 3:  
KV<sub>B</sub> on S<sub>3</sub> (LT side)

$$KV_B \text{ on } S_3 \text{ (LT side)} = \frac{20}{138} \times 138 = 20 \text{ kV}$$

Section 4:  
KV<sub>B</sub> on S<sub>4</sub> (HT side)

$$KV_B \text{ on } S_4 \text{ (HT side)} = \frac{138}{20} \times 20 = 138 \text{ kV}$$

$$\frac{KV_B \text{ (HT)}}{LT} \times KV_{B \text{ old}}$$

Section 5:  
KV<sub>B</sub> on S<sub>5</sub> (HT side)

$$KV_B \text{ on } S_5 \text{ (HT side)} = \frac{138}{20} \times 20 = 138 \text{ kV}$$

Section 6:  
KV<sub>B</sub> on S<sub>6</sub> (LT side)

$$KV_B \text{ on } S_6 \text{ (LT side)} = KV_B \text{ on } S_4/S_5 \times \frac{LT \text{ rating}}{HT \text{ rating}} \\ = \frac{13.8}{138} \times 138 = 13.8 \text{ kV}$$

Generator 1

$$X_{pu, new} = j0.2 \times \left[ \frac{18}{20} \right]^2 \times \frac{50}{20} = j0.405 \text{ pu}$$

Transformer 1

$$X_{pu, new} = j0.1 \times \left[ \frac{20}{20} \right]^2 \times \frac{50}{20} = j0.25 \text{ pu}$$

Transformer 2

$$X_{pu, new} = j0.1 \times \left[ \frac{138}{138} \right]^2 \times \frac{50}{20} \\ = j0.25 \text{ pu}$$

Transformer 3

U1.37

$$X_{pu, new} = j0.1 \times \left[ \frac{20}{20} \right]^2 \times \frac{50}{20}$$

$$= j0.25 \text{ pu}$$

Transformer 4

$$X_{pu, new} = j0.1 \times \left( \frac{20}{20} \right)^2 \times \frac{50}{20} = j0.25 \text{ pu}$$

Transformer 5

$$X_{pu, new} = j0.1 \times \left( \frac{138}{138} \right)^2 \times \frac{50}{15} = j0.3333 \text{ pu}$$

Transformer 6

$$X_{pu, new} = j0.1 \times \left[ \frac{138}{138} \right]^2 \times \frac{50}{15}$$

$$= j0.3333 \text{ pu}$$

Transmission line 1

Transmission line 2, 3

$$X_{pu} = \frac{X_{act}}{X_{base}}$$

$$= \frac{j40}{380}$$

$$= j0.1050 \text{ pu}$$

$$X_b = \frac{kV_b^2}{MVA_b}$$

$$= \frac{138^2}{50}$$

$$= 380 \text{ ohm}$$

$$X_{pu} = \frac{X_{act}}{X_{base}}$$

$$X_b = \frac{138^2}{50}$$

$$= 380 \text{ ohm}$$

$$X_{pu} = \frac{j20}{380}$$

$$= j0.0526 \text{ pu}$$

For Generator 2:


$$X_{pu, new} = j0.2 \times \left[ \frac{18}{20} \right]^2 \times \frac{50}{20}$$

$$= j0.405 \text{ pu}$$


For motor:

$$X_{pu, new} = j0.3 \times \left[ \frac{13.8}{13.8} \right]^2 \times \frac{50}{30}$$

$$= j0.333 \text{ pu}$$

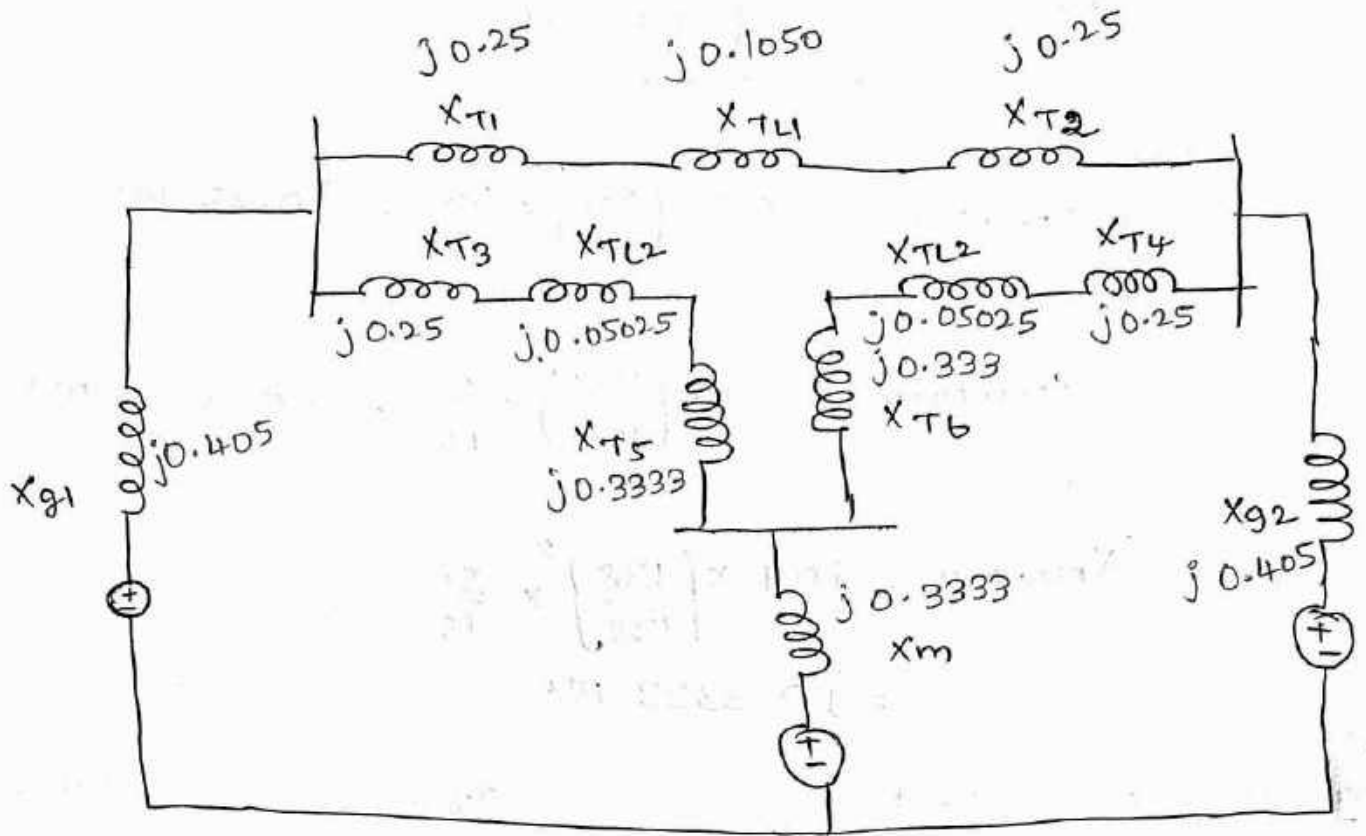

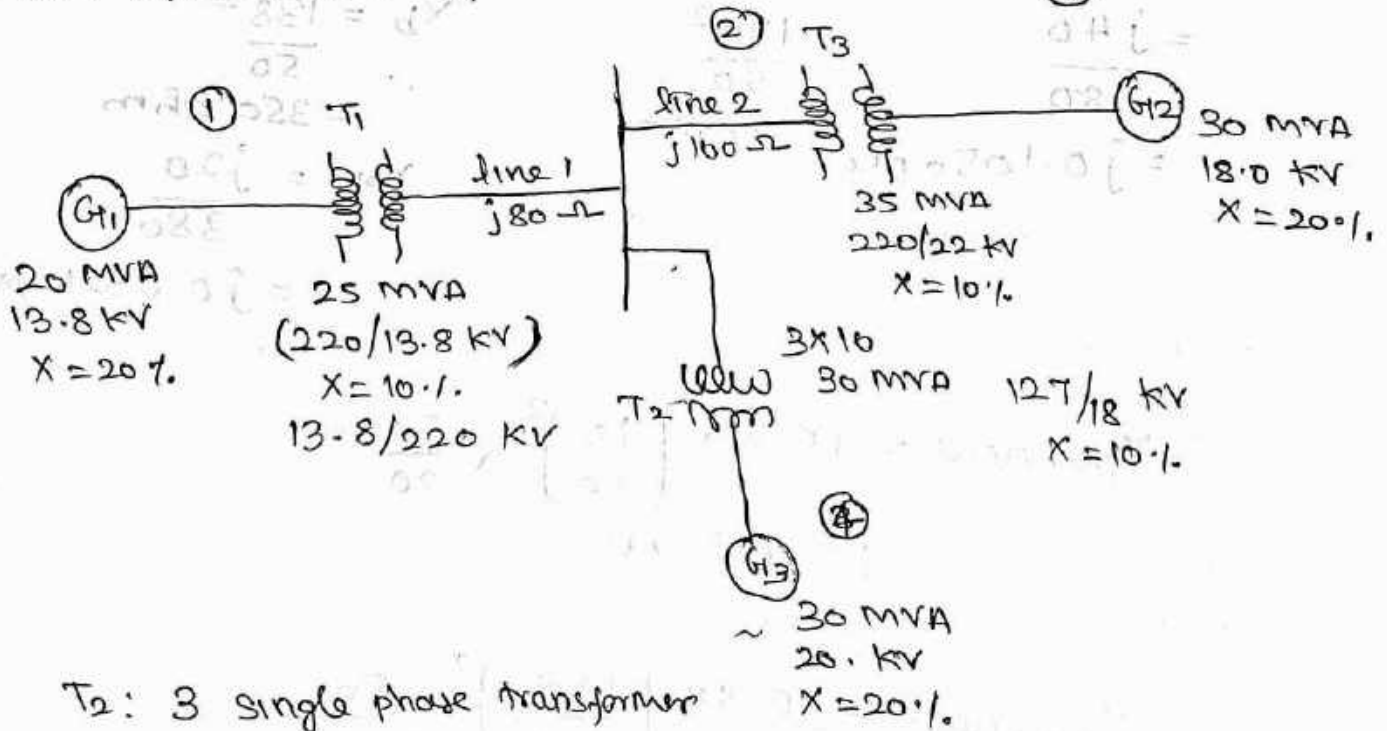Draw the reactance diagram using a base of 50 MVA, 13.8 kV on Generator G<sub>1</sub>



T<sub>2</sub>: 3 single phase transformer

$$\frac{127 \times \sqrt{3}}{18} = 220/18 \text{ KV}$$

$$MVA_{b, \text{new}} = 50 \text{ MVA}$$

Section 1:

$$kV_{b, \text{new}} = 13.8 \text{ kV}$$

Section 2:

$$kV_B \text{ on HT (T1)} : kV_B \text{ on HT section} \times \frac{\text{HT Rating}}{\text{HT Rating}_L}$$

$$= \frac{220}{13.8} \times 13.8 = 220 \text{ kV}$$

Section A:

$$kV_B \text{ on LT side T2} = \frac{\text{LT rating}}{\text{HT rating}} \times kV_B \text{ on section 2}$$

$$= \frac{18}{220} \times 220 = 18 \text{ kV}$$

Section B:

$$kV_B \text{ on LT section T2} = kV_B \text{ on section 2} \times \frac{\text{LT rating}}{\text{HT rating}}$$

$$= \frac{22}{220} \times 220 = 22 \text{ kV}$$

Generator 1:

$$X_{pu, \text{new}} = j0.2 \times \left[ \frac{13.8}{13.8} \right]^2 \times \frac{50}{20}$$

$$= j0.5 \text{ pu}$$

Transformer 1:

$$X_{pu, \text{new}} = X_{pu, \text{old}} \times \left[ \frac{kV_{b, \text{old}}}{kV_{b, \text{new}}} \right]^2 \times \frac{MVA_{b, \text{new}}}{MVA_{b, \text{old}}}$$

$$= j0.1 \times \left[ \frac{13.8}{13.8} \right]^2 \times \frac{50}{25} = j0.2 \text{ pu}$$

Transformer 2:

$$X_{pu, \text{new}} = j0.1 \times \left[ \frac{220}{220} \right]^2 \times \frac{50}{30}$$

$$= j0.1667 \text{ pu}$$

Transmission line 1 ( $j80 \Omega$ )

$$X_{pu} = \frac{X_{act}}{X_{base}}$$

$$X_{base} = \frac{220^2}{50} = 968 \Omega$$

$$X_{pu} = \frac{j80}{968} = j0.0826 \text{ pu}$$

Transmission line 2 ( $j100 \Omega$ )

$$X_{pu} = \frac{j100}{968}$$

$$= j0.1033 \text{ pu}$$

For Generator 2:


$$X_{pu, new} = j0.2 \times \left[ \frac{18}{18} \right]^2 \times \frac{50}{30} = j0.333 \text{ pu}$$

Transformer 3:

$$X_{pu, new} = j0.1 \times \left[ \frac{220}{220} \right]^2 \times \frac{50}{30} = j0.1429 \text{ pu}$$

Generator 3:
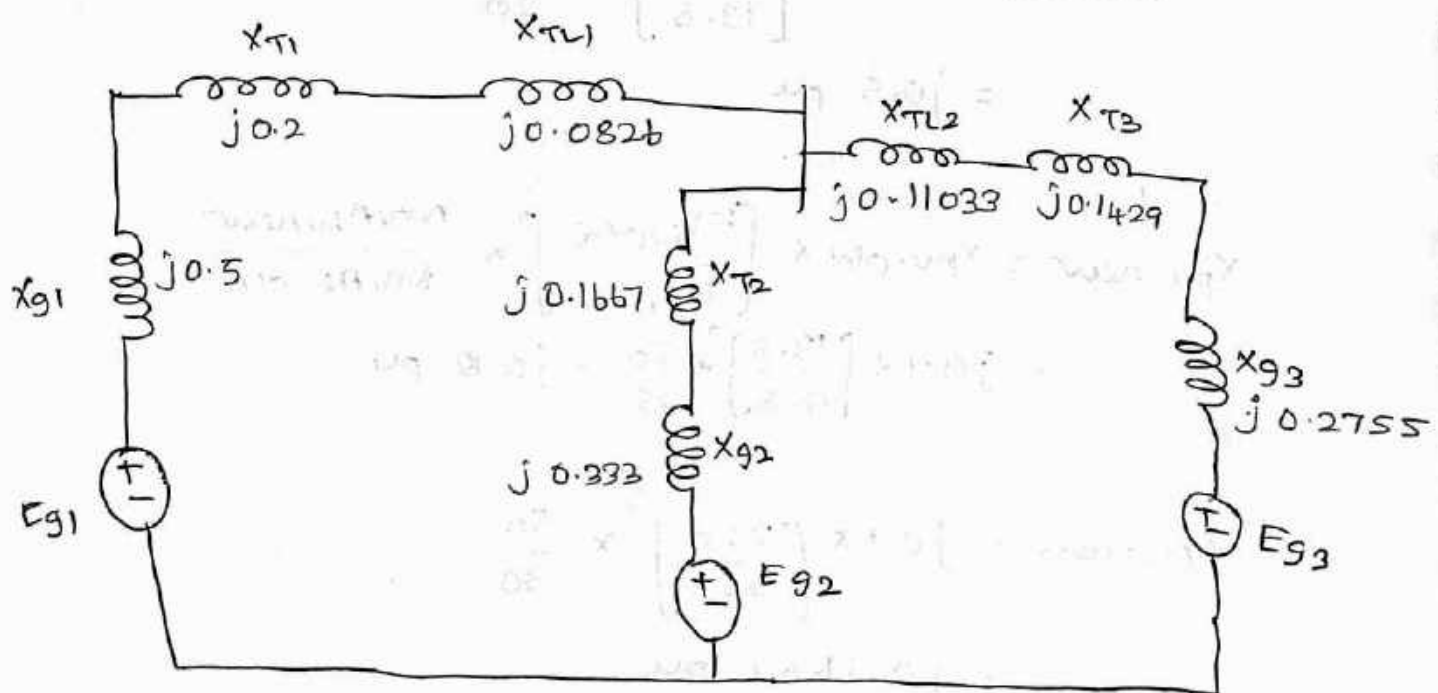
$$X_{pu, new} = j0.2 \times \left[ \frac{20}{20} \right]^2 \times \frac{50}{30} = j0.2755 \text{ pu}$$



# Bus Admittance Matrix ( $Y_{bus}$ )

U1.41

\* Matrix consisting of self and mutual admittance of the power system network

\* Diagonal elements of each node is sum of admittances connected to it. - self admittance  
driving point admittance

$$Y_{ii} = \sum_{j=0}^n Y_{ij}, j \neq i$$

\* off-diagonal elements is equal to the negative of the admittance connected between the nodes.  
- mutual admittance  
- transfer admittance

$$Y_{ij} = Y_{ji} = -Y_{ij}$$

Methods available for  $Y_{bus}$  formation

\* Direct (or) Inspection method

\* Singular transformation method

$$\text{Admittance (Y)} = \frac{1}{Z} = \frac{1}{R + jX}$$

$$= \frac{R - jX}{(R + jX)(R - jX)}$$

$$= \frac{R - jX}{R^2 + X^2}$$

$$= \frac{R}{R^2 + X^2} - \frac{jX}{R^2 + X^2}$$

$$= G - jB$$


$G \rightarrow$  Conductance

$B \rightarrow$  susceptance

- \* Load flow analysis
  - \* stability analysis
  - \* optimal power flow analysis
  - \* reduce computer memory - sparse matrix
- } Application of  $Y_{bus}$  matrix.

Formation of  $Y_{bus}$  matrix

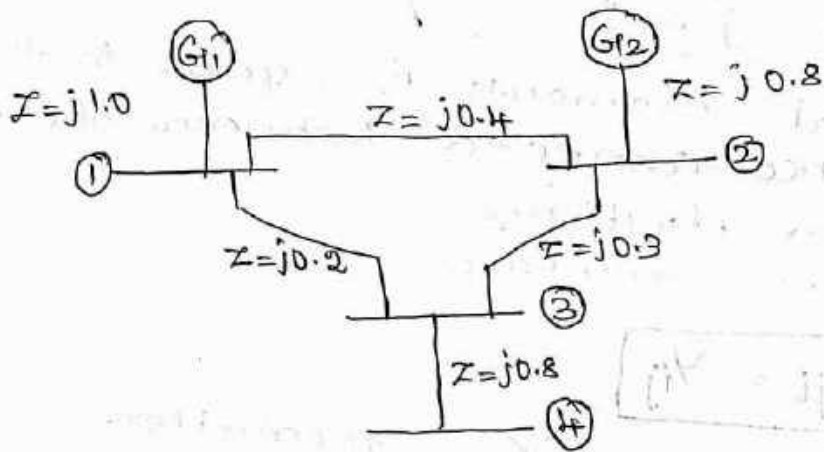01. Find out the  $Y_{bus}$  matrix of the sample power system shown in figure



$$Y_{11} = Y_{10} + Y_{12} + Y_{13} = \frac{1}{j1.0} + \frac{1}{j0.4} + \frac{1}{j0.2}$$

$$= -j1.0 - j2.5 - j5$$

$$= -j8.5$$

$$Y_{12} = Y_{21} = -Y_{12} = -(-2.5j) = 2.5j \quad Y_{14} = 0$$

$$Y_{13} = Y_{31} = -Y_{13} = -\left(\frac{1}{j0.2}\right) = 5j \quad Y_{24} = 0$$

$$Y_{22} = Y_{20} + Y_{21} + Y_{23} = -j7.08$$

$$Y_{23} = Y_{32} = -Y_{23} = 3.33j$$

$$Y_{33} = Y_{31} + Y_{32} + Y_{34} = -9.58j$$

$$Y_{34} = Y_{43} = -Y_{34} = +j1.25$$


$$Y_{44} = +\frac{1}{j0.8} = -1.25j$$



$$Y_{bus} = \begin{bmatrix} -j8.5 & +j2.5 & j5.0 & 0 \\ +j2.5 & -j7.08 & j3.33 & 0 \\ j5.0 & j3.33 & -j9.58 & j1.25 \\ 0 & 0 & j1.25 & -j1.25 \end{bmatrix}$$

Q2. Form the bus admittance matrix.

line i-j	R (pu)	X (pu)
1-2	0.1	j0.3
1-3	0.2	j0.2
2-3	0.1	j0.4
2-4	0.3	j0.4
3-4	0.1	j0.3

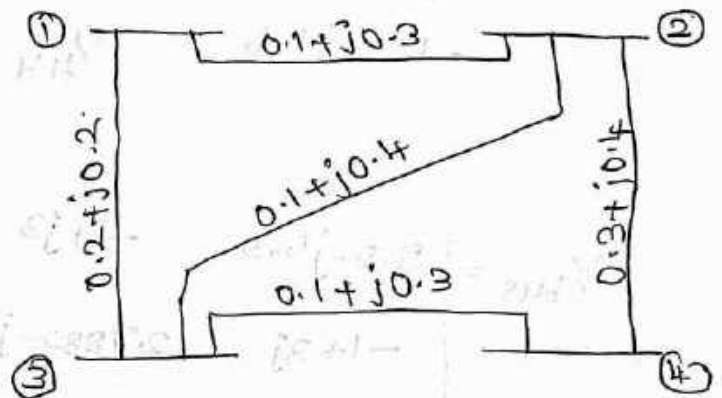

$$Y_{11} = Y_{12} + Y_{13}$$

$$= 3.5 - j5.5$$

$$Y_{12} = -Y_{21}$$

$$= -1 + j3$$

$$Y_{13} = +2.5 - j2.5 \quad Y_{14} = 0$$

$$Y_{21} = -Y_{12}$$

$$= -1 + j3$$

$$Y_{22} = Y_{21} + Y_{23} + Y_{24}$$

$$= 1 - j3 + 0.5882 - j2.353 + 1.2 - j1.6$$

$$= 2.7882 - j6.953$$

$$Y_{23} = 0.588 - j2.3529$$

$$Y_{32} = -Y_{23}$$

$$= -0.588 + j2.353$$

$$Y_{24} = 1.2 - j1.6$$

$$Y_{13} = Y_{31}$$

$$= -Y_{31} = -2.5 + j2.5$$

$$Y_{34} = 1 - j3$$

$$Y_{33} = Y_{31} + Y_{32} + Y_{34}$$

$$= 4.0882 - j7.853$$

$$Y_{41} = -Y_{14}$$

$$= 0$$

$$Y_{43} = -Y_{34}$$

$$= -1 + j3$$

$$Y_{42} = -Y_{24}$$


$$= -1.2 + j1.6$$

$$Y_{44} = 2.2 - j4.6$$

$$Y_{bus} = \begin{bmatrix} 3.5 - j5.5 & -1 + j3 & -2.5 + j2.5 & 0 \\ -1 + j3 & 2.7882 - j6.953 & -0.5882 + j2.353 & -1.2 + j1.6 \\ -2.5 + j2.5 & -0.5882 + j2.353 & 4.0882 - j7.853 & -1 + j3 \\ 0 & -1.2 + j1.6 & -1 + j3 & 2.2 - j4.6 \end{bmatrix}$$

The line data for 4-bus system is given below.  
Find the bus admittance matrix

line $i-j$	$R$	$X$	Half line charging admittance
1-2	0	$j0.15$	$j0.05$
1-3	0	$j0.2$	$j0.01$
2-3	0	$j0.3$	$j0.02$
2-4	0	$j0.4$	$j0.05$

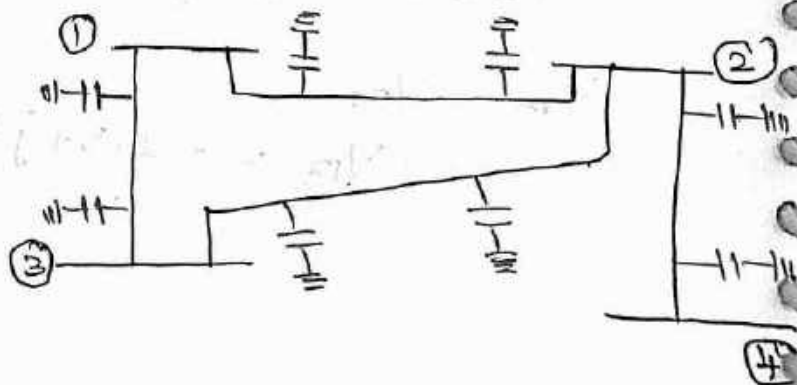

Line charging admittance

U1.45

$$Y_{10} = j0.05 + j0.01 \\ = +j0.06$$

$$Y_{20} = j0.05 + j0.02 + j0.05 = j0.12$$

$$Y_{30} = j0.01 + j0.02 = j0.03$$

$$Y_{40} = j0.05$$

$$Y_{12} = \frac{1}{Z_{12}} = -j6.667$$

$$Y_{13} = -j5$$

$$Y_{24} = -j2.5$$

$$Y_{23} = -j3.333$$

$$Y_{11} = Y_{12} + Y_{13} + Y_{10} \\ = -j11.61$$

$$Y_{22} = Y_{20} + Y_{21} + Y_{23} + Y_{24} \\ = -j12.38$$

$$Y_{33} = Y_{30} + Y_{31} + Y_{32} = -j8.3$$

$$Y_{44} = Y_{42} + Y_{40} = -j2.45$$

$$Y_{21} = -Y_{12} = j6.667$$

$$Y_{14} = Y_{41} = 0$$

$$Y_{31} = -Y_{13} = j5$$

$$Y_{34} = Y_{43} = 0$$

$$Y_{23} = Y_{32} = -Y_{23}$$


$$= j3.33$$

$$Y_{42} = -Y_{24} = j2.5$$

$$Y_{Bus} = \begin{bmatrix} -j11.61 & j6.667 & j5 & 0 \\ j6.667 & -j12.38 & j3.33 & j2.5 \\ j5 & j3.33 & -j8.3 & 0 \\ 0 & j2.5 & 0 & -j2.45 \end{bmatrix}$$

Compute  $Y_{bus}$  matrix of the sample power system.

Bus code	Impedance	Half line charging
1-2	$0.02 + j0.06$	$j0.03$
1-3	$0.08 + j0.24$	$j0.025$
2-3	$0.06 + j0.18$	$j0.020$

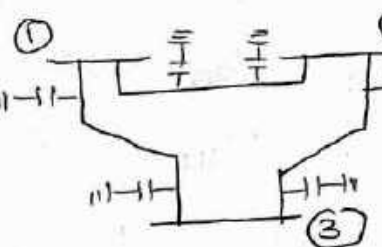

$$Y_{10} = j0.025 + j0.03 = j0.055$$

$$Y_{20} = j0.03 + j0.02 = j0.05$$

$$Y_{30} = j0.025 + j0.020 = j0.045$$

$$Y_{12} = \frac{1}{0.02 + j0.06} = 15.82 \angle -71.56^\circ = 5.004 - 15.007j$$

$$Y_{13} = 3.955 \angle -71.56^\circ = 1.249 - 3.747j$$

$$Y_{23} = 5.273 \angle -71.56^\circ = 1.668 - 5.002j$$

$$Y_{11} = Y_{10} + Y_{12} + Y_{13} = 6.255 - j18.704$$

$$Y_{22} = 6.672 - j19.96 = Y_{12} + Y_{23} + Y_{20}$$

$$Y_{33} = Y_{30} + Y_{13} + Y_{23} = 2.918 - j8.709$$


$$Y_{21} = -Y_{12} = -5 + 15j$$

$$Y_{31} = -Y_{13} = -1.25 + 3.75j$$

$$Y_{32} = -Y_{23} = -1.667 + 5j$$

$$Y_{bus} = \begin{bmatrix} 6.255 - j18.704 & -5 + 15j & -1.25 + 3.75j \\ -5 + 15j & 6.672 - j19.96 & -1.667 + 5j \\ -1.25 + 3.75j & -1.667 + 5j & 2.918 - j8.709 \end{bmatrix}$$

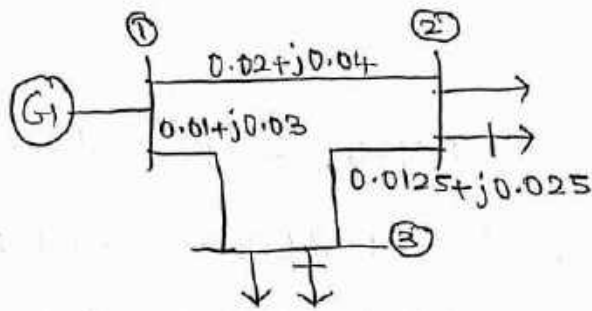Consider the system shown in figure. Compute  $Y_{bus}$  matrix. U1.47  
 It shown a transmission network with impedance of transmission lines all pu as shown.



$$Y_{12} = 10 - j20$$

$$Y_{13} = 10 - j30$$

$$Y_{32} = 16 - j32$$

$$Y_{bus} = \begin{bmatrix} 20 - j50 & -10 + j20 & -10 + j30 \\ -10 + j20 & 26 - j52 & -16 - j52 \\ -10 + j30 & -16 + j32 & 26 - j62 \end{bmatrix}$$

Form the  $Y_{bus}$  matrix by inspection method for a 3-bus system as shown in table

Bus code	Impedance	line charging admittance
1-2	$0.02 + j0.04$	$j0.05$
1-3	$0.01 + j0.03$	$j0.04$
2-3	$0.0125 + j0.025$	$j0.06$

Bus code	Half line charging admittance
1-2	$j0.025$
1-3	$j0.02$
2-3	$j0.03$

$$Y_{10} = j0.045$$

$$Y_{20} = j0.55$$

$$Y_{30} = j0.05$$

$$Y_{bus} = \begin{bmatrix} 16.69 - j25.69 & -1.336 + j2.66 & -15.36 + j23.04 \\ -1.336 + j2.66 & 22.51 - j6.82 & -1.176 + j4.704 \\ -15.365 + j23.04 & -1.176 + j4.704 & 16.542 - j27.702 \end{bmatrix}$$

The bus admittance matrix is given by  $Y_{bus} = \begin{bmatrix} -j5 & j3 \\ j3 & -j8 \end{bmatrix}$   
Determine bus impedance matrix

$$Z_{bus} = [Y_{bus}]^{-1}$$
$$= \begin{bmatrix} -j5 & j3 \\ j3 & -j8 \end{bmatrix}^{-1}$$

$$Z_{bus} = \begin{bmatrix} j0.258 & j0.097 \\ j0.097 & j0.161 \end{bmatrix}$$

Addition of a line

Removal of line

$$Y_{ii, new} = Y_{ii, old} + y$$

$$Y_{ii, new} = Y_{ii, old} - y$$

$$Y_{ij, new} = Y_{ij, old} - y$$

$$Y_{ij, new} = Y_{ij, old} + y$$

$$Y_{ji, new} = Y_{ji, old} - y$$

$$Y_{ji, new} = Y_{ji, old} + y$$

$$Y_{jj, new} = Y_{jj, old} + y$$

$$Y_{jj, new} = Y_{jj, old} - y$$

The parameters of (A) bus system are as follows: U 1.49

Bus code	line impedance	line charging admittance
1-2	$0.2 + j0.8$	$j0.02$
2-3	$0.3 + j0.9$	$j0.03$
2-4	$0.25 + j1.0$	$j0.04$
3-4	$0.2 + j0.8$	$j0.02$
1-3	$0.1 + j0.4$	$j0.01$

Draw the network and find the admittance matrix.

$$Y_{bus} = \begin{bmatrix} 0.882 - j3.514 & -0.294 + j1.176 & -0.588 + j2.353 & 0 \\ -0.294 + j1.176 & 0.862 - j3.072 & -0.333 + j1 & -0.235 + j0.941 \\ -0.588 + j2.353 & -0.333 + j1 & 1.215 - j4.49 & -0.294 + j1.176 \\ 0 & -0.235 + j0.941 & -0.294 + j1.176 & 0.529 - j2.088 \end{bmatrix}$$

Remove the line between (2) and (4) for the above example and determine new  $Y_{bus}$ .

$$\begin{aligned} Y_{22, new} &= Y_{22, old} - Y \\ &= 0.862 - j3.072 - \frac{1}{0.25 + j1} - j0.02 \\ &= 0.627 - j2.15 \end{aligned}$$

$$\begin{aligned} Y_{24, new} &= Y_{42, new} = Y_{42, old} + Y \\ &= -0.235 + j0.941 + \frac{1}{0.25 + j1} = 0 \end{aligned}$$

$$\begin{aligned} Y_{44, new} &= Y_{44, old} - Y \\ &= 0.529 - j2.088 - \frac{1}{0.25 + j1} - j0.02 \\ &= 0.294 - j1.166 \end{aligned}$$



$$Y_{bus, new} = \begin{bmatrix} 0.882 - j3.514 & -0.294 + j1.176 & -0.588 + j2.353 & 0 \\ -0.294 + j1.176 & 0.627 - j2.15 & -0.33 + j1 & 0 \\ -0.588 + j2.353 & -0.333 + j1 & 1.215 - j4.49 & -0.294 + j1.176 \\ 0 & 0 & -0.294 + j1.176 & 0.294 - j1.176 \end{bmatrix}$$

Elimination of a node or Bus  
(Gaussian Elimination or Kron reduction method)

$$Y_{ij, new} = Y_{ij, old} - \frac{Y_{in} \cdot Y_{nj}}{Y_{nn}}$$


where

$n \rightarrow$  node which is to be removed

$i = 1, 2, \dots, n \quad i \neq n$

$j = 1, 2, \dots, n \quad j \neq n$

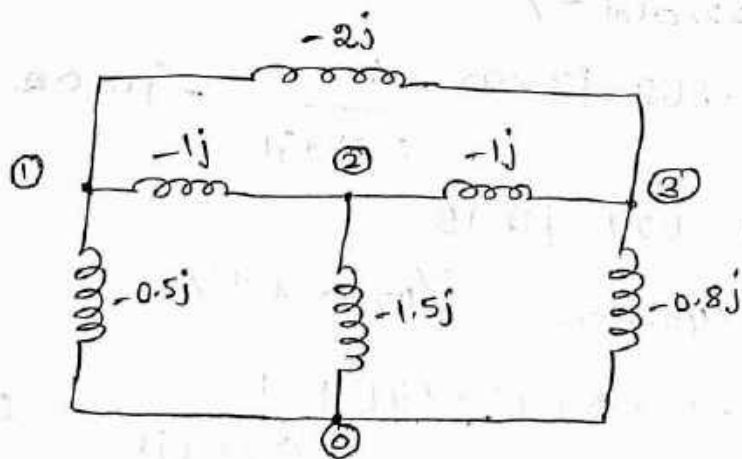Determine the bus admittance matrix of the system is shown in figure. Determine the reduced bus admittance matrix after eliminating node 3.



$$Y_{bus} = \begin{bmatrix} -0.5j - j1.0 - j2.0 & j1.0 & j2.0 \\ j1.0 & -j1.0 - j1.0 - j1.5 & j1.0 \\ j2.0 & j1.0 & -j2 - j1 - j0.8 \end{bmatrix}$$

$$= \begin{bmatrix} -j3.5 & j1 & j2 \\ j1 & -j3.5 & j1.0 \\ j2 & j1.0 & -j3.8 \end{bmatrix}$$

$$Y_{11, \text{new}} = Y_{11, \text{old}} - \frac{Y_{13} \cdot Y_{31}}{Y_{33}} = -j2.45$$


$$Y_{12, \text{new}} = Y_{12, \text{old}} - \frac{Y_{13} \cdot Y_{32}}{Y_{33}} = j1.526$$

$$Y_{22, \text{new}} = Y_{22, \text{old}} - \frac{Y_{23} \cdot Y_{32}}{Y_{33}} = -j3.237$$


$$\text{Reduced } Y_{\text{bus}} = \begin{bmatrix} -j2.45 & j1.526 \\ j1.526 & -j3.237 \end{bmatrix}$$

Formation of  $Y_{\text{bus}}$  by singular transformation

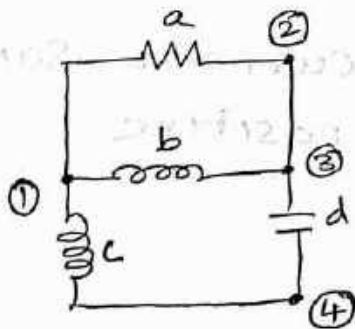
Network - interconnection of elements in various branches at different nodes.



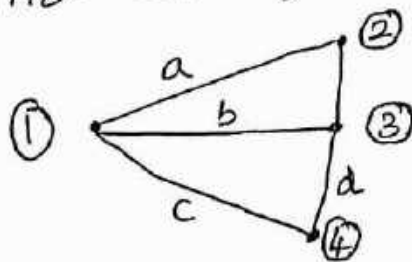Graph: representation of n/w obtained by replacing every element of n/w by a line segment and every junction point by a node.




## Oriented graph

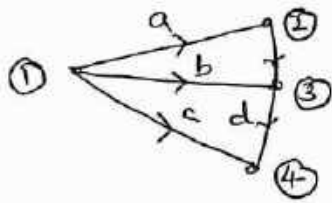

every branch of a graph has direction

## Tree or twig

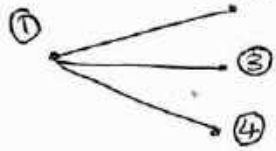

Subgraph of a network which interconnect all the nodes

\* Number of tree branches = Nodes - 1

\* Rank of tree = Rank of graph


\* Every connected graph has at least one tree

Link (or) chord branches not belonging to the tree - links.

## Primitive Impedance matrix ( $Z_{primitive}$ )


Matrix which contain info. about transmission line (impedance).

### Assumptions

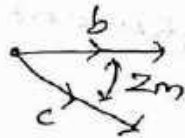

Direction of current same then

$Z_m$  (mutual impedance) is positive

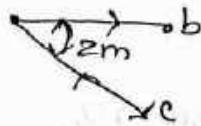


Direction of current different then  $Z_m$  (mutual impedance) is negative


Primitive admittance Matrix ( $Y_{primitive}$ )  
 Matrix which contains info. about transmission line admittance

$$Y_{primitive} = [Z_{primitive}]^{-1}$$

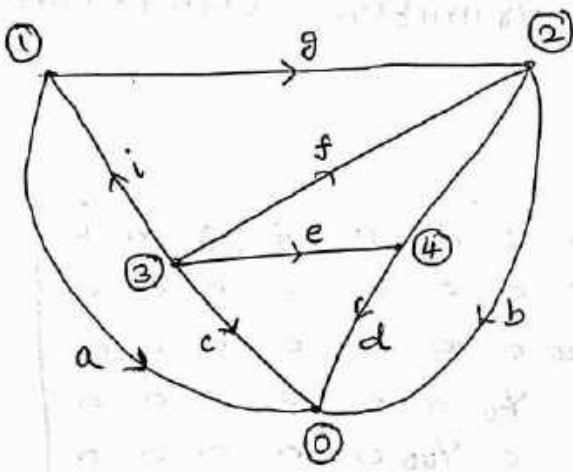Find  $Y_{Bus}$  using singular transformation for the system shown.



Step 1: Draw a tree

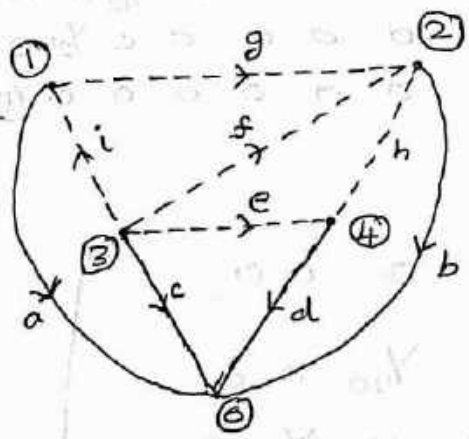

- \* Outward from node (+1)
- \* Toward the node (-1)

Step 2: Find  $[A]$  and  $[A^T]$

Bus incidence Matrix  $[A] =$

	a	b	c	d	e	f	g	h
(1)	1	0	0	0	0	0	+1	0
(2)	0	1	0	0	0	-1	-1	-1
(3)	0	0	1	0	1	1	0	0
(4)	0	0	0	1	-1	0	0	1

$$A^T = a \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & -1 \\ 0 & -1 & 1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & -1 & 0 & 1 \\ -1 & 0 & 1 & 0 \end{bmatrix}_{9 \times 4}$$

Step 3: Calculate primitive admittance matrix  
 $[Y_{\text{primitive}}]$

$$Y_{\text{primitive}} = \begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \\ h \\ i \end{matrix} \begin{bmatrix} a & b & c & d & e & f & g & h & i \\ Y_{10} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Y_{20} & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Y_{30} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & Y_{40} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & Y_{34} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Y_{23} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Y_{12} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & Y_{24} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & Y_{13} \end{bmatrix}_{9 \times 9}$$


$$[Y_{\text{primitive}}][A^T] = \begin{bmatrix} Y_{10} & 0 & 0 & 0 \\ 0 & Y_{20} & 0 & 0 \\ 0 & 0 & Y_{30} & 0 \\ 0 & 0 & 0 & Y_{40} \\ 0 & 0 & Y_{34} & -Y_{34} \\ 0 & -Y_{23} & Y_{23} & Y_{10} \\ Y_{12} & -Y_{12} & 0 & 0 \\ 0 & -Y_{24} & 0 & Y_{24} \\ -Y_{13} & 0 & Y_{13} & 0 \end{bmatrix}_{9 \times 4}$$

Step 4: calculate bus admittance matrix  $Y_{bus}$

$$Y_{bus} = [A] [Y_{primitive}] [A^T]$$



$$Y_{primitive} = \begin{bmatrix} Y_{10} + Y_{12} + Y_{13} & -Y_{12} & -Y_{13} & 0 \\ -Y_{12} & Y_{20} + Y_{12} + Y_{23} + Y_{24} & -Y_{23} & -Y_{24} \\ Y_{13} & -Y_{23} & Y_{30} + Y_{31} + Y_{23} + Y_{24} & -Y_{34} \\ 0 & -Y_{24} & -Y_{34} & Y_{40} + Y_{24} + Y_{34} \end{bmatrix}$$

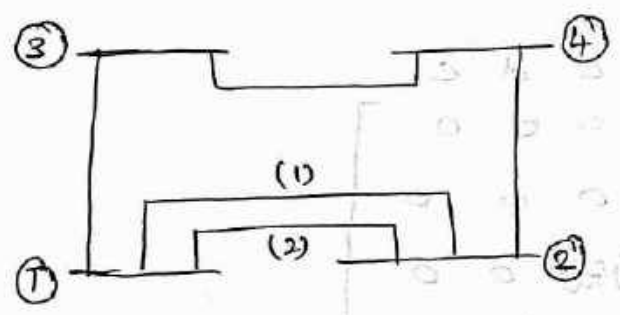Form  $Y_{bus}$  by singular transformation for the n/w shown in figure. The impedance data is given in table. Take (1) as reference node.



Bus code	Self impedance
1-2(1)	0.6
1-3	0.5
3-4	0.5
1-2(2)	0.4
2-4	0.2

oriented graph

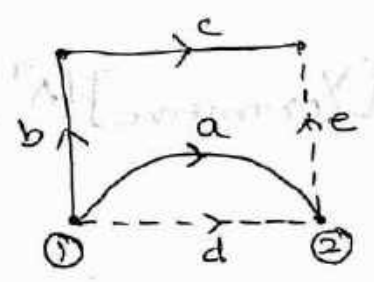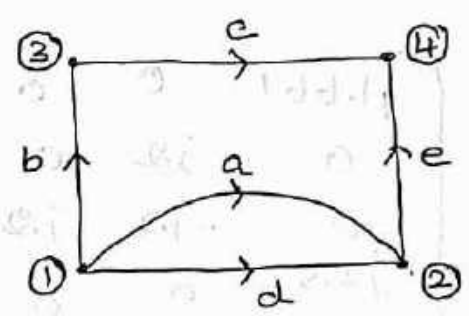

Incidence matrix  $[A] = \begin{matrix} & a & b & c & d & e \\ \begin{matrix} 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} -1 & 0 & 0 & -1 & 1 \\ 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 \end{bmatrix} \end{matrix}$

$$A^T = \begin{matrix} & \begin{matrix} (2) & (3) & (4) \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \\ e \end{matrix} & \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix} \end{matrix}$$

$$Z_{\text{primitive}} = \begin{matrix} & \begin{matrix} a & b & c & d & e \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \\ e \end{matrix} & \begin{bmatrix} j0.6 & 0 & 0 & 0 & 0 \\ 0 & j0.5 & 0 & 0 & 0 \\ 0 & 0 & j0.5 & 0 & 0 \\ 0 & 0 & 0 & j0.4 & 0 \\ 0 & 0 & 0 & 0 & j0.2 \end{bmatrix} \end{matrix}$$

$$Y_{\text{primitive}} = [Z_{\text{primitive}}]^{-1}$$

$$= \begin{matrix} & \begin{matrix} a & b & c & d & e \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \\ e \end{matrix} & \begin{bmatrix} -j1.667 & 0 & 0 & 0 & 0 \\ 0 & -j2 & 0 & 0 & 0 \\ 0 & 0 & -j2 & 0 & 0 \\ 0 & 0 & 0 & -j2.5 & 0 \\ 0 & 0 & 0 & 0 & -j5 \end{bmatrix} \end{matrix}$$



$$[Y_{\text{primitive}}][A^T] = \begin{bmatrix} j1.667 & 0 & 0 \\ 0 & j2 & 0 \\ 0 & -j2 & j2 \\ j2.5 & 0 & 0 \\ -j5 & 0 & j5 \end{bmatrix}$$

$$Y_{\text{Bus}} = [A][Y_{\text{primitive}}][A^T] = \begin{bmatrix} -j9.167 & 0 & j5 \\ 0 & -j4 & j2 \\ j5 & j2 & -j7 \end{bmatrix}$$



shows in figure. Take node 1 as reference

Bus code	Self Impedance	Bus code	Mutual Impedance
1-2	0.5	1-2	0.1
1-3	0.6		
3-4	0.4		
2-4	0.3		

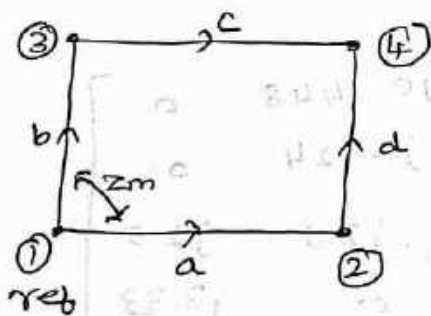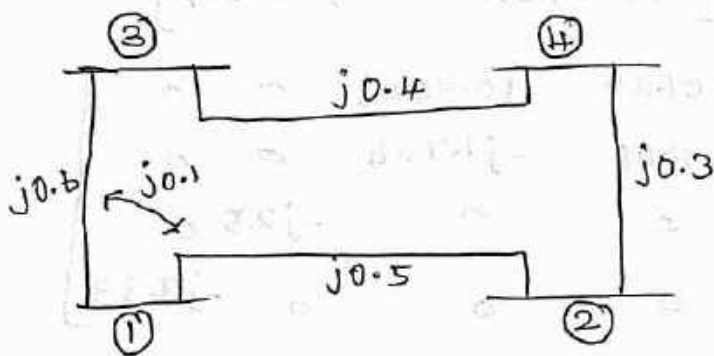

Incidence matrix  $[A] = \begin{matrix} & \begin{matrix} (a) & (b) & (c) & (d) \end{matrix} \\ \begin{matrix} (1) \\ (2) \\ (3) \\ (4) \end{matrix} & \begin{bmatrix} -1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & -1 \end{bmatrix} \end{matrix}$

$A^T = \begin{matrix} \begin{matrix} (2) & (3) & (4) \end{matrix} \\ \begin{matrix} (a) \\ (b) \\ (c) \\ (d) \end{matrix} & \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & -1 \end{bmatrix} \end{matrix}$

$$Z_{\text{primitive}} = \begin{matrix} & \begin{matrix} a & b & c & d \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \end{matrix} & \begin{bmatrix} j0.5 & j0.1 & 0 & 0 \\ j0.1 & j0.6 & 0 & 0 \\ 0 & 0 & j0.4 & 0 \\ 0 & 0 & 0 & j0.3 \end{bmatrix} \end{matrix}$$

consider this matrix  $\begin{bmatrix} j0.5 & j0.1 \\ j0.1 & j0.6 \end{bmatrix}^{-1} = \frac{1}{-0.29} \begin{bmatrix} j0.6 & -j0.1 \\ -j0.1 & j0.5 \end{bmatrix}$

$$= \begin{bmatrix} -j2.0689 & j0.3448 \\ j0.3448 & -j1.724 \end{bmatrix}$$

$$Y_{\text{primitive}} = \begin{bmatrix} -j2.0689 & j0.3448 & 0 & 0 \\ j0.3448 & -j1.724 & 0 & 0 \\ 0 & 0 & -j2.5 & 0 \\ 0 & 0 & 0 & -j3.33 \end{bmatrix}$$

$$Y_{\text{bus}} = [A][Y_{\text{primitive}}][A^T]$$

$$[Y_{\text{primitive}}][A^T] = \begin{bmatrix} +j2.0689 & -j0.3448 & 0 \\ -j0.3448 & j1.724 & 0 \\ 0 & -j2.5 & j2.5 \\ -j3.33 & 0 & j3.33 \end{bmatrix}$$

$$[A][Y_{\text{primitive}}][A^T] = \begin{bmatrix} -j5.4019 & j0.3448 & j3.33 \\ j0.3448 & j4.224 & +j2.5 \\ j3.33 & j2.5 & -j5.833 \end{bmatrix}$$

Advantages of this technique are: (1) easy, (2) simple, (3) no need for complex machinery.

Disadvantages of this technique are: (1) it is not very accurate, (2) it is not very sensitive, (3) it is not very specific.

- Advantages of this technique
- Easy to use
- Simple and accurate

Type 1 medication: having a new use or indication, but not the same as the original use.

Type 2 medication: having a new use or indication, but not the same as the original use.

Type 3 medication: having a new use or indication, but not the same as the original use.

Type 4 medication: having a new use or indication, but not the same as the original use.

Example: Type 1 medication

$$I_{\text{new}} = \begin{bmatrix} I_{\text{old}} & 0 \\ \vdots & \vdots \\ 0 \dots 0 & 1 \end{bmatrix}$$

## Formula Type 2 Modification

$$Z_{Bus}(new) = \left[ \begin{array}{c|c} Z_{Bus,old} & \begin{matrix} Z_{1i} \\ Z_{2i} \\ \vdots \\ Z_{ni} \end{matrix} \\ \hline \begin{matrix} (Z_{i1} \ Z_{i2} \ \dots \ Z_{in}) \\ Z_i^T \end{matrix} & Z_{ii} + Z_i \end{array} \right]$$

## Formula Type 3 Modification

Step 1: Proceed with type 2 modification


$$Z_{Bus}(new) = \left[ \begin{array}{c|c} Z_{Bus,old} & \begin{matrix} Z_{i1} \\ Z_{i2} \\ \vdots \\ Z_{in} \end{matrix} \\ \hline \begin{matrix} Z_{j1} \ Z_{j2} \ \dots \ Z_{jn} \\ Z_j^T \end{matrix} & Z_{jj} + Z_j \end{array} \right]$$

Step 2: then Apply Kron's Reduction technique


## Formula Type 4 Modification

$$Z_{Bus,new} = \left[ \begin{array}{c|c} Z_{Bus,old} & \begin{matrix} i^{th} - j^{th} \text{ column} \\ \vdots \\ \vdots \end{matrix} \\ \hline \begin{matrix} i^{th} - j^{th} \text{ row} \\ \vdots \\ \vdots \end{matrix} & Z_{ii} + Z_{jj} - 2Z_{ij} + Z_i \end{array} \right]$$

Obtain the Z-Bus matrix

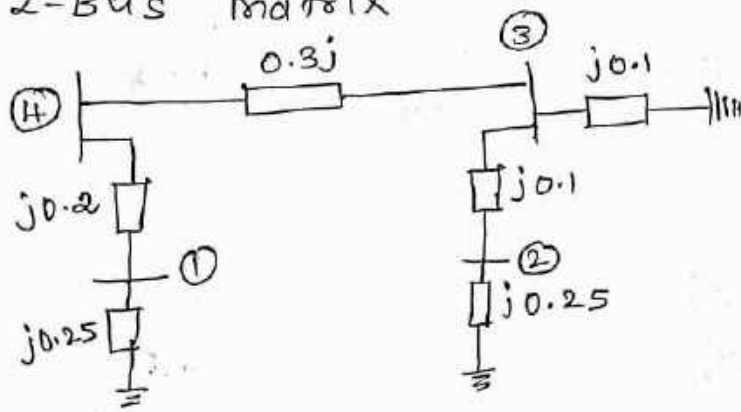


Step 1:  
Type 1

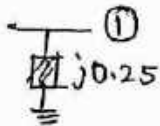

$$Z_{bus} = [j0.25]$$

Step 2:


Type 1

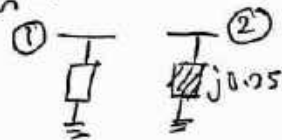

$$Z_{bus} = \begin{bmatrix} j0.25 & 0 \\ 0 & j0.25 \end{bmatrix}$$

Step 3:


Type 1

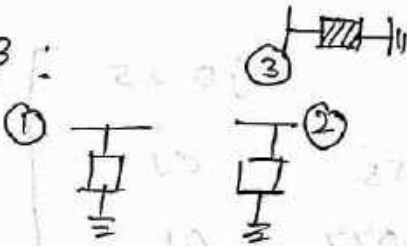

$$Z_{bus} = \begin{bmatrix} j0.25 & 0 & 0 \\ 0 & j0.25 & 0 \\ 0 & 0 & j0.1 \end{bmatrix}$$

Step 4:

Type 4

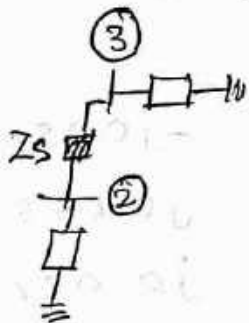

$$Z_{bus} = \begin{bmatrix} j0.25 & 0 & 0 & 0 \\ 0 & j0.25 & 0 & j0.25 \\ 0 & 0 & j0.1 & j0.1 \\ 0 & j0.25 & j0.1 & j0.45 \end{bmatrix}$$

$$\begin{aligned} Z_{44} &= Z_{22} + Z_{33} - 2Z_{23} + Z_s \\ &= j0.25 + j0.1 - 2(0) + j0.1 \\ &= j0.45 \end{aligned}$$

Apply Kron's reduction (or) Gauss elimination technique

$$Z_{ij}(\text{new}) = Z_{ij}(\text{old}) - \frac{Z_{in} \cdot Z_{nj}}{Z_{nn}} \quad n=4$$

$$Z_{11, \text{new}} = 0.25j$$

$$Z_{12, \text{new}} = Z_{21, \text{new}} = 0j$$

$$Z_{13, \text{new}} = Z_{31, \text{new}} = 0j$$

$$Z_{22, \text{new}} = j0.111$$


$$Z_{23, \text{new}} = Z_{32, \text{new}} = j0.0555$$

$$Z_{33, \text{new}} = j0.0777$$

$$Z_{\text{bus}} = \begin{bmatrix} j0.25 & 0j & 0j \\ 0j & j0.111 & j0.0555 \\ 0j & j0.055 & j0.0777 \end{bmatrix}$$

Type 2


Step 5

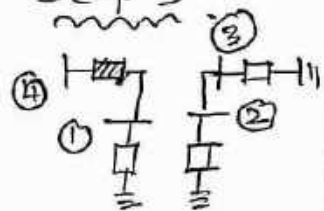

$$Z_{\text{bus}} = \begin{bmatrix} j0.25 & 0j & 0j & j0.25 \\ 0j & j0.111 & j0.055 & 0j \\ 0 & j0.055 & j0.077 & 0j \\ j0.25 & 0 & 0 & j0.45 \end{bmatrix}$$

$$Z_{44} = Z_{11} + Z_s = 0.45j$$

Type 4  
Step 6

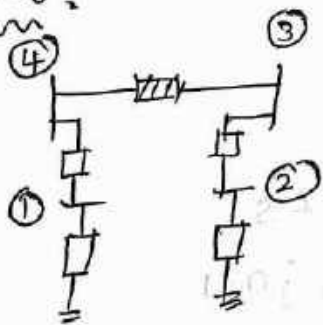

$$Z_{\text{bus}} = \begin{bmatrix} j0.25 & 0j & 0j & j0.25 & -j0.25 \\ 0j & j0.111 & j0.055 & 0j & j0.055 \\ 0j & j0.055 & j0.077 & 0j & j0.077 \\ j0.25 & 0 & 0 & j0.45 & -j0.45 \\ j0.25 & j0.055 & j0.077 & j0.45 & j0.8277 \end{bmatrix}$$


$$\begin{aligned} Z_{55} &= Z_{33} + Z_{44} - 2Z_{34} + Z_s \\ &= j0.8277 \end{aligned}$$

Apply Kron's reduction technique

$$n=5 \quad Z_{ij, new} = Z_{ij, old} - \frac{Z_{in} \cdot Z_{ni}}{Z_{nn}}$$

$$\therefore Z_{bus} = \begin{bmatrix} j0.1745 & j0.01676 & j0.02346 & j0.1141 \\ j0.01676 & j0.1673 & j0.0503 & j0.0302 \\ j0.02346 & j0.0503 & j0.0705 & j0.0423 \\ j0.1141 & j0.0302 & j0.0423 & j0.2053 \end{bmatrix}$$

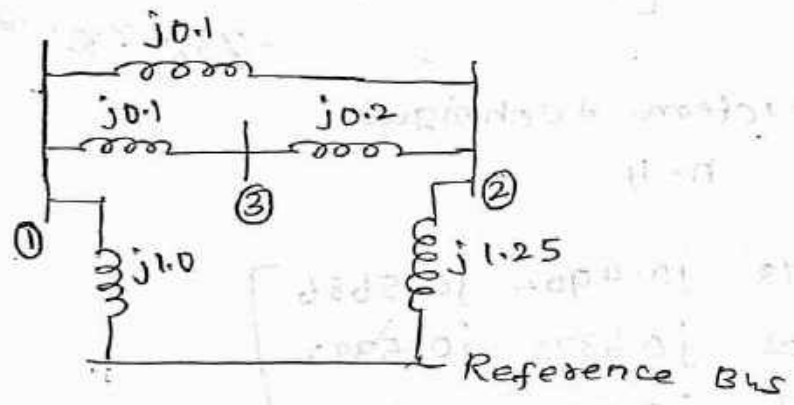Determine the  $Z_{bus}$  for a 3-bus system as shown in figure, where impedances are shown and the values are in pu.



Step 1: Type 1


$$\textcircled{1} \quad Z_{bus} = [j1.0]$$

Step 2:

$$\textcircled{1} \quad \textcircled{2} \quad Z_{bus} = \begin{bmatrix} j1.0 & 0 \\ 0 & j1.25 \end{bmatrix}$$




Step 3: Type 2

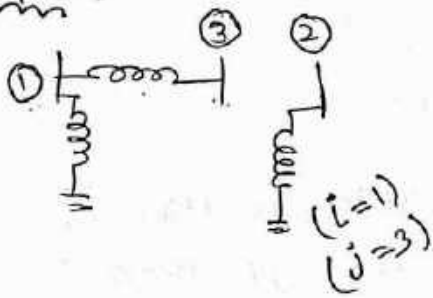

$$Z_{Bus} = \begin{bmatrix} j1.0 & 0 & j1.0 \\ 0 & j1.25 & 0 \\ j1.0 & 0 & j1.1 \end{bmatrix}$$

$$= Z_{11} + Z_3 \\ = j1.0 + j0.1 \\ = j1.1$$

Step 4: Type 4

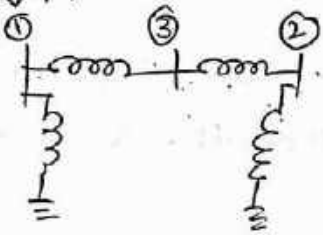

$$Z_{Bus} = \begin{bmatrix} j1.0 & 0 & j1.0 & j1.0 \\ 0 & j1.25 & 0 & -j1.25 \\ j1.0 & 0 & j1.1 & j1.1 \\ j1.0 & -j1.25 & j1.1 & j2.55 \end{bmatrix} \quad \begin{matrix} (i=3) \\ (j=2) \end{matrix}$$

$$= Z_{22} + Z_{33} - 2Z_{23} + Z_5$$

Apply Kron's reduction technique

$$n=4$$

$$Z_{Bus} = \begin{bmatrix} j0.6078 & j0.4902 & j0.5686 \\ j0.4902 & j0.6372 & j0.5392 \\ j0.5686 & j0.5392 & j0.6255 \end{bmatrix}$$

Step 5 Type 4


$$Z_{Bus} = \begin{bmatrix} j0.6078 & j0.4902 & j0.5686 & -j0.1176 \\ j0.4902 & j0.6372 & j0.5392 & j0.147 \\ j0.5686 & j0.5392 & j0.6255 & -j0.029 \\ -j0.1176 & j0.147 & -j0.0294 & j0.3646 \end{bmatrix} \quad \begin{matrix} i=2 \\ j=1 \end{matrix}$$

Apply Kron's Reduction

$$Z_{11} + Z_{22} - 2Z_{12} + Z_5$$


$$Z_{Bus} = \begin{bmatrix} j0.5699 & j0.5376 & j0.5591 \\ j0.5376 & j0.5779 & j0.5511 \\ j0.5591 & j0.5511 & j0.6231 \end{bmatrix}$$

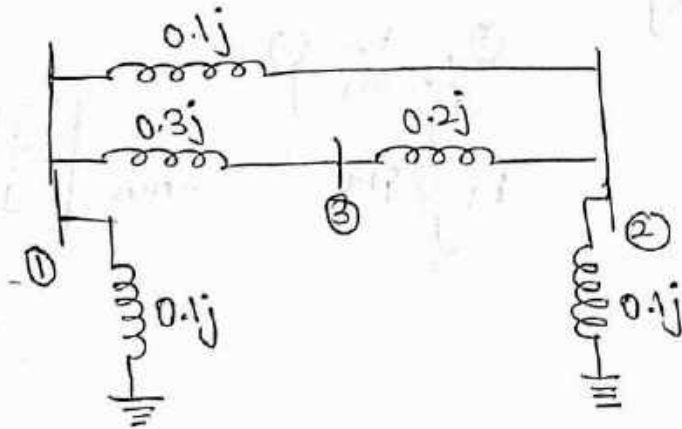Determine the Z-bus for a 3 Bus s/m shown in figure




$$Z_{Bus} = \begin{bmatrix} j0.1422 & j0.1078 & j0.1164 \\ j0.1078 & j0.1422 & j0.1376 \\ j0.1164 & j0.1376 & j0.21402 \end{bmatrix}$$

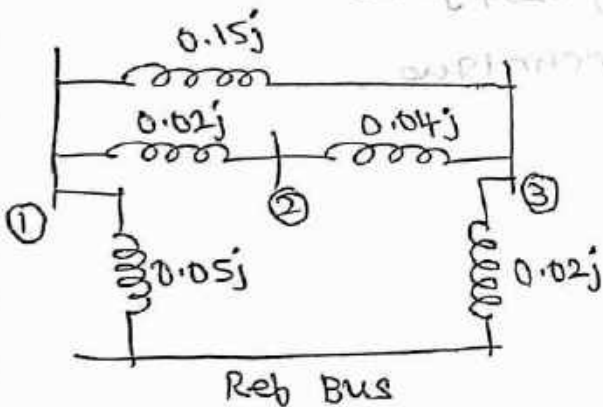Determine  $Z_{Bus}$  for the network shown in figure where the impedances are in per unit.



$$Z_{Bus} = \begin{bmatrix} j0.0279 & j0.02153 & j0.0088 \\ j0.02153 & j0.03145 & j0.0113 \\ j0.0088 & j0.0113 & j0.0164 \end{bmatrix}$$

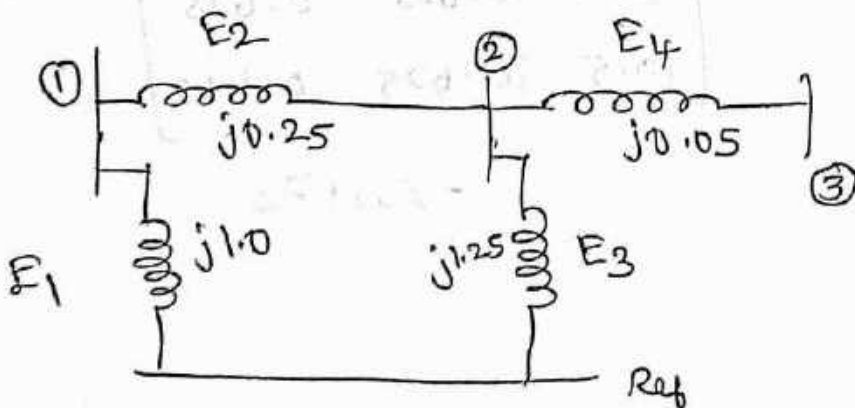Determine  $Z_{Bus}$  using Building algorithm by adding the lines as per increasing element number.




Step 1:



$$Z_{Bus} = [j1.0]$$


Step 2 Type 2

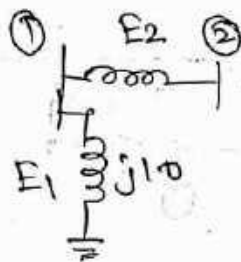

$$Z_{Bus} = \begin{bmatrix} j1.0 & j1.0 \\ j1.0 & j1.25 \end{bmatrix}$$

$$= Z_{11} + Z_s \\ = j1.0 + j0.25$$

Step 3: Type 3

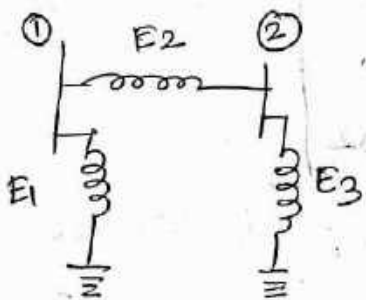


$$Z_{Bus} = \begin{bmatrix} j1.0 & j1.0 & j1.0 \\ j1.0 & j1.25 & j1.25 \\ j1.0 & j1.25 & j2.5 \end{bmatrix}$$

$$= Z_{kk} + Z_s \\ = j1.25 + j1.25$$

Apply Kron's reduction technique

$$Z_{Bus} = \begin{bmatrix} 0.6j & 0.5j \\ 0.5j & 0.625j \end{bmatrix}$$

Step 4 Type 2

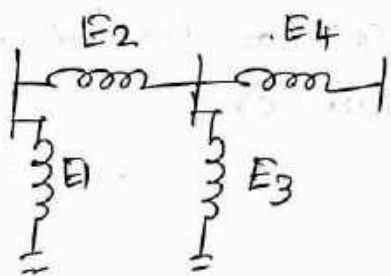

$$Z_{Bus} = \begin{bmatrix} j0.6 & j0.5 & j0.5 \\ j0.5 & j0.625 & j0.625 \\ j0.5 & j0.625 & j0.675 \end{bmatrix}$$

$$= Z_{22} + Z_s$$

# Z<sub>Bus</sub> Building Algorithm

$$Z_{Bus(Old)} \xrightarrow{Z_b = \text{Branch Impedance}} Z_{Bus(New)}$$

$i, j = \text{old buses}$

$r = \text{reference Bus}$

$k = \text{new Bus}$

Type 1 modification:

$$Z_{bus(new)} = \begin{bmatrix} Z_{bus(Old)} & 0 \\ \vdots & \vdots \\ 0 \dots 0 & Z_b \end{bmatrix}$$

Type 2 modification:

$$Z_{bus(new)} = \begin{bmatrix} Z_{bus(Old)} & Z_{ij} \\ \vdots & \vdots \\ Z_j^i \ Z_j^2 \dots Z_j^n & Z_{jj} + Z_b \end{bmatrix}$$


Type 3 modification:

$$Z_{bus(new)} = Z_{bus(Old)} - \frac{1}{Z_{jj} + Z_b} \begin{bmatrix} Z_{ij} \\ \vdots \\ Z_{nj} \end{bmatrix} [Z_{j1} \dots Z_{jn}]$$

Type 4 modification:

$$Z_{Bus}(new) = Z_{Bus}(old) - \frac{1}{Z_b + Z_{ii} + Z_{jj} - 2Z_{ij}} \begin{bmatrix} Z_{i1} & \dots & Z_{ij} \\ \vdots & & \vdots \\ Z_{ni} & \dots & Z_{nj} \end{bmatrix}$$

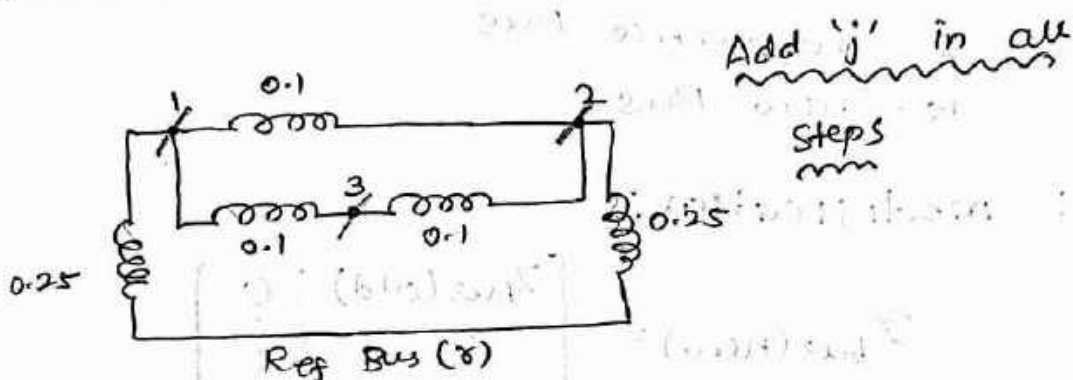① For the 3-bus network shown in figure, build Bus Impedance matrix



Step 1: Add branch  $Z_{1r} = 0.25$  (bus 1 (new) to bus r)

$$Z_{Bus} = j \begin{bmatrix} 0.25 \end{bmatrix} \text{ [Type 1]}$$

Step 2: Add branch  $Z_{21} = 0.1$  (from bus 2 (new) to bus 1 (old))

$$Z_{Bus} = j \begin{bmatrix} 0.25 & 0.25 \\ 0.25 & 0.35 \end{bmatrix} \text{ [Type 2]}$$

$0.25 + 0.1$

Step 3: Add branch  $Z_{13} = 0.1$  (from bus (3) new to bus 1 (old))

$$Z_{Bus} = j \begin{bmatrix} 0.25 & 0.25 & 0.25 \\ 0.25 & 0.35 & 0.25 \\ 0.25 & 0.25 & 0.35 \end{bmatrix} \text{ [Type 2]}$$

$0.35 + 0.1$

Step 4: Add branch  $Z_{2r} = 0.25$  (bus 2(olds) to bus r)

$$Z_{bus} = \begin{bmatrix} 0.25 & 0.25 & 0.25 \\ 0.25 & 0.35 & 0.25 \\ 0.25 & 0.25 & 0.35 \end{bmatrix} - \frac{1}{0.35 + 0.25} \begin{bmatrix} 0.25 \\ 0.35 \\ 0.25 \end{bmatrix} \begin{bmatrix} 0.25 & 0.35 & 0.25 \end{bmatrix}$$

Column  
2 Row  
2 column

$$= \begin{bmatrix} 0.1458 & 0.1042 & 0.1458 \\ 0.1042 & 0.1458 & 0.1042 \\ 0.1458 & 0.1042 & 0.2458 \end{bmatrix}$$


Type 3

Step 5: Add branch  $Z_{23} = 0.1$  (from bus 2(olds) to bus 3(olds))

$$Z_{bus} = Z_{bus,old} - \frac{1}{(0.1 + 0.1458 + 0.2458 - 2 \times 0.1042)} \begin{bmatrix} -0.0416 \\ 0.0417 \\ -0.0417 \end{bmatrix} \begin{bmatrix} -0.0416 & 0.0417 & -0.0417 \end{bmatrix}$$

Type 4
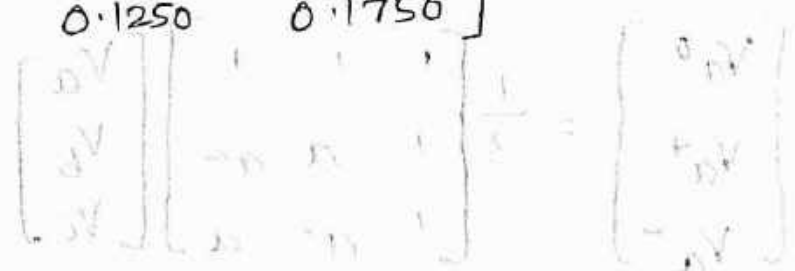
$$Z_{bus} = \begin{bmatrix} 0.1397 & 0.1103 & 0.1250 \\ 0.1103 & 0.1397 & 0.1250 \\ 0.1250 & 0.1250 & 0.1750 \end{bmatrix}$$



$$\textcircled{1} \quad \frac{dV}{c} = \dots$$




POWER SYSTEM ANALYSIS - UNIVERSITY SOLVED PROBLEMS  
LECTURE NOTES PAPER


Unit-1

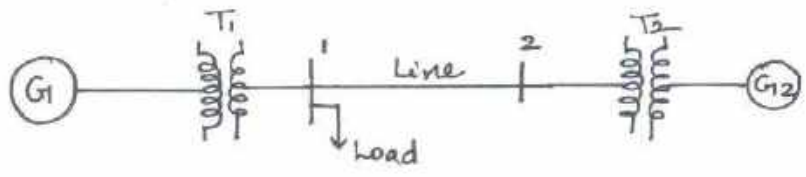1. Draw the impedance diagram for the electric power system shown in figure showing all impedances in per unit on a 100 MVA base. Choose 20KV as the voltage base for generator. The three phase power and line-line ratings are given below (April/May 2011)

- $G_1$  : 90MVA 20KV  $X=9\%$
- $T_1$  : 80MVA 20/200KV  $X=16\%$
- $T_2$  : 80MVA 200/20KV  $X=20\%$
- $G_2$  : 90MVA 18KV  $X=9\%$
- Line: 200KV  $X=120\Omega$
- load: 200KV,  $S=48MW + j64MVar$



Soln:-

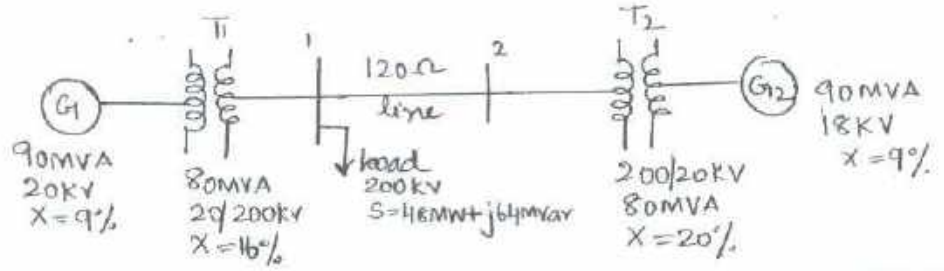

Impedance of  $G_1$

$KV_{b,new} = 20KV$      $MVA_{b,new} = 100MVA$

$$Z_{pu, G1} = Z_{pu,old} \times \left( \frac{KV_{bold}}{KV_{b,new}} \right)^2 \times \left( \frac{MVA_{b,new}}{MVA_{bold}} \right)$$

$$Z_{pu,old} = \frac{9}{100} = j0.09pu$$

$$KV_{bold} = 20KV$$

$$KV_{b,new} = 20KV$$

$$MVA_{b,new} = 100MVA$$

$$MVA_{bold} = 90MVA$$

$$Z_{pu, G1} = j0.09 \times \left( \frac{20}{20} \right)^2 \times \left( \frac{100}{90} \right)$$

$$Z_{pu, G1} = j0.1pu$$



Impedance of  $T_1$  (with referred to primary)

$$KV_{b\text{old}} = 20 \text{ KV}$$

$$KV_{b\text{new}} = 20 \text{ KV}$$

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$MVA_{b\text{old}} = 80 \text{ MVA}$$

$$Z_{pu\text{old}} = \frac{16}{100} = j0.16 \text{ pu}$$

$$\begin{aligned} Z_{pu,\text{new } T_1} &= Z_{pu,\text{old}} \times \left( \frac{KV_{b\text{old}}}{KV_{b\text{new}}} \right)^2 \times \left( \frac{MVA_{b\text{new}}}{MVA_{b\text{old}}} \right) \\ &= j0.16 \times \left( \frac{20}{20} \right)^2 \times \left( \frac{100}{80} \right) \end{aligned}$$

$$Z_{pu,\text{new } T_1} = j0.2 \text{ pu}$$

Impedance of transmission line

$$KV_{b\text{new HT side of } T_1} = KV_{b\text{new on LT side of } T_1} \times \frac{\text{HT voltage rating}}{\text{LT voltage rating}}$$

$$KV_{b\text{new on HT of } T_1} = 20 \times \frac{200}{20} = 200 \text{ KV}$$

$$\text{now } KV_{b\text{new}} = 200 \text{ KV}$$

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$Z_{\text{actual}} = j120 \Omega$$

$$\text{Base impedance } Z_b = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(200)^2}{100}$$

$$Z_b = 400 \Omega$$

$$Z_{pu \text{ of line}} = \frac{\text{Actual value}}{\text{Base impedance}} = \frac{j120}{400}$$

$$Z_{pu \text{ of line}} = j0.3 \text{ pu}$$

Impedance of load

$$S = 48 \text{ MW} + j64 \text{ Mvar} \Rightarrow S^* = 48 - j64$$

$$V_L = 200 \text{ KV}$$

$$\text{Actual load impedance } Z_L = \frac{V_L^2}{S^*} = \frac{V_L^2}{P - jQ}$$

$$Z_L = \frac{200^2}{48 - j64} = 300 + 400j = 500 \angle 53.13^\circ \Omega$$

$$\text{Base impedance } Z_b = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(200)^2}{100} = 400 \Omega$$

$$Z_{pu} \text{ of load} = \frac{\text{Actual value}}{\text{Base impedance}}$$

$$Z_{pu} \text{ of load} = \frac{300 + 400j}{400} = 0.75 + j1.0 \text{ pu}$$

$$Z_{pu} \text{ of load} = 0.75 + j1.0 \text{ pu}$$

Impedance of T<sub>2</sub> referred to primary

$$KV_{b\text{old}} = 200 \text{ KV}$$

$$KV_{b\text{new}} = 200 \text{ KV}$$

$$MVA_{b\text{old}} = 80 \text{ MVA}$$

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$Z_{pu \text{ old}} = \frac{20}{100} = j0.2 \text{ pu}$$

$$Z_{pu \text{ new } T_2} = j0.2 \times \left(\frac{200}{200}\right)^2 \times \left(\frac{100}{80}\right)$$

$$Z_{pu \text{ new } T_2} = j0.25 \text{ pu}$$

Impedance of G2

$$KV_{b\text{new}} \text{ on LT side of } T_2 = KV_{b\text{new}} \text{ on HT side of } T_2 \times \frac{\text{LT voltage rating}}{\text{HT voltage rating}}$$

$$KV_{b\text{new}} \text{ on LT side of } T_2 = 200 \times \frac{20}{200} = 20 \text{ KV}$$

$$\text{now, } KV_{b\text{new}} = 20 \text{ KV}$$

$$Z_{pu \text{ old}} = \frac{9}{100} = j0.09 \text{ pu}$$


$$KV_{b\text{old}} = 18 \text{ KV}$$

$$MVA_{b\text{old}} = 90 \text{ MVA}$$

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$Z_{pu} \text{ of } G_2 = j0.09 \times \left(\frac{18}{20}\right)^2 \times \left(\frac{100}{90}\right)$$

$$Z_{pu} \text{ of } G_2 = j0.081 \text{ pu}$$

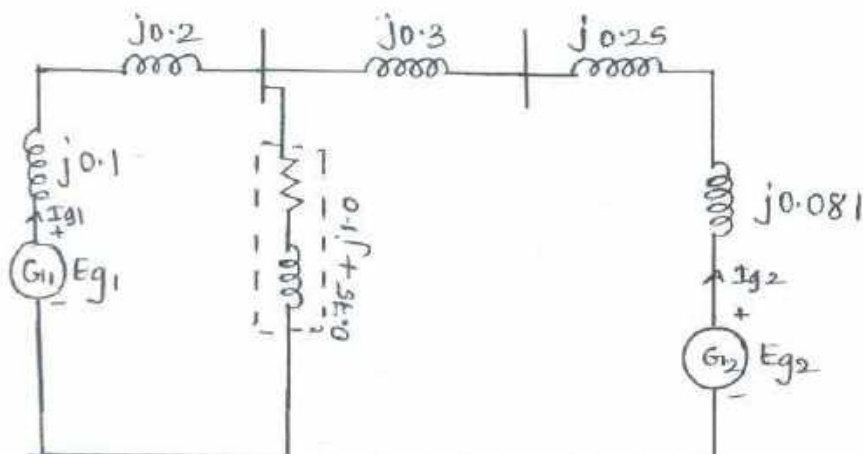Impedance Diagram

2. Draw the reactance diagram for the power system shown. Neglect resistance and use a base of 100MVA, 220KV in 50 $\Omega$  line. The ratings of the generator, motor and transformer are given below


Generator: 40MVA, 25KV,  $X'' = 20\%$

Synchronous motor: 50MVA, 11KV,  $X'' = 30\%$


Y-Y Transformer: 40MVA, 33/220KV,  $X = 15\%$

Y- $\Delta$  Transformer: 30MVA, 11/220KV ( $\Delta/Y$ ),  $X = 15\%$

(May/June 2012)

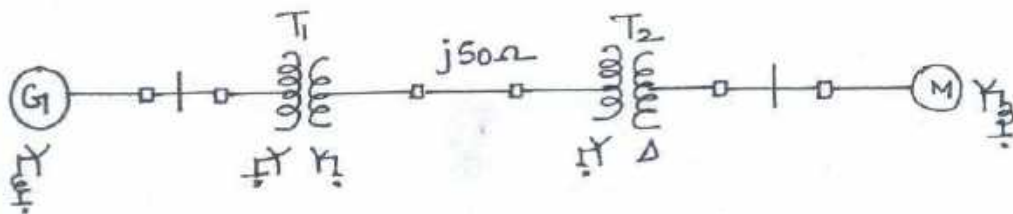

Soln:-

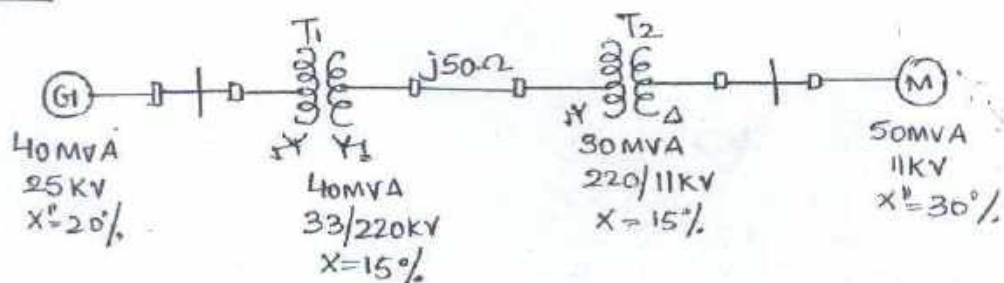

$$MVA_{bnew} = 100MVA$$

$$KV_{bnew} = 220KV \text{ (on } 50\Omega \text{ line)}$$

Reactance of 50 $\Omega$  line

$$X_{pu} \text{ of line} = \frac{\text{Actual value}}{\text{Base reactance}}$$

$$\text{Base reactance } X_b = \frac{(KV_{bnew})^2}{MVA_{bnew}} = \frac{(220KV)^2}{100} = 484\Omega$$



LECTURE NOTES PAPER

Actual value =  $j50 \Omega$

$$X_{pu} \text{ of line} = \frac{j50}{484}$$

$$X_{pu \text{ new of line}} = j0.1033 \text{ pu}$$

Reactance of  $T_1$  referred to primary

$$KV_{b \text{ new on LT side of } T_1} = KV_{b \text{ new on HT side}} \times \frac{\text{LT voltage rating}}{\text{HT voltage rating}}$$

$$= 220 \times \frac{33}{220} = 33 \text{ KV}$$

now  $KV_{b \text{ new}} = 33 \text{ KV}$

$$KV_{b \text{ old}} = 33 \text{ KV}$$

$$MVA_{b \text{ old}} = 40 \text{ MVA}$$

$$MVA_{b \text{ new}} = 100 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{15}{100} = j0.15 \text{ pu}$$

$$X_{pu \text{ new}} = X_{pu \text{ old}} \times \left( \frac{KV_{b \text{ old}}}{KV_{b \text{ new}}} \right)^2 \times \left( \frac{MVA_{b \text{ new}}}{MVA_{b \text{ old}}} \right)$$

$$X_{pu \text{ new } T_1} = j0.15 \times \left( \frac{33}{33} \right)^2 \times \left( \frac{100}{40} \right)$$

$$X_{pu \text{ new } T_1} = j0.375 \text{ pu}$$

Reactance of  $G_1$

$$KV_{b \text{ old}} = 25 \text{ KV}$$

$$KV_{b \text{ new}} = 33 \text{ KV}$$

$$MVA_{b \text{ new}} = 100 \text{ MVA}$$

$$MVA_{b \text{ old}} = 40 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{20}{100} = j0.2 \text{ pu}$$

## LECTURE NOTES PAPER

T

$$X_{pu \text{ new of } G1} = j0.2 \times \left(\frac{25}{33}\right)^2 \times \left(\frac{100}{40}\right)$$

$$X_{pu \text{ new of } G1} = j0.286 \text{ pu}$$

Reactance of  $T_2$  referred to secondary

$$KV_{b \text{ new on LT side of } T_2} = KV_{\text{new on HT side of } T_2} \times \frac{\text{LT rating}}{\text{HT rating}}$$

$$KV_{b \text{ new on LT of } T_2} = \frac{220 \times 11}{220} = 11 \text{ KV}$$

$$\text{now } KV_{b \text{ new}} = 11 \text{ KV}$$

$$KV_{b \text{ old}} = 11 \text{ KV}$$

$$MVA_{b \text{ new}} = 100 \text{ MVA}$$

$$MVA_{b \text{ old}} = 30 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{15}{100} = j0.15 \text{ pu}$$

$$X_{pu \text{ new of } T_2} = j0.15 \times \left(\frac{11}{11}\right)^2 \times \left(\frac{100}{30}\right)$$

$$X_{pu \text{ new of } T_2} = j0.5 \text{ pu}$$

Reactance of Motor

$$KV_{b \text{ new}} = 11 \text{ KV}$$

$$KV_{b \text{ old}} = 11 \text{ KV}$$

$$MVA_{b \text{ old}} = 50 \text{ MVA}$$

$$MVA_{b \text{ new}} = 100 \text{ MVA}$$


$$X_{pu \text{ old}} = \frac{30}{100} = j0.3 \text{ pu}$$

LECTURE NOTES PAPER

$$X_{pu \text{ new of } M} = j0.3 \times \left(\frac{11}{11}\right)^2 \times \left(\frac{100}{50}\right)$$

$$X_{pu \text{ new of } M} = j0.6 \text{ pu}$$

Reactance Diagram

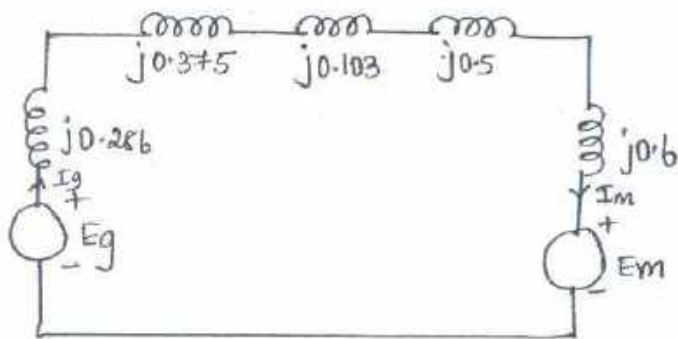

3. The one-line diagram of a power system is shown in fig. The three phase power and line-line ratings are given below


- G<sub>1</sub> : 80MVA    22KV    X=9%
- T<sub>1</sub> : 50MVA    22/220KV    X=10%
- T<sub>2</sub> : 40MVA    220/22KV    X=6.0%
- T<sub>3, T<sub>4</sub></sub> : 40MVA    22/110KV    X=6.4%
- Line1 : 220KV    X=121Ω
- Line2 : 110KV    X=42.35Ω
- M : 68.85MVA    20KV    X=22.5%
- Load : 10MVA    4KV    Δ-connected capacitor.

Draw an impedance diagram showing all impedances in perunit on a 100MVA base. Choose 22KV as the voltage base for generator.


(NOV/Dec 2012)



LECTURE NOTES PAPER

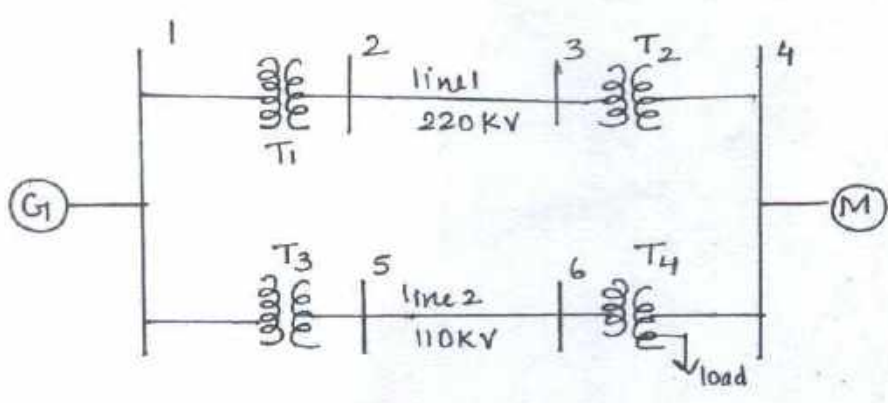

Soln:-

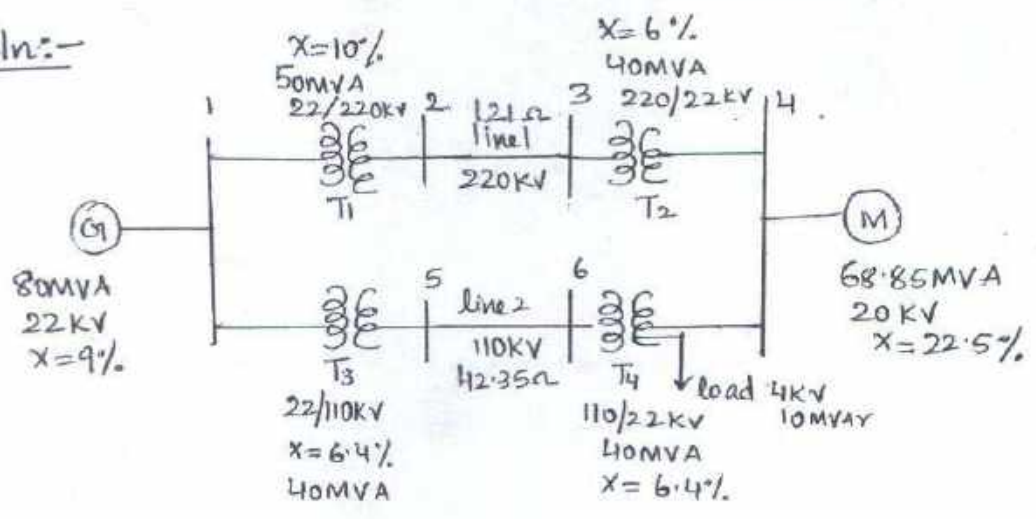

$MVA_{b\ new} = 100MVA$

$KV_{b\ new} = 22KV$

Impedance of G1

$KV_{b\ new} = 22KV$

$MVA_{b\ new} = 100MVA$

$MVA_{b\ old} = 80MVA$

$KV_{b\ old} = 22KV$

$Z_{pu\ old} = \frac{9}{100} = j0.09 pu$

$Z_{pu\ new} = Z_{pu\ old} \times \left(\frac{KV_{b\ old}}{KV_{b\ new}}\right)^2 \times \left(\frac{MVA_{b\ new}}{MVA_{b\ old}}\right)$

$Z_{pu\ new\ G1} = j0.09 \times \left(\frac{22}{22}\right)^2 \times \left(\frac{100}{80}\right)$

$Z_{pu\ new\ of\ G1} = j0.1125 pu$

Impedance of T<sub>1</sub> referred to primary

$$KV_{b\text{old}} = 22 \text{ KV}$$

$$KV_{b\text{new}} = 22 \text{ KV}$$

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$MVA_{b\text{old}} = 50 \text{ MVA}$$

$$Z_{pu\text{old}} = \frac{10}{100} = j \cdot 0.10 \text{ pu}$$

$$Z_{pu\text{new } T_1} = j \cdot 0.10 \times \left( \frac{22}{22} \right)^2 \times \left( \frac{100}{50} \right)$$

$$Z_{pu\text{new } T_1} = j \cdot 0.2 \text{ pu}$$

Impedance of line 1 (220KV line)

$$KV_{b\text{new}} \text{ on HT side of } T_1 = KV_{b\text{new}} \text{ on LT side} \times \frac{\text{HT rating}}{\text{LT rating}}$$

$$= 22 \times \frac{220}{22} = 220 \text{ KV}$$

$$\text{now } KV_{b\text{new}} = 220$$

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$\text{Base impedance} = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}}$$

$$Z_b = \frac{(220)^2}{100} = 484 \Omega$$

$$\text{Actual value} = j121 \Omega$$

$$Z_{pu\text{new of line 1}} = \frac{\text{Actual value}}{\text{Base value}}$$

$$Z_{pu\text{new line 1}} = \frac{j121}{484}$$

$$Z_{pu\text{new line}} = j \cdot 0.25 \text{ pu}$$

## LECTURE NOTES PAPER

Impedance of  $T_2$  with referred to secondary

$$KV_{b\text{new}} \text{ on LT side of } T_2 = KV_{b\text{new}} \text{ on HT side} \times \frac{LT \text{ rating}}{HT \text{ rating}}$$

$$= \frac{220 \times 22}{220} \quad 22 \text{KV}$$

$$\text{now } KV_{b\text{new}} = 22 \text{KV}$$

$$KV_{b\text{old}} = 22 \text{KV}$$

$$MVA_{b\text{new}} = 100 \text{MVA}$$

$$MVA_{b\text{old}} = 40 \text{MVA}$$

$$Z_{\text{pu old}} = \frac{6}{100} = j0.06 \text{ pu}$$

$$Z_{\text{pu new } T_2} = j0.06 \times \left(\frac{22}{22}\right)^2 \times \left(\frac{100}{40}\right)$$

$$Z_{\text{pu new } T_2} = j0.15 \text{ pu}$$

Impedance of M

$$KV_{b\text{new}} = 22 \text{KV}$$

$$KV_{b\text{old}} = 20 \text{KV}$$

$$MVA_{b\text{old}} = 68.85 \text{MVA}$$

$$MVA_{b\text{new}} = 100 \text{MVA}$$

$$Z_{\text{pu old}} = \frac{22.5}{100} = j0.225 \text{ pu}$$

$$Z_{\text{pu new of M}} = j0.225 \times \left(\frac{20}{22}\right)^2 \times \left(\frac{100}{68.85}\right)$$

$$Z_{\text{pu new of M}} = j0.2700 \text{ pu}$$

Impedance of  $T_3$  referred to primary

$$KV_{b\text{old}} = 22KV$$

$$KV_{b\text{new}} = 22KV$$

$$MVA_{b\text{old}} = 40MVA$$

$$MVA_{b\text{new}} = 100MVA$$

$$Z_{pu\text{old}} = \frac{6.4}{100} = j0.064pu$$

$$Z_{pu\text{new } T_3} = j0.064 \times \left(\frac{22}{22}\right)^2 \times \left(\frac{100}{40}\right)$$

$$Z_{pu\text{new } T_3} = j0.16pu$$

Impedance of line 2 (110KV line)

$$KV_{b\text{new on HT side of } T_3} = KV_{b\text{new on LT side } T_3} \times \frac{HT\text{ rating}}{LT\text{ rating}}$$

$$= \frac{22 \times 110}{22} = 110KV$$

$$\text{new } KV_{b\text{new}} = 110KV$$

$$MVA_{b\text{new}} = 100MVA$$

$$\text{Base impedance} = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(110)^2}{100} = 121\Omega$$

$$Z_{\text{actual}} = j42.35\Omega$$

$$Z_{pu\text{new of line 2}} = \frac{\text{Actual Value}}{\text{Base impedance}} = \frac{j42.35}{121}$$

$$Z_{pu\text{new line 2}} = j0.35pu$$

LECTURE NOTES PAPER

Impedance of T<sub>4</sub> referred to primary

$KV_{bnew} = 110KV$

$KV_{bold} = 110KV$

$MVA_{bold} = 40MVA$

$MVA_{bnew} = 100MVA$

$Z_{pu\ old} = \frac{6.4}{100} = j0.064pu$

$Z_{pu\ new\ T_4} = j0.064 \times \left(\frac{110}{110}\right)^2 \times \left(\frac{100}{40}\right)$

$Z_{pu\ new\ of\ T_4} = j0.16pu$

Impedance of load

$Q = 10MVar$

$V_L = 4KV$  sine  $\Delta$  load  $P = 0$

$Z_L = \frac{3V_L^2}{P - jQ}$

$= \frac{3 \times 4^2}{0 - j10} = 4.8j$

Base impedance  $= \frac{(KV_{bnew})^2}{MVA_{bnew}}$

$KV_{bnew\ on\ HT\ side\ of\ T_4} = KV_b\ on\ HT\ side \times \frac{LT\ rating}{HT\ rating}$

$= 110 \times \frac{22}{110} = 22KV$


now  $KV_{bnew} = 22KV$

$Z_b = \frac{(22)^2}{100} = 4.84j$


$Z_{pu\ new\ of\ load} = \frac{4.8j}{4.84} = j0.991pu$



Impedance Diagrams:-

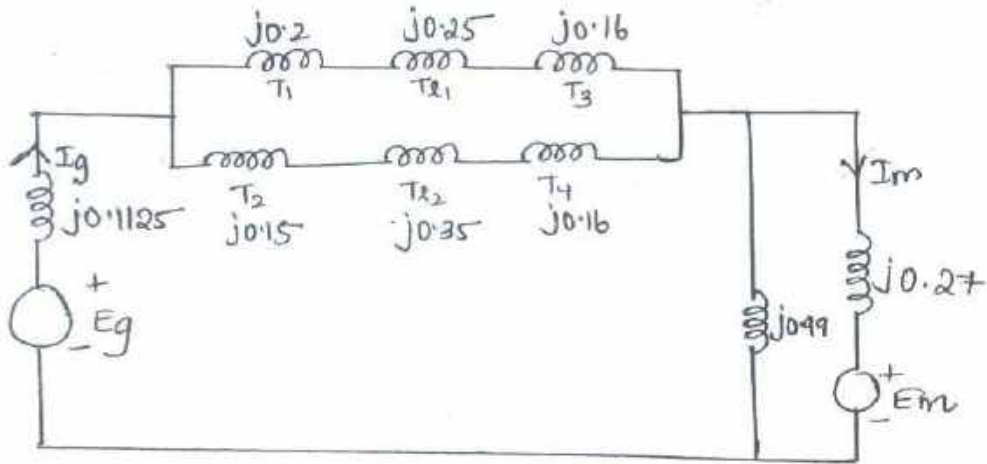

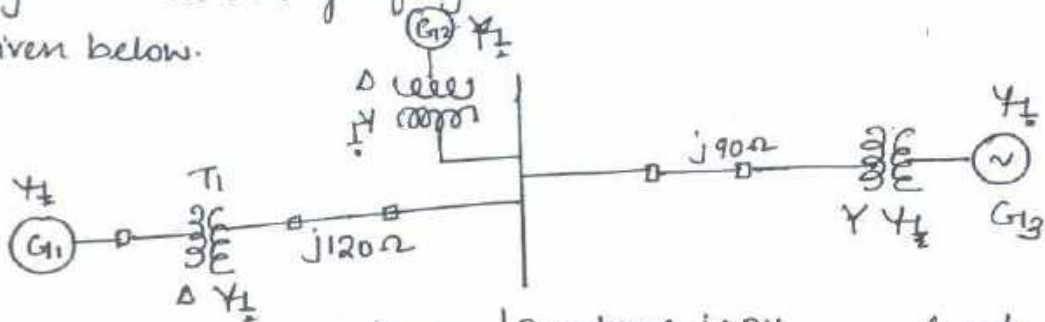4. The single line diagram of unloaded three generator power system with interconnection between the generators by means of three transformers and a transmission line with two sections with their impedances marked on the diagram. The ratings of generators and transformers are given below.



Generator	MVA	KV	Reactance in pu
1	25	6.6	0.2
2	15	6.6	0.15
3	30	13.2	0.15

(Nov/Dec 2013)

Transformer 1: 30MVA, 6.9Δ - 115Y KV, X=10%


Transformer 2: 15MVA, 6.9Δ - 115Y KV, X=10%

Transformer 3: Single phase units each rated 10MVA, 6.9/6.9KV, X=10%.

Draw an impedance diagram. Choosing a base 30MVA, 6.6KV in G1 circuit

LECTURE NOTES PAPER

Soln:-

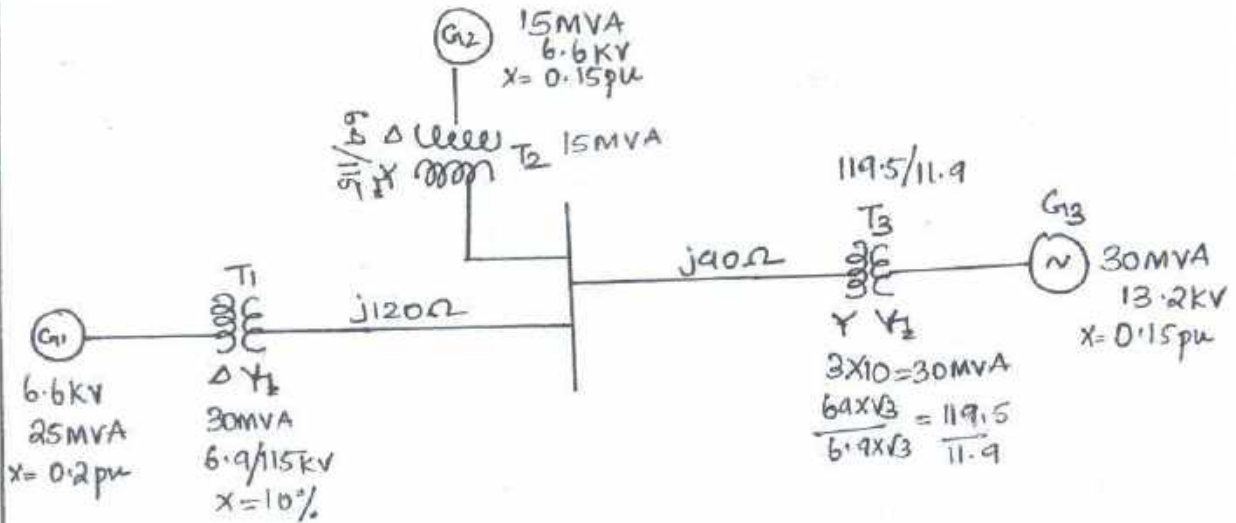

$MVA_{b \text{ new}} = 30 \text{ MVA}$

$KV_{b \text{ new}} = 6.6 \text{ KV}$

Impedance of  $G_1$

$$Z_{pu \text{ new}} = Z_{pu \text{ old}} \times \left( \frac{KV_{b \text{ old}}}{KV_{b \text{ new}}} \right)^2 \left( \frac{MVA_{b \text{ new}}}{MVA_{b \text{ old}}} \right)$$

$$Z_{pu \text{ new } G_1} = j0.2 \times \left( \frac{6.6}{6.6} \right)^2 \times \left( \frac{30}{25} \right)$$

$Z_{pu \text{ new } G_1} = j0.24 \text{ pu}$

$KV_{b \text{ new}} = 6.6 \text{ KV}$

$KV_{b \text{ old}} = 6.6 \text{ KV}$

$MVA_{b \text{ old}} = 25 \text{ MVA}$

$MVA_{b \text{ new}} = 30 \text{ MVA}$

$Z_{pu \text{ old}} = j0.2 \text{ pu}$

Impedance of  $T_1$  referred to Secondary

$$KV_{b \text{ new on HT side of } T_1} = KV_{b \text{ new on LT of } T_1} \times \frac{HT \text{ rating}}{LT \text{ rating}}$$

$$= 6.6 \times \frac{115}{6.9} = 110 \text{ KV}$$

now  $KV_{b \text{ new}} = 110 \text{ KV}$  ;  $KV_{b \text{ old}} = 115 \text{ KV}$

$MVA_{b \text{ new}} = 30 \text{ MVA}$  ;  $MVA_{b \text{ old}} = 30 \text{ MVA}$

$$Z_{pu \text{ old}} = \frac{10}{100} = j0.1 \text{ pu}$$



## LECTURE NOTES PAPER

$$Z_{pu \text{ new } T_1} = j0.1 \times \left(\frac{115}{110}\right)^2 \times \left(\frac{30}{30}\right)$$

$$Z_{pu \text{ new of } T_1} = j0.1092 \text{ pu}$$

Impedance of line 1 (j120  $\Omega$  line)

$$KV_{b \text{ new}} = 110 \text{ KV}$$

$$MVA_{b \text{ new}} = 30 \text{ MVA}$$

$$\text{Base impedance } Z_b = \frac{(KV_{b \text{ new}})^2}{MVA_{b \text{ new}}} = \frac{(110)^2}{30} = 403.33 \Omega$$

$$\text{Actual value} = j120 \Omega$$

$$Z_{pu \text{ of line 1}} = \frac{\text{Actual value}}{\text{Base value}} = \frac{j120}{403.33}$$

$$Z_{pu \text{ new of line 1}} = j0.297 \text{ pu}$$

Impedance of line 2 (j90  $\Omega$  line)

$$KV_{b \text{ new}} = 110 \text{ KV}$$

$$MVA_{b \text{ new}} = 30 \text{ MVA}$$

$$Z_b = \frac{(110)^2}{30} = 403.33 \Omega$$

$$\text{Actual value} = j90 \Omega$$

$$Z_{pu \text{ new of line 2}} = \frac{j90}{403.33}$$

$$Z_{pu \text{ new of line 2}} = j0.2231 \text{ pu}$$

Impedance of  $T_2$

$$KV_{b \text{ new}} = 110 \text{ KV} ; KV_{b \text{ old}} = 115 \text{ KV}$$

$$MVA_{b \text{ new}} = 30 \text{ MVA} ; MVA_{b \text{ old}} = 15 \text{ MVA}$$

$$Z_{pu \text{ old}} = \frac{10}{100} = j0.1 \text{ pu}$$

LECTURE NOTES PAPER

$$Z_{pu \text{ new of } T_2} = j0.1 \times \left(\frac{115}{110}\right)^2 \times \left(\frac{30}{15}\right)$$

$$Z_{pu \text{ new of } T_2} = j0.2185 \text{ pu}$$

Impedance of G12

$$KV_{b \text{ new on LT side of } T_2} = KV_{b \text{ new HT side of } T_2} \times \frac{LT \text{ rating}}{HT \text{ rating}}$$

$$= 110 \times \frac{6.9}{115} = 6.6 \text{ KV}$$

now  $KV_{b \text{ new}} = 6.6 \text{ KV}$

$KV_{b \text{ old}} = 6.6 \text{ KV}$

$MVA_{b \text{ old}} = 15 \text{ MVA}$

$MVA_{b \text{ new}} = 30 \text{ MVA}$

$Z_{pu \text{ old}} = j0.15 \text{ pu}$

$$Z_{pu \text{ new of } G_{12}} = j0.15 \times \left(\frac{6.6}{6.6}\right)^2 \times \left(\frac{30}{15}\right)$$

$$Z_{pu \text{ new of } G_{12}} = j0.3 \text{ pu}$$

Impedance of T3 referred to secondary

since it is formed 3, 1ϕ transformer, voltage rating of 3ϕ transformer

$$= \frac{\sqrt{3} \times 6.9}{\sqrt{3} \times 6.9} = 11.95 / 11.9 \text{ KV}$$

MVA rating of 3ϕ transformer = 3 × 10 = 30 MVA

$$KV_{b \text{ new on LT side of } T_3} = KV_{b \text{ new on HT side}} \times \frac{LT \text{ rating}}{HT \text{ rating}}$$

$$= 110 \times \frac{11.9}{119.5} = 10.9 \approx 11 \text{ KV}$$

now  $KV_{b \text{ new}} = 11 \text{ KV}$  ;  $MVA_{b \text{ new}} = 30 \text{ MVA}$

$KV_{b \text{ old}} = 11.9 \text{ KV}$  ;  $MVA_{b \text{ old}} = 30 \text{ MVA}$

$$Z_{pu\ old} = \frac{10}{100} = j0.1\ pu$$

$$Z_{pu\ new\ of\ T_3} = j0.1 \times \left(\frac{11.9}{11}\right)^2 \times \left(\frac{30}{30}\right)$$

$$Z_{pu\ new\ of\ T_3} = j0.117\ pu$$

Impedance of  $G_{13}$

$$KV_{b\ old} = 13.2\ KV; \quad KV_{b\ new} = 11\ KV$$


$$MVA_{b\ old} = 30\ MVA; \quad MVA_{b\ new} = 30\ MVA$$

$$Z_{pu\ old} = j0.15\ pu$$


$$Z_{pu\ new\ of\ G_{13}} = j0.15 \times \left(\frac{13.2}{11}\right)^2 \times \left(\frac{30}{30}\right)$$

$$Z_{pu\ new\ of\ G_{13}} = j0.216\ pu$$


Impedance Diagrams :-

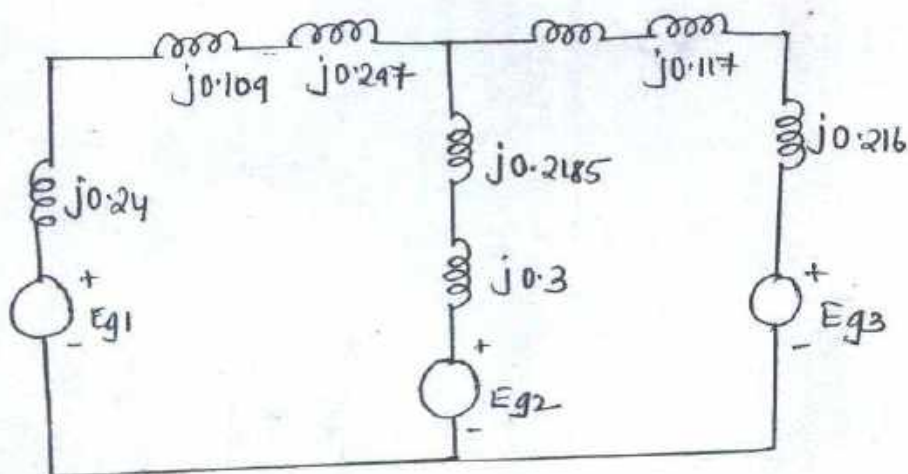

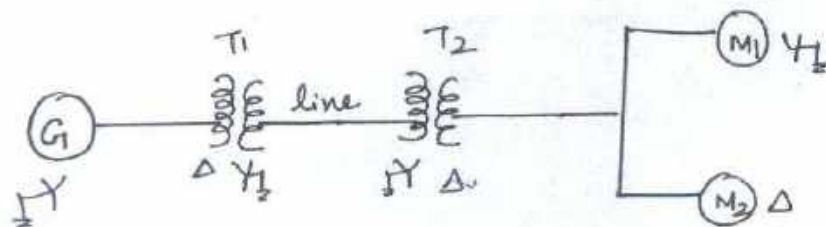5) A 90MVA 11KV 3 phase generator has a reactance of 25%. The generator supplies two motors through transformer and transmission line as shown in fig. The transformer T<sub>1</sub> is a 3 phase transformer, 100MVA, 10/132KV, 6% reactance. The transformer T<sub>2</sub> is composed of 3 single phase units each rated 300MVA, 66/10KV with 5% reactance. The connection of T<sub>1</sub> and T<sub>2</sub> are shown. The motors are rated at 50MVA and 400MVA both 10KV and 20% reactance. Taking the generator rating as base, draw reactance diagram & indicate the reactance in p.u. The reactance of line is 100Ω (Nov/Dec 2013)



Soln:-

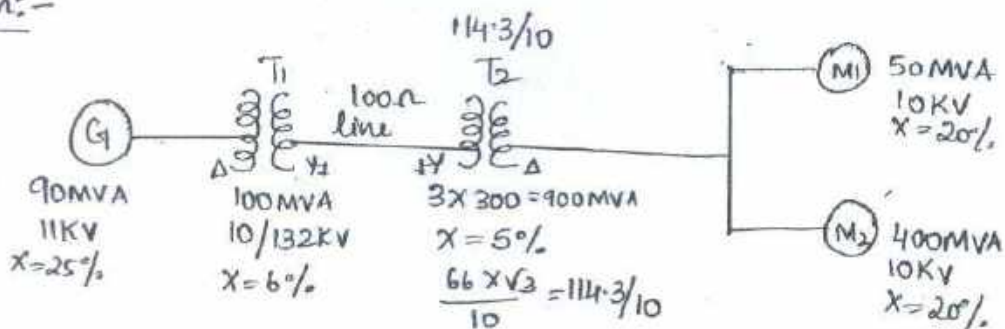

$$KV_b \text{ new} = 11KV$$

$$MVA_b \text{ new} = 90MVA$$



LECTURE NOTES PAPER

Reactance of G1

$$KV_{bnew} = 11KV; KV_{bold} = 11KV; MVA_{bnew} = 90MVA$$

$$MVA_{bold} = 90MV$$

$$X_{pu old} = \frac{25}{100} = j0.25pu$$

$$X_{pu new of G1} = j0.25 \times \left(\frac{11}{11}\right)^2 \times \left(\frac{90}{90}\right)$$

$$\boxed{X_{pu new of G1} = j0.25pu}$$

Reactance of T1 referred to primary

$$KV_{bnew} = 11KV; KV_{bold} = 10KV; MVA_{bold} = 100MVA; MVA_{bnew} = 90MVA$$

$$X_{pu old} = \frac{6}{100} = j0.06pu$$

$$X_{pu new of T1} = j0.06 \times \left(\frac{10}{11}\right)^2 \times \left(\frac{90}{100}\right)$$

$$\boxed{X_{pu new of T1} = j0.0446pu}$$

Reactance of line (100Ω line)

$$KV_{bnew \text{ on HT side of } T1} = KV_{bnew \text{ on LT side of } T1} \times \frac{HT \text{ rating}}{LT \text{ rating}}$$

$$= 11 \times \frac{132}{10} = 145.2KV$$

$$\text{now } KV_{bnew} = 145.2KV$$

$$\text{Base reactance } X_b = \frac{(KV_{bnew})^2}{MVA_{bnew}}$$

$$= \frac{(145.2)^2}{90} = 234.25\Omega$$

LECTURE NOTES PAPER

Actual value = 100 Ω

$$X_{pu} \text{ of line} = \frac{\text{Actual value}}{\text{Base value}} = \frac{100}{234.25}$$

$$X_{pu \text{ new of line}} = j0.426 \text{ pu}$$

Reactance of T<sub>2</sub> referred to secondary

Since T<sub>2</sub> is formed by 3, 1ϕ transformers.

$$\text{voltage rating of } T_2 = \frac{66 \times \sqrt{3}}{10} = 114.3/10$$

$$\text{MVA rating of } 3 \phi \text{ transformer} = 3 \times 300 = 900 \text{ MVA}$$

$$\begin{aligned} KV_{b \text{ new on LT of } T_2} &= KV_{b \text{ new on HT side}} \times \frac{\text{LT rating}}{\text{HT rating}} \\ &= 145.2 \times \frac{10}{114.3} = 12.7 \text{ KV} \end{aligned}$$

$$\text{now } KV_{b \text{ new}} = 12.7 \text{ KV}$$

$$KV_{b \text{ old}} = 10 \text{ KV}$$

$$X_{pu \text{ old}} = \frac{5}{100} = j0.05 \text{ pu}$$

$$KV_{A_b \text{ new}} = 90 \text{ MVA}$$

$$MVA_{b \text{ old}} = 900 \text{ MVA}$$

$$X_{pu \text{ new of } T_2} = j0.05 \times \left(\frac{10}{12.7}\right)^2 \times \left(\frac{900}{90}\right)$$

$$X_{pu \text{ new of } T_2} = j0.0031 \text{ pu}$$

Reactance of M<sub>1</sub>

$$KV_{b \text{ new}} = 12.7 \text{ KV}; KV_{b \text{ old}} = 10 \text{ KV}$$

$$MVA_{b \text{ new}} = 90 \text{ MVA}; MVA_{b \text{ old}} = 50 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{20}{100} = j0.2 \text{ pu}$$

LECTURE NOTES PAPER

$$X_{pu \text{ new of } M_1} = j0.2 \times \left(\frac{10}{12.7}\right)^2 \times \left(\frac{90}{50}\right)$$

$$X_{pu \text{ new of } M_1} = j0.223 \text{ pu}$$

Reactance of  $M_2$ :-

$$KV_{b \text{ new}} = 12.7 \text{ kV}; \quad KV_{b \text{ old}} = 10 \text{ kV}$$


$$MVA_{b \text{ new}} = 90 \text{ MVA}; \quad MVA_{b \text{ old}} = 400 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{20}{100} = j0.2 \text{ pu}$$

$$X_{pu \text{ new of } M_2} = j0.2 \times \left(\frac{10}{12.7}\right)^2 \times \left(\frac{90}{400}\right)$$

$$X_{pu \text{ new of } M_2} = j0.027 \text{ pu}$$

Reactance Diagram:-

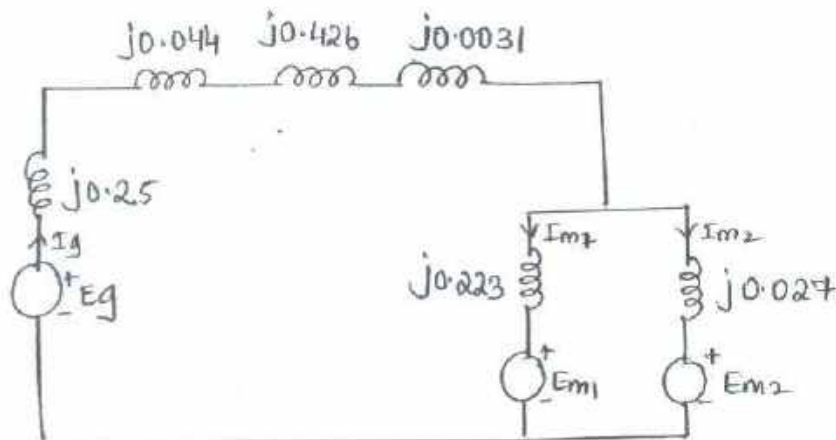



LECTURE NOTES PAPER

6. Prepare a per phase schematic of the system shown in figure showing all the impedance in perunit on a 100MVA, 132 kV base in the transmission line circuit. The necessary data are given as follows,


$G_1$ : 50MVA, 12.2KV,  $X=0.15pu$

$G_2$ : 20MVA, 13.8KV,  $X=0.15pu$


$T_1$ : 80MVA, 12.2/161KV,  $X=0.1pu$

$T_2$ : 40MVA, 13.8/161KV,  $X=0.1pu$

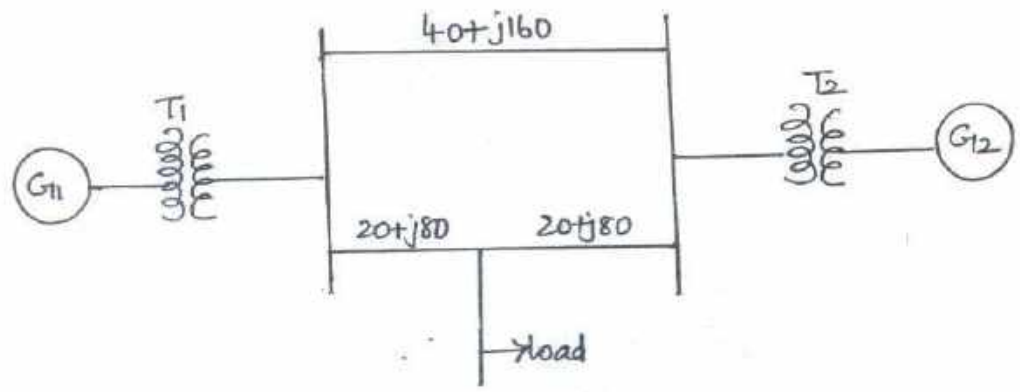Load: 50MVA, 0.8 pf lag operating at 154KV. Determine the pu impedance of the load. (May/June 2009)



Soln:-

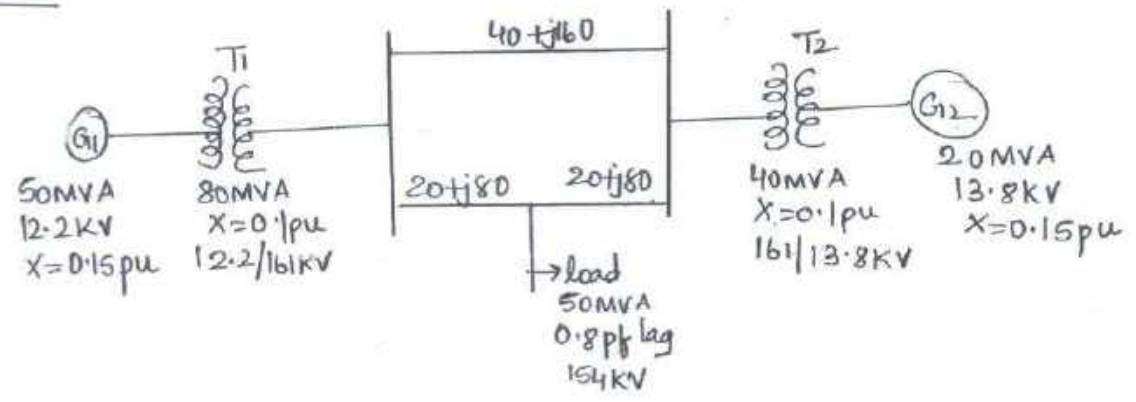

LECTURE NOTES PAPER

$$MVA_{bnew} = 100 \text{ MVA} ; KV_{bnew} = 132 \text{ KV (on transmission line)}$$

Impedance of (40+j160) transmission line

$$KV_{bnew} = 132 \text{ KV}$$

$$MVA_{bnew} = 100 \text{ MVA}$$

$$\text{Base impedance} = \frac{(KV_{bnew})^2}{MVA_{bnew}} = \frac{(132)^2}{100} = 174.24 \Omega$$

$$\text{Actual value} = 40 + j160 \Omega$$

$$Z_{pu \text{ new of transmission line}} = \frac{\text{Actual value}}{\text{Base value}} = \frac{40 + j160}{174.24}$$

$$Z_{pu \text{ of } (20 + j80) \text{ line}} = 0.229 + j0.918 \text{ pu}$$

Impedance of (20+j80) a transmission line

$$KV_{bnew} = 132 \text{ KV} ; MVA_{bnew} = 100 \text{ MVA}$$

$$\text{Base impedance} = 174.24 \Omega$$

$$\text{Actual value} = 20 + j80 \Omega$$

$$Z_{pu \text{ of } (20 + j80) \text{ a line}} = \frac{(20 + j80)}{174.24}$$

$$Z_{pu \text{ of } (20 + j80) \text{ a line}} = 0.1147 + j0.459 \text{ pu}$$

Impedance of load

$$MVA = 50 \text{ MVA} = S$$

$$P_f = \cos \phi = 0.8 \Rightarrow \phi = \cos^{-1}(0.8) = 36.86^\circ$$

$$V_L = 154 \text{ KV}$$

$$S_L(3\phi) = S \angle \phi = 50 \angle 36.87^\circ \quad S_L^* = 50 \angle -36.87^\circ$$

$$\text{Base impedance} = \frac{KV_{bnew}^2}{MVA_{bnew}} = \frac{(132)^2}{100} = 174.24 \Omega$$

## LECTURE NOTES PAPER

$$Z_L = \frac{V_{LL}^2}{S_L^*} = \frac{154^2}{50 \angle -36.87^\circ} = 474.32 \angle 36.87^\circ \Omega$$

$$= 379.45 + j284.59$$

$$Z_{pu} \text{ of load} = \frac{\text{Actual value}}{\text{Base impedance}} = \frac{Z_L}{Z_b}$$

$$= \frac{379.45 + j284.59}{174.24}$$

$$Z_{pu} \text{ of load} = 2.177 + j1.633 \text{ pu}$$

Impedance of  $T_1$  (referred to primary)

$$KV_{b \text{ new}} \text{ on LT side of } T_1 = KV_{b \text{ new}} \text{ on HT side} \times \frac{\text{LT voltage rating}}{\text{HT voltage rating}}$$

$$= 132 \times \frac{12.2}{161} = 10 \text{ KV}$$

$$\text{hence } KV_{b \text{ new}} = 10 \text{ KV}$$

$$KV_{b \text{ old}} = 12.2 \text{ KV}$$

$$MVA_{b \text{ new}} = 100 \text{ MVA}$$

$$MVA_{b \text{ old}} = 80 \text{ MVA}$$

$$\therefore Z_{pu \text{ old}} = j0.1 \text{ pu}$$

$$Z_{pu \text{ new}} \text{ of } T_1 = Z_{pu \text{ old}} \times \left( \frac{KV_{b \text{ old}}}{KV_{b \text{ new}}} \right)^2 \times \left( \frac{MVA_{b \text{ new}}}{MVA_{b \text{ old}}} \right)$$

$$= j0.1 \times \left( \frac{12.2}{10} \right)^2 \times \left( \frac{100}{80} \right)$$

$$Z_{pu \text{ new}} \text{ of } T_1 = j0.186 \text{ pu}$$

Impedance of G11

$$KV_{b\text{new}} = 10KV$$

$$KV_{b\text{old}} = 12.2KV$$

$$MVA_{b\text{old}} = 50MVA$$

$$MVA_{b\text{new}} = 100MVA$$

$$Z_{pu\text{old}} = j0.15pu$$

$$Z_{pu\text{new of G11}} = j0.15 \times \left(\frac{12.2}{10}\right)^2 \times \left(\frac{100}{50}\right)$$

$$Z_{pu\text{new of G11}} = j0.446pu$$

Impedance of T2 referred to secondary

$$KV_{b\text{new}} \text{ on LT side of } T_2 = KV_{b\text{new}} \text{ on HT side of } T_2 \times \frac{L\text{rating}}{H\text{rating}}$$

$$= 132 \times \frac{13.8}{161} = 11.31KV$$

$$\text{now } KV_{b\text{new}} = 11.31KV$$

$$KV_{b\text{old}} = 13.8KV; MVA_{b\text{new}} = 100MVA; MVA_{b\text{old}} = 40MVA$$

$$Z_{pu\text{old}} = j0.1pu$$

$$Z_{pu\text{new of } T_2} = j0.1 \times \left(\frac{13.8}{11.31}\right)^2 \times \left(\frac{100}{40}\right)$$

$$Z_{pu\text{new of } T_2} = j0.372pu$$

Impedance of G12

$$KV_{b\text{new}} = 11.31KV; KV_{b\text{old}} = 13.8KV$$

$$MVA_{b\text{old}} = 20MVA; MVA_{b\text{new}} = 100MVA$$


$$Z_{pu\text{old}} = j0.15pu$$

$$Z_{pu\text{new of } G12} = j0.15 \times \left(\frac{13.8}{11.31}\right)^2 \times \left(\frac{100}{20}\right)$$


$$Z_{pu\text{new of } G12} = j1.118pu$$



Impedance Diagram

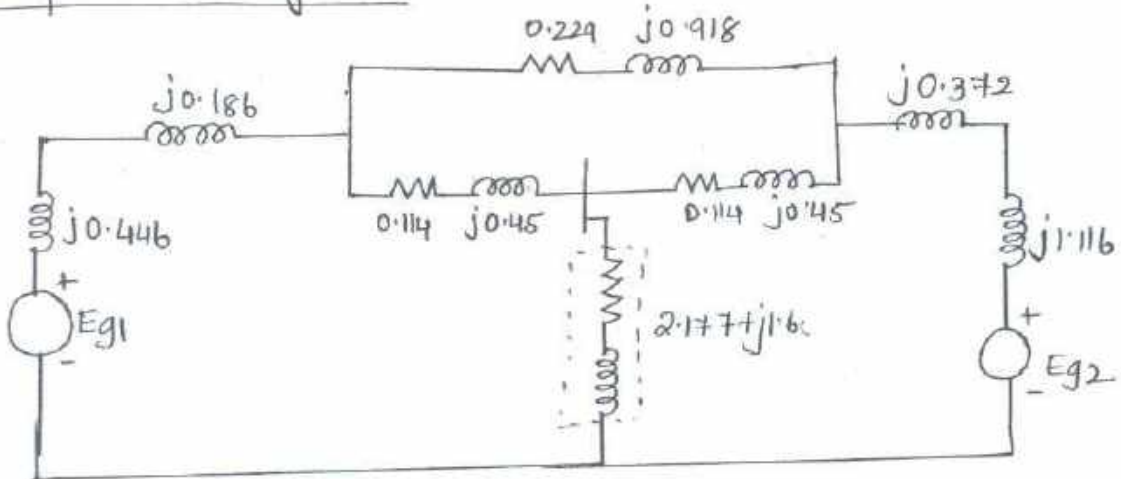

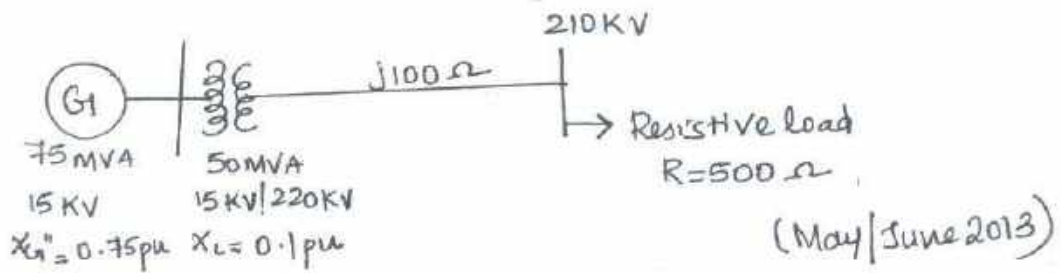7. For the system shown in figure (a) determine the generator voltage. Take a base of 100MVA and 210KV in the transmission line.



Soln:-

$$MVA_{b\text{new}} = 100 \text{ MVA}$$

$$KV_{b\text{new}} = 210 \text{ KV (on transmission line)}$$

Impedance of transmission line

$$Z_{\text{actual}} = j100 \text{ } \Omega$$

$$\text{Base impedance} = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(210)^2}{100} = 441 \text{ } \Omega$$

$$Z_{pu} \text{ of transmission line} = \frac{Z_{\text{actual}}}{Z_{\text{base}}} = \frac{j100}{441}$$

$$Z_{pu} \text{ of line} = j0.226 \text{ pu}$$

LECTURE NOTES PAPER

Impedance of transformer (referred to primary)

$$KV_{b \text{ new on LT side of T}} = KV_{b \text{ new on HT of T}} \times \frac{\text{LT voltage rating}}{\text{HT voltage rating}}$$

$$= 210 \times \frac{15}{220} = 14.318 \text{ KV}$$

Now  $KV_{b \text{ new}} = 14.318 \text{ KV}$

$KV_{b \text{ old}} = 15 \text{ KV}$

$MVA_{b \text{ new}} = 100 \text{ MVA}$

$MVA_{b \text{ old}} = 50 \text{ MVA}$

$Z_{p \text{ old}} = j0.1 \text{ pu}$

$Z_{p \text{ new of T}} = j0.1 \times \left(\frac{15}{14.3}\right)^2 \times \left(\frac{100}{50}\right)$

$Z_{p \text{ new of T}} = j0.220 \text{ pu}$

Impedance of Generator

$KV_{b \text{ new}} = 14.31$

$MVA_{b \text{ new}} = 100 \text{ MVA}$

$KV_{b \text{ old}} = 15 \text{ KV}$

$MVA_{b \text{ old}} = 75 \text{ MVA}$

$Z_{p \text{ old}} = j0.75 \text{ pu}$

$Z_{p \text{ new of G}} = j0.75 \times \left(\frac{15}{14.31}\right)^2 \times \left(\frac{100}{75}\right)$

$Z_{p \text{ new of G}} = j1.098 \text{ pu}$

Impedance of load:-

$KV_{b \text{ new}} = 210 \text{ KV}$      $MVA_{b \text{ new}} = 100 \text{ MVA}$


$Z_b = \frac{(KV_{b \text{ new}})^2}{MVA_{b \text{ new}}} = \frac{(210)^2}{100} = 441 \Omega$

$Z_{\text{actual}} = 500 \Omega$

$Z_{\text{pu of R load}} = \frac{500}{441}$

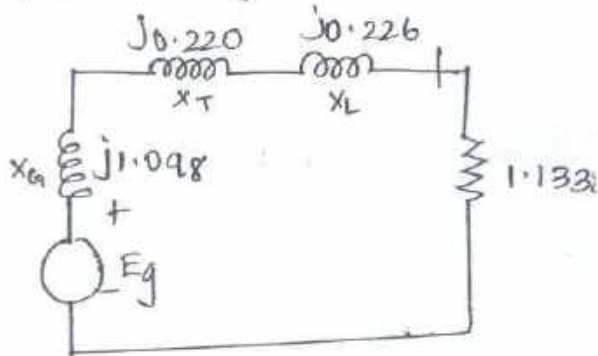$\Rightarrow Z_{\text{pu of R load}} = 1.133 \text{ pu}$



Impedance diagrams:-

At the load bus

$$V_{pu} = 1 \text{ pu}$$

$$R_{pu} = 1.1338$$

$$\therefore I_{pu} = \frac{V_{pu}}{R_{pu}} = \frac{1}{1.133} = 0.882 \text{ pu}$$

Let  $I_{pu}$  taken as the reference phasor

$$I_{pu} = 0.882 \angle 0^\circ = 0.882 + j0$$

By KVL, the voltage drop in the network

$$V_{pu} = I_{pu} [R_{pu} + j(X_G + X_T + X_L)]$$

$$= 0.882 [1.133 + j(1.098 + 0.220 + 0.226)]$$

$$= 0.882 [1.133 + j1.544]$$

$$= 0.882 \times 1.915 \angle 53.72^\circ$$

$$V_{pu} = 1.689 \text{ pu}$$

Actual generator terminal voltage,

$$V_{G1} = V_{pu} \times \text{Base KV at generator terminals}$$


$$V_{G1} = V_{pu} \times \text{KV}_{base} \text{ at generator}$$

$$= 1.689 \times 14.31$$

$$V_{G1} = 24.16 \text{ KV}$$

LECTURE NOTES PAPER

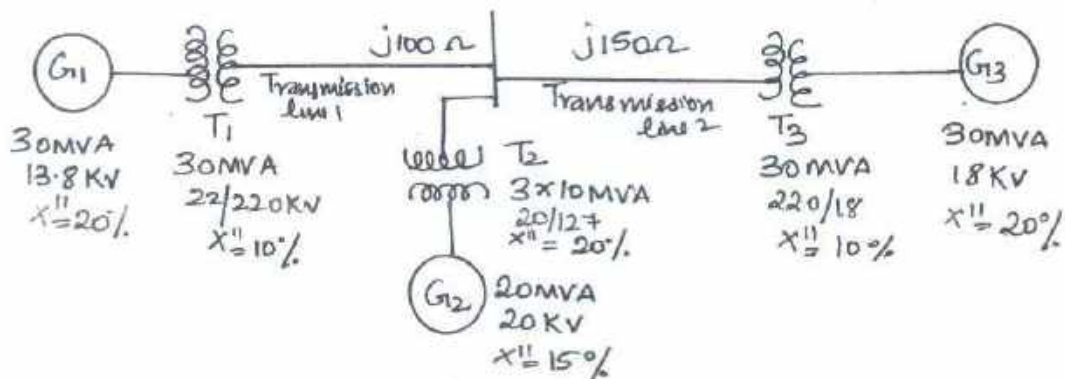8. The single line diagram of a power system is shown in fig along with the components data. Determine the new per unit value and draw the reactance diagram. Assume 25MVA and 20KV as new base on generator G<sub>1</sub>.



Soln:-

$$KV_{bnew} = 20KV$$

$$MVA_{bnew} = 25MVA$$

Reactance of G<sub>1</sub>

$$KV_{bnew} = 20KV$$

$$KV_{bold} = 13.8KV$$

$$MVA_{bold} = 30MVA$$

$$MVA_{bnew} = 25MVA$$

$$X_{pu old} = \frac{20}{100} = j0.2 pu$$

$$X_{pu new of G1} = X_{pu old} \times \left( \frac{KV_{bold}}{KV_{bnew}} \right)^2 \times \left( \frac{MVA_{bnew}}{MVA_{bold}} \right)$$

$$= j0.2 \times \left( \frac{13.8}{20} \right)^2 \times \left( \frac{25}{30} \right)$$

$$X_{pu new of G1} = j0.0793 pu$$

## LECTURE NOTES PAPER

Reactance of  $T_1$  referred to secondary

$$KV_{b \text{ new}} \text{ on HT side of } T_1 = KV_{b \text{ new}} \text{ on LT side of } T_1 \times \frac{\text{HT rating}}{\text{LT rating}}$$

$$= 20 \times \frac{220}{22} = 200 \text{ KV}$$

$$\text{Now } KV_{b \text{ new}} = 200 \text{ KV}$$

$$KV_{b \text{ old}} = 220 \text{ KV}$$

$$MVA_{b \text{ old}} = 30 \text{ MVA}$$

$$MVA_{b \text{ new}} = 25 \text{ MVA}$$

$$X_{p \text{ old}} = \frac{10}{100} = 0.1 \text{ pu}$$

$$X_{p \text{ new}} \text{ of } T_1 = 0.1 \times \left(\frac{220}{200}\right)^2 \times \left(\frac{25}{30}\right)$$

$$X_{p \text{ new}} \text{ of } T_1 = 0.1 \text{ pu}$$

Reactance of transmission line 1 :-

$$KV_{b \text{ new}} = 200 \text{ KV}$$

$$MVA_{b \text{ new}} = 25 \text{ MVA}$$

$$X_{\text{actual}} = j100 \Omega$$

$$\text{Base reactance } X_b = \frac{(KV_{b \text{ new}})^2}{MVA_{b \text{ new}}} = \frac{(200)^2}{25} = 1600 \Omega$$

$$X_{p \text{ u}} \text{ of line 1} = \frac{\text{Actual value}}{\text{Base value}} = \frac{X_{\text{actual}}}{X_b} = \frac{j100}{1600}$$

$$X_{p \text{ u}} \text{ of line 1} = 0.0625 \text{ pu}$$

Reactance of transmission line 2

$$KV_{b \text{ new}} = 200 \text{ KV}; MVA_{b \text{ new}} = 25 \text{ MVA}; X_{\text{actual}} = j150$$

$$X_b = \frac{(200)^2}{25} = 1600 \Omega$$

$$X_{p \text{ u}} \text{ of line 2} = \frac{j150}{1600}$$

$$X_{p \text{ u}} \text{ of line 2} = 0.09375 \text{ pu}$$

Reactance of T<sub>3</sub> referred to secondary

$$KV_{bnew} \text{ on LT side of } T_3 = KV_{bnew} \text{ on HT side of } T_3 \times \frac{L_{Trating}}{H_{Trating}}$$

$$= 200 \times \frac{18}{220} = 16.36 \text{ KV}$$

$$\text{new } KV_{bnew} = 16.36 \text{ KV}$$

$$KV_{bold} = 18 \text{ KV}$$

$$MVA_{bnew} = 25 \text{ MVA}$$

$$MVA_{bold} = 30 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{10}{100} = j0.10 \text{ pu}$$

$$X_{pu \text{ new of } T_3} = j0.1 \times \left(\frac{18}{16.36}\right)^2 \times \left(\frac{25}{30}\right)$$

$$X_{pu \text{ new of } T_3} = j0.1 \text{ pu}$$

Reactance of G<sub>3</sub>

$$KV_{bnew} = 16.36 \text{ KV}; KV_{bold} = 18 \text{ KV}$$

$$MVA_{bnew} = 25 \text{ MVA}; MVA_{bold} = 30 \text{ MVA}$$

$$X_{pu \text{ old}} = \frac{20}{100} = j0.2 \text{ pu}$$

$$X_{pu \text{ new of } G_3} = j0.2 \times \left(\frac{18}{16.36}\right)^2 \times \left(\frac{25}{30}\right)$$

$$X_{pu \text{ new of } G_3} = j0.2017 \text{ pu}$$

Reactance of T<sub>2</sub> referred to Secondary

Since it is formed by 3 single phase transformer

$$\text{voltage rating of 3 phase transformer} = \frac{12 \times \sqrt{3}}{20} = \frac{220}{20}$$

$$\text{MVA rating of 3 phase transformer} = 3 \times 10 = 30 \text{ MVA}$$

$$KV_{bnew} \text{ on LT side of } T_2 = KV_{bnew} \text{ on HT side} \times \frac{L_{Trating}}{H_{Trating}}$$

$$= 200 \times \frac{20}{220} = 18.18 \text{ KV}$$



LECTURE NOTES PAPER

new  $KV_{bnew} = 18.18 \text{ KV}$

$MVA_{bold} = 30 \text{ MVA}$

$MVA_{bnew} = 25 \text{ MVA}$

$KV_{bold} = 20 \text{ KV}$

$X_{puold} = \frac{20}{100} = j0.2 \text{ pu}$

$X_{pu\ new\ of\ T_2} = j0.2 \times \left(\frac{20}{18.18}\right)^2 \times \left(\frac{25}{30}\right)$

$X_{pu\ new\ of\ T_2} = j0.2017 \text{ pu}$

Reactance of  $G_2$

$KV_{bnew} = 18.18 \text{ KV}$      $MVA_{bnew} = 25 \text{ MVA}$


$KV_{bold} = 20 \text{ KV}$      $MVA_{bold} = 20 \text{ MVA}$

$X_{puold} = \frac{15}{100} = j0.15 \text{ pu}$

$X_{pu\ new\ of\ G_2} = j0.15 \times \left(\frac{20}{18.18}\right)^2 \times \left(\frac{25}{20}\right)$


$X_{pu\ new\ of\ G_2} = j0.226 \text{ pu}$

Reactance diagram

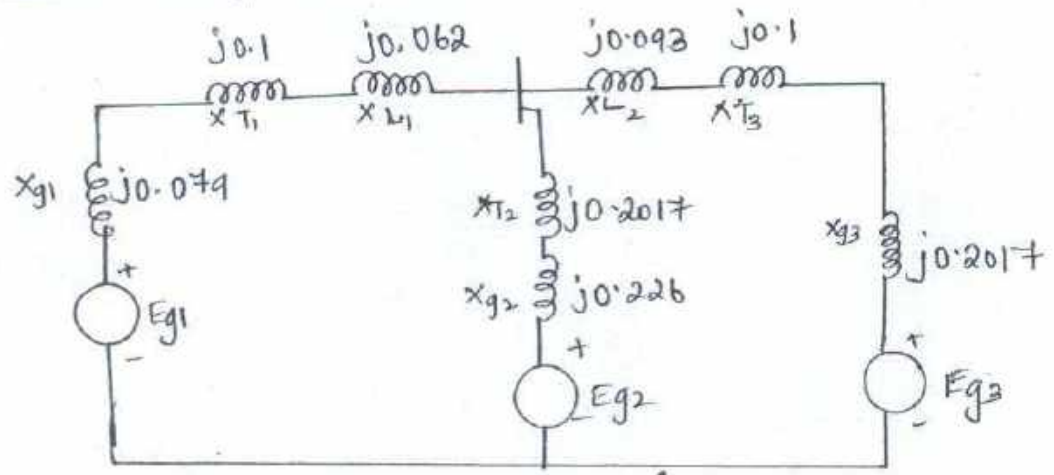

LECTURE NOTES PAPER

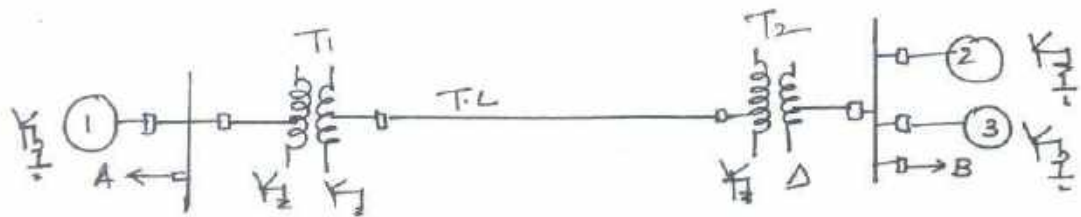9. Obtain per unit impedance diagram of the power system of fig shown below



Generator No 1 : 30 MVA, 10.5KV,  $X'' = 1.6$  ohms

Generator No 2 : 15 MVA, 6.6 KV,  $X'' = 1.2$  ohms

Generator No:3 : 25 MVA, 6.6 KV,  $X'' = 0.56$  ohms

Transformer  $T_1$  (3 phase) : 15 MVA, 33/11 KV,  $X = 15.2$  ohms per phase on high tension side

Transformer  $T_2$  (3 phase) : 15 MVA, 33/6.2 KV,  $X = 16$  ohms per phase on high tension side

Transmission line : 20.5 ohms/phase

load A : 15 MW, 11 KV, 0.9 lagging power factor

load B : 40 MW, 6.6 KV, 0.85 lagging power factor

Soln:-

High-tension of  $T_1$  and  $T_2$  is specified, so start from transmission line

$$MVA_{b, \text{new}} = 30 \text{ MVA} \quad (\text{high rating of machine})$$

$$KV_{b, \text{new}} = 10.5 \text{ KV}$$

Impedance of Generator

$$MVA_{b, \text{new}} = 30 \text{ MVA}$$

$$KV_{b, \text{new}} = 10.5 \text{ KV}$$

$$\text{Actual impedance} = 1.6 \text{ ohms}$$



LECTURE NOTES PAPER

$$\text{Base Impedance} = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(10.5)^2}{30} = 3.675 \Omega$$

$$Z_{pu\text{new}} = \frac{\text{Actual impedance}}{\text{Base impedance}}$$

$$Z_{pu\text{new of } G_1} = \frac{j1.6}{3.675}$$

$$Z_{pu\text{new of } G_1} = j0.435 \text{ pu}$$

Impedance of T<sub>1</sub> (referred to Secondary)

$$KV_{b\text{new on HT of } T_1} = KV_{b\text{new on LT of } T_1} \times \frac{HT\text{ rating}}{LT\text{ rating}}$$

$$= 10.5 \times \frac{33}{11} = 31.5 \text{ KV}$$

$$\text{now } KV_{b\text{new}} = 31.5 \text{ KV}$$

$$\text{Actual impedance of } T_1 \text{ on HT} = 15.2 \Omega/\text{ph}$$

$$\text{Base impedance} = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(31.5)^2}{30} = 33.07$$

$$Z_{pu \text{ of } T_1} = \frac{\text{Actual value}}{\text{Base value}} = \frac{j15.2}{33.07}$$

$$Z_{pu \text{ of } T_1} = j0.4595 \text{ pu}$$

Impedance of Transmission line

$$KV_{b\text{new}} = 31.5 \text{ KV}$$

$$MVA_{b\text{new}} = 30 \text{ MVA}$$

$$\text{Actual impedance} = 20.5 \Omega/\text{ph}$$

$$\text{Base impedance } Z_b = \frac{(31.5)^2}{30} = 33.07 \Omega$$

$$Z_{pu \text{ of T.L.}} = \frac{j20.5}{33.07}$$

$$Z_{pu \text{ of T.L.}} = j0.6198$$

## LECTURE NOTES PAPER

Impedance of  $T_2$  referred to primary

$$KV_{b\text{new}} = 31.5 \text{ KV}$$

$$MVA_{b\text{new}} = 30 \text{ MVA}$$

$$Z_{\text{actual on HT side}} = 16 \Omega/\text{ph}$$

$$Z_b = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{(31.5)^2}{30} = 33.07 \Omega$$

$$Z_{\text{pu of } T_2} = \frac{Z_{\text{actual}}}{Z_b} = \frac{j16}{33.07}$$

$$Z_{\text{pu of } T_2} = j0.4838 \text{ pu}$$

Impedance of  $G_{12}$ 

$$KV_{b\text{new on LT side of } T_2} = KV_{b\text{new on HT side of } T_2} \times \frac{LT \text{ rating}}{HT \text{ rating}}$$

$$= 31.5 \times \frac{6.2}{33} = 6 \text{ KV}$$

$$\text{now } KV_{b\text{new}} = 6 \text{ KV}$$

$$MVA_{b\text{new}} = 30 \text{ MVA}$$

$$Z_{\text{actual}} = 1.2 \Omega$$

$$Z_b = \frac{(KV_{b\text{new}})^2}{MVA_{b\text{new}}} = \frac{6^2}{30} = 1.2 \Omega$$

$$Z_{\text{pu of } G_{12}} = \frac{Z_{\text{actual}}}{Z_b} = \frac{j1.2}{1.2} = j1 \text{ pu}$$

$$Z_{\text{pu of } G_{12}} = j1 \text{ pu}$$

## LECTURE NOTES PAPER

Impedance of G3

$$KV_{bnew} = 6KV$$

$$MVA_{bnew} = 30MVA$$

$$Z_{actual} = 0.56 \Omega$$

$$\text{Base impedance } Z_b = \frac{(KV_{bnew})^2}{MVA_{bnew}} = \frac{6^2}{30} = 1.2 \Omega$$

$$Z_{pu} \text{ of } G3 = \frac{Z_{actual}}{Z_b} = \frac{j0.56}{1.2} = j0.466 pu$$

$$\boxed{Z_{pu} \text{ of } G3 = j0.466 pu}$$

Impedance of load A

$$KV_{bnew} = 10.5KV$$

$$MVA_{bnew} = 30MVA$$

$$P_L = 15MW$$

$$\cos \phi = 0.9 \quad \phi = \cos^{-1}(0.9) = 25.84$$

$$P_L = S \cos \phi$$

$$S = \frac{P_L}{\cos \phi} \quad \text{--- (1)}$$

$$Q_L = S \sin \phi$$

$$S = \frac{Q_L}{\sin \phi} \quad \text{--- (2)}$$

from (1) & (2)

$$\frac{P_L}{\cos \phi} = \frac{Q_L}{\sin \phi}$$

$$Q_L = \frac{P_L \times \sin \phi}{\cos \phi} = \frac{P_L \times \sin(25.84)}{0.8}$$

$$= \frac{15 \times \sin(25.84)}{0.8}$$

$$Q_L = 8.17 MVar$$

LECTURE NOTES PAPER

$$Z_L = \frac{V_L^2}{P_L - jQ_L} = \frac{11^2}{15 - j8.17} = 6.22 + j3.388$$

$$Z_b = \frac{KV_{b\text{new}}^2}{MVA_{b\text{new}}} = \frac{(10.5)^2}{30} = 3.675$$

$$Z_{pu \text{ of load A}} = \frac{Z_L}{Z_b} = \frac{6.22 + j3.338}{3.675}$$

$$Z_{pu \text{ of load A}} = 1.69 + j0.90 \text{ pu}$$

Impedance of load B.

$$KV_{b\text{new}} = 6 \text{KV} \quad MVA_{b\text{new}} = 30$$

$$Z_b = \frac{6^2}{30} = 1.2$$

$$Z_L = \frac{V_L^2}{P_L - jQ_L}$$

$$P_L = 40 \text{MW} \quad \cos \phi = 0.85 \Rightarrow \phi = \cos^{-1}(0.85) = 31.7$$


$$Q_L = \frac{P_L \times \sin \phi}{\cos \phi} = \frac{40 \times \sin(31.7)}{0.85} = 24.72 \text{MVAr}$$

$$Z_L = \frac{(6.6)^2}{40 - j24.72} = 0.788 + j0.487$$

$$Z_{pu \text{ of load B}} = \frac{Z_L}{Z_b} = \frac{0.788 + j0.487}{1.2}$$

$$Z_{pu \text{ of load B}} = 0.656 + j0.405 \text{ pu}$$

Impedance Diagram

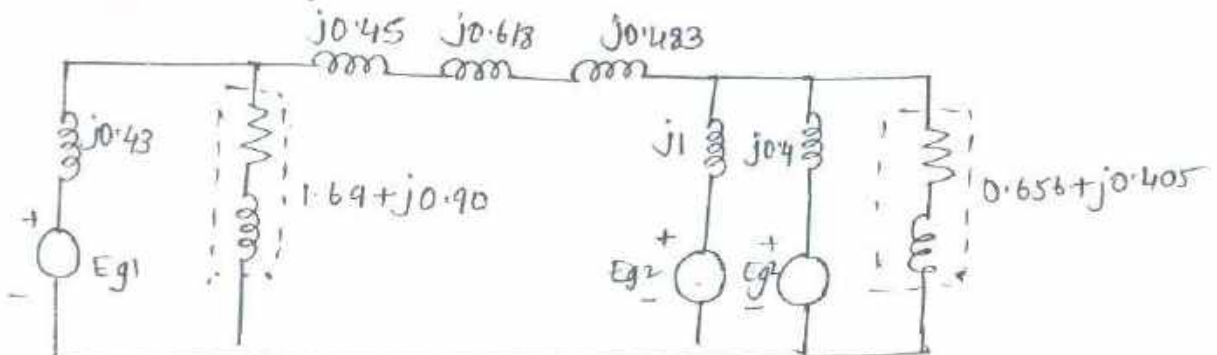



## LECTURE NOTES PAPER

- 10) The subtransient reactance of a 500MVA, 18 KV generator is 0.25 pu on its ratings. It is connected to a network through a 20/400 KV transformer. Find out the subtransient reactance of a generator on a base of 100MVA and 20KV  
(April/May 2010)


Soln:-

$$\text{given } KV_{b\text{old}} = 18 \text{ KV} \quad KV_{b\text{new}} = 20 \text{ KV}$$

$$MVA_{b\text{old}} = 500 \text{ MVA}, \quad MVA_{b\text{new}} = 100 \text{ MVA}$$

$$X_{pu\text{old}} = j0.25 \text{ pu}$$
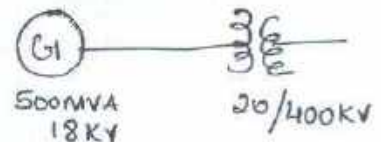
$$X_{pu\text{new}} = X_{pu\text{old}} \times \left( \frac{KV_{b\text{old}}}{KV_{b\text{new}}} \right)^2 \times \left( \frac{MVA_{b\text{new}}}{MVA_{b\text{old}}} \right)$$



$$X_{pu\text{new of } G1} = j0.25 \times \left( \frac{18}{20} \right)^2 \times \left( \frac{100}{500} \right)$$

$$\boxed{X_{pu\text{ of } G1} = j0.0405}$$

- 11) A three phase,  $\Delta$ -Y transformer with rating 100KVA, 11KV/400V has its primary and secondary leakage reactance as 12  $\Omega$ /phase and 0.05  $\Omega$ /phase respectively. Calculate the p.u reactance of transformer  
(Nov/Dec 2011)

Soln(i) The HV side (primary) rating are chosen as base values

$$KV_{b1} = 11 \text{ KV}$$

$$KVA_{b1} = 100 \text{ KVA}$$

$$\text{Base reactance } X_b = \frac{(KV_{b1})^2}{MVA_{b1}} = \frac{(11)^2}{100 \times 10^3} = 1210 \Omega$$

## LECTURE NOTES PAPER

transformer line voltage ratio  $K = \frac{KV_{b2}}{KV_{b1}} = \frac{400}{11000} = 0.0364$

total leakage reactance referred to primary  $\left\{ \begin{aligned} X_{01} &= X_1 + X_2' = X_1 + \frac{X_2}{K^2} \\ &= 12 + \frac{0.05}{(0.0364)^2} \\ X_{01} &= 49.737 \text{ } \Omega/\text{phase} \end{aligned} \right.$

$$X_{pu} = \frac{\text{Total leakage reactance}}{\text{Base reactance}} = \frac{X_{01}}{X_b}$$

$$X_{pu} = \frac{49.737}{1210} \Rightarrow \boxed{X_{pu} = 0.0411 \text{ pu}}$$

Case (ii) The LV side (secondary) rating are chose as base values

$$KV_{b2} = 400 \text{ V} = 0.4 \text{ KV}$$

$$KVA_{b2} = 100 \text{ KVA}$$

$$\text{Base reactance } X_b = \frac{(KV_{b2})^2}{\text{MVA}_{b2}} = \frac{(0.4)^2}{100 \times 10^3} = 1.6 \Omega$$

$$K = 0.0364$$

total leakage reactance referred to secondary  $\left\{ \begin{aligned} X_{02} &= X_1' + X_2 = X_1 K^2 + X_2 \\ &= (0.0364)^2 \times 12 + 0.05 \\ &= 0.0659 \text{ } \Omega/\text{phase} \end{aligned} \right.$

$$X_{pu} = \frac{\text{total leakage reactance}}{\text{Base reactance}} = \frac{X_{02}}{X_b}$$

$$= \frac{0.0659}{1.6}$$

$$\boxed{X_{pu} = 0.0411 \text{ pu}}$$



## LECTURE NOTES PAPER

- 12) Draw the p.u reactance diagram of a three winding transformer whose three phase ratings are primary (P), Wye grounded, 15 MVA, 66 KV; Secondary (S), wye-grounded, 10 MVA, 13.2 KV; tertiary (T), delta connected, 5 MVA, 2.3 KV. Mark the appropriate values of the impedances. The measured data for impedances are  $Z_{ps} = 7\%$  on 15 MVA & 66 KV;  $Z_{pt} = 9\%$  on 15 MVA and 66 KV;  $Z_{st} = 8\%$  on 10 MVA and 13.2 KV  
(April/May 2010)

Soln:-

$$\text{Choose } KV_b = 66 \text{ KV}$$

$$MVA_b = 15 \text{ MVA}$$

$$\text{pu value of } Z_{ps} = \frac{7}{100} = j0.07 \text{ pu}$$

$$\text{pu value of } Z_{pt} = \frac{9}{100} = j0.09 \text{ pu}$$

$$\text{pu value of } Z_{st} = \frac{8}{100} = j0.08 \text{ pu}$$

The pu value of  $Z_{st}$  on a base of 10 MVA, 13.2 KV can be change to base of 15 MVA, 66 KV by using

$$Z_{pu, \text{new}} = Z_{pu, \text{old}} \times \left( \frac{KV_{\text{bold}}}{KV_{\text{bnew}}} \right)^2 \times \left( \frac{MVA_{\text{bnew}}}{MVA_{\text{bold}}} \right)$$

$$KV_{\text{bnew}} = 13.2 \times \frac{66}{13.2} = 66 \text{ KV}$$

$$Z_{st}^1 = Z_{st, \text{old}} \times \left( \frac{KV_{\text{bold}}}{KV_{\text{bnew}}} \right)^2 \times \left( \frac{MVA_{\text{bnew}}}{MVA_{\text{bold}}} \right)$$

$$= j0.08 \times \left( \frac{66}{66} \right)^2 \times \left( \frac{15}{10} \right) = j0.12 \text{ pu}$$

$$Z_p = \frac{1}{2} [Z_{ps} + Z_{pt} - Z_{t'}] = \frac{1}{2} [j0.07 + j0.09 - j0.12]$$

$$\boxed{Z_p = j0.02 \text{ pu}}$$

$$Z_s' = \frac{1}{2} [Z_{ps} + Z_{s't'} - Z_{pt}] = \frac{1}{2} [j0.07 + j0.12 - j0.09]$$


$$\boxed{Z_s' = j0.05 \text{ pu}}$$

$$Z_{t'} = \frac{1}{2} [Z_{pt} + Z_{s't'} - Z_{ps}]$$


$$= \frac{1}{2} [j0.09 + j0.12 - j0.07]$$

$$\boxed{Z_{t'} = j0.07 \text{ pu}}$$

Reactance diagram:-

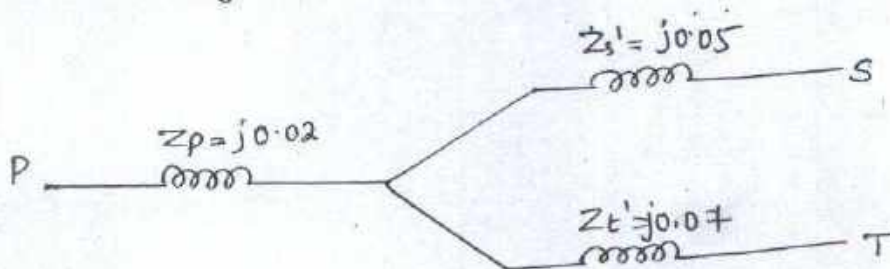

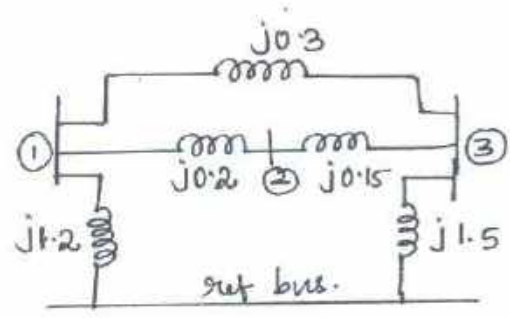
13) Determine  $Z_{bus}$  for system whose reactance diagram is shown below. Where the impedance is given in p.u. Preserve all the nodes (Nov/Dec 2011)



Soln:-

Step 1:- Add bus (1) to ref bus through  $j1.2$


$$Z_{bus} = [j1.2]$$

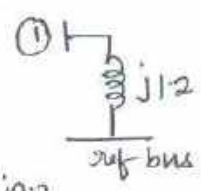

Step 2:- Connect bus (2) to bus (1) through  $j0.2$

$$Z_{bus} = \begin{bmatrix} j1.2 & j1.2 \\ j1.2 & j1.2 + j0.2 \end{bmatrix}$$

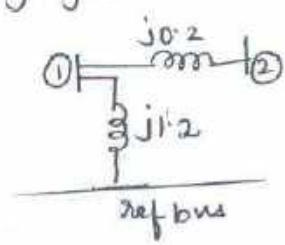
$$Z_{bus} = \begin{bmatrix} j1.2 & j1.2 \\ j1.2 & j1.4 \end{bmatrix}$$



Step 3:- Connect bus (3) to bus (2) through  $j0.15$

$$Z_{bus} = \begin{bmatrix} j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.4 \\ j1.2 & j1.4 & j1.4 + j0.15 \end{bmatrix}$$

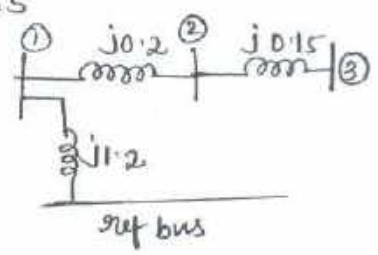
$$Z_{bus} = \begin{bmatrix} j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.4 \\ j1.2 & j1.4 & j1.55 \end{bmatrix}$$



LECTURE NOTES PAPER

Step 4:- Connect bus (3) to ref bus through  $j1.5$
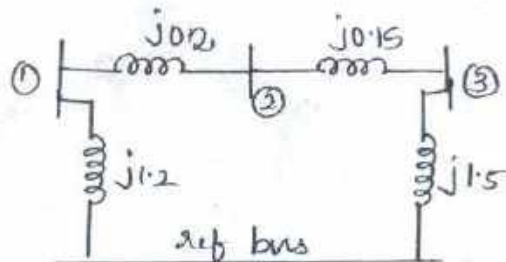
$$Z_{bus} = \begin{bmatrix} j1.2 & j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.4 & j1.4 \\ j1.2 & j1.4 & j1.55 & j1.55 \\ j1.2 & j1.4 & j1.55 & j1.55+j1.5 \end{bmatrix}$$



$$Z_{bus} = \begin{bmatrix} j1.2 & j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.4 & j1.4 \\ j1.2 & j1.4 & j1.55 & j1.55 \\ j1.2 & j1.4 & j1.55 & j3.05 \end{bmatrix}$$

Reduce the  $Z_{bus}$  to  $n \times n$  (ie  $3 \times 3$ ) by Kron reduction technique

$$Z_{jk\text{new}} = Z_{jk\text{old}} - \frac{Z_{j(n+1)}Z_{(n+1)k}}{Z_{(n+1)(n+1)}} \quad \begin{matrix} n=3 \\ j=1,2,3 \\ k=1,2,3 \end{matrix}$$

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{14}Z_{41}}{Z_{44}} = j1.2 - \frac{j1.2 \times j1.2}{j3.05} = j0.728$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{14}Z_{42}}{Z_{44}} = j1.2 - \frac{j1.2 \times j1.4}{j3.05} = j0.649$$

$$Z_{13\text{new}} = Z_{13} - \frac{Z_{14}Z_{43}}{Z_{44}} = j1.2 - \frac{j1.2 \times j1.55}{j3.05} = j0.590$$

$$Z_{21\text{new}} = Z_{12\text{new}} = j0.649$$

$$Z_{22\text{new}} = Z_{22} - \frac{Z_{24}Z_{42}}{Z_{44}} = j1.4 - \frac{j1.4 \times j1.4}{j3.05} = j0.757$$



## LECTURE NOTES PAPER

$$Z_{23\text{new}} = Z_{23} - \frac{Z_{24}Z_{43}}{Z_{44}} = j1.4 - \frac{j1.4j1.55}{j3.05} = j0.689$$

$$Z_{31\text{new}} = Z_{13\text{new}}$$

$$Z_{32\text{new}} = Z_{23\text{new}}$$

$$Z_{33\text{new}} = Z_{33} - \frac{Z_{34}Z_{43}}{Z_{44}} = j1.55 - \frac{j1.55 \times j1.55}{j3.05} = j0.762$$


$$\therefore Z_{\text{bus}} = \begin{bmatrix} j0.728 & j0.649 & j0.590 \\ j0.649 & j0.757 & j0.689 \\ j0.590 & j0.689 & j0.762 \end{bmatrix}$$

Step 5:-

Connect  $j0.3$  between bus ① and bus ③

Column ① - column ③ = 4<sup>th</sup> column

row ① - row ③ = 4<sup>th</sup> row

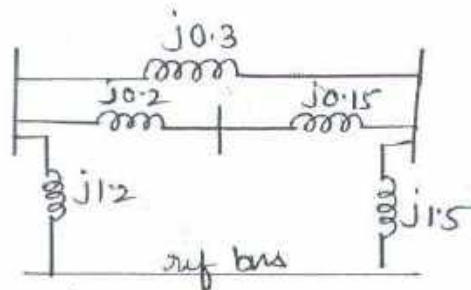

$$Z_{44} = Z_b + Z_{11} + Z_{33} - 2Z_{13}$$

$$= j0.3 + j0.728 + j0.762 - 2(j0.590)$$

$$Z_{44} = j0.61$$

$$Z_{\text{bus}} = \begin{bmatrix} j0.728 & j0.649 & j0.590 & j0.138 \\ j0.649 & j0.757 & j0.689 & -j0.04 \\ j0.590 & j0.689 & j0.762 & -j0.172 \\ j0.138 & -j0.04 & -j0.172 & j0.61 \end{bmatrix}$$

Reduce the matrix to  $3 \times 3$  by Kron reduction technique.

## LECTURE NOTES PAPER

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{14}Z_{41}}{Z_{44}} = j0.728 - \frac{j0.138 \times j0.138}{j0.61} = j0.697$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{14}Z_{42}}{Z_{44}} = j0.649 - \frac{j0.138 \times (-j0.04)}{j0.61} = j0.658$$

$$Z_{13\text{new}} = Z_{13} - \frac{Z_{14}Z_{43}}{Z_{44}} = j0.59 - \frac{j0.138 \times (-j0.172)}{j0.61} = j0.629$$

$$Z_{21\text{new}} = Z_{12\text{new}} = j0.658$$

$$Z_{22\text{new}} = Z_{22} - \frac{Z_{24}Z_{42}}{Z_{44}} = j0.757 - \frac{(-j0.04)(-j0.04)}{j0.61} = j0.754$$

$$Z_{23\text{new}} = Z_{23} - \frac{Z_{24}Z_{43}}{Z_{44}} = j0.689 - \frac{(-j0.04)(-j0.172)}{j0.61} = j0.678$$

$$Z_{31\text{new}} = Z_{13\text{new}} = j0.629$$

$$Z_{32\text{new}} = Z_{23\text{new}} = j0.678$$


$$Z_{33\text{new}} = Z_{33} - \frac{Z_{34}Z_{43}}{Z_{44}} = j0.762 - \frac{(-j0.172)(-j0.172)}{j0.61} = j0.714$$

$$Z_{bus} = \begin{bmatrix} j0.697 & j0.658 & j0.629 \\ j0.658 & j0.754 & j0.678 \\ j0.629 & j0.678 & j0.714 \end{bmatrix}$$



LECTURE NOTES PAPER

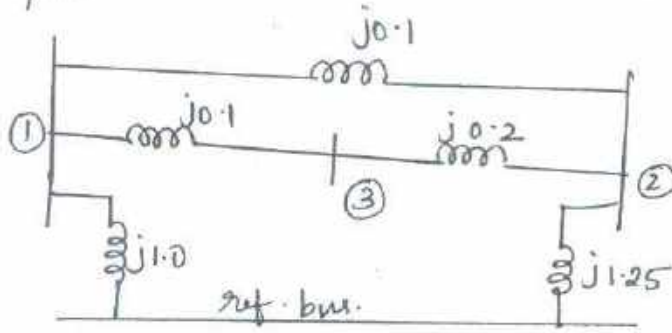14) Determine the  $Z_{bus}$  for a 3 bus system as shown in fig. where the impedances are shown and the values are in pu




(May/June 2009)

Soln:-

Step 1:-

Add  $j0.1$  between bus ① and reference bus


$$Z_{bus} = [j1.0]$$

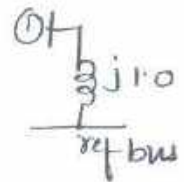

Step 2:-

Add bus (2) to ref. bus through  $j1.25$

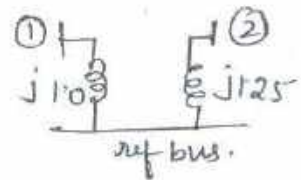
$$Z_{bus} = \begin{bmatrix} j1.0 & 0 \\ 0 & j1.25 \end{bmatrix}$$



Step 3:-

Adding  $j0.1$  between ① and ③
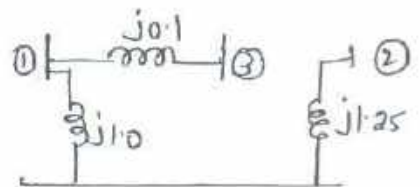
$$Z_{bus} = \begin{bmatrix} j1.0 & 0 & j1.0 \\ 0 & j1.25 & 0 \\ j1.0 & 0 & j1+j1 \end{bmatrix}$$




$$Z_{bus} = \begin{bmatrix} j1 & 0 & j1 \\ 0 & j1.25 & 0 \\ j1 & 0 & j1.1 \end{bmatrix}$$

Step 4:-

Adding  $j0.2$  between buses (2) and (3)
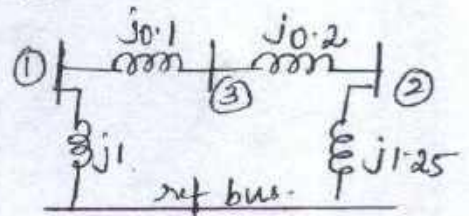
$$Z_{bus} = \begin{bmatrix} j1.0 & 0 & j1 & j1-0 \\ 0 & j1.25 & 0 & 0-j1.25 \\ j1.0 & 0 & j1.1 & j1.1-0 \\ j1-0 & 0-j1.25 & j1.1-0 & Z_{44} \end{bmatrix}$$



column 4 = column 3 - column 2

row 4 = row 3 - row 2

$$Z_{44} = j0.2 + j1.25 + j1.1 - 2 \times 0 = j2.55$$

$$Z_{bus} = \begin{bmatrix} j1 & 0 & j1 & j1 \\ 0 & j1.25 & 0 & -j1.25 \\ j1 & 0 & j1.1 & j1.1 \\ j1 & -j1.25 & j1.1 & j2.55 \end{bmatrix}$$

By Kron reduction reduce the matrix to  $n \times n$  (i.e.  $3 \times 3$ )

$$Z_{jk\text{ new}} = Z_{jk\text{ actual}} - \frac{Z_{j(n+1)} Z_{(n+1)k}}{Z_{(n+1)(n+1)}} \quad \begin{matrix} n=3 \\ j, k=1, 2, 3 \end{matrix}$$

$$Z_{11\text{ new}} = Z_{11} - \frac{Z_{14} Z_{41}}{Z_{44}} = j1 - \frac{j1 \times j1}{j2.55} = j0.608$$

$$Z_{12\text{ new}} = Z_{12} - \frac{Z_{14} Z_{42}}{Z_{44}} = 0 - \frac{j1(-j1.25)}{j2.55} = j0.4902$$

$$Z_{13\text{ new}} = Z_{13} - \frac{Z_{14} Z_{43}}{Z_{44}} = j1 - \frac{j1(j1.1)}{j2.55} = j0.5686$$

$$Z_{21\text{ new}} = Z_{12\text{ new}} = j0.4902$$

LECTURE NOTES PAPER

$$Z_{22 \text{ new}} = Z_{22} - \frac{Z_{24} Z_{42}}{Z_{44}} = j1.25 - \frac{(-j1.25)(-j1.25)}{j2.55} = j0.6372$$

$$Z_{23 \text{ new}} = Z_{23} - \frac{Z_{24} Z_{43}}{Z_{44}} = 0 - \frac{(-j1.25)(j1.1)}{j2.55} = j0.5392$$

$$Z_{31 \text{ new}} = Z_{13 \text{ new}} = j0.5686$$

$$Z_{32 \text{ new}} = Z_{23 \text{ new}} = j0.5392$$

$$Z_{33 \text{ new}} = Z_{33} - \frac{Z_{34} Z_{43}}{Z_{44}} = j1.1 - \frac{(j1.1)(j1.1)}{j2.55} = j0.6255$$


$$Z_{bus} = \begin{bmatrix} j0.6078 & j0.4902 & j0.5686 \\ j0.4902 & j0.6372 & j0.5392 \\ j0.5686 & j0.5392 & j0.6255 \end{bmatrix}$$

Step 5:-

Adding j0.1 between buses ① and ②

Column 4 = Column ② - Column ①

row 4 = row ② - row ①

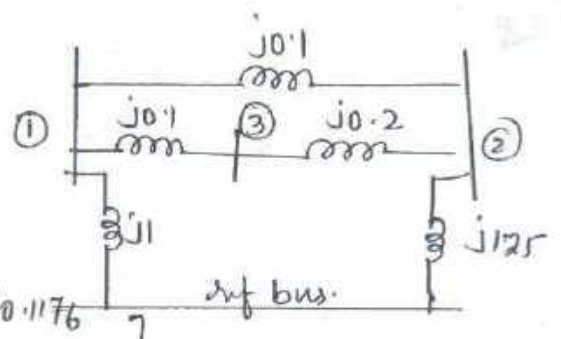

$$Z_{bus} = \begin{bmatrix} j0.6078 & j0.4902 & j0.5686 & -j0.1176 \\ j0.4902 & j0.6372 & j0.5392 & j0.147 \\ j0.5686 & j0.5392 & j0.6255 & -j0.0294 \\ -j0.1176 & j0.147 & -j0.0294 & j0.3646 \end{bmatrix}$$

$$Z_{44} = j0.1 + j0.6078 + j0.6372 - 2(j0.4902)$$

$$Z_{44} = j0.3646$$

## LECTURE NOTES PAPER

reduce the matrix to 3x3 by Kron reduction

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{14}Z_{41}}{Z_{44}} = j0.6078 - \frac{(-j0.1176 \times -j0.1176)}{j0.3646} = j0.5699$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{14}Z_{42}}{Z_{44}} = j0.4902 - \frac{(-j0.1176 \times j0.147)}{j0.3646} = j0.5376$$

$$Z_{13\text{new}} = Z_{13} - \frac{Z_{14}Z_{43}}{Z_{44}} = j0.5686 - \frac{(-j0.1176 \times -j0.0294)}{j0.3646} = j0.5591$$

$$Z_{21\text{new}} = Z_{12\text{new}} = j0.5376$$

$$Z_{22\text{new}} = Z_{22} - \frac{Z_{24}Z_{42}}{Z_{44}} = j0.6372 - \frac{(j0.147 \times j0.147)}{j0.3646} = j0.5779$$

$$Z_{23\text{new}} = Z_{23} - \frac{Z_{24}Z_{43}}{Z_{44}} = j0.5392 - \frac{(j0.147 \times -j0.0294)}{j0.3646} = j0.5511$$

$$Z_{31\text{new}} = Z_{13\text{new}} = j0.5591$$


$$Z_{32\text{new}} = Z_{23\text{new}} = j0.5511$$

$$Z_{33\text{new}} = Z_{33} - \frac{Z_{34}Z_{43}}{Z_{44}} = j0.6255 - \frac{(-j0.0294 \times -j0.0294)}{j0.3646} = j0.6231$$

$$Z_{\text{bus}} = \begin{bmatrix} j0.5699 & j0.5376 & j0.5591 \\ j0.5376 & j0.5779 & j0.5511 \\ j0.5591 & j0.5511 & j0.6231 \end{bmatrix}$$



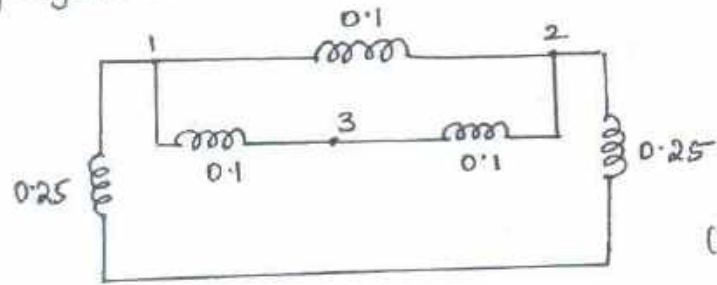5) For the 3-bus network shown below obtain  $Z_{bus}$  by building algorithm




(Nov/Dec 2014)

Soln:-

Step 1:- Add bus ① to reference bus


$$Z_{bus} = [j0.25]$$

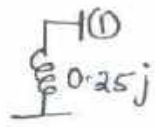

Step 2:- Add bus ② to bus ① through  $j0.1$

$$Z_{bus} = \begin{bmatrix} j0.25 & j0.25 \\ j0.25 & j0.25 + j0.1 \end{bmatrix}$$

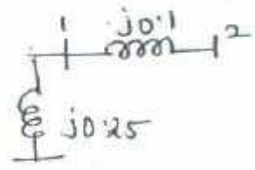
$$Z_{bus} = \begin{bmatrix} j0.25 & j0.25 \\ j0.25 & j0.35 \end{bmatrix}$$



Step 3:- Add bus ③ to ref. bus

$$Z_{bus} = \begin{bmatrix} j0.25 & j0.25 & j0.25 \\ j0.25 & j0.35 & j0.35 \\ j0.25 & j0.35 & j0.35 + j0.25 \end{bmatrix}$$
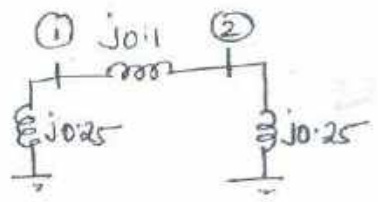
$$Z_{bus} = \begin{bmatrix} j0.25 & j0.25 & j0.25 \\ j0.25 & j0.35 & j0.35 \\ j0.25 & j0.35 & j0.6 \end{bmatrix}$$



Reduce the matrix to 2x2 by Kron reduction

$$Z_{jk\ new} = Z_{jk} - \frac{Z_j^{(n+1)} Z_{(n+1)k}}{Z_{(n+1)(n+1)}}$$



LECTURE NOTES PAPER

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{13}Z_{31}}{Z_{33}} = j0.25 - \frac{(j0.25)(j0.25)}{j0.6} = j0.1458$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{13}Z_{32}}{Z_{33}} = j0.25 - \frac{(j0.25)(j0.35)}{j0.6} = j0.10416$$


$$Z_{22\text{new}} = Z_{22} - \frac{Z_{23}Z_{32}}{Z_{33}} = j0.35 - \frac{(j0.35)(j0.35)}{j0.6} = j0.1458$$

$$Z_{\text{bus}} = \begin{bmatrix} 0.1458j & j0.10416 \\ j0.10416 & j0.1458 \end{bmatrix}$$

Step 4:-

Add bus (3) to bus (2) through  $j0.1$
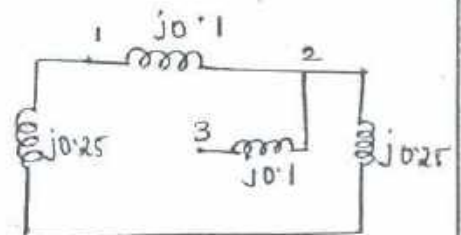
$$Z_{\text{bus}} = \begin{bmatrix} j0.1458 & j0.10416 & j0.10416 \\ j0.10416 & j0.1458 & j0.1458 \\ j0.10416 & j0.1458 & j0.1458 + j0.1 \end{bmatrix}$$




$$Z_{\text{bus}} = \begin{bmatrix} j0.1458 & j0.10416 & j0.10416 \\ j0.10416 & j0.1458 & j0.1458 \\ j0.10416 & j0.1458 & j0.2458 \end{bmatrix}$$

Step 5:-

Add buses (1) and (3) through  $j0.1$
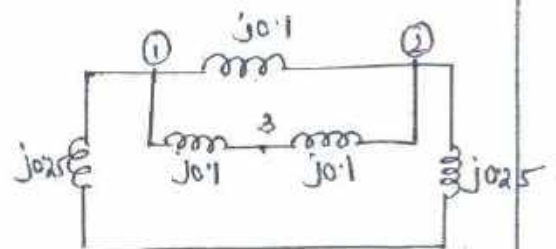
$$Z_{\text{bus}} = \begin{bmatrix} j0.1458 & j0.10416 & j0.10416 & -j0.0416 \\ j0.10416 & j0.1458 & j0.1458 & j0.0416 \\ j0.10416 & j0.1458 & j0.2458 & j0.1416 \\ -j0.0416 & j0.0416 & j0.1416 & j0.2832 \end{bmatrix}$$



Column 4 = Column 3 - Column 1

row 4 = row 3 - row 1

$$Z_{44} = j0.1 + j0.1458 + j0.2458 - 2(j0.10416)$$

$$Z_{44} = j0.2832$$

## LECTURE NOTES PAPER

Reduce the matrix to  $n \times n$  (i.e.  $3 \times 3$ ) by Kron reduction technique.

$$Z_{k\text{new}} = Z_{jk} - \frac{Z_{j(n+1)} Z_{(n+1)k}}{Z_{(n+1)(n+1)}}$$

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{14} Z_{41}}{Z_{44}} = j0.1458 - \frac{(-j0.0416)(-j0.0416)}{j0.2832} = j0.1396$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{14} Z_{42}}{Z_{44}} = j0.10416 - \frac{(-j0.0416)(j0.0416)}{j0.2832} = j0.1102$$

$$Z_{13\text{new}} = Z_{13} - \frac{Z_{14} Z_{43}}{Z_{44}} = j0.10416 - \frac{(-j0.0416)(j0.1416)}{j0.2832} = j0.12496$$

$$Z_{21\text{new}} = Z_{21\text{new}} = j0.1102$$

$$Z_{22\text{new}} = Z_{22} - \frac{Z_{24} Z_{42}}{Z_{44}} = j0.1458 - \frac{(j0.0416)(j0.0416)}{j0.2832} = j0.13968$$

$$Z_{23\text{new}} = Z_{23} - \frac{Z_{24} Z_{43}}{Z_{44}} = j0.1458 - \frac{(j0.0416)(j0.1416)}{j0.2832} = j0.125$$

$$Z_{31\text{new}} = Z_{31\text{new}} = j0.12496$$


$$Z_{32\text{new}} = Z_{32\text{new}} = j0.125$$

$$Z_{33\text{new}} = Z_{33} - \frac{Z_{34} Z_{43}}{Z_{44}} = j0.2458 - \frac{(j0.1416)(j0.1416)}{j0.2832} = j0.175$$

$$Z_{\text{bus}} = \begin{bmatrix} j0.1396 & j0.1102 & j0.1249 \\ j0.1102 & j0.1396 & j0.125 \\ j0.1249 & j0.125 & j0.175 \end{bmatrix}$$

LECTURE NOTES PAPER

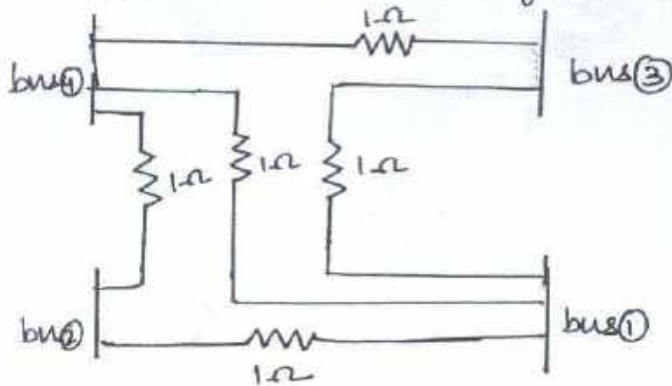16) Find the bus impedance matrix for the 4 bus system shown in figure. Consider bus 4 as the reference bus.




(May/June 2012)

Soln:-

Step 1:- Add an element between ref bus (ie bus 4) and bus 1

$$Z_{bus} = [1]$$

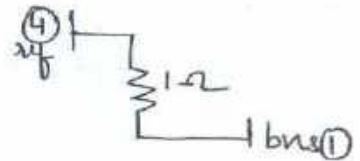


Step 2:-

Add 1-ohm between bus 2 and bus 1

$$Z_{bus} = \begin{bmatrix} 1 & 1 \\ 1 & 1+1 \end{bmatrix}$$
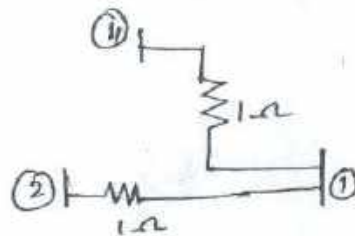
$$Z_{bus} = \begin{bmatrix} 1 & 1 \\ 1 & 2 \end{bmatrix}$$




Step 3:-

Add 1-ohm between bus 3 and bus 1

$$Z_{bus} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 2 & 1 \\ 1 & 1 & 1+1 \end{bmatrix}$$
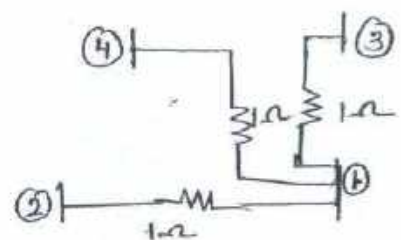
$$Z_{bus} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 2 & 1 \\ 1 & 1 & 2 \end{bmatrix}$$




Step 4:-

Add  $1\Omega$  between bus (2) and bus(4) (ie ref bus)

$$Z_{bus} = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & 2 & 1 & 2 \\ 1 & 1 & 2 & 1 \\ 1 & 2 & 1 & 2 \end{bmatrix}$$
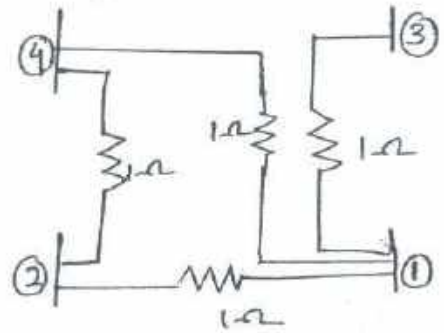
$$Z_{bus} = \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & 2 & 1 & 2 \\ 1 & 1 & 2 & 1 \\ 1 & 2 & 1 & 3 \end{bmatrix}$$



Reduce the matrix to  $3 \times 3$  by Kron reduction

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{14}Z_{41}}{Z_{44}} = 1 - \frac{1 \times 1}{3} = 0.66$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{14}Z_{42}}{Z_{44}} = 1 - \frac{1 \times 2}{3} = 0.33$$

$$Z_{13\text{new}} = Z_{13} - \frac{Z_{14}Z_{43}}{Z_{44}} = 1 - \frac{1 \times 1}{3} = 0.66$$

$$Z_{21\text{new}} = Z_{12\text{new}} = 0.33$$

$$Z_{22\text{new}} = Z_{22} - \frac{Z_{24}Z_{42}}{Z_{44}} = 2 - \frac{2 \times 2}{3} = 0.66$$

$$Z_{23\text{new}} = Z_{23} - \frac{Z_{24}Z_{43}}{Z_{44}} = 1 - \frac{2 \times 1}{3} = 0.33$$

$$Z_{31\text{new}} = Z_{13\text{new}} = 0.66$$

$$Z_{32\text{new}} = Z_{23\text{new}} = 0.33$$

$$Z_{33\text{new}} = Z_{33} - \frac{Z_{34}Z_{43}}{Z_{44}} = 2 - \frac{1 \times 1}{3} = 1.66$$


## LECTURE NOTES PAPER

$$Z_{bus} = \begin{bmatrix} 0.66 & 0.33 & 0.66 \\ 0.33 & 0.66 & 0.33 \\ 0.66 & 0.33 & 1.66 \end{bmatrix}$$

Step 5:-

Adding an element between ③ and ref bus ④
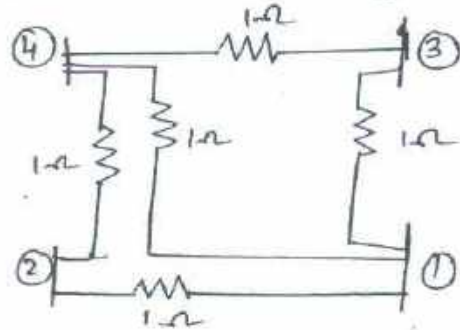
$$Z_{bus} = \begin{bmatrix} 0.66 & 0.33 & 0.66 & 0.66 \\ 0.33 & 0.66 & 0.33 & 0.33 \\ 0.66 & 0.33 & 1.66 & 1.66 \\ 0.66 & 0.33 & 1.66 & 1.66+1 \end{bmatrix}$$



$$Z_{bus} = \begin{bmatrix} 0.66 & 0.33 & 0.66 & 0.66 \\ 0.33 & 0.66 & 0.33 & 0.33 \\ 0.66 & 0.33 & 1.66 & 1.66 \\ 0.66 & 0.33 & 1.66 & 2.66 \end{bmatrix}$$

Reduce the matrix to 3x3 by Kron reduction.

$$Z_{jk(new)} = Z_{jk} - \frac{Z_{j(n+1)} Z_{(n+1)k}}{Z_{(n+1)(n+1)}}$$

$$Z_{11(new)} = Z_{11} - \frac{Z_{14} Z_{41}}{Z_{44}} = 0.66 - \frac{0.66 \times 0.66}{2.66} = 0.496$$

$$Z_{12(new)} = Z_{12} - \frac{Z_{14} Z_{42}}{Z_{44}} = 0.33 - \frac{0.66 \times 0.33}{2.66} = 0.248$$

$$Z_{13(new)} = Z_{13} - \frac{Z_{14} Z_{43}}{Z_{44}} = 0.66 - \frac{0.66 \times 1.66}{2.66} = 0.248$$

$$Z_{21(new)} = Z_{12(new)} = 0.248$$

$$Z_{22(new)} = Z_{22} - \frac{Z_{24} Z_{42}}{Z_{44}} = 0.66 - \frac{0.33 \times 0.33}{2.66} = 0.619$$



LECTURE NOTES PAPER

$$Z_{23(new)} = Z_{23} - \frac{Z_{24} Z_{43}}{Z_{44}} = 0.33 - \frac{0.33 \times 1.66}{2.66} = 0.124$$


$$Z_{31(new)} = Z_{13(new)} = 0.248$$

$$Z_{32(new)} = Z_{23(new)} = 0.124$$

$$Z_{33(new)} = Z_{33} - \frac{Z_{34} Z_{43}}{Z_{44}} = 1.66 - \frac{1.66 \times 1.66}{2.66} = 0.624$$

$$Z_{bus} = \begin{bmatrix} 0.496 & 0.248 & 0.248 \\ 0.248 & 0.619 & 0.124 \\ 0.248 & 0.124 & 0.624 \end{bmatrix}$$

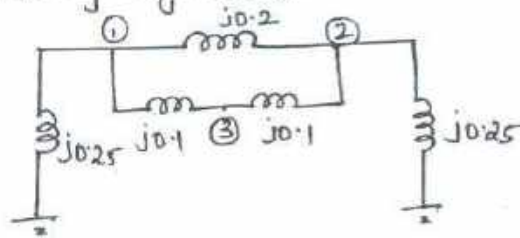
17) Form the bus impedance matrix for the network shown in fig by bus building algorithm. (May/June 2013)



Soln:-


Step 1:- Add bus ① to ref bus.

$$Z_{bus} = [0.25j]$$

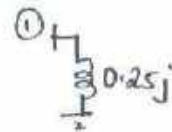

Step 2:- Adding bus ② to bus ① through j0.2
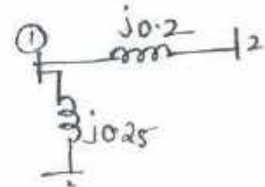
$$Z_{bus} = \begin{bmatrix} 0.25j & 0.25j \\ 0.25j & 0.25j + 0.2j \end{bmatrix}$$




$$Z_{bus} = \begin{bmatrix} 0.25j & 0.25j \\ 0.25j & 0.45j \end{bmatrix}$$
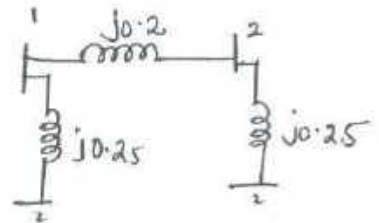
## LECTURE NOTES PAPER

Step 3:-Adding bus (2) to ref bus through  $j0.25$ 

$$Z_{bus} = \begin{bmatrix} j0.2 & j0.25 & j0.25 \\ j0.25 & j0.45 & j0.45 \\ j0.25 & j0.45 & j0.45 + j0.25 \end{bmatrix}$$



$$Z_{bus} = \begin{bmatrix} j0.2 & j0.25 & j0.25 \\ j0.25 & j0.45 & j0.45 \\ j0.25 & j0.45 & j0.7 \end{bmatrix}$$

reduce the matrix to  $2 \times 2$  by Kron reduction

$$Z_{11} = Z_{11} - \frac{Z_{13}Z_{31}}{Z_{33}} = j0.25 - \frac{j0.25 \times j0.25}{j0.7} = j0.1607$$


$$Z_{12} = Z_{12} - \frac{Z_{13}Z_{32}}{Z_{33}} = j0.25 - \frac{j0.25 \times j0.45}{j0.7} = j0.0892$$

$$Z_{22} = Z_{22} - \frac{Z_{23}Z_{32}}{Z_{33}} = j0.45 - \frac{j0.45 \times j0.45}{j0.7} = j0.1607$$

$$Z_{bus} = \begin{bmatrix} 0.1607j & 0.0892j \\ 0.0892j & 0.1607j \end{bmatrix}$$

Step 4:-Adding bus (3) to bus (2) through  $j0.1$ 
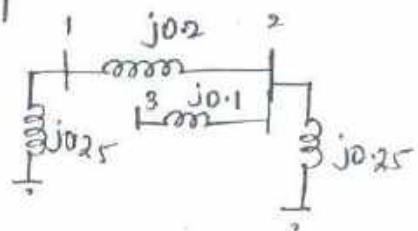
$$Z_{bus} = \begin{bmatrix} 0.1607j & 0.0892j & 0.0892j \\ 0.0892j & 0.1607j & 0.1607j \\ 0.0892j & 0.1607j & 0.2607j + j0.1 \end{bmatrix}$$




$$Z_{bus} = \begin{bmatrix} 0.1607j & 0.0892j & 0.0892j \\ 0.0892j & 0.1607j & 0.1607j \\ 0.0892j & 0.1607j & 0.2607j \end{bmatrix}$$

LECTURE NOTES PAPER

Step 5:-

Add bus ③ to bus ① through  $j0.1$

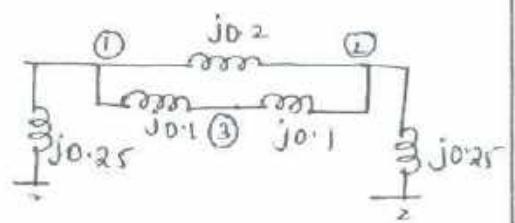

$$Z_{bus} = \begin{bmatrix} 0.1607j & 0.0892j & 0.0892j & 0.0715j \\ 0.0892j & 0.1607j & 0.1607j & -0.0715j \\ 0.0892j & 0.1607j & 0.2607j & -0.175j \\ 0.0715j & -0.0715j & -0.175j & 0.343j \end{bmatrix}$$

Column 4 = Column 1 - Column 2  
 Row 4 = row 1 - row 2

$$Z_{44} = Z_{13} + Z_{33} + Z_6 - 2Z_{13}$$

$$= 0.1607j + 0.2607j + j0.1 - 2 \times 0.0892j = 0.343j$$

reduce the matrix to 3x3 by Kron reduction

$$Z_{11\text{new}} = Z_{11} - \frac{Z_{14}Z_{41}}{Z_{44}} = 0.1607j - \frac{0.0715 \times 0.0715}{0.343j} = j0.145$$

$$Z_{12\text{new}} = Z_{12} - \frac{Z_{14}Z_{42}}{Z_{44}} = 0.0892j - \frac{0.0715j \times (-0.0715j)}{0.343j} = j0.104$$

$$Z_{13\text{new}} = Z_{13} - \frac{Z_{14}Z_{43}}{Z_{44}} = 0.0892j - \frac{0.0715j \times (-0.175j)}{0.343j} = j0.125$$

$$Z_{21\text{new}} = Z_{12\text{new}} = j0.104$$

$$Z_{22\text{new}} = Z_{22} - \frac{Z_{24}Z_{42}}{Z_{44}} = 0.1607j - \frac{(-0.0715j \times -0.0715j)}{0.343j} = j0.1458$$

$$Z_{23\text{new}} = Z_{23} - \frac{Z_{24}Z_{43}}{Z_{44}} = 0.1607j - \frac{(-0.0715j) \times (-0.175j)}{0.343j} = j0.125$$

$$Z_{31\text{new}} = Z_{13\text{new}} = j0.125$$

$$Z_{32\text{new}} = Z_{23\text{new}} = j0.125$$

$$Z_{33} = Z_{33} - \frac{Z_{34}Z_{43}}{Z_{44}} = 0.2607j - \frac{(-0.175j \times -0.175j)}{0.343j} = j0.171$$

$$Z_{bus} = \begin{bmatrix} j0.145 & j0.104 & j0.125 \\ j0.104 & j0.1458 & j0.125 \\ j0.125 & j0.125 & j0.171 \end{bmatrix}$$


LECTURE NOTES PAPER

18. The parameters of a 4 bus system are as under:-

Bus code	line impedance (pu)	Charging admittance (pu)
1-2	$0.2 + j0.8$	$j0.02$
2-3	$0.3 + j0.9$	$j0.03$
2-4	$0.25 + j1$	$j0.04$
3-4	$0.2 + j0.8$	$j0.02$
1-3	$0.1 + j0.4$	$j0.01$

Draw the network and find the bus admittance matrix  
(Nov/Dec 2011)  
(April/May 2010)

Soln:-

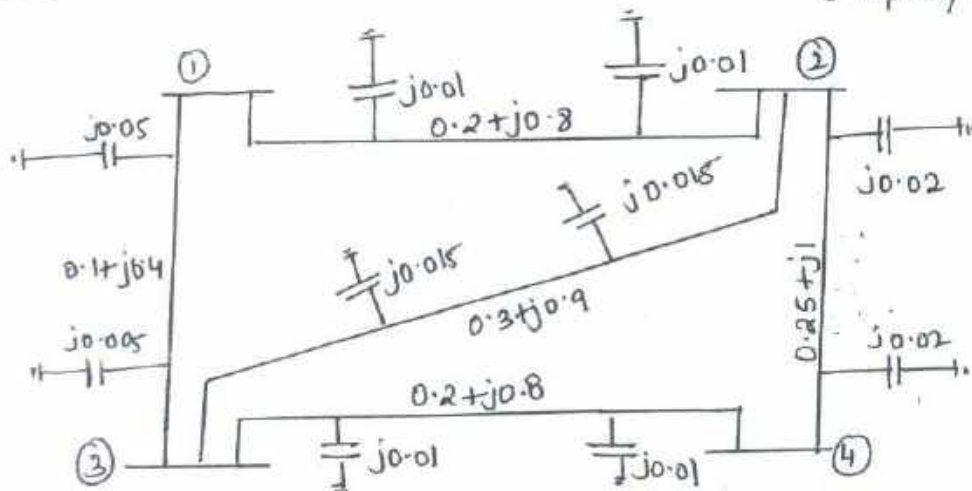

Half line charging admittance  $Y_{i0} = \frac{\text{line charging admittance}}{2}$

$$Y_{11} = Y_{12} + Y_{13} + Y_{10}$$

$$= \frac{1}{0.2 + j0.8} + \frac{1}{0.1 + j0.4} + j0.01 + j0.05$$

$$Y_{11} = 0.8822 - j3.514$$

$$Y_{12} = Y_{21} = -Y_{12} = -\frac{1}{0.2 + j0.8}$$

$$Y_{12} = Y_{21} = -0.294 + j1.176$$

## LECTURE NOTES PAPER

$$Y_{13} = Y_{31} = -Y_{13} = \frac{-1}{0.1 + j0.4}$$

$$Y_{13} = Y_{31} = -0.5882 + j2.353$$

$$Y_{14} = Y_{41} = 0$$

$$Y_{22} = Y_{21} + Y_{24} + Y_{23} + Y_{20}$$

$$= \frac{1}{0.2 + j0.8} + \frac{1}{0.25 + j1} + \frac{1}{0.3 + j0.9} + j0.01 + j0.02 + j0.015$$

$$Y_{22} = 0.862 - j3.072$$

$$Y_{23} = Y_{32} = -Y_{23} = \frac{-1}{0.3 + j0.4}$$

$$Y_{23} = Y_{32} = -0.333 + j1$$

$$Y_{24} = Y_{42} = -Y_{24} = \frac{-1}{0.25 + j1}$$

$$Y_{24} = Y_{42} = -0.235 + j0.941$$

$$Y_{33} = Y_{31} + Y_{34} + Y_{32} + Y_{30}$$

$$= \frac{1}{0.1 + j0.4} + \frac{1}{0.2 + j0.8} + \frac{1}{0.3 + j0.9} + j0.05 + j0.015 + j0.01$$

$$Y_{33} = 1.215 - j4.49$$

$$Y_{44} = Y_{42} + Y_{43} + Y_{40}$$

$$= \frac{1}{0.25 + j0.1} + \frac{1}{0.2 + j0.8} + j0.01 + j0.02$$

$$Y_{44} = 0.529 - j2.087$$




## LECTURE NOTES PAPER

$$Y_{bus} = \begin{bmatrix} 0.8822 - j3.514 & -0.2914 + j1.176 & -0.5883 + j2.353 & 0 \\ -0.2914 + j1.176 & 0.862 - j3.072 & -0.333 + j1 & -0.235 + j0.941 \\ -0.5883 + j2.353 & -0.333 + j1 & 1.215 - j4.499 & -0.294 + j1.176 \\ 0 & -0.235 + j0.941 & -0.294 + j1.176 & 0.529 - j2.037 \end{bmatrix}$$

19. Determine  $Y_{bus}$  for the 3-bus system shown in figure. The line series impedance as follows

Line (bus to bus)	Impedance (pu)
1-2	$0.06 + j0.18$
1-3	$0.03 + j0.09$
2-3	$0.08 + j0.24$

(NOV/DEC 2013)

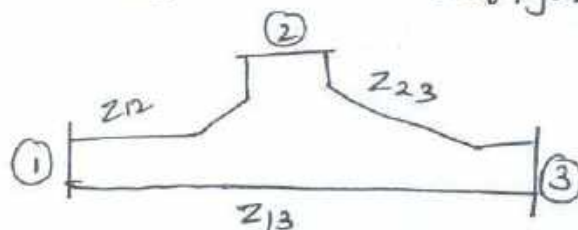soln:-

$$Y_{11} = Y_{12} + Y_{13} = \frac{1}{0.06 + j0.18} + \frac{1}{0.03 + j0.09} = 1.666 - 5j + 3.33 - 10j$$

$$Y_{11} = 4.996 - 15j$$

$$Y_{12} = Y_{21} = -\frac{1}{0.06 + j0.18}$$

$$Y_{12} = Y_{21} = -1.666 + 5j$$

## LECTURE NOTES PAPER

$$Y_{13} = Y_{31} = -Y_{13} = \frac{-1}{0.03 + j0.09}$$

$$Y_{13} = Y_{31} = -3.33 + 10j$$

$$Y_{22} = Y_{12} + Y_{23}$$

$$= \frac{1}{0.06 + j0.18} + \frac{1}{0.08 + j0.24}$$

$$Y_{22} = 2.916 - 8.7j$$

$$Y_{23} = Y_{32} = -\frac{1}{0.08 + j0.24}$$

$$Y_{23} = Y_{32} = -1.25 + 3.7j$$

$$Y_{33} = Y_{13} + Y_{23}$$

$$= \frac{1}{0.03 + j0.09} + \frac{1}{0.08 + j0.24}$$

$$Y_{33} = 4.58 - 13.7j$$

$$Y_{bus} = \begin{bmatrix} 4.996 - 15j & -1.666 + 5j & -3.33 + 10j \\ -1.666 + 5j & 2.916 - 8.7j & -1.25 + 3.7j \\ -3.33 + 10j & -1.25 + 3.7j & 4.58 - 13.7j \end{bmatrix}$$